


**RF Circuit Design****Prof. Salvatore Levantino**

Available time: 2 hours

Jul. 13, 2020

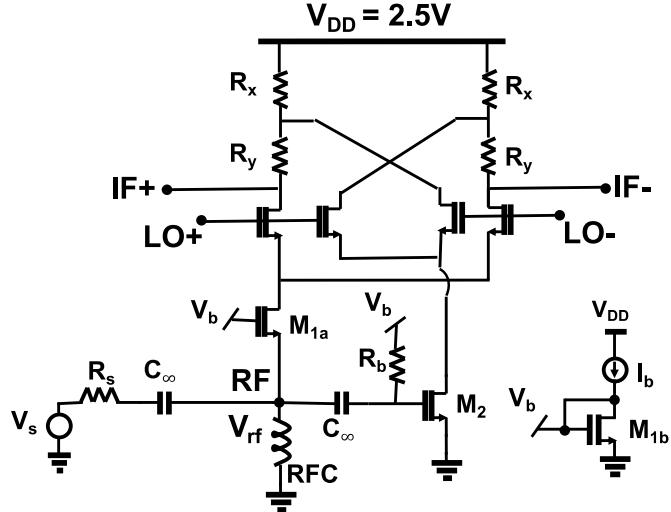**Problem #1**

In the LNA/mixer cascade in figure, let the MOSFET aspect ratios  $(W/L)_{M1a} = (W/L)_{M1b} = 500$ ,  $(W/L)_{M2} = 2000$ , and the resistor  $R_b = 1 \text{ M}\Omega$ . Let RFC inductance and  $C_\infty$  capacitances tend to infinity. Let the transistors threshold  $V_T = 0.5\text{V}$ , constants  $\frac{1}{2}\mu_n C'_\text{ox} = 0.2 \text{ mA/V}^2$  and  $\gamma/\alpha = 2/3$ . The LO signal is such that it fully steers the current of the differential pairs at  $f_{LO} = 1 \text{ GHz}$ , but maintains M1-M2 always in saturation region.  $V_s$  is a signal at  $f_{RF} = 0.9 \text{ GHz}$ .




- a) Calculate the **value of  $R_y/R_x$  ratio**

which cancels the thermal noise of  $M_1$  at IF port, after imposing conjugate matching at RF port.

- b) Set the **value of  $R_x$ ,  $R_y$  and  $I_b$**  to get conversion gain  $G_C = 20\log(|V_{if}/V_{rf}|) = 28\text{dB}$  (where  $V_{if} = V_{IF+} - V_{IF-}$ ), imposing the condition in a) and conjugate matching at RF port.
- c) Calculate the **noise figure NF in dB** at  $f_{RF}$ , accounting only for the thermal noise of  $R_s$ ,  $R_x$ ,  $R_y$  resistors and  $M_1$  and  $M_2$  transistors. (Assume  $R_s$  to model a resonator, whose noise is white passband around  $f_{RF}$ ).

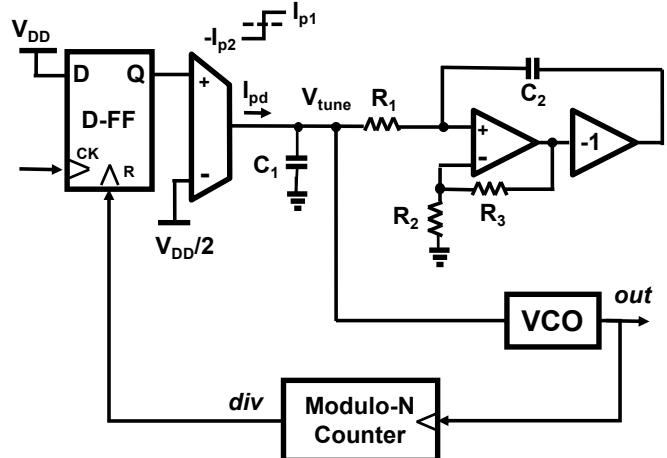**Problem #2**

The PLL in figure has VCO frequency ranging from 1.8GHz to 2.2GHz sweeping  $V_{tune}$  from 0 to  $V_{dd} = 3.3\text{V}$ . The phase detector is a D-type flip-flop (D-FF) sensitive to rising-edge transitions. Let the reference frequency  $f_{ref} = 10\text{MHz}$  and the frequency division factor  $N = 200$ . Let  $R_2 = 1\text{k}\Omega$ ,  $C_1 = 80\text{pF}$ ,  $C_2 = 100\text{pF}$ . Let the charge-pump currents  $I_{p1} = 50\mu\text{A}$  and  $I_{p2} = 30\mu\text{A}$ .




- a) Calculate the **values of  $R_1$  and  $R_3$**  to

have (i) unity-gain frequency of PLL loop gain of 15 kHz, (ii) phase margin of 60 degree.

- b) Calculate the **steady-state time shift (in seconds)** between  $ref$  and  $div$  signals. Evaluate **frequency (Hz) and level (dBc)** of the dominant spur in the output spectrum.
- c) Determine the **value of the output phase noise PSD** accounting only for the thermal noise of  $R_1$  at the offset frequency of 100Hz.

## EX 1 SOLUTION

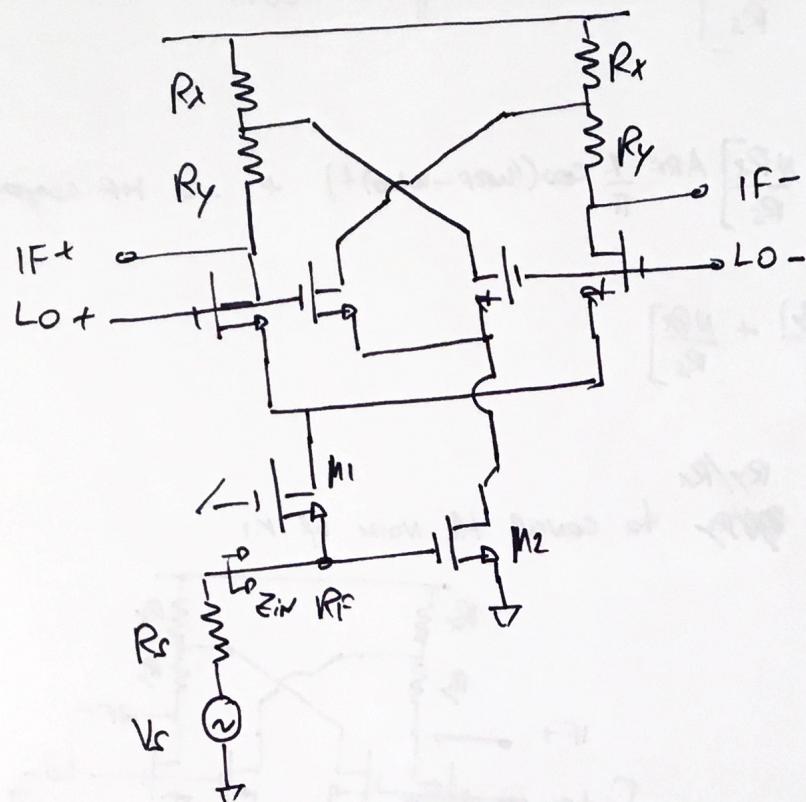


a) • INPUT MATCHING :  $Z_{IN} = 1/g_m = 50 \Omega = R_S$   
     • CONVERSION GAIN  $G^{REF-DIF}$

$$V_{IF}(t) = \left[ g_{m1} (R_X + R_Y) + g_{m2} R_X \right] V_{RF}(t) X_L(t)$$

$$N = \frac{g_m 2}{g_m 1} = \frac{(V/L)_2}{(V/L)_1} = 4$$

$$V_{IF}(t) = \left[ \frac{(R_x + R_y)}{R_s} + \frac{N R_x}{R_s} \right] V_{RF}(t) \times L_o(t)$$

A<sub>RF</sub> cos(w<sub>RF</sub>t)

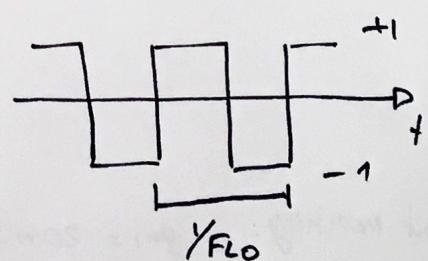

$$x_{L0}(t) \approx 0 + \frac{q}{\pi} \cos(\omega_{L0} t) + 0 - \frac{q}{3\pi} \cos(3\omega_{L0} t) + \dots$$


$$V_{IF}(1) \approx \left[ \frac{(R_x + R_y)}{R_s} + \frac{N R_x}{R_s} \right] A_{RF} \cos(\omega_{RF} t) + \cos(\omega_{LO} t)$$

$$\approx \frac{1}{2} \left[ \frac{(R_x + R_y)}{R_s} + \frac{N R_x}{R_s} \right] A_{RF} \frac{1}{\pi} \cos((\omega_{RF} - \omega_{LO})t) + \dots \text{HF component}$$

$$G^{RF-DIF} = \frac{2}{\pi} \left[ \frac{(R_x + R_y)}{R_s} + \frac{N R_x}{R_s} \right]$$

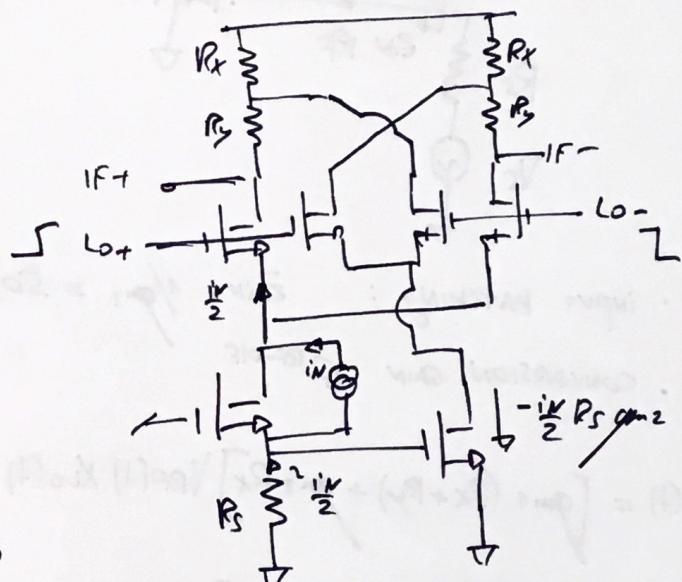b) DETERMINE THE RATIO  $R_y/R_x$  TO CANCEL THE NOISE OF M1

consider  $V_{LO} > 0$ , the  
some result holds for  
 $V_{LO} < 0$ .



~~$\frac{1}{2} R_s (R_x + R_y) = 0$~~

$$V_{IF} = \frac{iV}{2} (R_x + R_y) - \frac{iV}{2} R_s g_m^2 R_x = 0$$

$$\Rightarrow (R_x + R_y) - N R_x = 0$$

$$R_y = R_x [N - 1]$$

$$\Rightarrow \frac{R_y}{R_x} = (N - 1)$$

- INPUT MATCHING:  $g_{m1} = 20 \text{ mS} = \frac{1}{50 \Omega}$

$$I_b = \frac{(g_{m1}/2)^2}{k_2 \mu n C_{ox} (\frac{V}{L})} = 1 \text{ mA}$$

$$G_{AIN} = G_{RF \rightarrow IF} = \frac{2}{\pi} \frac{1}{R_S} [R_X + R_Y + N R_X] = \frac{2}{\pi R_S} [2 N R_X]$$

$R_Y = (N-1) R_X$

$$G = \frac{4 N R_X}{\pi R_S} = 10^{28/20} \rightarrow R_X \approx 247 \Omega$$

$$R_Y = (N-1) R_X = 741 \Omega$$

c) Noise Figure:

$$M_1 = \infty$$


$$R_S: S_{VIF}^{RS} = 4 K T R_S \left[ \frac{G_{RF \rightarrow IF}}{2} \right]^2$$

$$R_X, R_Y: S_{VIF}^{R_X R_Y} = 2 \times 4 K T (R_X + R_Y)$$

M2

$$V_{IF}(t) = i_N(t) X_{LO}(t) \cdot R_X$$

~~Since  $R_X \approx R_Z$~~

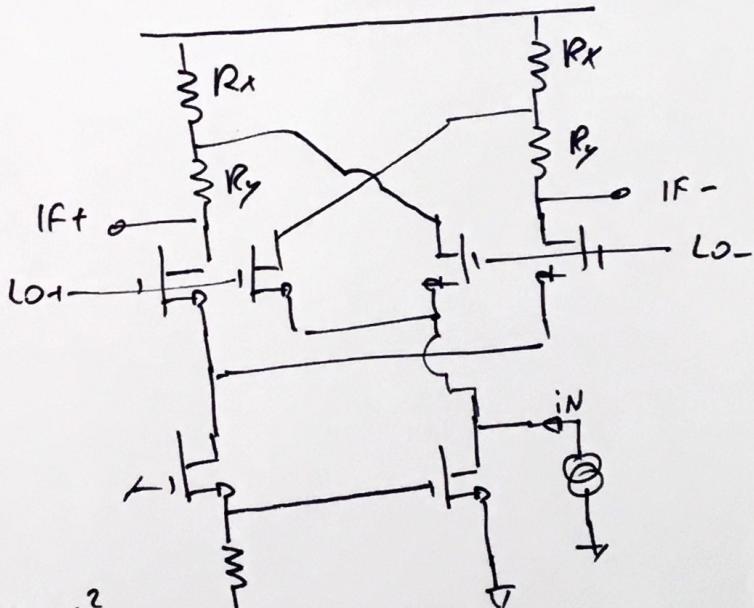

$$S_{VIF}^{M2} = 4 K T \sum_{\alpha} N_{\alpha m} R_X^2 \sum_{J=1}^{+\infty} \frac{1}{2} |Z_J|^2$$

R COEFFICIENTS FOURIER SERIES.


$$\sum_{J=1}^{+\infty} \left| \frac{Z_J}{2} \right|^2 = \int_0^{+\infty} S_{VL0}(f) df = \frac{1}{T_{LO}} \int_{-T_{LO}/2}^{T_{LO}/2} |X_{LO}(t)|^2 dt = 1$$

PARSEVAL'S THEOREM

$$S_{V_{IF}}^{\text{m}^2}(f) = 4kT \frac{R}{\alpha} g_m N R_x^2$$


$$NF = 1 + \frac{2 \times 4kT (R_x + R_y)}{4kTR_s \left(\frac{G}{2}\right)^2} + \frac{4kT \frac{R}{\alpha} g_m N R_x^2}{4kTR_s \left(\frac{G}{2}\right)^2}$$
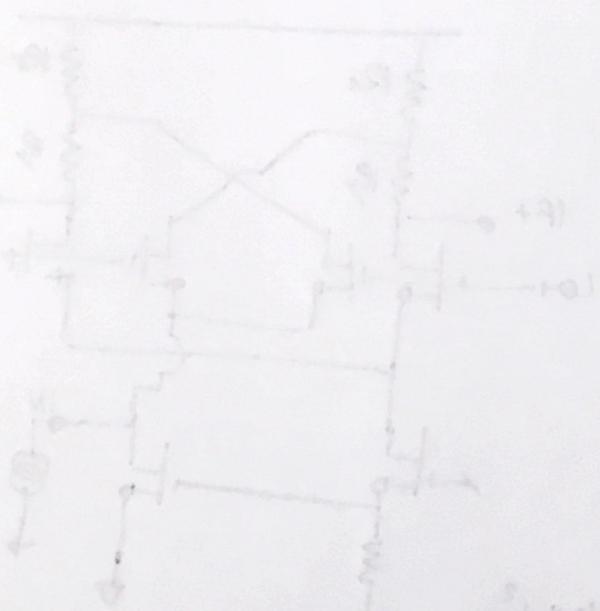
$$= 1 + \frac{2 (R_x + R_y) + \frac{R}{\alpha} \frac{NR_x^2}{R_s}}{\left(\frac{G}{2}\right)^2} = 2.21 \text{ dB}$$





# EX 2 - SOLUTION

①


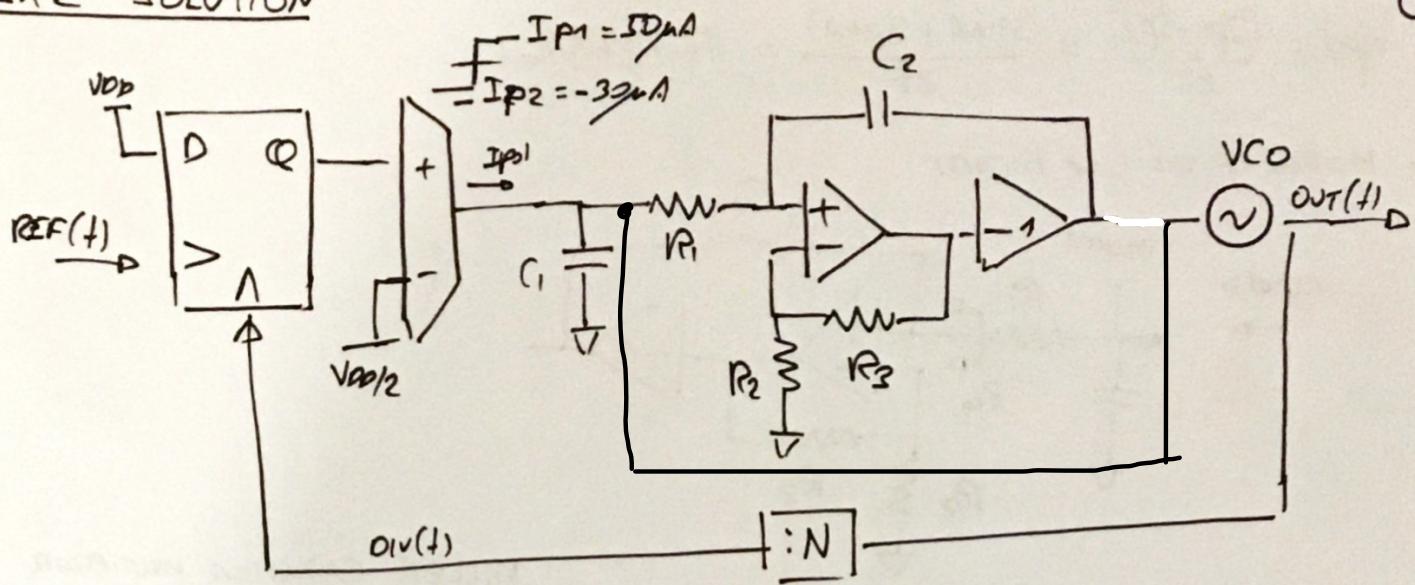


a) Eq Model im phase domain

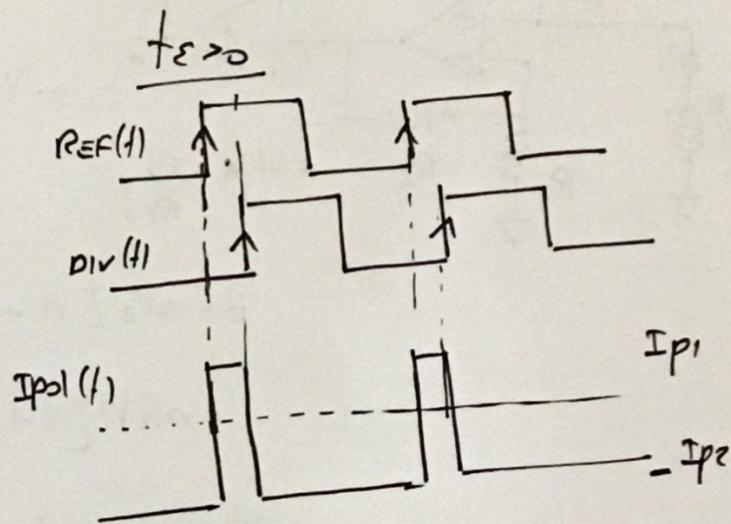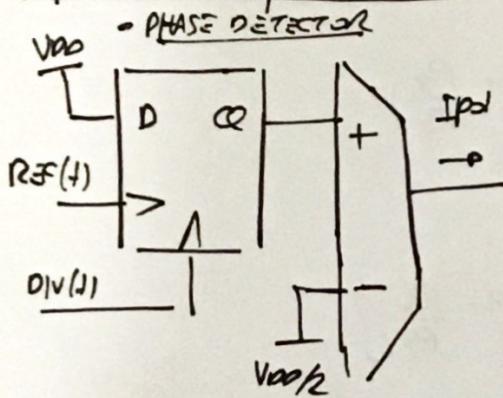

$$\langle \overline{IPD1} \rangle = \frac{1}{TR} \int_{-TR/2}^{TR/2} IPD1(t) dt \rightarrow \langle \overline{IPD1} \rangle = \frac{\pi_1 + \varepsilon}{TR} - \frac{IP2}{TR} \left[ \frac{TR - \varepsilon}{TR} \right]$$
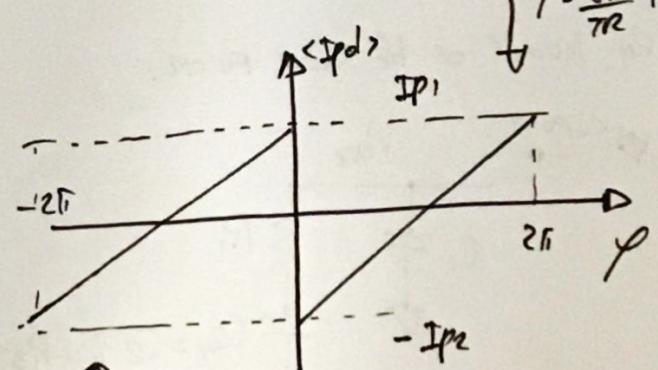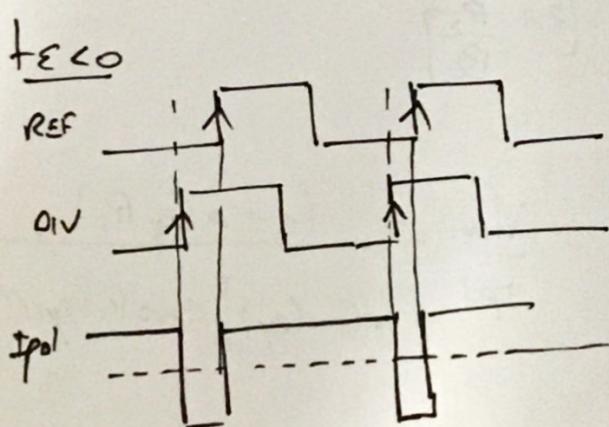
$$= (IP1 + IP2) \frac{\varepsilon}{TR} - IP2.$$




$$\langle \overline{IPD2} \rangle = -\frac{IP2 \varepsilon}{TR} + \frac{IP1 (TR - \varepsilon)}{TR}$$

$$= -(IP1 + IP2) \frac{\varepsilon}{TR} + IP1$$


$$K_{PD} = \frac{\partial \langle \overline{IPD} \rangle}{\partial \varphi} = \frac{(IP1 + IP2)}{2\pi}$$

$$K_{pd} = \frac{(I_{p1} + I_{p2})}{2\pi} = \frac{(53mA + 32mA)}{2\pi} = 12.73mA/\text{rad}$$

- MODEL OF THE LOOP FILTER:

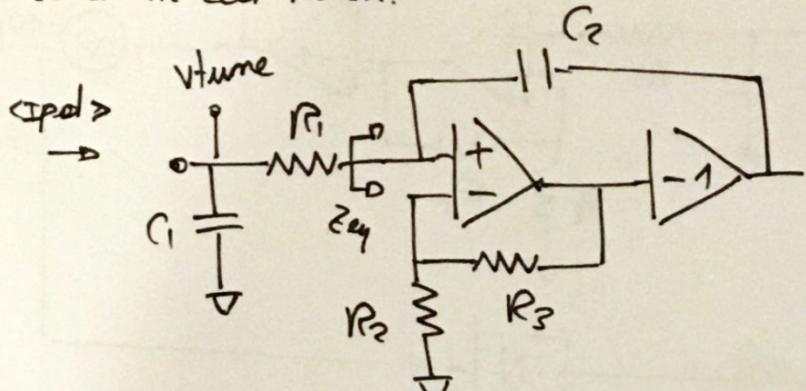

MILLER CAPACITOR MULTIPLIER

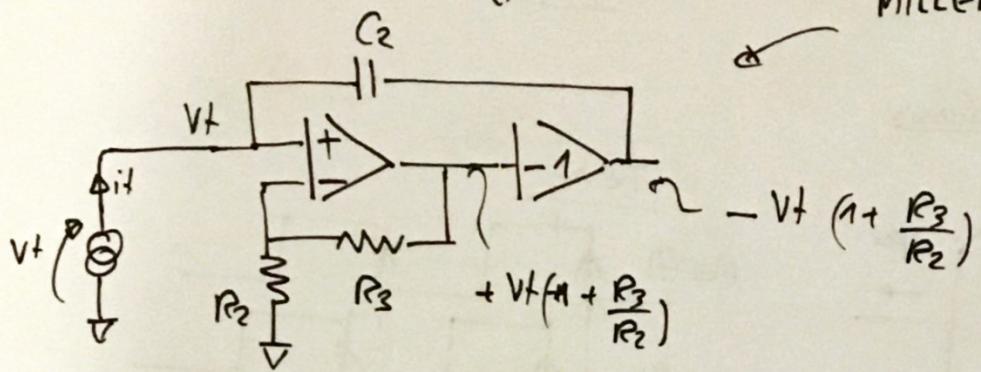


$$\begin{aligned} i_t &= nC_2 [Vt + Vt(1 + \frac{R_3}{R_2})] \\ &= nC_2 Vt [2 + \frac{R_3}{R_2}] \end{aligned}$$

$$\frac{Vt}{i_t} = \frac{1}{nC_2 [2 + \frac{R_3}{R_2}]} = \frac{1}{nC_{eq}}$$


$$C_{eq} = C_2 \left[ 2 + \frac{R_3}{R_2} \right]$$

$C_{eq}$  Model of the Loop Filter:

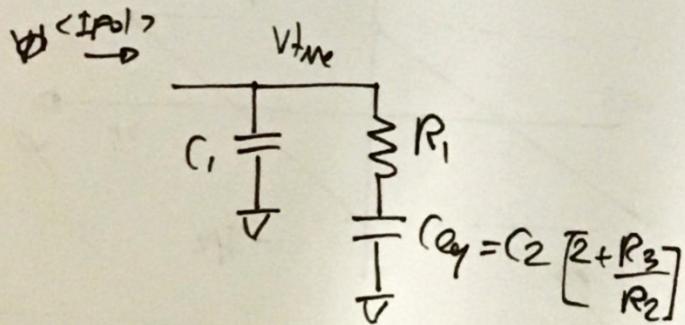

$$\frac{Vt_{me}}{I_{pd}} = \frac{(1 + nC_{eq}R_1)}{n(C_1 + C_{eq})[1 + nR_1(C_{eq}/C_1)]}$$

• COMPLETE PHASE MODEL:

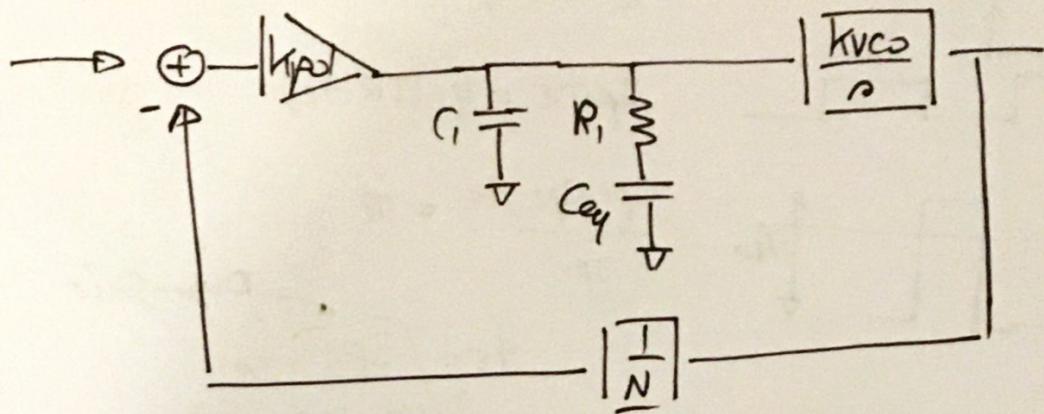

$$k_{VCO} = \frac{(2.2 - 1.8) \text{ GHz} \cdot 2\pi}{3.3V} = 761.6 \frac{\text{MHz}}{V}$$

$$G_{loop}(\omega) = k_{pd} \frac{(1 + \omega R_1 C_{eq})}{\omega(C_1 + C_{eq}) [1 + \omega R_1 (C_{eq} // C_1)]} \frac{k_{VCO}}{\omega} \frac{1}{N}$$

- $f_{WCF} = 15 \text{ kHz}$  size  $R_1$  and  $C_2, R_3$ .
- $\phi_m = 60^\circ$

$$|G_{loop}(WCF)| \approx \frac{k_{pd} R_1 k_{VCO}}{WCF \cdot N} = 1 \rightarrow \boxed{R_1 = \frac{(2\pi 15 \text{ kHz}) N}{k_{pd} k_{VCO}}} \\ = 1.94 \text{ k}\Omega$$

$$\rho_z = \frac{1}{2\pi R_1 C_{eq}}$$

$$f_p = \frac{1}{2\pi R_1 (C_{eq} // C_1)} \approx \frac{1}{2\pi R_1 C_1} = 1.023 \text{ MHz}$$

$$\phi_m = 180 - 90 - 90 + \text{atan} \left( \frac{f_{WCF}}{\rho_z} \right) - \underbrace{\text{atan} \left( \frac{f_{WCF}}{f_p} \right)}_{0.89^\circ} = 60$$

$$\rho_z = \frac{f_{WCF}}{\tan(60 + 0.89^\circ)} = 8.37 \text{ kHz}$$


$$C_{eq} = \frac{1}{2\pi f_z R_1} = 9.8 \text{ nF}$$

$$\rightarrow C_{eq} = C_2 \left[ 1 + \frac{R_3}{R_2} \right] \rightarrow \boxed{R_3 = 96 \text{ k}\Omega}$$

$$C_2 = 100 \text{ pF}$$

$$R_2 = 1 \text{ k}\Omega$$

b) TIME ERROR @ STEADY STATE:

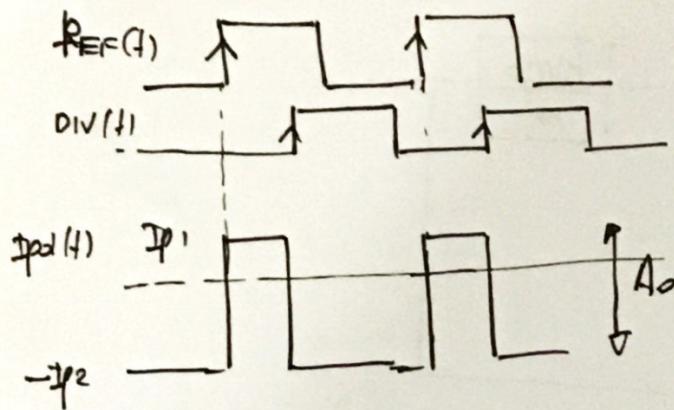

@ STEADY STATE

$$I_{pd} \cdot \varepsilon = I_p 2 (T_R - \varepsilon)$$

$$\frac{(I_p 1 + I_p 2) + \varepsilon}{I_p 2} = T_R$$

$$\varepsilon = \left( \frac{I_p 2}{I_p 1 + I_p 2} \right) T_R$$

Duty-Gross

$$= \frac{30}{80} 100 \text{ nsec} = 37.5 \text{ nsec.}$$


• FREQUENCY AND LEVEL OF THE DOMINANT SPUR.

$$I_{pd}(t) = \gamma_0 + 2|\gamma_1| \cos(\omega_{REF} t + \delta\phi_1) + \dots$$

AVERAGE =  $\gamma_0$

$$\gamma_1 = A_b \cdot \beta \sin \frac{\pi D}{\pi \beta}$$

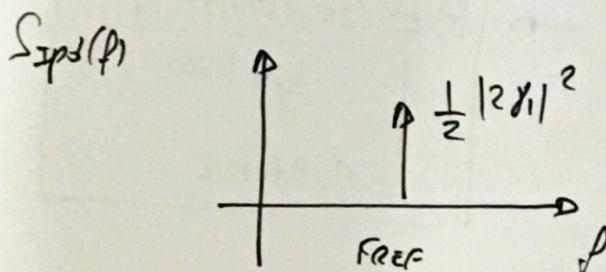
$$= (I_p 1 + I_p 2) \cdot 0.924 = 23.53 \text{ mA}$$



• OUTPUT LEVEL:


$$P(D = F_{REF}) = \frac{S_I(f_{REF})}{2} = \frac{1}{2} \left( \frac{1}{2} |2\gamma_1|^2 \right) \left| \frac{K V_C}{(2\pi f_{REF})^2 C_1} \right|^2 = -24.92 \text{ dBc.}$$

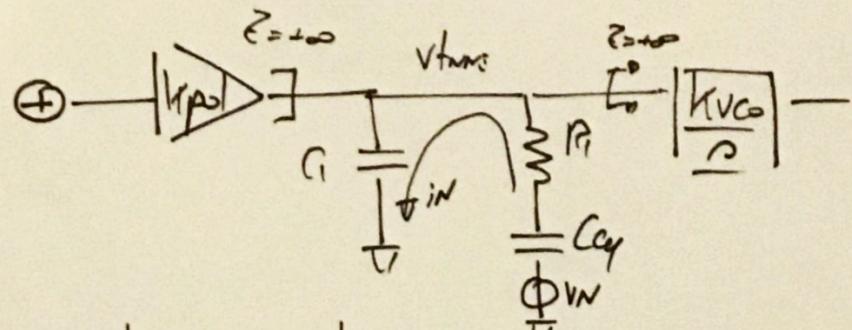c) OUTPUT PHASE NOISE DUE TO  $R_i$  THERMAL NOISE. @ 100Hz OFFSET



$$V_{TUNE} = V_N \cdot \frac{1}{\left( R_i + \frac{1}{\alpha C_1} + \frac{1}{\alpha C_{eq}} \right)} \frac{1}{2C_1} \approx \frac{1}{(1 + \alpha R_i C_1)} V_N$$

- input-referred.

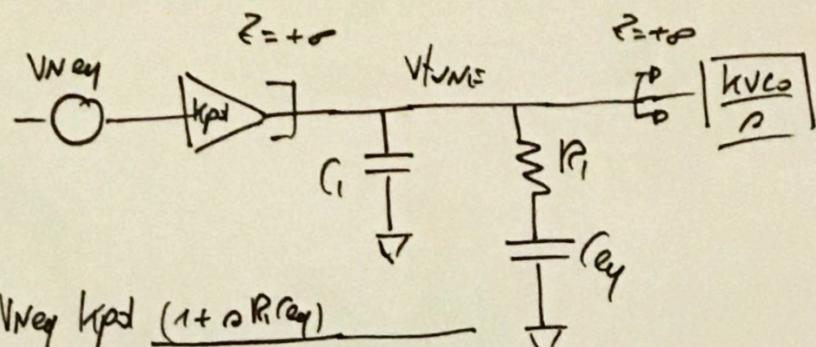


$$V_{TUNE} = V_{Ney} k_{pd} \frac{(1 + \alpha R_i C_{eq})}{\alpha (C_1 + C_{eq}) [1 + \alpha R_i (C_1 // C_{eq})]}$$

$$\approx V_{Ney} k_{pd} \frac{(1 + \alpha R_i C_{eq})}{\alpha C_{eq} [1 + \alpha R_i C_1]}$$

$$V_{Ney} = \frac{V_{TUNE} \alpha C_{eq} [1 + \alpha R_i C_1]}{k_{pd} (1 + \alpha R_i C_{eq})} = \frac{V_N \alpha C_{eq}}{k_{pd} (1 + \alpha R_i C_{eq})}$$

- Closed-loop:

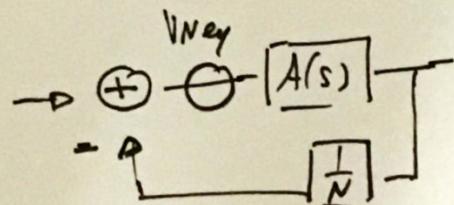

$$S_{\text{PD}}(f) = S_{\text{Ney}}(f) |T_{PL}|^2$$

@ 100Hz

$$S_{\text{PD}}(f) = 4kT R_i \frac{(2\pi/100\text{Hz})^2 C_{eq}^2}{k_{pd}^2} N^2 = -125,22 \text{ dBc/Hz}$$

