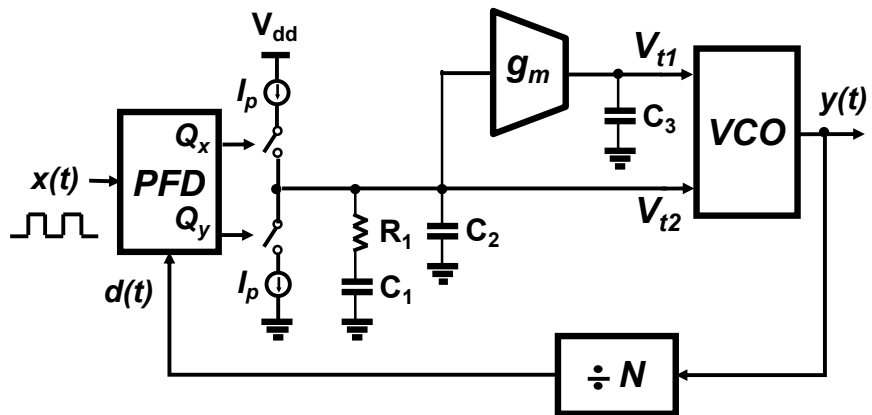


RF Circuit Design**Prof. Salvatore Levantino**Available time: 90 minutesApril 10th, 2019**Mid-term Test****Problem #1**

Assume that $x(t)$ and $d(t)$ are square-wave signals between 0V and $V_{dd} = 2.5\text{V}$, with $x(t)$ being a 20-MHz signal. The VCO has 1-GHz free-running frequency and two tuning nodes V_{t1} and V_{t2} , which vary the frequency linearly when their voltages are swept from 0V to V_{dd} .



Let $R_1 = 3\text{k}\Omega$, $C_1 = 1\text{nF}$, $C_2 = 27\text{pF}$, $N = 60$, $g_m = 10\mu\text{S}$, $K_{vco,1} = 1.3\text{ Grad}/(\text{sV})$ (from V_{t1}) and $K_{vco,2} = 330\text{ Mrad}/(\text{sV})$ (from V_{t2}).


- Calculate the **values of I_p and C_3** to have the loop-gain crossover frequency at 500kHz with 60-degree phase margin. **How do the crossover frequency and phase margin change at $g_m = 0$?**
- Calculate the values of the **tuning voltages V_{t1} and V_{t2} at steady-state**.
- Assume that the stand-alone VCO has $1/f^3$ phase noise such that $\mathcal{L}_{vco}(1\text{kHz}) = -40\text{dBc}/\text{Hz}$. For **both cases ($g_m = 10\mu\text{S}$ and $g_m = 0$)**, calculate the **value of the output phase noise $\mathcal{L}_y(1\text{kHz})$** .

[Sol.: a) $C_3 = 71\text{pF}$, $I_p = 1.2\text{mA}$; $f_u = 500\text{kHz}$, $\text{PM} = 70\text{deg}$; b) $V_{t1} = 0.97\text{V}$, $V_{t2} = 0\text{V}$; c) $\mathcal{L}_y = -167\text{dBc}/\text{Hz}$ ($g_m = 10\mu\text{S}$), $-128\text{dBc}/\text{Hz}$ ($g_m = 0$)]

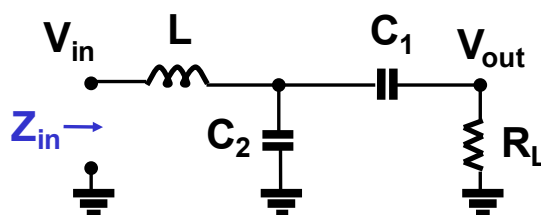Problem #2

The circuit in figure is used to transform the load impedance $R_L = 50\Omega$ to have an input impedance of $Z_{in} = 10\Omega + j0\Omega$ at $f_0 = 5\text{GHz}$ frequency.

- Find the **values of the inductance L and the capacitance $C_1 = C_2$** .
- Calculate the **gain V_{out}/V_{in} at $f = f_0$** (magnitude and phase), and estimate the **shape** of the frequency response of V_{out}/V_{in} .



[Sol.: a) $C_1 = C_2 = 0.63\text{pF}$, $L = 0.96\text{nH}$; b) $|V_{out}/V_{in}| = \sqrt{5} = 2.23$, $\text{Phase}(V_{out}/V_{in}) = -26\text{deg}$, **bandpass**]