
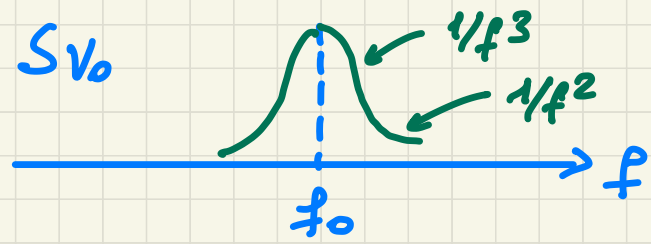


RF Circuit Design

L14

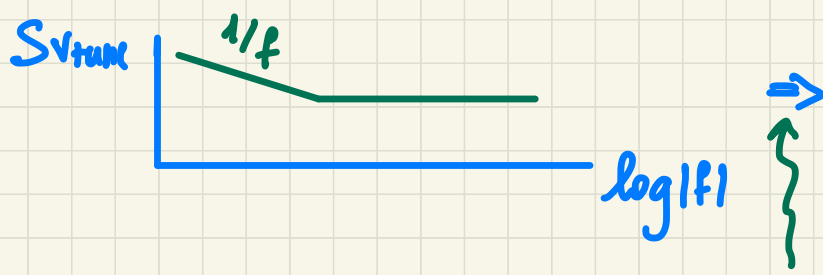




$$\mathcal{L}(f) \approx \frac{1}{2} S_{\varphi}(\omega) = \frac{1}{2} K_{VCO}^2 \cdot \frac{S_{V_{tune}}(\omega)}{\omega^2}$$

• Direct mechanism


$i_n(t)$ is noise associated to tank losses (resistor R)

$$S_{i_n}(f) = \frac{4KT}{R}$$

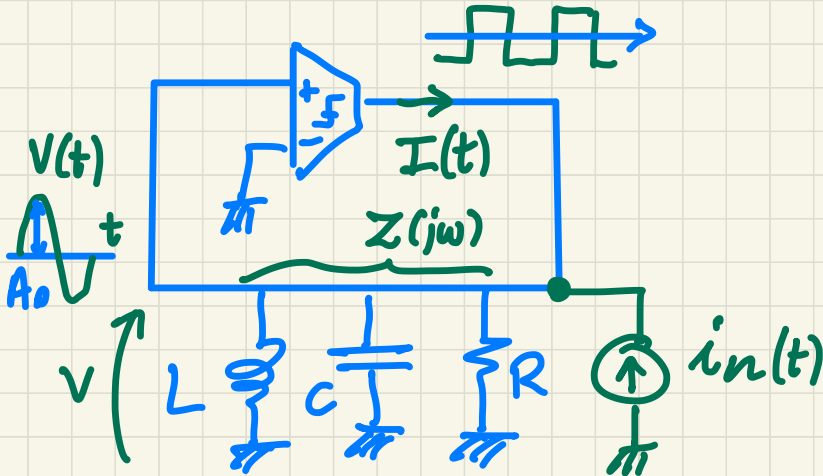

$$Z(j\omega) = R \cdot \frac{j\omega \cdot \omega_n / Q}{\omega_n^2 - \omega^2 + j\omega \frac{\omega_n}{Q}}$$

$$Q = \omega_n RC$$

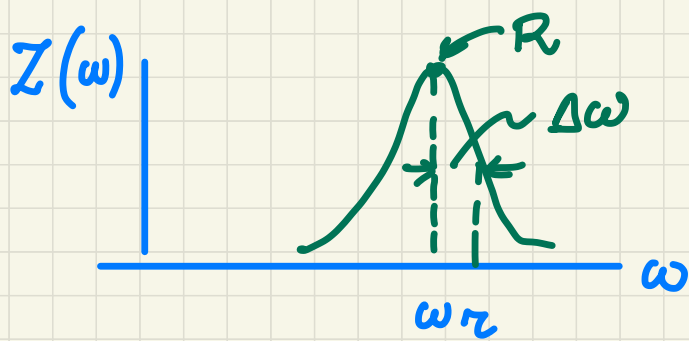

$$\omega = \omega_r \pm \Delta\omega$$

$$\begin{aligned}
 Z(j\omega_r \pm j\Delta\omega) &= R \cdot \frac{j(\omega_r \pm \Delta\omega)\omega_r/Q}{\cancel{\omega_r^2} - (\omega_r \pm \Delta\omega)^2 + j(\omega_r \pm \Delta\omega)\frac{\omega_r}{Q}} = \\
 &\quad -(\cancel{\omega_r^2} + \Delta\omega^2 \pm 2\omega_r\Delta\omega) = \\
 &\quad = -\Delta\omega \cdot (\Delta\omega \pm 2\omega_r) \\
 &= R \cdot \frac{1}{1 + j \frac{\Delta\omega}{\frac{\omega_r}{Q}} \cdot \underbrace{\frac{\Delta\omega \pm 2\omega_r}{\omega_r + \Delta\omega}}_{\approx \pm 2}}
 \end{aligned}$$



тип: $\Delta\omega \ll \omega_r$

$$\Rightarrow Z(j\omega_c \pm j\Delta\omega) \simeq \frac{R}{1 \pm j \cdot \frac{\Delta\omega}{\frac{\omega_c}{2Q}}} = \frac{R}{1 \pm j 2RC \cdot \Delta\omega} =$$

a. frequency offset
from the
carrier

$$\triangleq Z'(\pm j\Delta\omega)$$

$$|Z'(j\Delta\omega)|$$

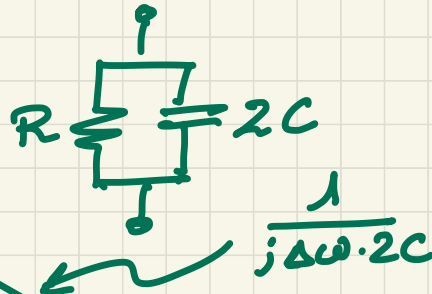
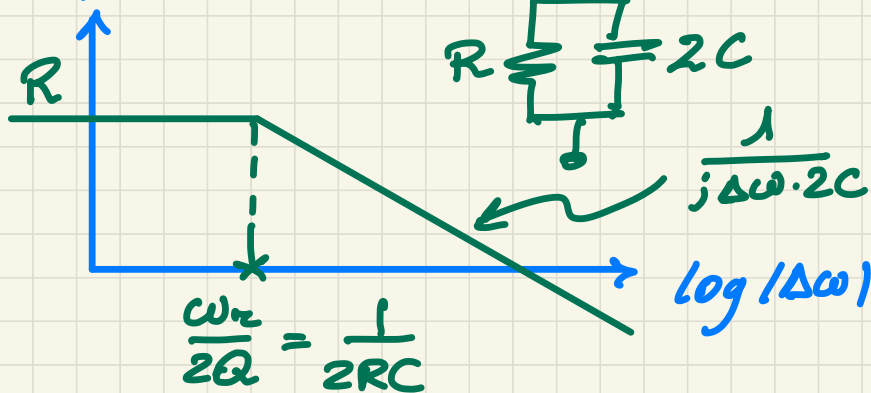


$$Q = \omega_c RC$$

\Downarrow

$$\frac{\omega_c}{2Q} = \frac{1}{2RC}$$

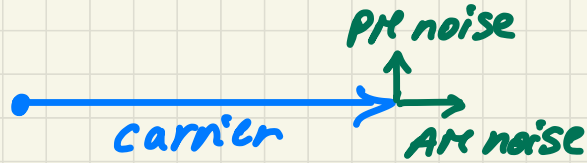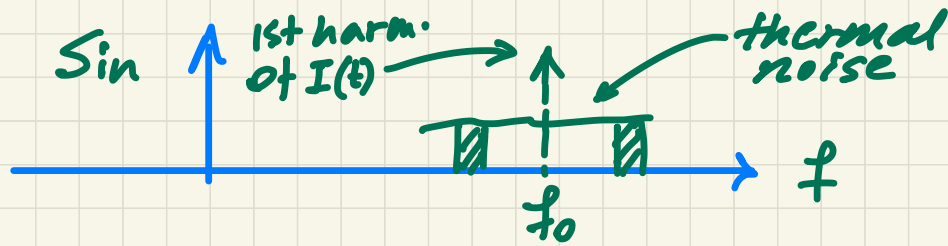Baseband equivalent of $Z(j\omega)$ of a RLC resonator
around resonance




in phase with the carrier

$$S_{inAM} = \frac{2kT}{R}$$


in quadrature with the carr.

$$S_{inPM} = \frac{2kT}{R}$$


• AM component:

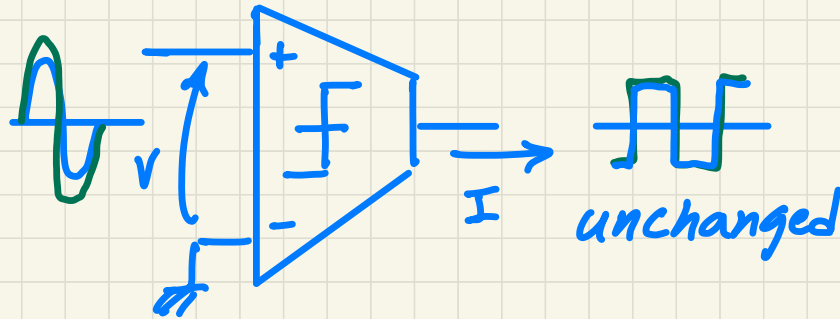





$$Z_{AM}(\omega) = Z(\omega)$$

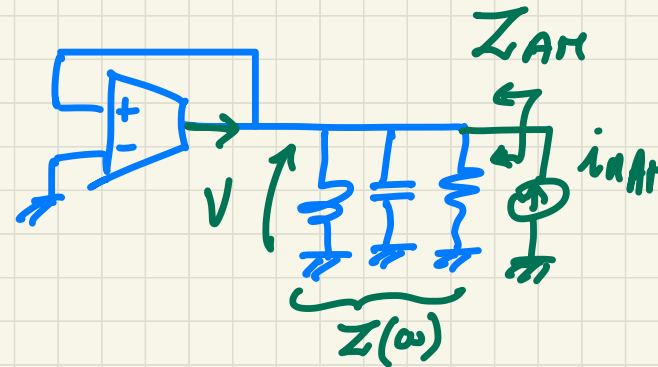

- PM component of noise

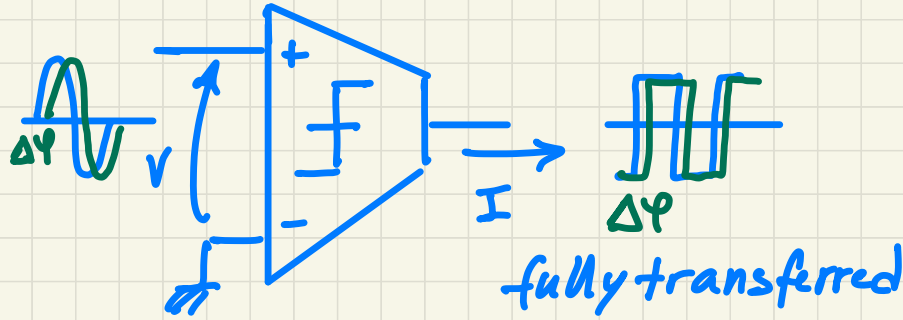

$$Z_{PM}(\omega) = Z(j\omega) \big|_{R \rightarrow \infty}$$

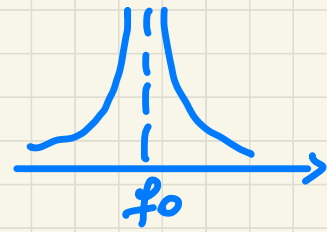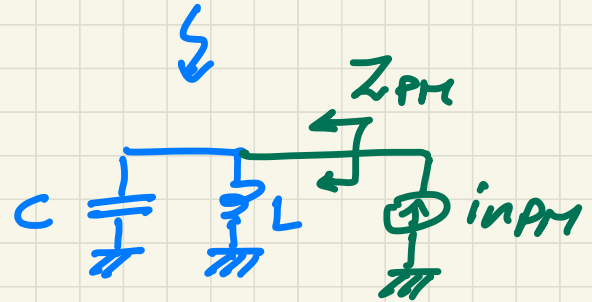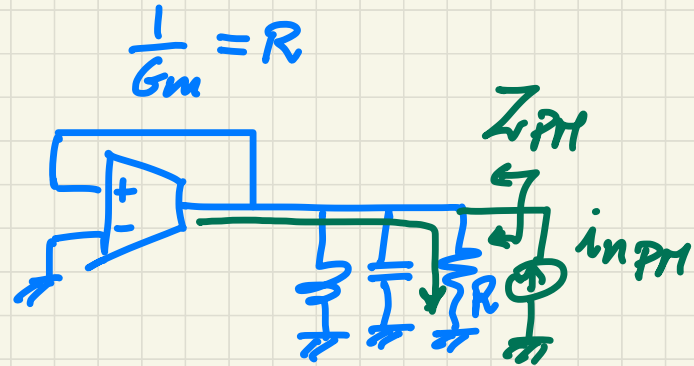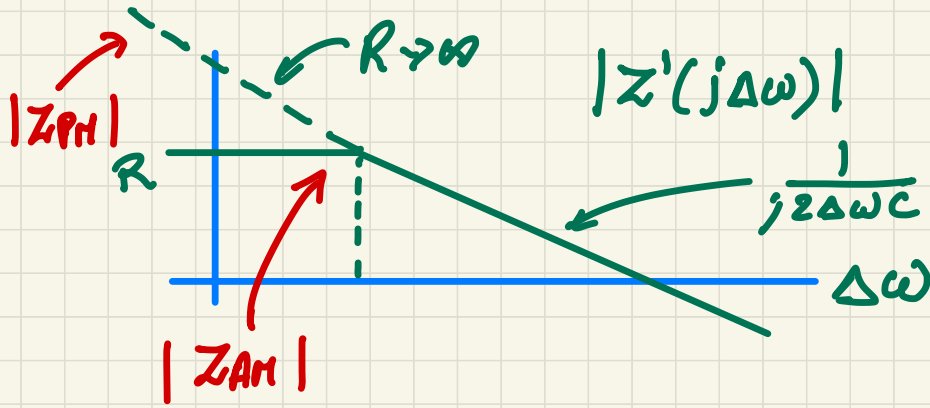

$$\leadsto S_V(\omega) = \frac{2KT}{R} \cdot |Z_{AM}(\omega)|^2 + \frac{2KT}{R} \cdot |Z_{PM}(\omega)|^2$$

$$\Delta\omega \ll \frac{\omega_c}{2Q}$$

$$\begin{aligned} Z_{AM}(\omega_c \pm \Delta\omega) &\approx R \\ Z_{PM}(\omega_c \pm \Delta\omega) &\approx \frac{1}{\pm j 2\Delta\omega C} \end{aligned}$$

$$F_a = \frac{S_{Va}}{S_{Vn}}$$

$$\Downarrow$$

$$S_V(\omega_c \pm \Delta\omega) \approx \frac{2KT}{R} \cdot R^2 + \frac{2KT}{R} \cdot \frac{1}{\Delta\omega^2 C^2} =$$

$$= 2KTR + \frac{KT \cdot R \cdot \omega_c^2}{2R \Delta\omega^2 C^2 \cdot R \cdot \omega_c^2} =$$

negligible Q^2

$$Q = \omega_c RC$$

$$= \underbrace{2KTR}_{\text{AM noise}} + \underbrace{\frac{1}{2} \cdot KT \cdot R \cdot \left(\frac{\omega_c}{Q}\right)^2 \cdot \frac{1}{\Delta\omega^2}}_{\text{PM noise}} \cdot F_a$$

accounts for
active
elem.
noise

$$\Rightarrow \mathcal{L}(\Delta\omega) \triangleq \frac{S_V(\omega_c + \Delta\omega)}{P_{\text{carrier}}} \approx \text{[dBc/Hz]}$$

Phase noise of oscillator

$$\approx \frac{\frac{1}{2} kT \cdot \left(\frac{\omega_c}{Q}\right)^2 \cdot R \cdot \frac{1}{\Delta\omega^2} \cdot F_a}{\frac{A_0^2}{2}} =$$

A_0 amplitude of $V(t)$

$$= \frac{kT}{2P_R} \cdot \left(\frac{\omega_c}{Q}\right)^2 \cdot \frac{1}{\Delta\omega^2} \cdot F_a$$

$P_R = \frac{A_0^2}{2R}$ [W]
power diss. in the reson.

$$P_R = \eta \cdot P_{\text{DC}} \quad \eta \triangleq P_R / P_{\text{DC}}$$

DC power from supply

$0 \leq \eta \leq 1$
Efficiency

$$\underline{L(\Delta\omega)} = \frac{kT}{2\eta \underline{P_{DC}}} \cdot \left(\frac{\omega_{osc}}{Q} \right)^2 \cdot \frac{1}{\Delta\omega^2} \cdot F_a$$

expresses the trade-off between phase noise and dissipated power

Define: Figure of merit of oscillators

$$FoM_{dB} \triangleq 10 \log_{10} \left\{ \frac{1}{L(\Delta\omega) \cdot \underline{P_{DC, mW}}} \cdot \left(\frac{\omega_{osc}}{\Delta\omega} \right)^2 \right\}$$

$$\Rightarrow FoM_{dB} = 10 \log_{10} \left\{ \frac{\left(\cancel{\omega_{osc}} / \cancel{\Delta\omega} \right)^2}{\frac{kT}{2\eta} \frac{1}{\cancel{P_{DC}}} \cdot \left(\frac{\cancel{\omega_{osc}}}{Q} \right)^2 \cdot \frac{1}{\cancel{\Delta\omega^2}} \cdot F_a \cdot \cancel{P_{DC, mW}}} \right\} =$$

10^3

$$FOM_{dB} = 10 \log_{10} \left\{ 10^{-3} \cdot \frac{2\eta}{kT} \cdot Q^2 \cdot \frac{1}{F_a} \right\}$$

thermodynamic limit of FOM of oscillators :

- ideally : $\eta = 1$
 - ideally : $F_a = 1$
(only thermal noise of the resonator)
 - assume : $Q = 10$
- $\Rightarrow FOM_{max} =$
- $$= 10 \log_{10} \left\{ \frac{2}{kT} \cdot Q^2 \right\} - 30 =$$
- $$= 197 \text{ dB/Hz}$$

e.g. $f_{osc} = 1 \text{ GHz}$

$\Delta f = 1 \text{ MHz}$

$P_{DC} = 1 \text{ mW}$

$Q = 10$

$$L_{min}(\Delta f) = \frac{1}{FOM_{max}} \cdot \frac{1}{P_{DC, mW}} \cdot \left(\frac{f_{osc}}{\Delta f} \right)^2$$

$$\Downarrow$$

$$-FOM_{max} - 10 \log_{10} P_{DC, mW} + 20 \log \frac{f_{osc}}{\Delta f}$$


$$= -197 \text{ dB} - 0 \text{ dBm} + 60 = -137 \text{ dBc/Hz}$$

Circuit Simulators (e.g. Cadence Spectre Mentor Eldo ...)

- DC DC analysis bias point (non linear)
- AC AC analysis transfer functions (Linear*)
- NOISE NOISE analysis based on AC (Linear*)
 - ↖ LTI approximation
 - * nonlinear devices are replaced by equivalent linear circuits
- TRAN TRANSIENT analysis transient behavior (nonlinear)
- NOISETRAN noise sources does not account for noise sources
 - one modelled as random sequences
 - needs many runs to get statistics
 - time consuming

RF circuit simulators (e.g. Spectre RF
Eldo RF
...)

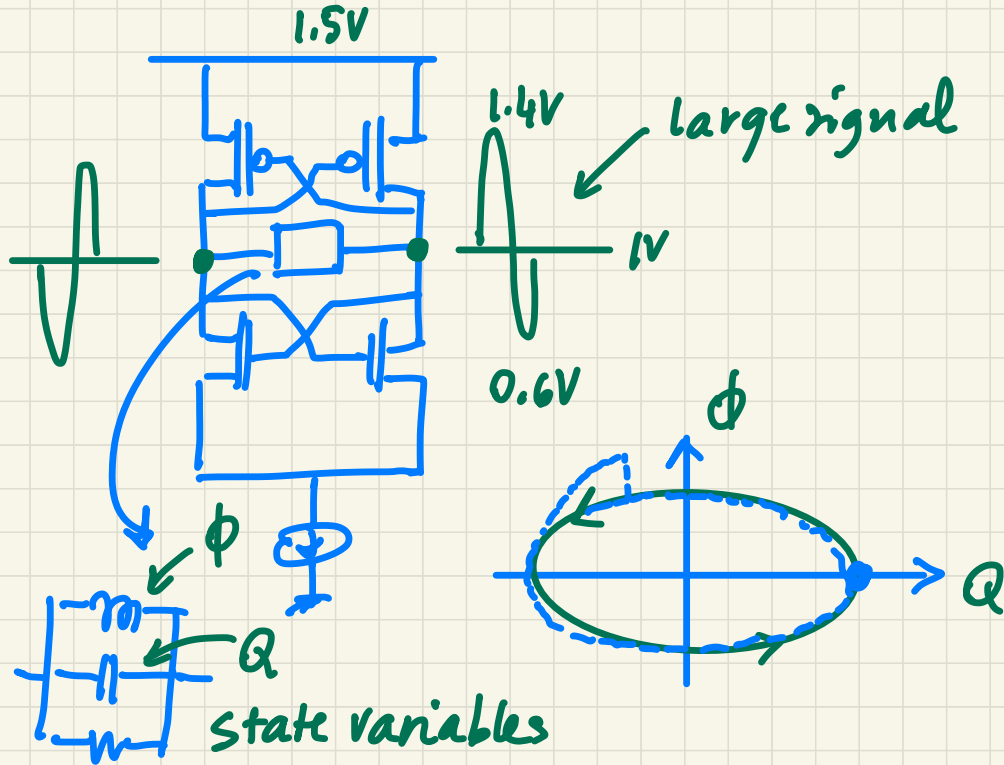• PSS periodic steady state analysis non-linear



$$V_1(t+T_0) = V_1(t)$$

$$V_2(t+T_0) = V_2(t)$$

⋮

For every voltage
and current
→ find T_0

• PAC

periodic AC analysis

transfer functions
of small-signal
perturbations

→ LTV approximation
(linear time-variant)

• PNOISE periodic noise analysis

Design of an LC oscillator

MOS devices:


$$V_T = 0.35V$$

$$\mu_n C_{ox} = 120 \mu A/V^2$$

$$\mu_p C_{ox} = 60 \mu A/V^2$$

Specifications:

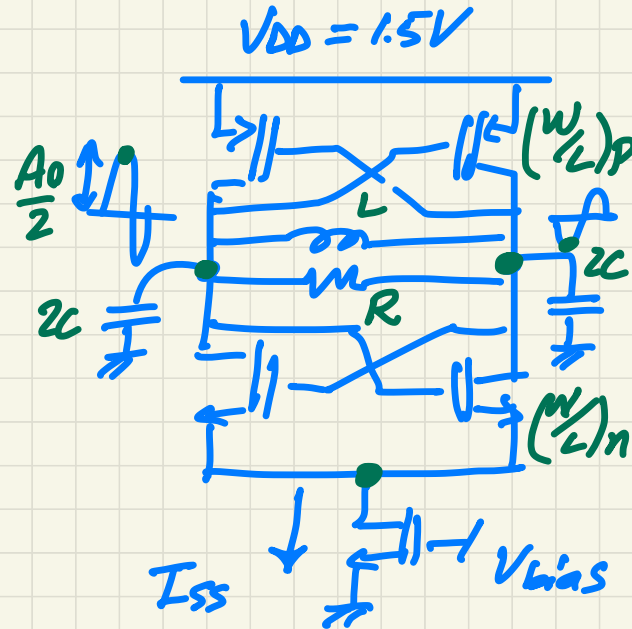- $f_0 = 1.5 GHz$
- $Q = 20$
- $I_{SS} = 3 \mu A$
- max. FoM



Unknowns : $(W/L)_n$, $(W/L)_p$, R , L , C , A_0 , L

Design ① Startup : $LG(j\omega_0) = EG$

$$G_m R = EG > 1$$

We choose Excess gain $EG = 5$

② $\max FOM \div \frac{2\eta}{kT} \cdot Q^2 \Leftrightarrow \max. \eta$


$$\eta = \frac{P_R}{P_{DC}} = \frac{A_0^2 / 2R}{I_{SS} \cdot V_{DD}} \Leftrightarrow \max. A_0$$

Oscillation amplitude : $\frac{4}{\pi} \cdot \frac{I_{SS}}{A_0} R = 1$;


$$G_{mH} \cdot R = 1$$

$$A_0 = \frac{4}{\pi} I_{SS} \cdot R$$

** only in current-limit

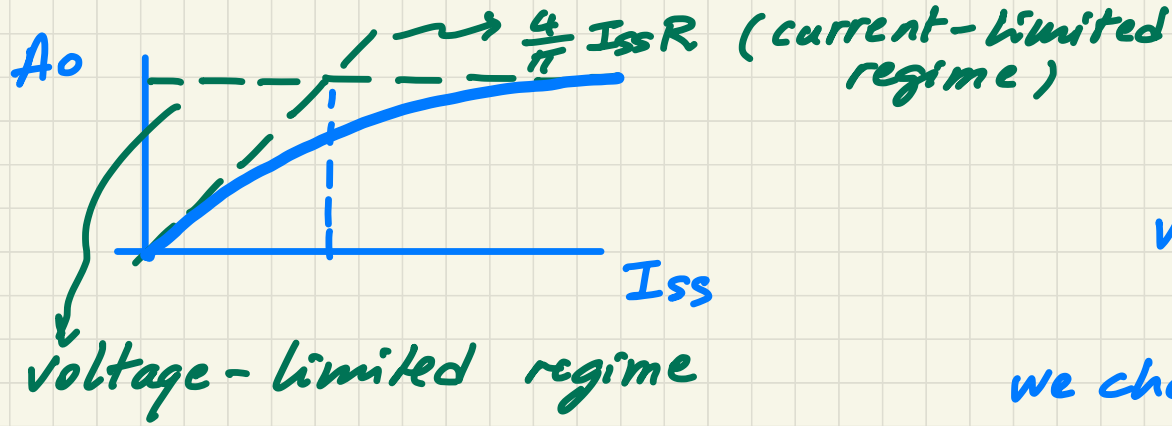

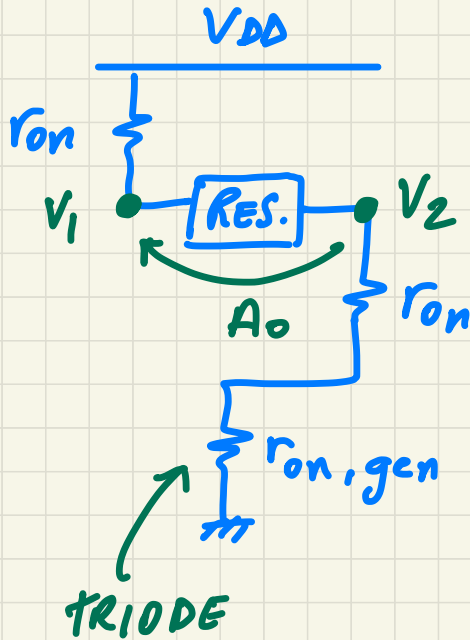$V_{DD} = 1.5V$
 \downarrow
 we choose $A_0 = 0.9V$



$$A_0 \approx V_{DD} \cdot \frac{R}{R + 2r_{on} + r_{on,gen}}$$

In a Spreadsheet :

Data

f_0	1.5 GHz
Q	10
V_{DD}	1.5 V
μC_{ox}	$\left\{ \begin{array}{l} 120 \\ 60 \end{array} \right. \mu A/V^2$
V_T	0.35 V
I_{SS}	3 mA
• E_G	5
• A_0	0.9 V

$$Q = \frac{R}{\omega_0 L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Equations

$$R = \frac{\pi}{4} \frac{A_0}{I_{SS}} \quad 236 \Omega$$

$$L = \frac{R}{\omega_0 Q} \quad 1.25 \text{ nH}$$

$$C = \frac{1}{\omega_0^2 L} \quad 9 \text{ pF}$$

$$G_m = E_G \cdot \frac{1}{R} \quad 2.12 \frac{\text{mA}}{\text{V}}$$

$$G_m = \frac{g_{mn} + g_{mp}}{2}$$

$$\text{Hyp. } g_{mn} = g_{mp} = g_m \Rightarrow G_m = g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_{ss/2}} \quad \underbrace{\frac{W}{L} I_{ss/2}}_{\text{DC cur.}}$$

$$\left(\frac{W}{L}\right)_n = \frac{g_m^2}{2 \mu_n C_{ox} I_{ss/2}} \quad 1250$$

$$\left(\frac{W}{L}\right)_p = \frac{g_m^2}{2 \mu_p C_{ox} I_{ss/2}} \quad 2500$$

MOSFET length
 $L = 60 \text{ nm}$

$$W_n \quad 75 \mu\text{m}$$

$$W_p \quad 150 \mu\text{m}$$

$$\mathcal{L}(\Delta\omega) = 10 \log_{10} \left\{ \frac{\overbrace{KT \cdot R}^{4 \cdot 10^{-21} \text{ J}}}{A_0^2} \cdot \frac{\omega_0^2}{Q^2} \cdot \frac{1 \cdot F_a}{\Delta\omega^2} \right\}^1$$

\uparrow
 $2\pi \cdot 1 \text{ M rad/s}$

-142 dBc/Hz

Exercise :

- calculate the power efficiency η
- calculate the FoM