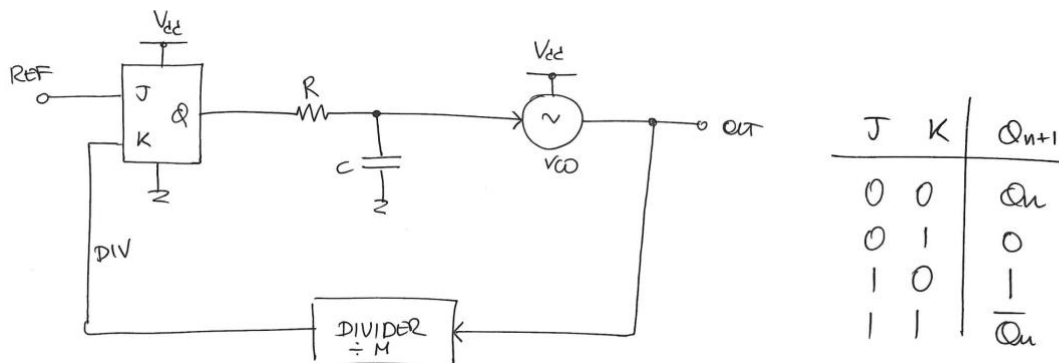


RF Circuit Design**Prof. Salvatore Levantino**Available time: 75 minutesMay 2nd, 2018**Mid-term Test****Exercise 1**

In the PLL in figure, the JK latch (a.k.a. “level-triggered” flip-flop) has CMOS levels 0V and $V_{DD} = 1.2V$, zero output impedance, and truth table shown below. Let the REF signal be a squarewave with frequency $f_{ref} = 10$ MHz, the frequency-division factor $M = 100$, and let the VCO have free-running frequency 957MHz and linear tuning range over input voltage between 0V and V_{DD} .




- Calculate and plot the **voltage-vs-phase characteristic of the JK latch** and calculate its **gain**.
- Set the **value of R , C , and VCO tuning range** to get (i) closed-loop poles at 100kHz, (ii) maximally flat PLL input-output frequency response, (iii) contribution of R thermal noise to the output phase noise \mathcal{L} equal to -146dBc/Hz at 1MHz offset.
- Calculate the **time delay (in seconds)** between two positive edges of REF and DIV signals at steady state, and the **level of the reference spur** in the output spectrum (in dBc).

[Sol: a) PD gain = 0.19 V/rad; b) $R = 11$ k Ω , $C = 100$ pF, $TR = 44.3$ MHz; c) Delay = 96 ns; Spur at 10MHz offset = -54 dBc]

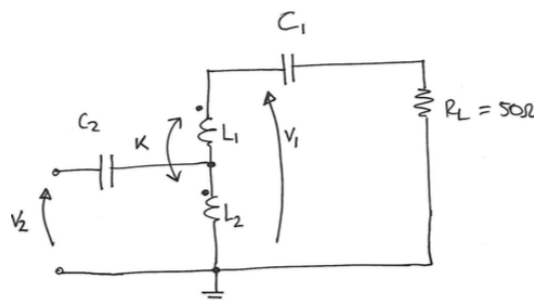Exercise 2


The circuit in figure is used to transform the impedance $R_L = 50\Omega$. Given $C_1 = 1$ pF, $L_1 = 0.8$ nH, find the **values of L_2 , k , C_2** to have an input impedance of $Z_{in} = 5\Omega + j0\Omega$ at 5GHz frequency.




[Sol: $L_2 = 317$ pH, $k = 0.43$, $C_2 = 3.78$ pF]

EX.




JK level-triggered FF $0, V_{DD} = 1.2V$

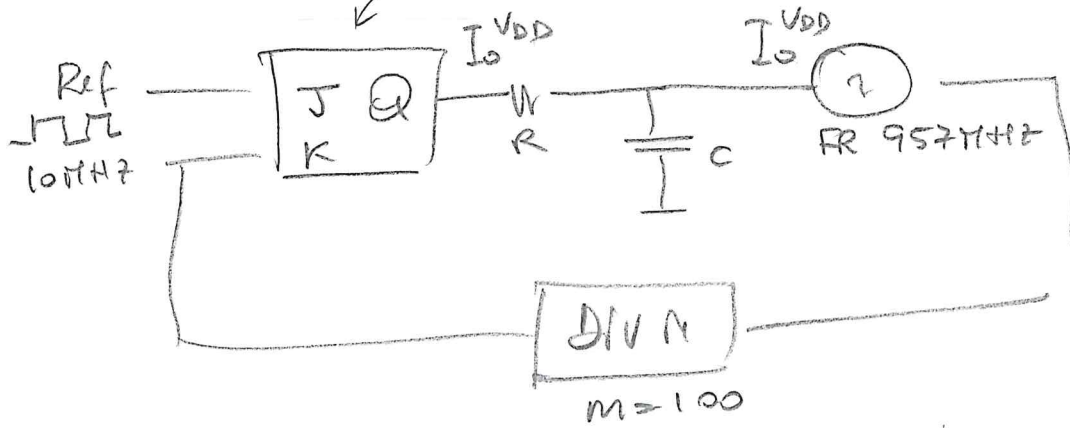

JK	Q_{n+1}
00	Q_n
01	0
10	1
11	\bar{Q}_n

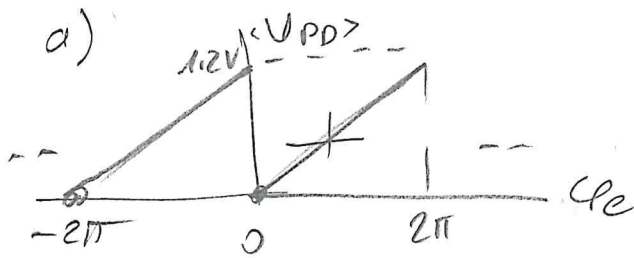
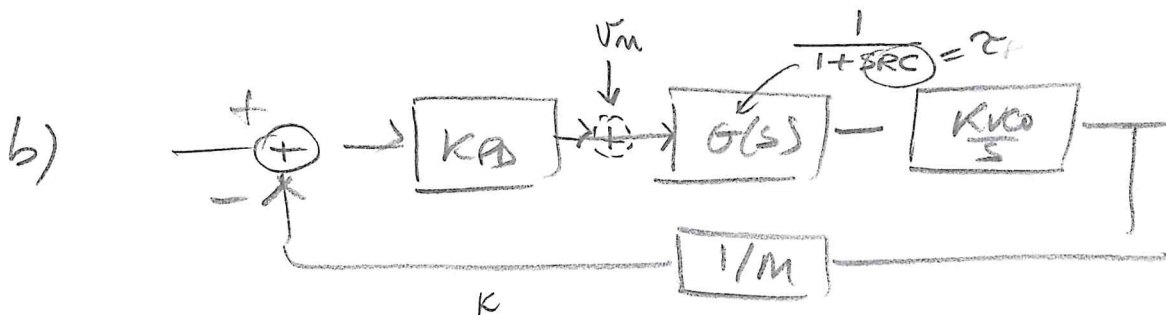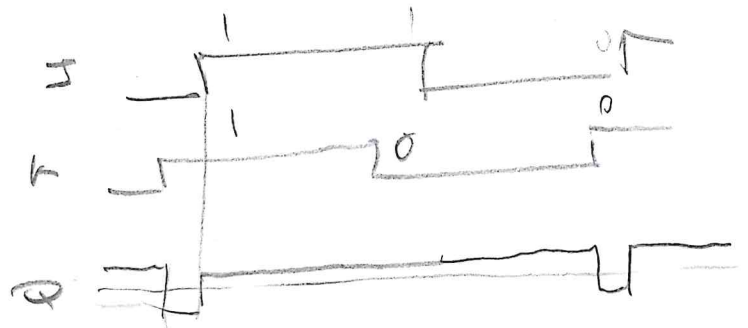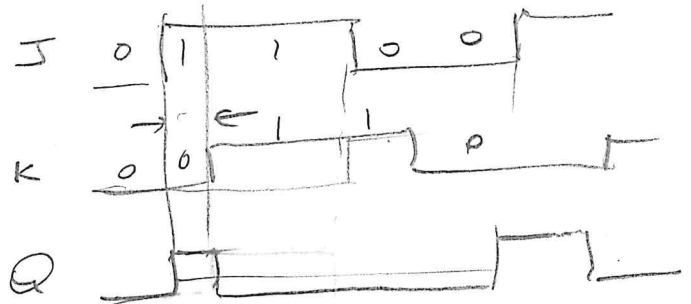
$$\text{Gain } K_{PD} = \frac{V_{DD}}{2\pi} = \frac{1.2}{6.28} = 0.19 \frac{V}{\text{rad}}$$



$$LG = \left(K_{PD} \cdot \frac{K_{VCO}}{s} \cdot \frac{1}{M} \right) \cdot \frac{1}{1+s\tau}$$


$$1 + LG = 0 \quad ; \quad 1 + \frac{K}{s^2} + \frac{2\zeta}{s} + 1 = 0$$

$$\omega_P = \sqrt{\frac{K}{\tau}}$$

$$\zeta = \frac{1}{2\sqrt{K\tau}} = \frac{\sqrt{2}}{2} \Rightarrow K = \frac{1}{2\tau} \Rightarrow \omega_P = \sqrt{2} \cdot K$$

$$(i) f_P = \frac{\sqrt{2} \cdot K_A K_{VCO}}{2\pi m} = 100 \text{ K}$$
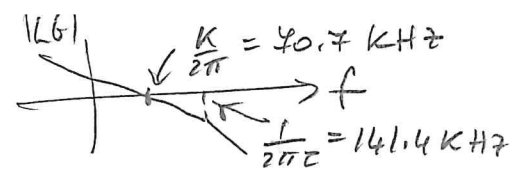
$$\Rightarrow K_{VCO} = \frac{2\pi \cdot 100 \text{ K} \cdot 100}{0.19 \cdot \sqrt{2}} = 23.37 \cdot 10^7 \frac{\text{rad}}{\text{Vs}}$$



$$K_{VCO} = 2\pi \cdot \frac{TR}{V_{DD}} \Rightarrow TR = \frac{K_{VCO}}{2\pi} \cdot V_{DD} =$$

$$= \frac{23.37 \cdot 10^7}{6.28} \cdot 1.2 =$$

$$= 44.66 \text{ MHz}$$

$$(iii) \frac{\varphi_{out}}{v_n}(s) = \frac{G(s) \cdot K_{VCO}/s}{1 + LG(s)}$$

$$\text{at } f = 1 \text{ MHz: } \left| \frac{\varphi_{out}(f)}{v_n} \right| \approx \frac{|G(f)| K_{VCO}}{2\pi f} =$$

$$= \sqrt{\frac{1}{1 + (2\pi f \tau)^2}} \frac{K_{VCO}}{2\pi f}$$

$$(iv) \tau = \frac{1}{2\pi K} =$$

$$= \frac{1}{2 \cdot 464 \text{ K}} =$$

$$= 1.126 \mu$$

$$\downarrow$$

$$141.4 \text{ K}$$

$$L = \frac{S_{out}}{2} = \frac{1}{2} \left| \frac{\varphi_{out}}{v_n} \right|^2 \cdot S_{vn} =$$

$$= \frac{1}{2} \cdot \frac{1}{1 + (2\pi f \tau)^2} \cdot \left(\frac{K_{VCO}}{2\pi f} \right)^2 \cdot 4kTR =$$

$$= \frac{1}{2} \cdot \frac{1}{51} \cdot \left(\frac{23.37 \cdot 10^7}{6.28 \cdot 10^6} \right)^2 \cdot 16 \cdot 10^{-21} \cdot R = 10^{-14.6}$$

$$R = \frac{10^{-14.6}}{10^{-21}} \cdot \frac{2 \cdot 51}{16} \cdot \frac{1}{1385} = 11.56 \text{ K}\Omega$$

$$\Rightarrow C = \frac{1.126 \mu}{11.56 \text{ K}} = 9.7 \text{ fF}$$

c) Delay


$$f_{out} = M \cdot f_{ref} = 10 \text{ MHz}$$

$$\Delta f = f_{out} - f_{ref} = 1000 - 957 = 43 \text{ MHz}$$

$$V_{tune} = \frac{2\pi \cdot \Delta f}{K_{VCO}} = 1.155 \text{ V}$$

$$\varphi_E = \frac{V_{tune}}{K_{PD}} = \frac{1.155}{0.19} = 6.079 \text{ rad}$$
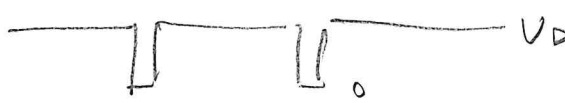
$$t_E = \frac{\varphi_E}{2\pi} \cdot T_R = \frac{6.079}{6.28} \cdot 100 \text{ ns} = \underline{96.8 \text{ ns}}$$



$$\Rightarrow \frac{2}{\pi} \cdot \Delta \cdot \sin \pi D$$

$$\frac{6.079}{6.28} = 96.8\%$$

$$78 \text{ mV} = V_{PD}$$

$$L_{SPUR} = \frac{S_{\varphi_{out}}}{2} = \frac{\Delta\varphi^2/2}{2} =$$

$$= \frac{1 \cdot K_{VCO}^2}{4 (2\pi f_{SPUR})^2} \cdot |G|^2 \cdot V_{PD}^2 =$$

$$= \frac{1}{4} \cdot \left(\frac{23.37 \cdot 10^7}{6.28 \cdot 10^7} \right)^2 \cdot \left(\frac{1}{2\pi \cdot 10^7 \cdot 1.126 \cdot 10^{-6}} \right)^2 \cdot (78 \text{ m})^2 =$$

$$= \left(\frac{1}{2} \cdot 3.72 \cdot 0.014 \cdot 0.078 \right)^2$$

$$\Rightarrow 20 \log_{10} (0.002) = -53.75 \text{ dBc}$$