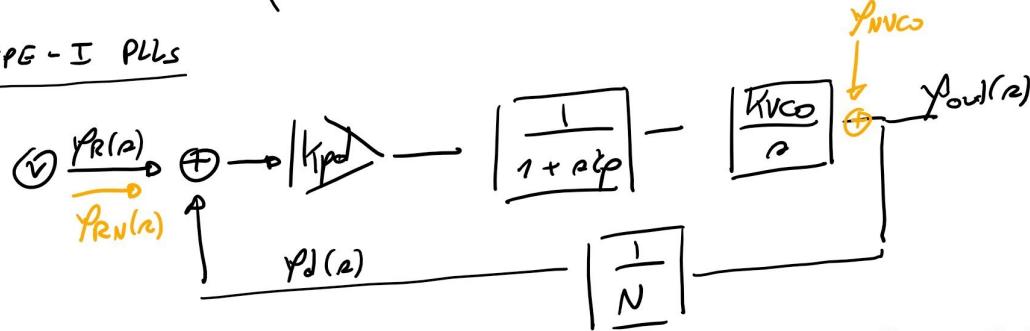


TYPE-II PLLS

- ISSUES OF TYPE-I PLLS
- TRI-STATE PHASE DETECTOR (PFD)
- CP-PLL

ISSUES OF TYPE-I PLLS




$$G_{\text{Loop}}(s) = K_{pd} \frac{1}{(1 + \alpha s)} \frac{K_{VCO}}{N} \quad \# \text{ TYPE-I SYSTEM} = 1 \text{ POLE IN ORIGIN}$$


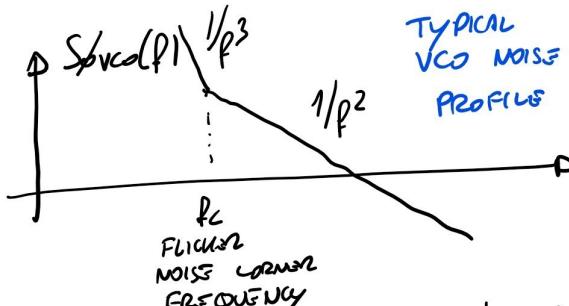
1) LIMITED VCO-NOISE FILTERING

$$\frac{V_{out}(s)}{V_{RN}(s)} = N T(s) = N \frac{G_{\text{Loop}}(s)}{(1 + G_{\text{Loop}}(s))}$$

$$\frac{V_{out}(s)}{V_{VCO}(s)} = 1 - T(s) = \frac{1}{1 + G_{\text{Loop}}(s)}$$




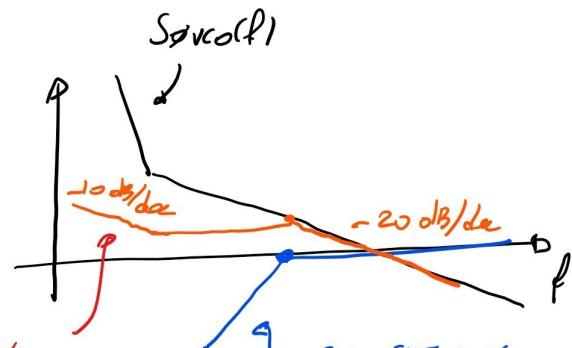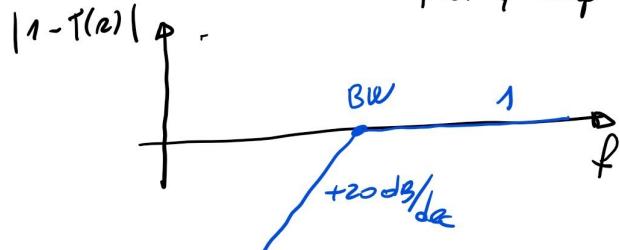IF we apply PLL FILTERING to \$S_{VCO}(f)\$



Star PLL (D)
due to VCO

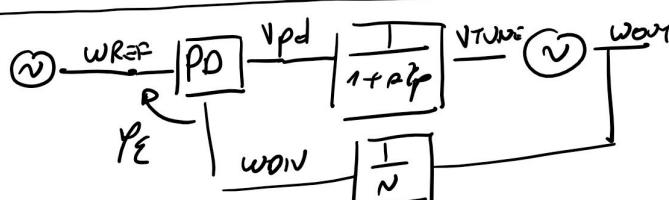2) STATIC PHASE ERROR @ PHASE DETECTOR INPUT




@ STEADY STATE

$$\begin{aligned} @ \text{STEADY STATE} \\ W_{OUT} &= N W_{REF} \\ &= W_{REF} + K_{VCO} \cdot V_{VCO} \end{aligned}$$

$$\Rightarrow V_{PE} = V_{VCO} = K_{pd} V_{PE}$$



$$V_{PE} = \frac{(N W_{REF} - W_{REF})}{K_{VCO} \cdot K_{pd}}$$

\$V_{PE}\$ is parameter dependent

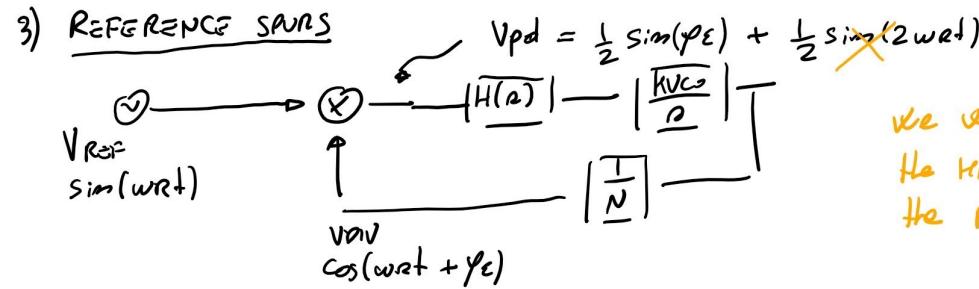

We want to remove the HF component from the PD output.

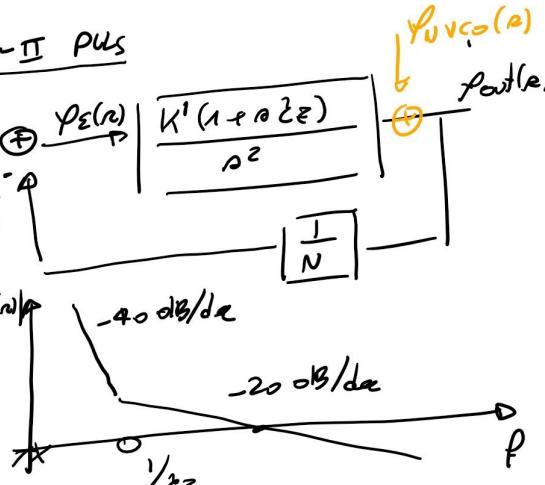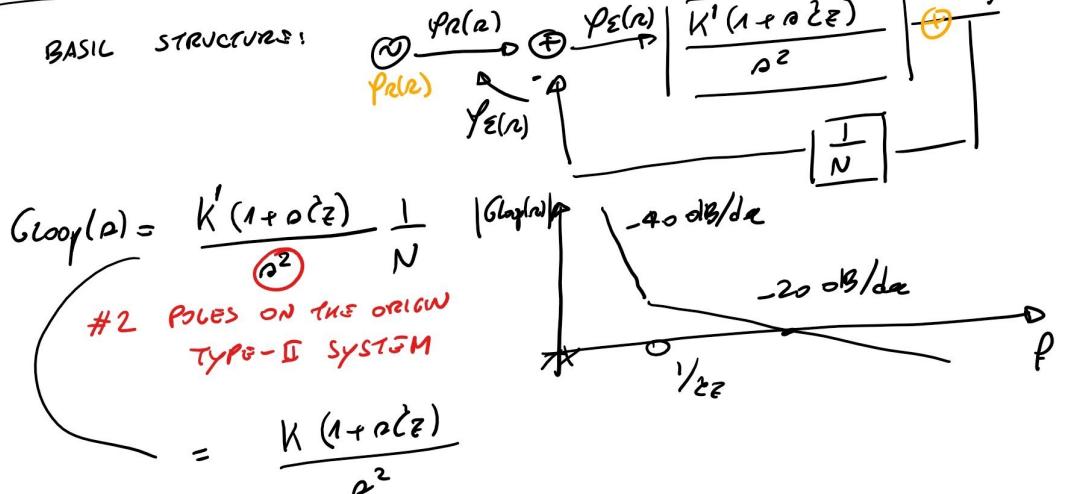- To solve these issues we move Type-II PLS





FEATURES:

1) BETTER VCO NOISE FILTERING

$$\frac{V_{out}(s)}{V_{VCO}(s)} = 1 - T(s) = \frac{1}{1 + G_{loop}(s)} = \frac{1}{1 + \frac{K(1+\alpha^2\zeta)}{\alpha^2}} = \frac{\alpha^2}{\alpha^2 + \alpha^2\zeta + K}$$

CONSIDER NOW THE FILTERING OF VCO NOISE: $|1 - T(s)|$

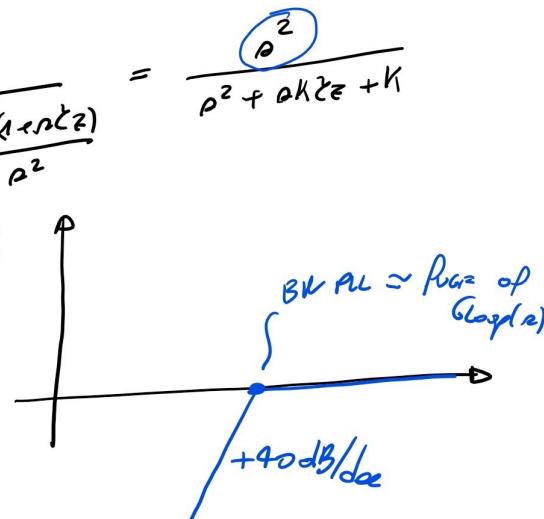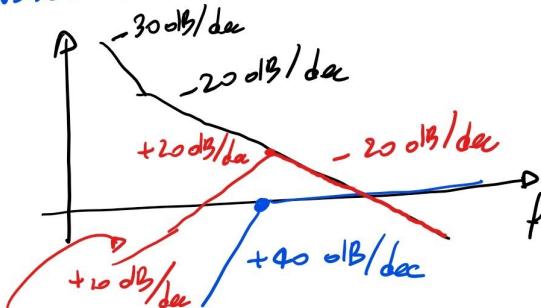

S_{VCO} Filtered by PLL


- 2) ZERO STEADY STATE ERROR @ PHASE DETECTOR INPUT

$$\frac{\phi_E(s)}{\phi_R(s)} = \frac{1}{1 + G_{loop}(s)} = 1 - T(s)$$

LET'S APPLY AN INPUT FREQUENCY STEP:

$$\omega_{REF}(s) = \frac{\Delta\omega}{s}$$
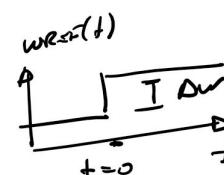
$$\phi_{REF}(s) = \frac{\Delta\omega}{s^2}$$



STATIONARY STATE ϕ_E^∞

$$\phi_E^\infty = \lim_{s \rightarrow 0} s \left(\frac{\Delta\omega}{s^2} \right) - \left(\frac{\phi_E(s)}{\phi_R(s)} \right) = \lim_{s \rightarrow 0} s \left(\frac{\Delta\omega}{s^2} \right) \frac{s^2}{s^2 + \alpha^2\zeta + K} = 0$$

3) REFERENCE SPURS

@ steady state $\dot{\rho}_E = 0$

WE CAN BUILD A PHASE DETECTOR


$$\text{out} = 0 \quad \text{when} \quad p_e = 0$$

AND NOT JUST $\angle \text{out} = 0$

• TRI-STATE PHASE DETECTOR



+ ε = 0 STATE 0

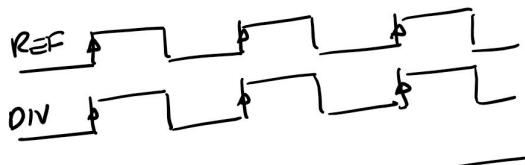

out = 0

(PFD)



RISING-EDGE
SENSITIVE

$t \epsilon > 0$ STATE 1


A timing diagram illustrating the relationship between two signals: REF (Reference) and DIV (Divide). The REF signal is a square wave starting at logic high. The DIV signal is a square wave starting at logic low. The two signals are synchronized, with the DIV signal rising at the same time as the REF signal's falling edge. This indicates that the DIV counter has been reset by the falling edge of the reference clock.

$$\text{CONT} = -\frac{t \varepsilon}{TR}$$

IMPLEMENTATION

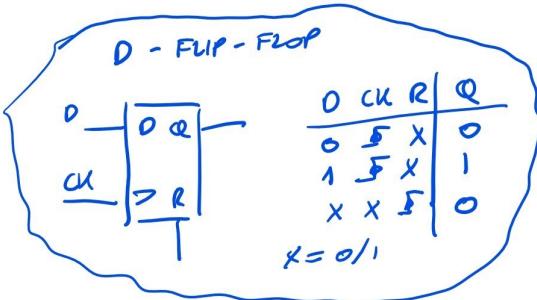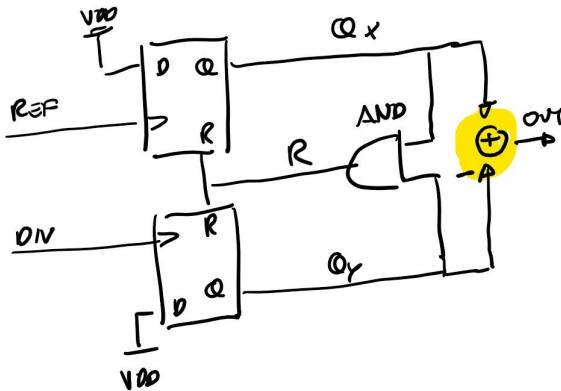

WORKING PRINCIPLE: $+ \varepsilon > 0$

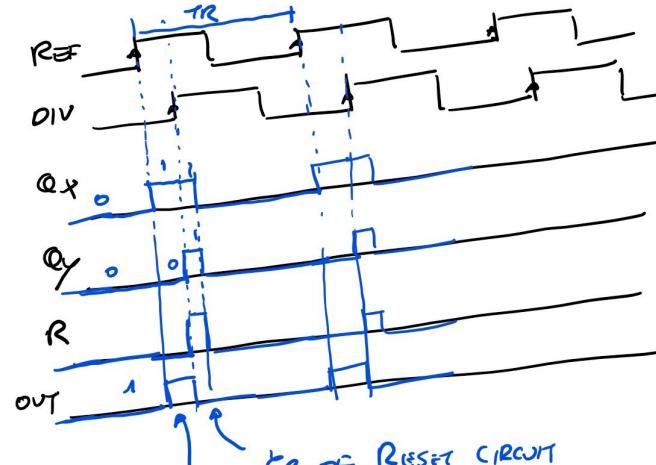


$$\text{COV17} = \frac{+ \varepsilon}{TR}$$

- The same happens for $t \in \omega$



$$\text{cov} \sigma = -\frac{t\varepsilon}{TR}$$

- BUILD THE CHARACTERISTIC!

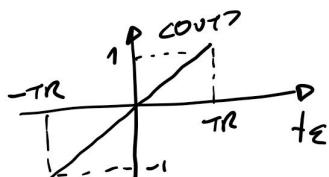


$$\varphi_\varepsilon = \frac{2\pi}{T\kappa} + \varepsilon$$
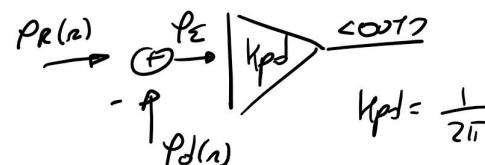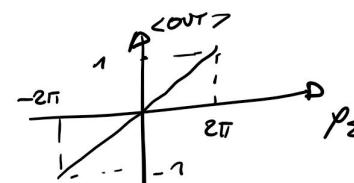
$$\text{cov} \sigma = \frac{\delta \Sigma}{\pi R} = \frac{\varphi \Sigma}{2\pi}$$



• WHY IS IT CALLED PHASE/FREQUENCY DETECTOR (PFD)


- DURING STARTUP: $F_{REF} \gg F_{DIV}$

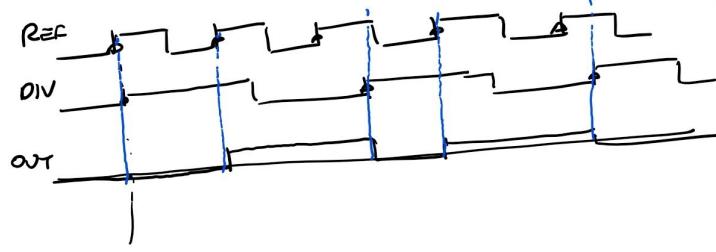

- PFD PROVIDES ONLY POSITIVE OUTPUT

The loop is forced only to increase frequency until $F_{DIV} = F_{REF}$.

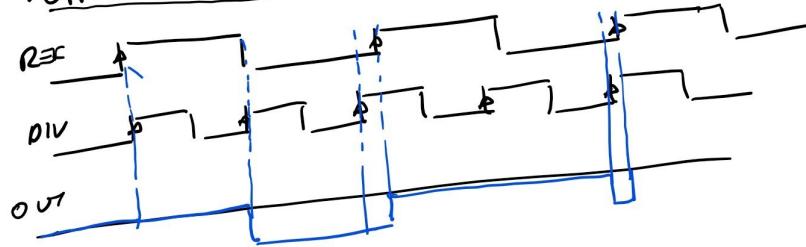- OPPOSITE SITUATION: $F_{REF} \ll F_{DIV}$




- FOR $F_{DIV} > F_{REF}$

The PFD output is NEGATIVE

THE LOOP DECREASE THE VCO FREQUENCY UNTIL $F_{DIV} = F_{REF}$

- PFD SENSE ALSO THE FREQUENCY DIFFERENCE BETWEEN F_{REF} AND F_{DIV}

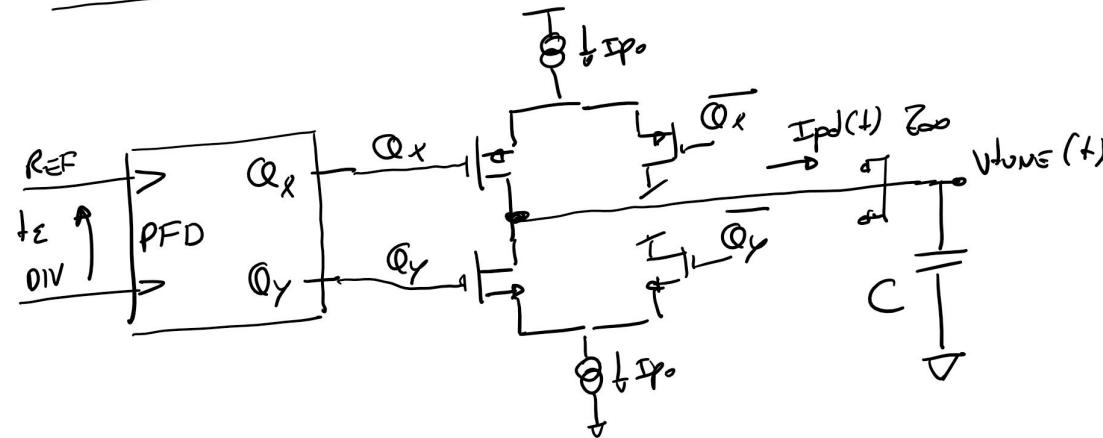- HOW TO IMPLEMENT THE SUM IN PFD : CHARGE-PUMP PULS



- SUM OF PFD OUT WITH CURRENT


- HIGH OUTPUT IMPEDANCE OF CP
- CONNECT C TO PERFORM INTEGRATION WITHOUT THE NEED OF OPAMP

• DERIVE THE EQ. MODEL

- CONSIDER TO APPLY A $t\tau_0$ STEP AT $t=0$

$$\varphi_{E0} = \frac{2\pi}{TR} t\tau_0 \quad \varphi_{E(t)} = \frac{\varphi_{E0}}{t}$$
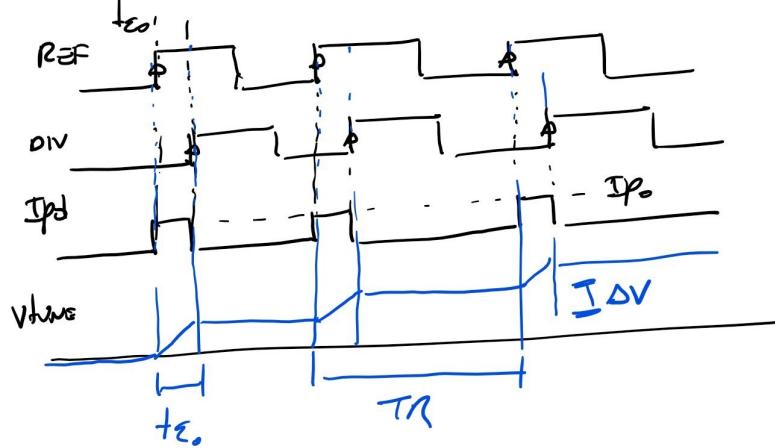
$$\Delta V = \frac{t\tau_0 \cdot I_p0}{C} \quad C = \frac{\Delta V}{\Delta \varphi} \quad i = \frac{dQ}{dt}$$



- GARDNER'S LIMIT FOR STABILITY:

$$BW \text{ PUL} < \frac{F_{REF}}{20}$$

$$V_{tune}(t) \approx \frac{\Delta V}{TR} + \frac{t\tau_0 I_p0}{C TR} +$$

$V_{tune}(t)$ CAN BE APPROXIMATED AS A RAMP DUE TO BW LIMITATION


$$V_{tunE}(t) = \frac{t\varepsilon_0 I_{po}}{C \cdot TR} + = \frac{I_{po}}{C} \frac{\varphi_{\varepsilon_0}}{2\pi} + \left(\varphi_{\varepsilon_0} = \frac{z\pi}{TR} + \varepsilon_0 \right)$$

LAPLACE TRANSFORM:


$$V_{tunE}(s) = \frac{I_{po}}{C} \frac{\varphi_{\varepsilon_0}}{2\pi} \frac{1}{s^2} = \left(\frac{I_{po}}{2\pi} \right) \left(\frac{1}{sC} \right) \underbrace{\left(\frac{\varphi_{\varepsilon_0}}{s} \right)}_{\stackrel{s}{\uparrow} \text{ kpd}} \xrightarrow[\text{WRT STEP}]{\text{CONNECTS TO HO CP}} \varphi_{\varepsilon}(s) = \frac{\varphi_{\varepsilon_0}}{s}$$

THE TRANSFER FUNCTION:
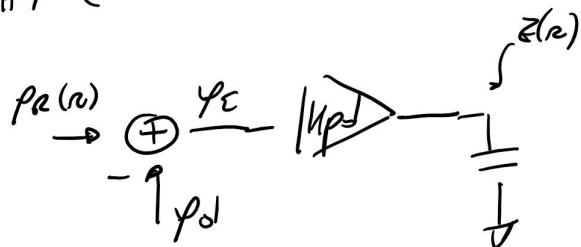
$$\frac{V_{tunE}(s)}{\varphi_{\varepsilon}(s)} = \left(\frac{I_{po}}{2\pi} \right) \left(\frac{1}{sC} \right) = k_{pd} Z(s)$$




• COMPLETE SYSTEM: CP - PUL WITH PFD

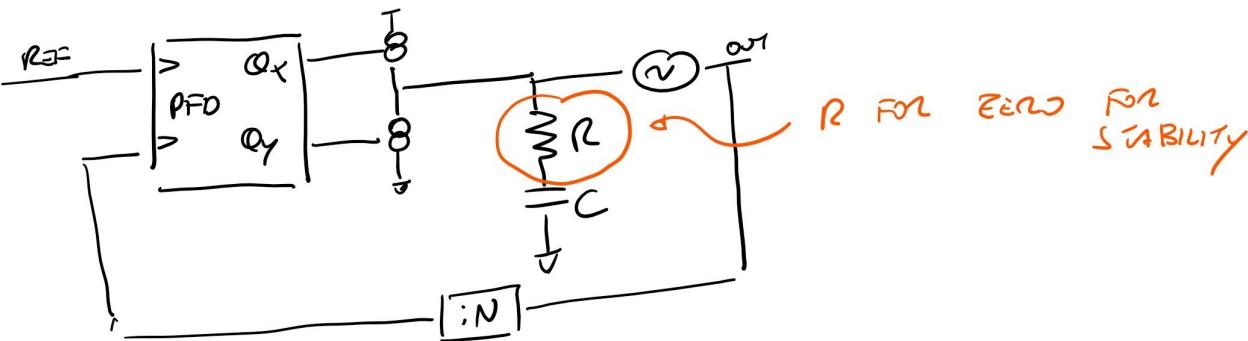

• CONSIDER THE MODEL IN PHASE DOMAIN:

$$\begin{aligned} p_{ref}(s) &\rightarrow (+) \rightarrow |k_{pd}| \rightarrow \left| \frac{(1 + \alpha RC)}{sC} \right| - \left| \frac{K_N C}{s} \right| \frac{\varphi_{out}(s)}{|N|} \\ &\quad \uparrow \end{aligned}$$

EXERCISE 3.1

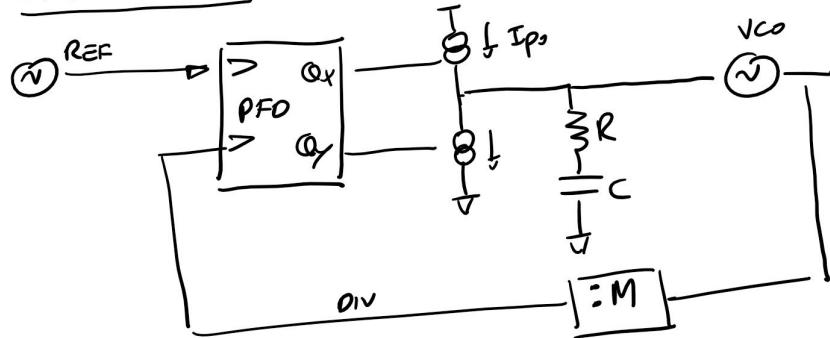

$$F_{FR} = 3 \text{ GHz}$$

$$K_{VCO} = 2\pi 300 \text{ MHz/V}$$

$$I_{PD} = 10 \mu\text{A}$$

$$M = 100$$

a) DERIVE THE EQUIVALENT LINEAR MODEL IN PHASE DOMAIN:

$$\text{PFD + CP: } \varphi_E \rightarrow \begin{cases} \varphi_E & I_{PD} \\ -\varphi_E & -I_{PD} \end{cases} \quad K_{PD} = \frac{I_{PD}}{\varphi_E} = \frac{I_{PD}}{2\pi}$$

$$\text{FILTER: } \begin{cases} I_{PD} \\ R \\ C \end{cases} \quad V_{tun}(s) = Z(s) = \frac{(1 + \alpha RC)}{\alpha C}$$

$$\text{VCO: } V_{tun} \rightarrow \omega_{out}$$


$$\omega_{out} = \omega_{FR} + K_{VCO} V_{tun}$$

$$\phi_{out}(t) = \int_{-\infty}^t \omega_{out}(t') dt = \omega_{FR} t + \underbrace{K_{VCO} \int_{-\infty}^t V_{tun}(t') dt}_{\text{Excess Phase}}$$

LAPLACE TRANSFORM OF EXCESS PHASE:

$$\phi_{out}(s) = \frac{K_{VCO}}{s} V_{tun}(s) \quad \frac{\phi_{out}(s)}{V_{tun}(s)} = \frac{K_{VCO}}{s}$$

FREQUENCY DIVIDER: $\frac{OUT}{IN} : M$

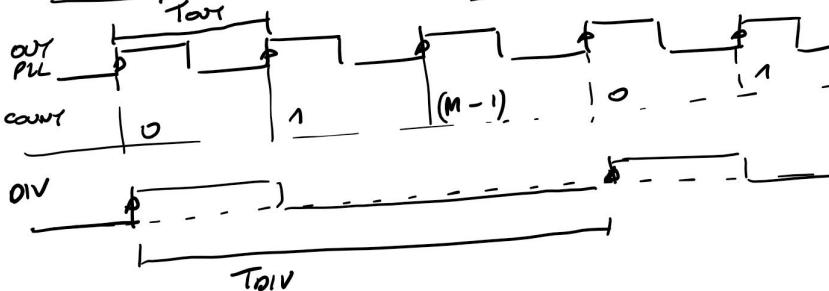

$$T_{out} = \frac{T_{DIV}}{N}$$


$$F_{out} = N F_{in}$$

$$p(s) = \frac{1}{N} w(s)$$

$$\frac{p_{out}(s)}{p_{in}(s)} = \frac{N F_{in}}{N F_{out}} = \frac{1}{N}$$

MODEL OF DIVIDER: LINEAR GAIN $p_{out}(s) \rightarrow \frac{1}{N} p_{in}(s)$

COMPLETE MODEL:

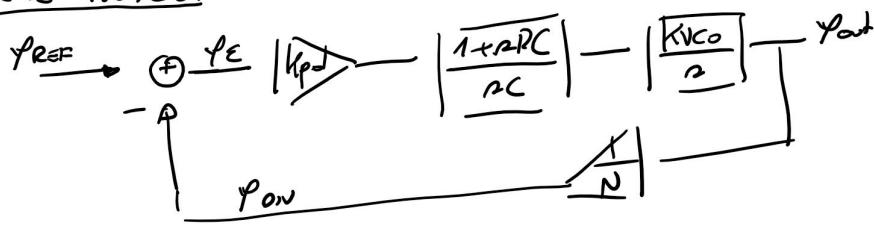

size R, C to have closed loop poles:

- $\omega_0 = 10 \text{ kHz} \cdot 2\pi$
- @ 45° in Gauss-Plane $\Rightarrow \zeta = \frac{\sqrt{2}}{2}$

$$G_{\text{loop}}(\alpha) = K_{PD} \frac{(1 + \alpha R C)}{\alpha C} \frac{K_{VCO}}{\alpha} \frac{1}{N} = K \frac{(1 + \alpha^2 \zeta^2)}{\alpha^2}$$

$$\zeta \zeta = R C$$

$$K = \frac{K_{PD} K_{VCO}}{C N} = \frac{1}{2\Omega}$$

TO FIND CLOSED-LOOP POLES:

$$1 + G_{\text{loop}}(\alpha) = 0$$

$$1 + K \frac{(1 + \alpha^2 \zeta^2)}{\alpha^2} = 0 \quad \alpha^2 + \alpha K \zeta \zeta + K = 0$$

compare with the form $\frac{\alpha^2}{\omega_n^2} + \frac{\alpha}{\omega_n \Omega} + 1 = 0$


$$K = \frac{K_{PD} K_{VCO}}{C N} = (2\pi 10 \text{ kHz})^2$$

$$\frac{\alpha^2}{\omega_n^2} + \frac{\alpha}{\omega_n \Omega} + 1 = 0$$


$$\zeta \zeta = R C = \frac{2\zeta}{\omega_n} \quad \zeta = 76 \text{ nF}$$

$$R = \frac{2\zeta}{\omega_n C} = 296 \text{ } \Omega$$

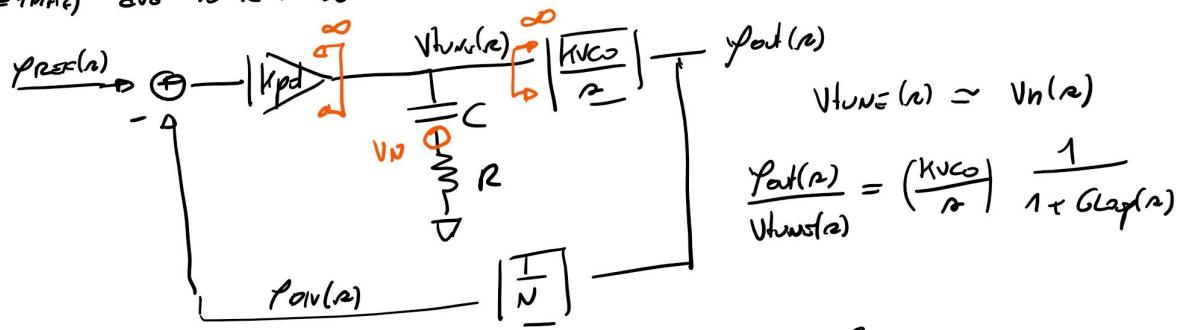b) $\mathcal{L}(\Delta f = 1\text{MHz})$ due to R noise




$$\mathcal{L}(\Delta f) = \frac{1}{2} S_p^{SSB}(f) = \frac{1}{2} (4KTR) \left| \frac{|K_{VCO}|}{2\pi f} \right|^2 \left| \frac{1}{1 + G_{loop}(j2\pi f)} \right|^2$$

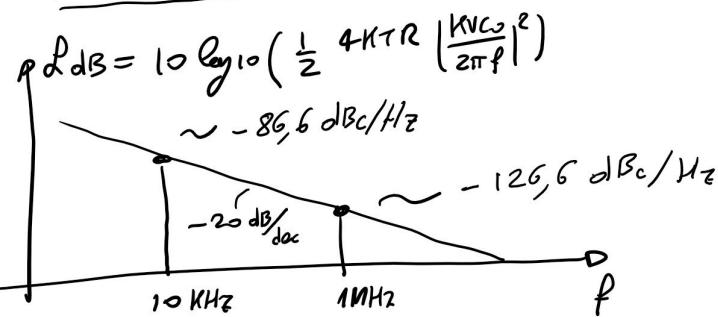


$$\frac{1}{1 + G_{loop}(n)} = \frac{\rho^2}{\rho^2 + nK^2z + K} = \frac{\rho^2}{\rho^2 + n\omega_N^2 z^2 + \omega_N^2}$$

$$\left| \frac{1}{1 + G_{loop}(j2\pi\omega_N)} \right| = \frac{1}{2z} = \frac{\sqrt{2}}{2} = -3 \text{ dB}$$

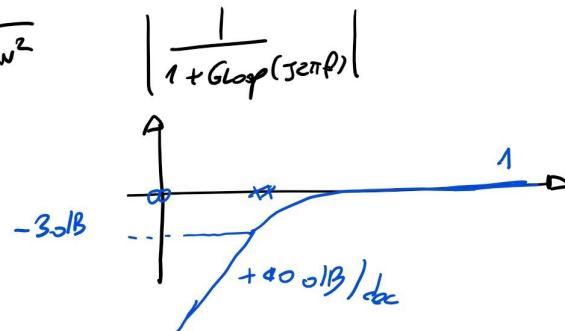

$$\bullet \mathcal{L}(\Delta f) = \frac{1}{2} 4KTR \left| \frac{|K_{VCO}|}{2\pi f} \right|^2 \left| \frac{1}{1 + G_{loop}(j2\pi f)} \right|^2$$

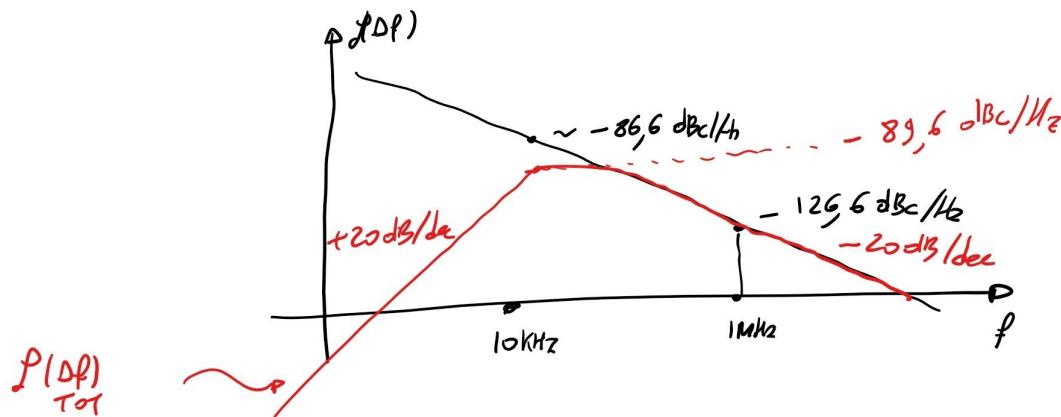

$\mathcal{L}(\Delta f = 1\text{MHz}) = -126 \text{ dBc/Hz}$ due to R.

c) DERIVE P_{out} DUE TO R AND TO REFERENCE NOISE

$$P_{\text{REF}} = \text{WHITE} = -140 \text{ dBc/Hz}$$

$$\frac{P_{\text{out}}(\alpha)}{P_{\text{REF}}(\alpha)} = \frac{N G_{\text{loop}}(\alpha)}{1 + G_{\text{loop}}(\alpha)} = \frac{N \left(1 + \alpha^2 \zeta^2\right)}{\frac{\alpha^2}{K} + \alpha^2 \zeta^2 + 1}$$

$$= N \frac{\left(1 + \frac{\alpha}{w_N Q}\right)}{\frac{\alpha^2}{w_N^2} + \frac{\alpha}{w_N Q} + 1}$$

REMEMBER:


$$\frac{\alpha^2}{w_N^2} + \frac{\alpha}{w_N Q} + 1 = 0$$

$$\zeta^2 = \frac{1}{2Q} \quad K = w_N^2$$

$$\left| \frac{P_{\text{out}}(jw_N)}{P_{\text{REF}}(jw_N)} \right| = \left| N \frac{\left(1 + \frac{j}{\zeta}\right)}{-1 + \frac{j}{\zeta} + 1} \right| = N \sqrt{1 + Q^2}$$


$$Q = \frac{1}{2\zeta} = \frac{\sqrt{2}}{2}$$
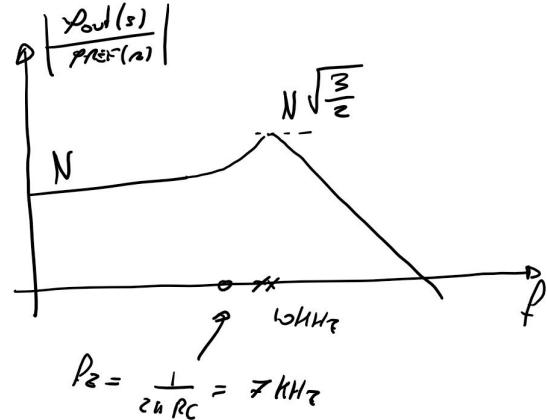
$$= N \sqrt{1 + \left(\frac{\sqrt{2}}{2}\right)^2} = N \sqrt{\frac{3}{2}}$$




• REFERENCE OUTPUT SPECTRUM:

$$P_{\text{out}} = P_{\text{REF}} \cdot \left| \frac{P_{\text{out}}(f)}{P_{\text{REF}}(f)} \right|^2$$

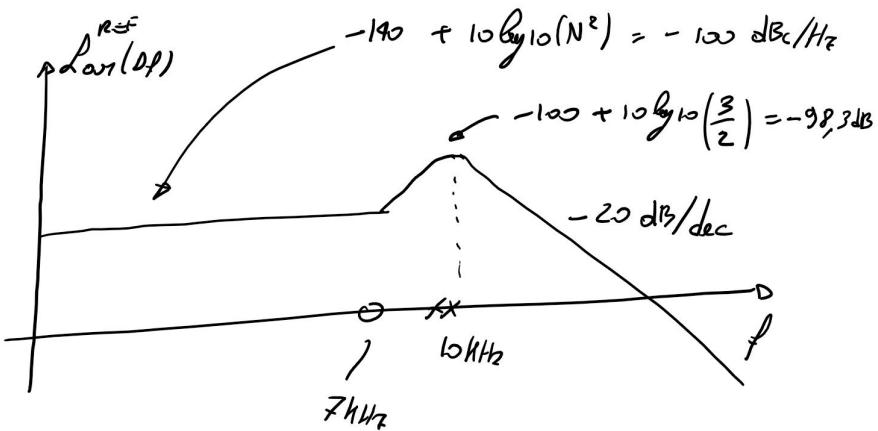

• COMPOSITION OF R NOISE WITH REF NOISE:

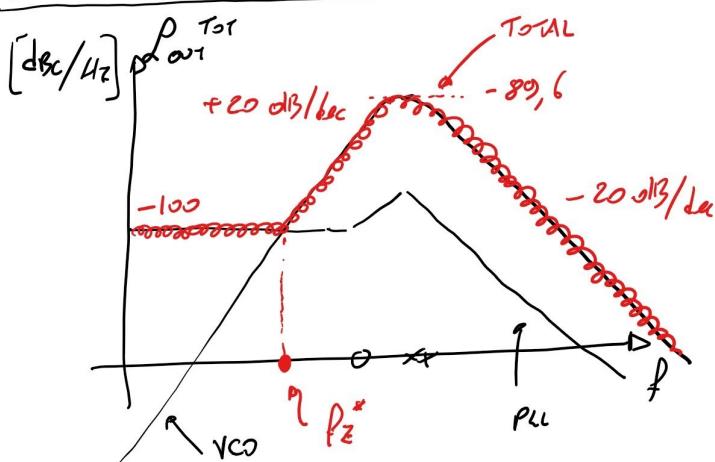

$P_z^* = \text{ZERO}$ at THE COMPOSITION

$$-100 + 20 \log_{10} \left(\frac{10 \text{ kHz}}{P_z^*} \right) = -89.6$$

$$P_z^* = \frac{10 \text{ kHz}}{\frac{(-89.6 + 100)}{20}} = 3 \text{ kHz}$$