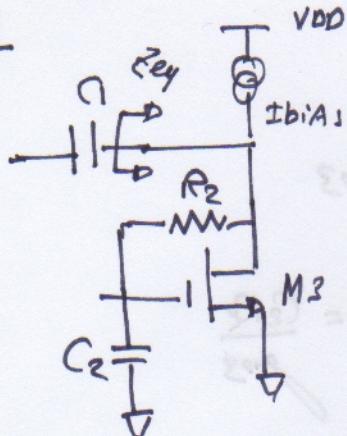
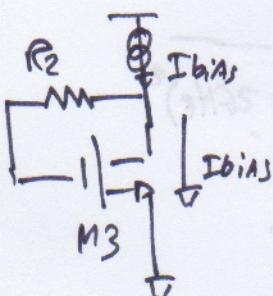



EX 9.1

a)

SIZE C<sub>1</sub>to resonates at  $f_0 = 26\text{GHz}$ the output network  $R_2, C_1, C_3, R_3$ • BIAS OF M<sub>3</sub>

$$g_{m3} = 2 \sqrt{\frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_3} I_{bias} = 60 \text{mA/V}$$

$0.2 \text{mA/V}^2$        $\uparrow$        $6 \text{mA}$   
 $250$

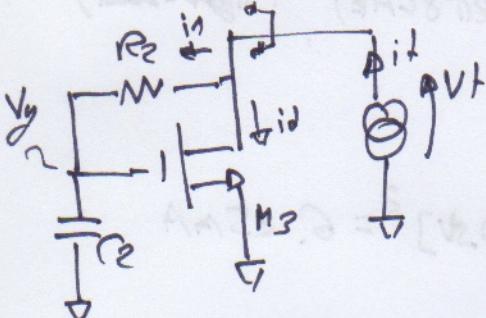• EVALUATE  $Z_{eq}$ 

$$i_t = i_d + i_s$$

$$i_s = \frac{V_t}{R_2 + \frac{1}{R_C}} = \frac{\rho C_2 V_t}{(1 + \rho C_2 R_2)}$$


$$i_d = g_{m3} V_g = g_{m3} \cdot i_s \cdot \frac{1}{\rho R_2} = g_{m3} \frac{V_t}{(1 + \rho C_2 R_2)}$$

$$i_t = \frac{\rho C_2}{(1 + \rho C_2 R_2)} V_t + \frac{g_{m3} V_t}{(1 + \rho C_2 R_2)} \Rightarrow \boxed{Z_{eq} = \frac{V_L}{i_t} = \frac{1}{g_{m3}} \frac{(1 + \rho C_2 R_2)}{(1 + \rho \frac{C_2}{g_{m3}})}}$$


$$f_L = \frac{1}{2\pi C_2 R_2} = 1,06 \text{GHz}$$

$$f_T = \frac{1}{2\pi C_2 g_{m3}} = 9,55 \text{GHz}$$

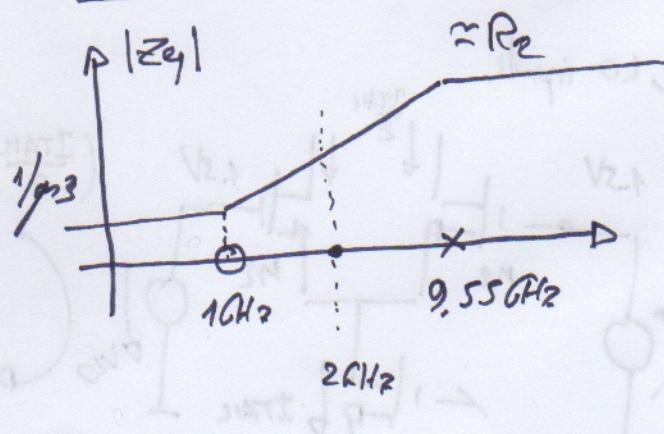
$$Z_{eq} \xrightarrow{\text{around } f} \approx \frac{1}{g_{m3}} + \rho \frac{C_2 R_2}{g_{m3}} \approx R_2$$



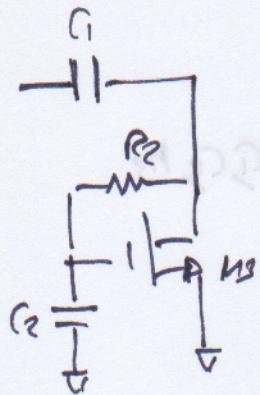$V_{DD} = 2.7 \text{V} \ll V_{max} = 22 \text{V}$  working region  
 bandwidth is very flat



AROUND  
F

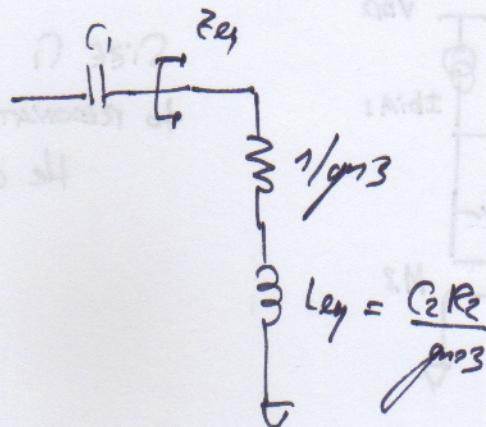


$$2\pi f_0 = \omega_0 = \sqrt{\frac{1}{C_1 + \frac{C_2 R_2}{g^3}}} \Rightarrow C_1 = \frac{1}{\frac{C_2 R_2}{g^3} (2\pi f_0)^2} \\ = 2.53 \text{ pF}$$


b) At RF port  $V_{RF} = V_0 + A_{RF} \cos(2\pi 10 \text{ GHz})$   
 $V_{LO} = 1.5V + 300mV \text{ SQUARE-WAVE } (2\pi 8 \text{ GHz}) \text{ (Single-ended)}$

### - BIAS point:

M1 TAIL

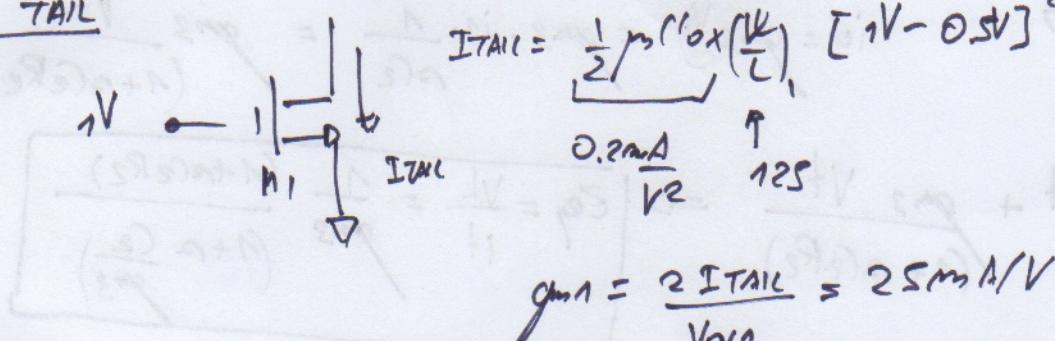


M2, LO imports.

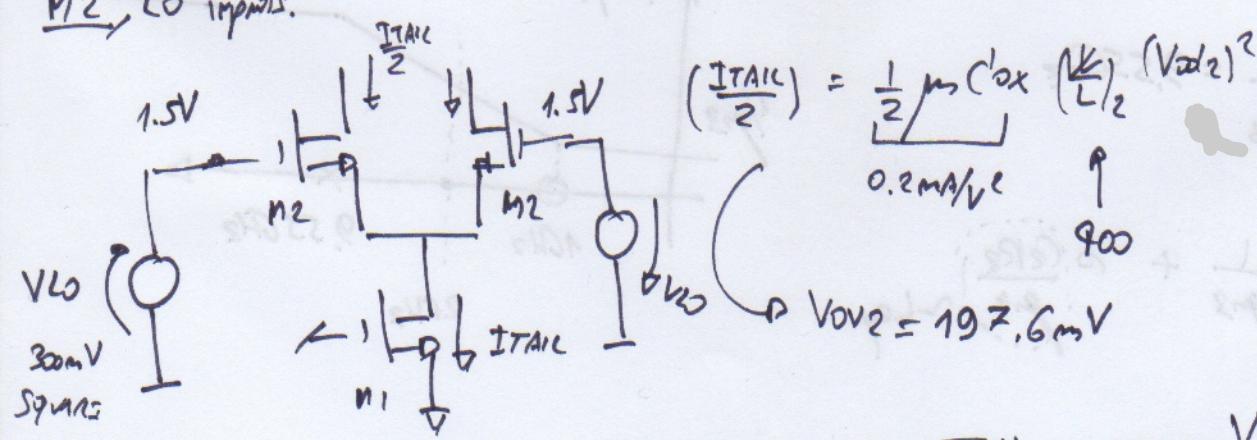


During operation  $V_{IN\text{ diff}} = 600mV \gg \sqrt{2} V_{OV_2} = 280mV$   
 $\hookrightarrow$  the pair is unbalanced

- AC Model

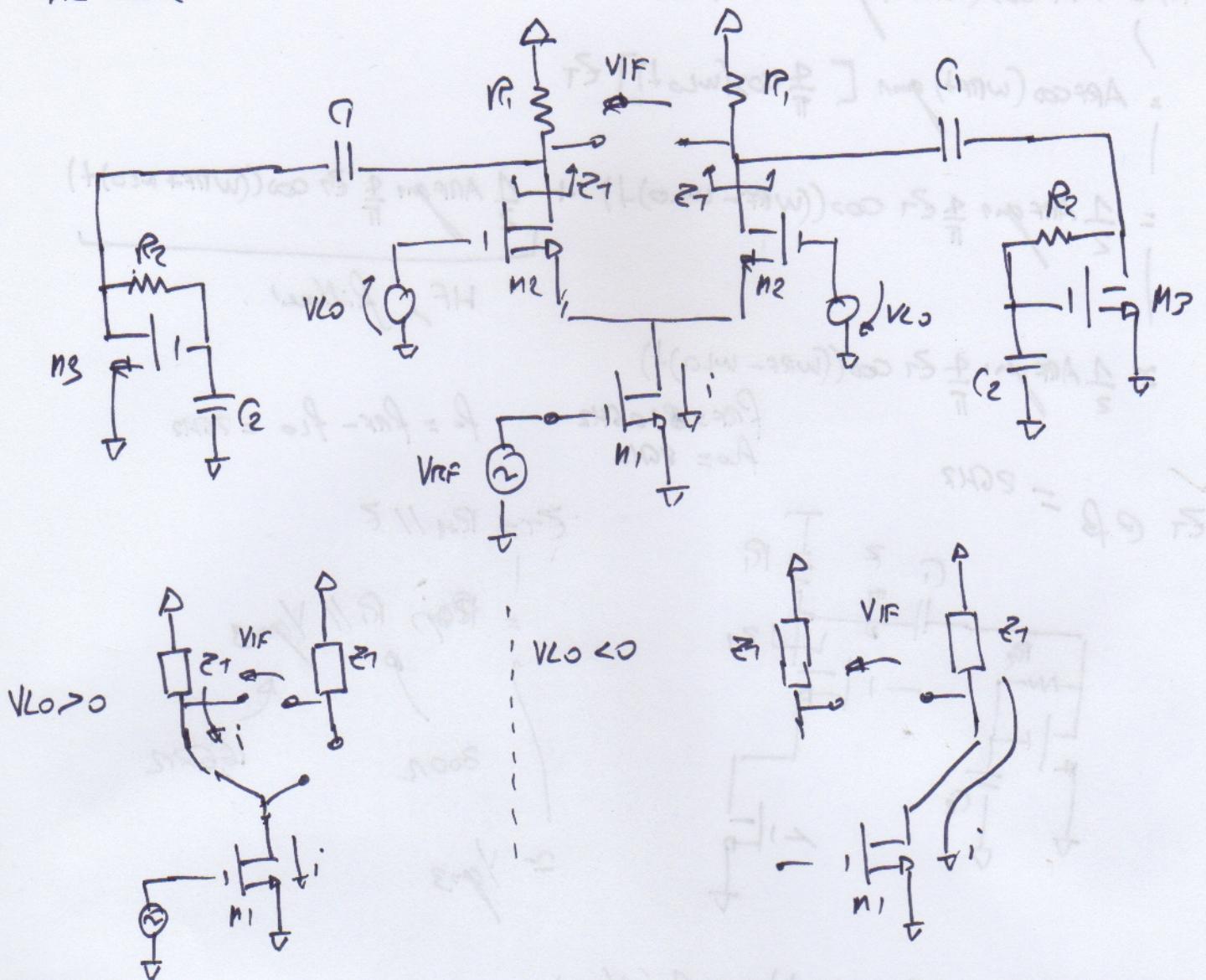

$$V_{IF}(t) = A_{RF} \cos(\omega_{RF} t) g_{m1} Z_1 X_{LO}(t)$$

$$\begin{aligned} X_{LO}(t) &= \text{SQUARE2 - AVG} \\ &= y_0 + \sum_{n=1}^{+\infty} 2|y_n| \cos\left(\frac{2\pi}{T_{LO}} nt + \phi_n\right) \end{aligned}$$

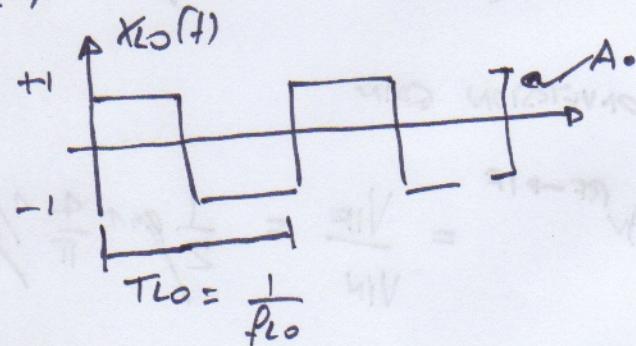

$$y_0 = \text{AVERAGE} = 0$$

$$y_N = A_0 D \sin(D_h)$$

$$= A_0 \frac{1}{2} \frac{\sin\left(\frac{\pi}{2} h\right)}{\pi \frac{1}{2} h}$$

$$y_1 = 2 \cdot \frac{1}{2} \frac{1}{\pi/2} = \frac{2}{\pi}$$

$$y_2 = 0$$


$$y_3 = -\frac{2}{3\pi}$$

$$X_{LO}(t) \approx 0 + \frac{4}{\pi} \cos(\omega_{LO} t) + 0 - \frac{4}{3\pi} \cos(3\omega_{LO} t) + \dots$$

$$\begin{aligned}
 V_{IF}(t) &= ARF \cos(\omega_{RF} t) g_m1 Z_T \\
 &= ARF \cos(\omega_{RF} t) g_m1 \left[ \frac{q}{\pi} \cos(\omega_L t) \right] Z_T \\
 &= \frac{1}{2} ARF g_m1 \frac{q}{\pi} Z_T \cos((\omega_{RF} - \omega_L)t) + \underbrace{\frac{1}{2} ARF g_m1 \frac{q}{\pi} Z_T \cos((\omega_{RF} + \omega_L)t)}_{HF, \text{ filtered}} \\
 &\approx \frac{1}{2} ARF g_m1 \frac{q}{\pi} Z_T \cos((\omega_{RF} - \omega_L)t)
 \end{aligned}$$

$$\begin{aligned}
 f_{RF} &= 10 \text{ GHz} \\
 f_{LO} &= 8 \text{ GHz} \\
 f_o &= f_{RF} - f_{LO} = 2 \text{ GHz}
 \end{aligned}$$

$$Z_T @ f = 2 \text{ GHz}$$

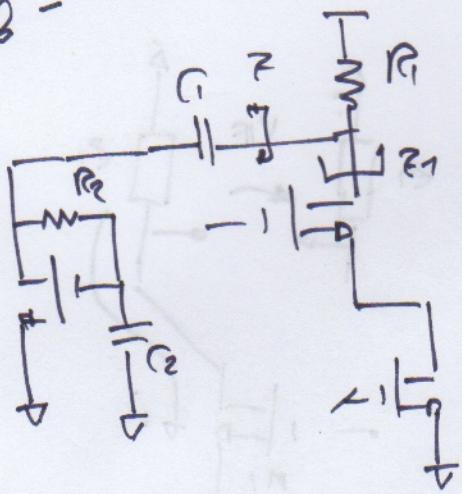

$$Z_T = R_m / |Z|$$

$$\begin{aligned}
 &= R_m / |Z| \\
 &= R_m / (R_m / |Z|) \\
 &= |Z| \\
 &\approx 16.67 \Omega
 \end{aligned}$$

$$V_{IF}(t) = \frac{1}{2} ARF \cos(2\pi 2 \text{ GHz} t) g_m1 \frac{q}{\pi} \left( \frac{1}{g_m3} \right)$$

### CONVERSION GAIN

$$A_{V_{RF} \rightarrow V_{IF}} = \frac{V_{IF}}{V_{IN}} = \frac{1}{2} g_m1 \frac{q}{\pi} \frac{1}{g_m3} = -11.53 \text{ dB}$$

$$\frac{1}{2} = \frac{1}{2\pi} \cdot \frac{1}{2} = \frac{1}{4\pi}$$

$$\begin{aligned}
 &= \frac{(1/2\pi) \cdot 1/2}{1/2} = 1/4\pi \\
 &\approx 0.08 \text{ dB}
 \end{aligned}$$

$$\begin{aligned}
 &+ (1/2\pi)^2 \cdot 1/2 = 0 + (1/2\pi)^2 \cdot 1/2 + 0 \approx 0.08 \text{ dB}
 \end{aligned}$$

c) NF ( $F_{RF} = F_{LO} = 8 \text{ GHz}$ ) with  $R_S = 50\Omega$



$$V_{IF}(t) = \frac{1}{2} A_{RF} g_m \frac{q}{\pi} \cos((\omega_{RF} - \omega_{LO})t) R_T$$

$\approx 0$   
Z is at DC


$$= \frac{1}{2} A_{RF} g_m \frac{q}{\pi} R_i$$

$Z_T = R_i$  because C is open at DC.

$$A_{VRF-0IF} = \frac{2}{\pi} g_m R_i$$

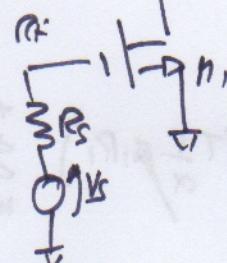
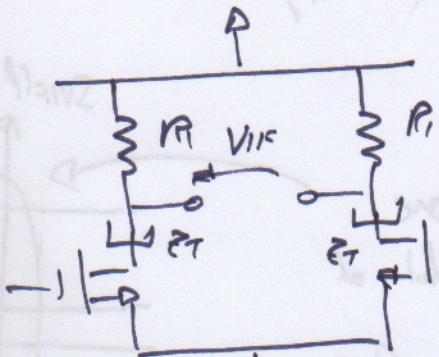


### CONTRIBUTION OF M1 (TAIL)

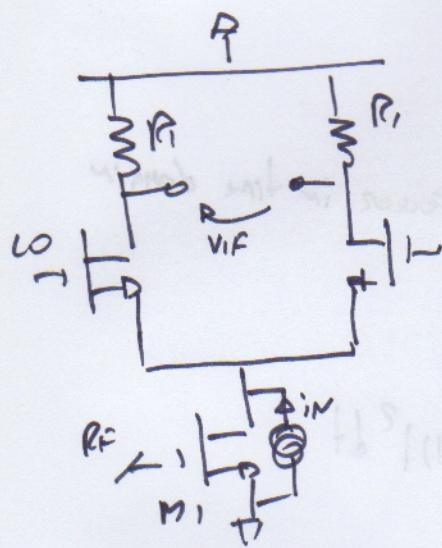


$$V_{IF} = i_N \cdot x_{LO} R_i$$
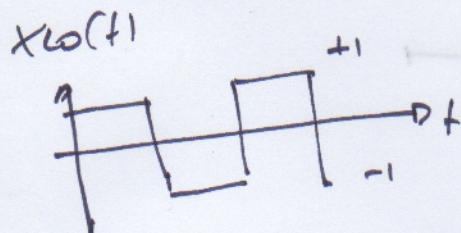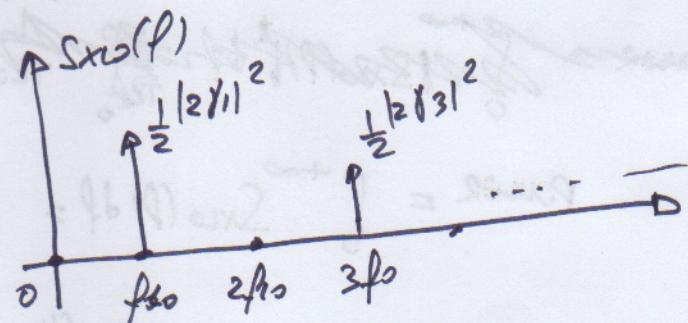
$$S_{VIF} = 4\pi f \frac{1}{2} g_m R_i^2 \otimes S_{x_{LO}}$$



$$x_{LO}(t) = j_0 + \sum_{n=1}^{\infty} 2|Y_n| \cos\left(\frac{2\pi n t}{T_{LO}} + \delta(Y_n)\right)$$
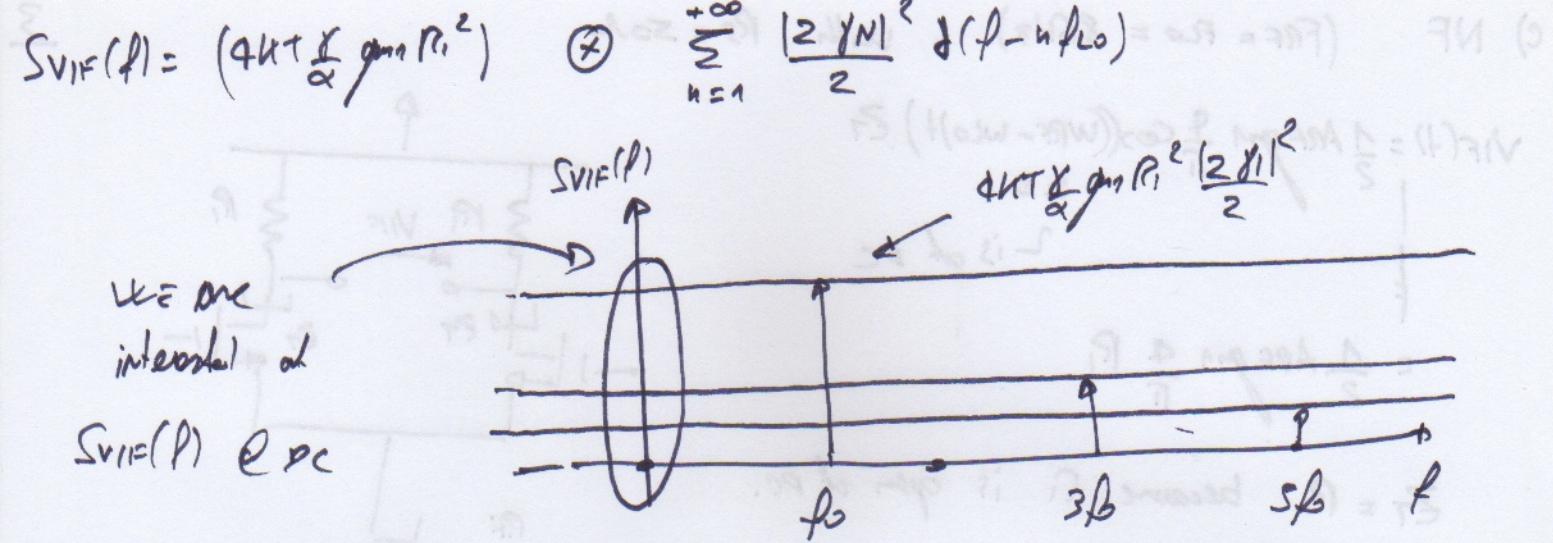
$$\Delta = \frac{1}{2\pi f_{LO}} \frac{1}{CT} = 500$$




$$S_{VIF}(f) = \left(4\pi T \frac{\chi}{\alpha} g_m R_i^2\right) \sum_{n=1}^{+\infty} \frac{|2\gamma_n|^2}{2}$$

$$\sum_{n=1}^{+\infty} \frac{|2\gamma_n|^2}{2} = \int_0^{+\infty} S_{xLO}(f) df = \text{Power in frequency domain}$$

sum of all the active components  
in the spectrum

**PARSEVAL'S THEOREM** : Power in frequency domain = Power in time domain

$$\text{POWER} = \int_0^{+\infty} S_{xLO}(f) df = \frac{1}{T_{LO}} \int_0^{T_{LO}} |x_{LO}(t)|^2 dt$$

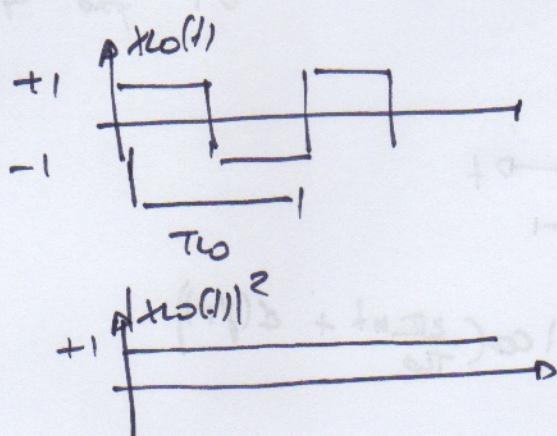


$$\text{POWER} = \frac{1}{T_{LO}} \int_0^{T_{LO}} 1 dt = 1$$

$$SVIF(f) = 4kT \frac{1}{\alpha} g_m R_i^2 \left( \sum_{n=1}^{+\infty} \frac{(2\pi n)^2}{2} \right)$$

$$SVIF(f) = 4kT \frac{1}{\alpha} g_m R_i^2$$


M2, considering the about switching.

OFF

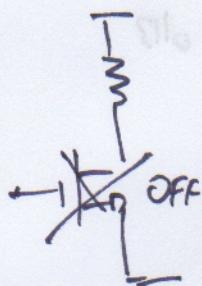


NO noise,  
the transistor  
is OFF

ON

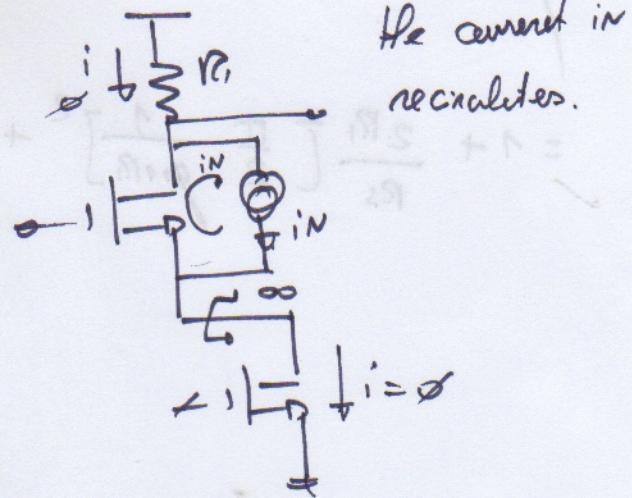

R<sub>i</sub> contributions:

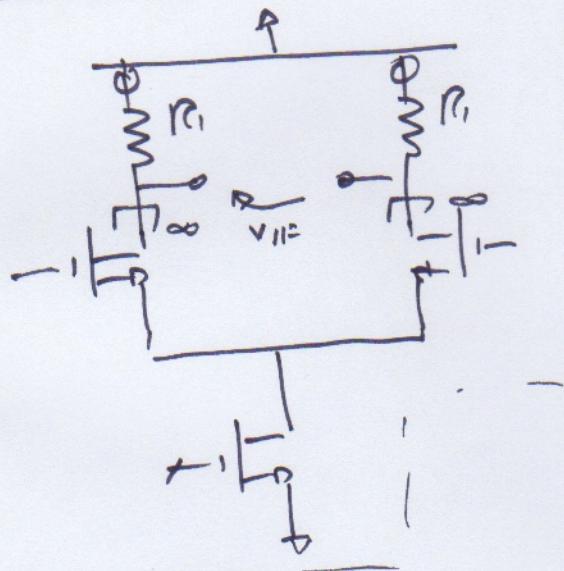

$$SVIF = 2 \times 4kT R_i$$



R<sub>S</sub> contribution:

We consider the noise of R<sub>S</sub>  
or a single tone @ f<sub>RF</sub>

$$V_{IF} = V_n g_m R_i XLO(Q)$$

$$= V_n g_m R_i \frac{1}{2} \frac{d}{d}$$


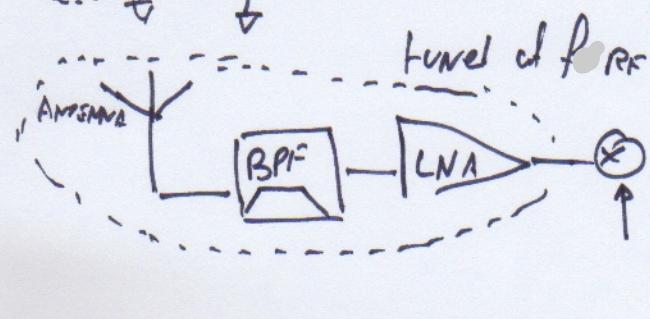
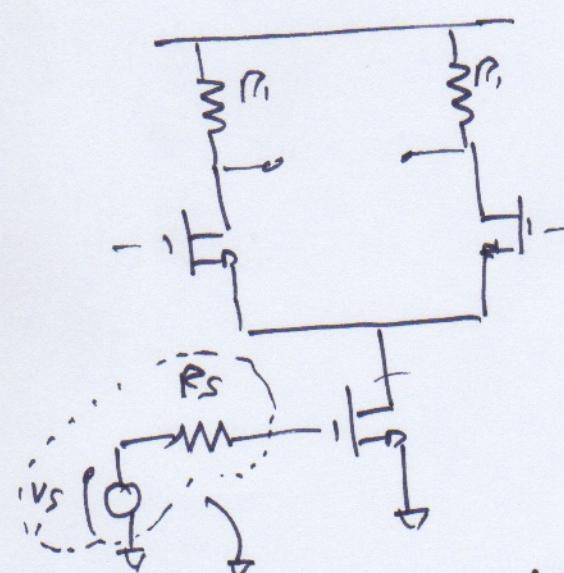
$$\begin{aligned} SVIF &= 4kT R_S A_v^2 \\ &= 4kT R_S \left( g_m R_i \frac{2}{\pi} \right)^2 \end{aligned}$$



$$NF = 1 + \frac{2 \times 4kT R_1}{qU T R_s A v^2} + \frac{4kT \frac{\chi}{\alpha} g_m R_1^2}{qU T R_s A v^2}$$


$$= 1 + \frac{2 R_1}{R_s g_m^2 R_1^2 \left(\frac{2}{\pi}\right)^2} + \frac{\frac{\chi}{\alpha} g_m R_1^2}{R_s g_m^2 R_1^2 \left(\frac{2}{\pi}\right)^2}$$
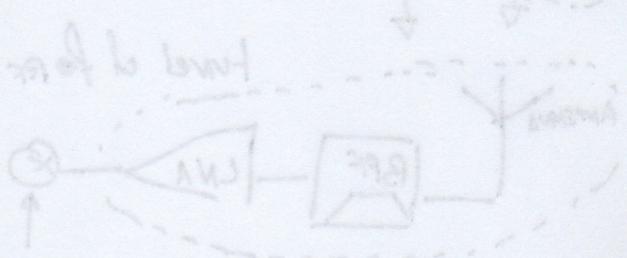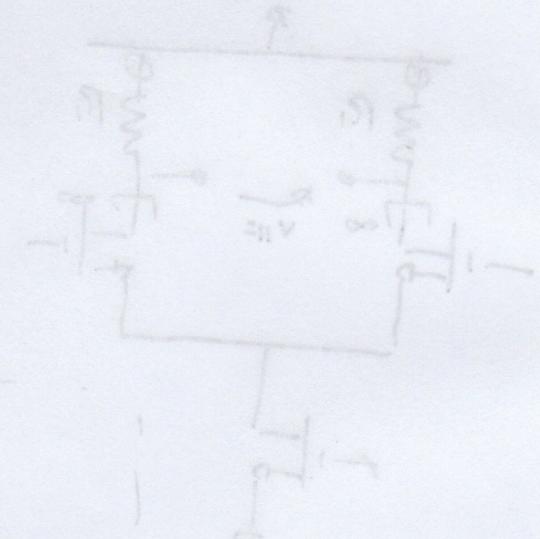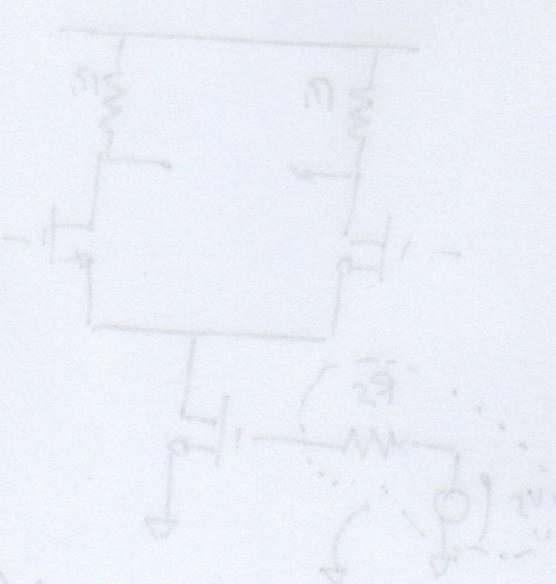
$$= 1 + \frac{2 R_1}{R_s} \left[ \frac{\pi}{2} \frac{1}{g_m R_1} \right]^2 + \frac{\frac{\chi}{\alpha} \left(\frac{\pi}{2}\right)^2}{g_m R_s} = 4,92 \text{e}^{13}$$




$$\frac{1}{\pi} \frac{1}{s} \text{Fluss } H =$$
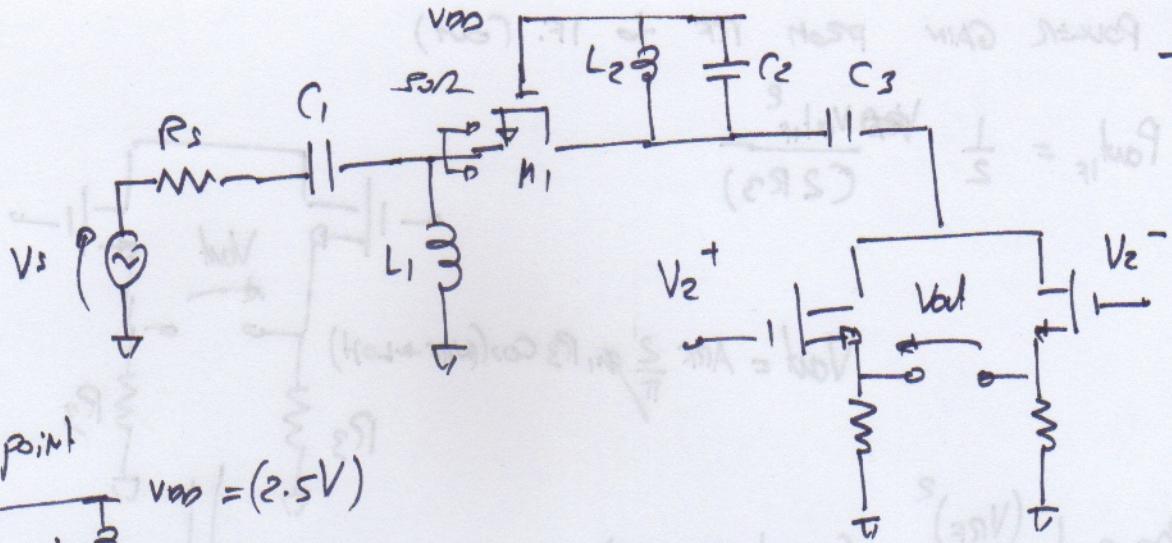
$$s \left( \frac{1}{\pi} \frac{1}{s} \text{Fluss } H \right) = \frac{1}{\pi} \text{Fluss } H$$



a) DERIVE BIAS POINT



$$V_{DD} = 2.5V$$

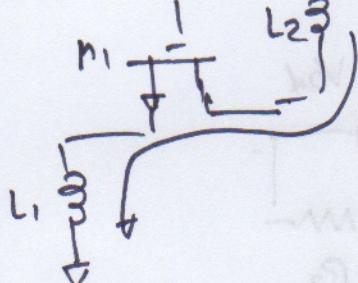

$$I_{M1} = \frac{1}{2} \mu C_{ox} (\frac{W}{L}) (2.5V - 0.5V)^2 = 20mA$$

$$g_{m1} = \frac{2 I_{M1}}{V_{DD}} = \frac{2 \cdot 20mA}{2V} = 20mA/V = \frac{1}{50\Omega}$$

• RF TO IF CONVERSION GAIN

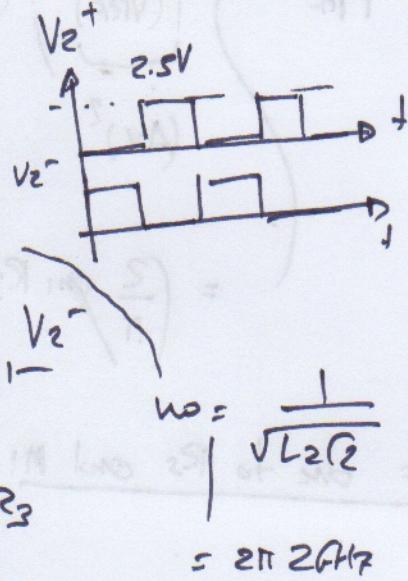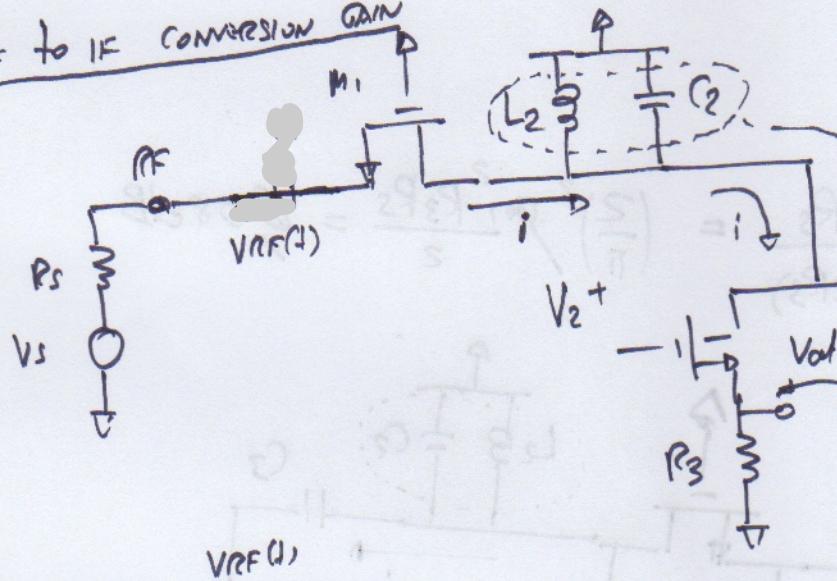

$$V_{out}(t) = A_{RF} \cos(\omega_{RF} t) g_{m1} R_3 \Delta I_0(t)$$

$$= A_{RF} \cos(\omega_{RF} t) g_{m1} R_3 \left[ \frac{q}{\pi} \cos(\omega_{LO} t) \right]$$


$$= \frac{1}{2} A_{RF} \cos((\omega_{RF} - \omega_{LO})t) g_{m1} R_3 \frac{q}{\pi} + \text{Higher freq. component} \sim \text{Filtered by Q system.}$$

$$2\pi(2.76\text{Hz} - 2\text{Hz}) = 2\pi 100\text{MHz}$$

$$A_{V_{RF \rightarrow IF}} = \frac{V_{out}}{V_{RF}} = \frac{2}{\pi} g_{m1} R_3 = 22.1 \text{ dB.}$$


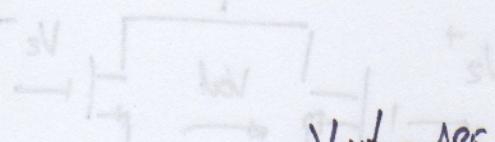
b) POWER GAIN from RF to IF (out)

$$P_{out,IF} = \frac{1}{2} \frac{V_{out,IF}^2}{(2R_3)}$$



$$V_{out} = A_{RF} \frac{2}{\pi} g_m R_3 \cos(\omega_{RF} t - \omega_L t)$$
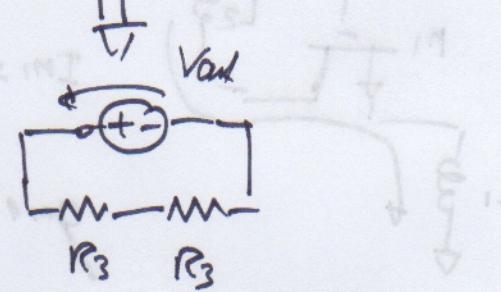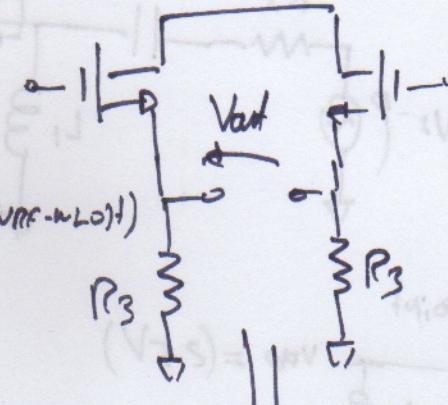
$$P_{RF} = \frac{1}{2} \frac{(V_{RF})^2}{R_S} \quad (\text{input matching})$$




$$G_p = \frac{P_{out,IF}}{P_{RF}} = \left[ \frac{\left( V_{out,IF} \right)^2}{\left( V_{RF} \right)^2} \right] \frac{R_S}{(2R_3)}$$

$$(AV)^2$$


$$= \left( \frac{2}{\pi} g_m R_3 \right)^2 \frac{R_S}{(2R_3)} = \left( \frac{2}{\pi} \right)^2 g_m^2 \frac{R_3 R_S}{2} = 6.08 \text{ dB}$$

c) NF due to  $R_S$  and  $M1$

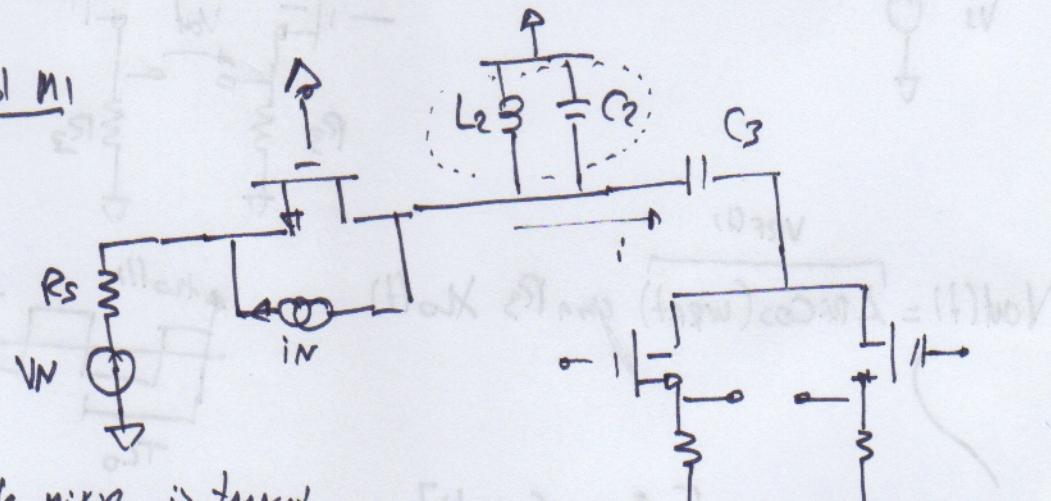

The noise going into the mixer is shared  
at  $P_{RF}$  by the two components  $L_2, C_2$ .

M1 Contribution:

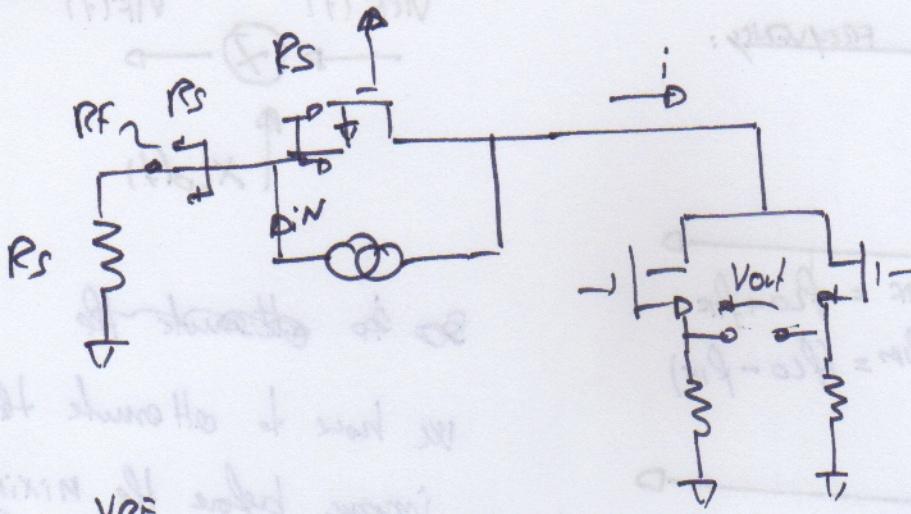


$$V_{out,IF}^{M1} = \left( i_D \cdot \frac{R_S}{2} \right) \cdot A_{v,RF \rightarrow IF} \quad \Rightarrow \quad \Delta V_{out,IF}^{M1} = 4kT \frac{1}{\alpha} g_{m1} \left( \frac{R_S}{2} \right)^2 (A_v)^2$$



$R_S$  contribution:

$$V_{out,IF}^{RS} = \left( V_R \frac{1}{2} \right) \cdot A_{v,RF \rightarrow IF}$$
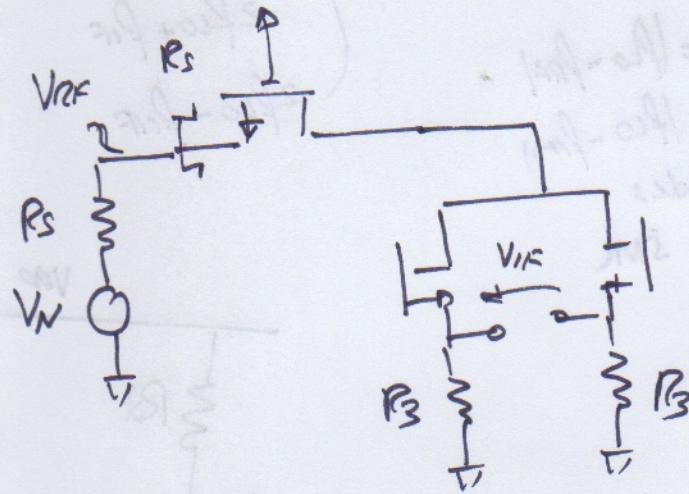
$$\Delta V_{out,IF}^{RS} = 4kT R_S \left( \frac{1}{2} \right)^2 A_v^2$$


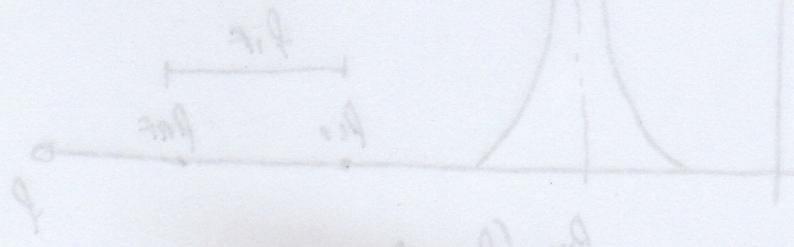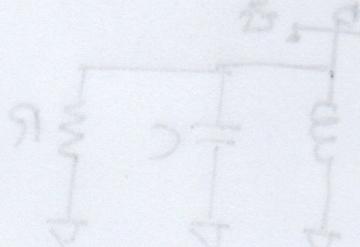
$$NF = 1 + \frac{4kT \frac{1}{\alpha} g_{m1} \left( \frac{R_S}{2} \right)^2 (A_v)^2}{4kT R_S \left( \frac{1}{2} \right)^2 A_v^2} = 1 + \frac{1}{\alpha} g_{m1} R_S = 1 + \frac{1}{\alpha} = 2,22 \text{ dB}$$




$$(20f - \omega_0) = 20$$


Ex 9.3

PROBLEM OF THE IMAGE FREQUENCY:


$$|V_{RF}(f)|$$

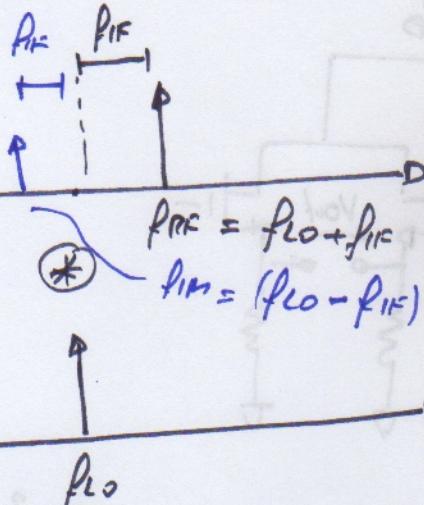


$$|V_{LO}(f)|$$

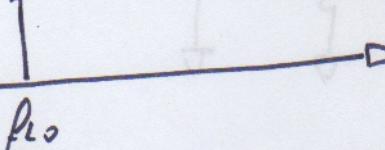

$$|V_{IF}(f)|$$

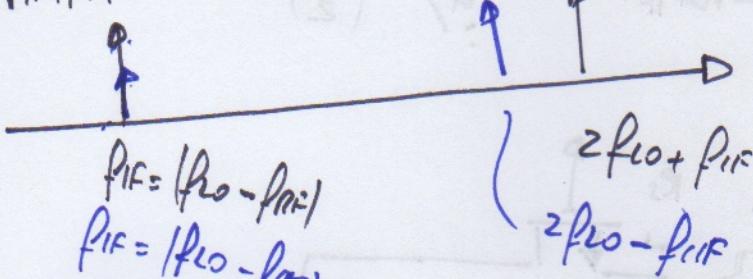


Decreases  
the SNR

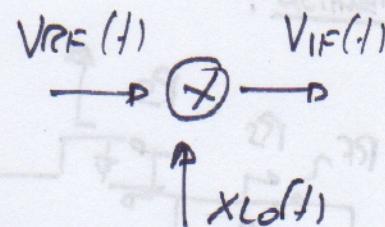


to cancel

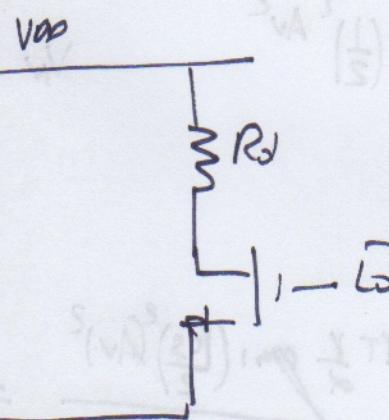We have to attenuate the image before the mixing.




IMPEDANCE  $Z_S$

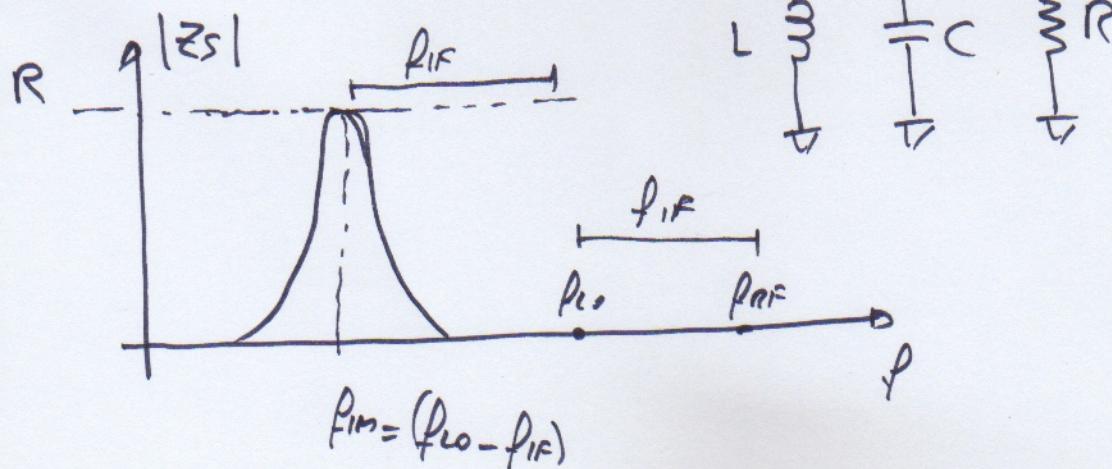


$$f_{IM} = (f_{LO} - f_{IF})$$


@  $\omega = \omega_{IM}$

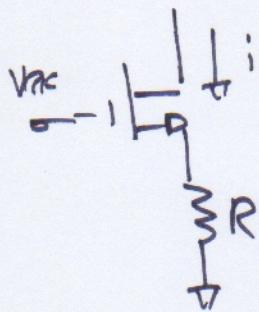


$$i^M = VRF \frac{gm_1}{(1 + gm_1 R)}$$

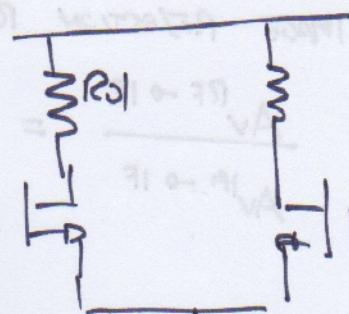

@  $\omega = \omega_{RF}$

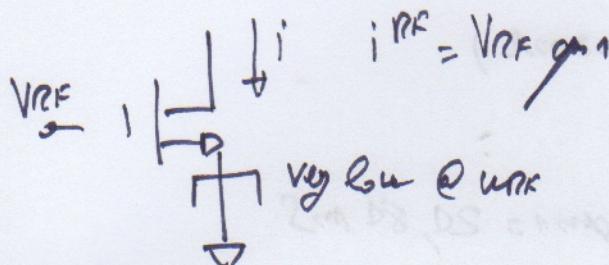

Very low @  $\omega_{RF}$

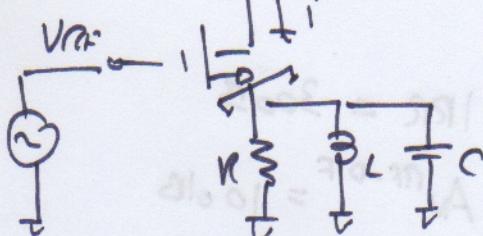


- CONVERSION GAIN:

@  $\omega_{RF}$

$$V_{IF}^{RF} = VRF \cos(\omega_{RF} t) gm_1 \left[ \frac{q}{\pi} \cos(\omega_{LO} t) \right] R_D$$

FIRST HARMONIC OF  $\chi_{LO}(t)$

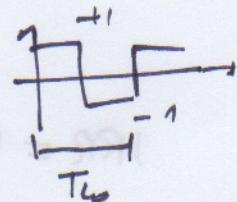

$$\approx \frac{1}{2} VRF \frac{q}{\pi} gm_1 R_D \cos \underbrace{(\omega_{RF} - \omega_{LO}) t}_{WIF} \quad (\text{Just LF component})$$

$$Av^{RF \rightarrow IF} = \frac{2}{\pi} gm_1 R_D$$

@  $\omega_{IM}$

$$V_{IF}^{IM} = VRF \cos(\omega_{IM} t) \frac{gm_1}{(1 + gm_1 R)} \left[ \frac{q}{\pi} \cos(\omega_{LO} t) \right] R_D$$

$$\approx \frac{1}{2} VRF \frac{gm_1}{(1 + gm_1 R)} \frac{q}{\pi} R_D \cos \underbrace{(\omega_{LO} - \omega_{IM}) t}_{WIF}$$

$$Av^{QIM \rightarrow IF} = \frac{2}{\pi} \frac{gm_1}{(1 + gm_1 R)} R_D$$

IRR = IMAGE REJECTION RATIO

$$= \frac{A_v^{RF \rightarrow IF}}{A_v^{IM \rightarrow IF}} = \frac{\frac{2}{F} g_m R_o}{\frac{2}{F} \frac{g_m R_o}{(1 + g_m R)}} = (1 + g_m R)$$


b)  $IRR = 300 \text{ dB}$  size  $(\frac{k}{L})$ , and  $R$

$$A_v^{RF \rightarrow IF} = 100 \text{ dB} \quad \leftarrow (R_o = 200 \text{ k}\Omega$$

$$A_v^{RF \rightarrow IF} = 10 \text{ dB} = \frac{2}{F} g_m R_o \quad \rightarrow g_m = 20,84 \text{ mS}$$

$$IRR = (1 + g_m R) = 300 \text{ dB} \quad \rightarrow R = 1,23 \text{ k}\Omega$$

BIAIS OF  $n1$

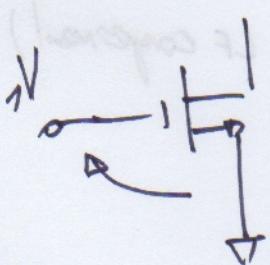

$$I = g_m \frac{V_{DD}}{2} = 6,21 \text{ mA}$$

$$I = \frac{1}{2} \mu C_{ox} \left(\frac{k}{L}\right) (V_{DD})^2$$

$$\rightarrow \left(\frac{k}{L}\right) = 125$$