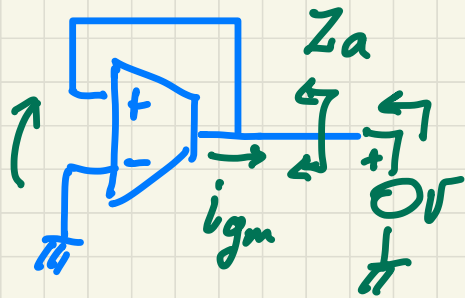


RF Circuit Design


L12





$$i_{gm} = G_m \cdot v ; \quad i = -G_m \cdot v$$

$$Z_a = \frac{v}{i} = -\frac{1}{G_m}$$

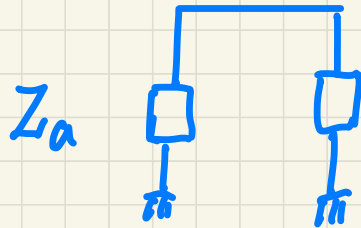

$$Z(s) = R \cdot \frac{s\omega_n/Q}{s^2 + s\frac{\omega_n}{Q} + \omega_n^2}$$

Oscillation condition: $Z_a(j\omega_0) + Z(j\omega_0) = 0$

$$-\frac{1}{G_m} + R \frac{j\omega_0 \omega_n / Q}{-\omega_0^2 + j\omega_0 \frac{\omega_n}{Q} + \omega_n^2} = 0 \quad \begin{cases} -\frac{1}{G_m} + R = 0 \\ \omega_0 = \omega_n \end{cases}$$


Practical Oscillator : amplitude stabilization mechanism

ex. LC oscillator


- $G_m R < 1$ poles in LHP

$V(t) \xrightarrow{\text{oscillation}} t$ $G_m \frac{A_0^2}{2} < \frac{A_0^2}{2R}$


energy provided < dissipated energy

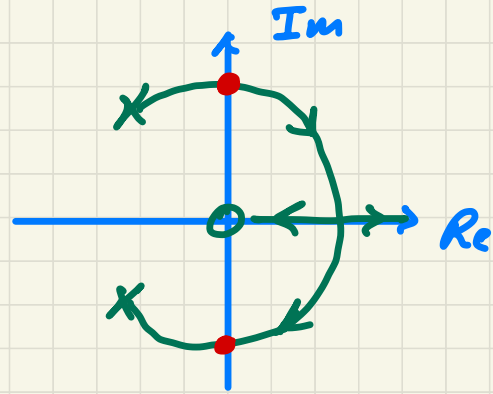

- $G_m R > 1$ poles in RHP

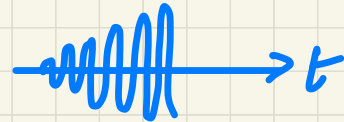


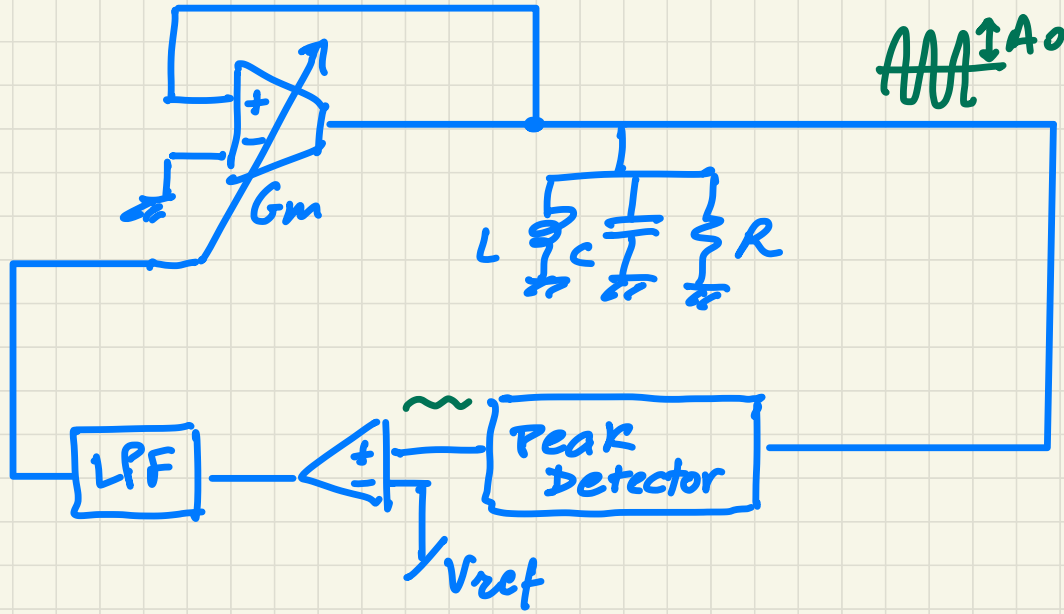1) Automatic amplitude control (negative feedback)



$$G_m = \frac{1}{R}$$

$$A_0 \rightarrow V_{ref}$$



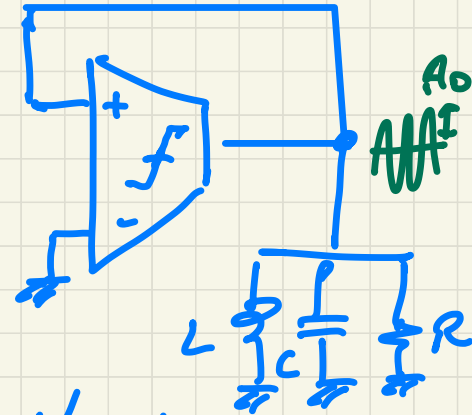


2) Nonlinearity of active devices

small-signal $G_m > 1/R$: oscillator starts up

Oscillation increases until the transconductor saturates

example :

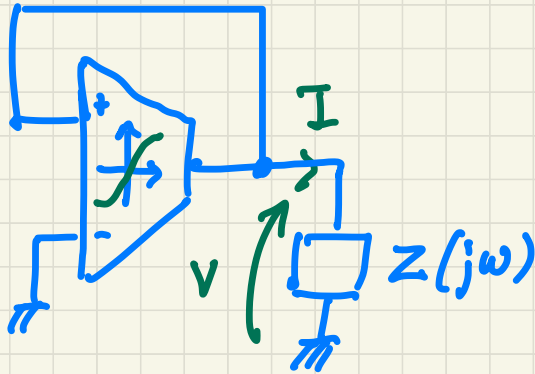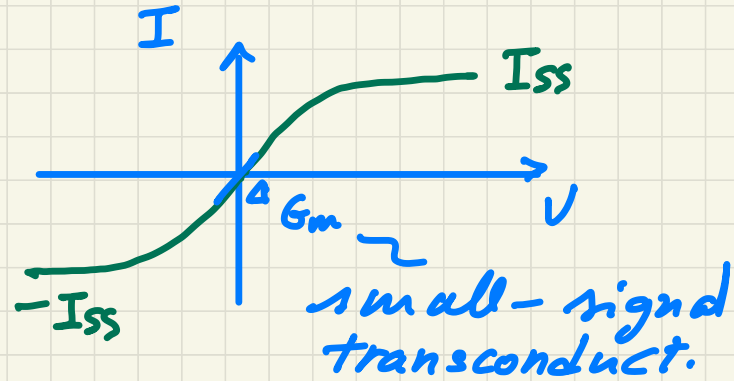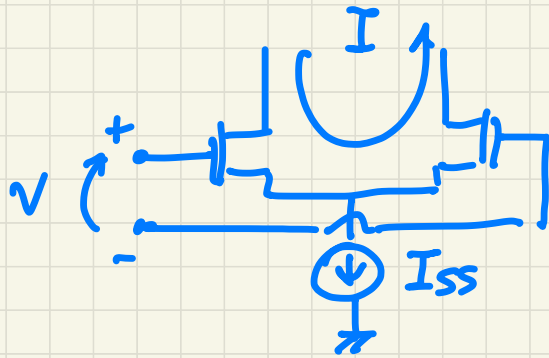

$$v(t) = \sum_{k=-\infty}^{+\infty} \bar{V}_k e^{jk\omega_0 t}$$

$v(t)$ is periodic with a. freq. ω_0

$$\begin{aligned} \text{a) } I(t) &= I[v(t)] = \\ &\uparrow \text{non linear device} \\ &\text{resonator} \\ &\downarrow \\ \text{b) } \bar{V}_k &= \bar{I}_k \cdot Z(k\omega_0) \end{aligned}$$

$$\begin{aligned} I(t) &= I[v(t)] = \\ &= I\left[\sum_k \bar{V}_k e^{jk\omega_0 t}\right] = \\ &= \sum_k \bar{I}_k e^{jk\omega_0 t} \end{aligned}$$

$$\begin{cases} \bar{I}_1 \cdot Z(\omega_0) = \bar{V}_1 \\ \bar{I}_2 \cdot Z(2\omega_0) = \bar{V}_2 \\ \vdots \\ \bar{I}_n \cdot Z(n\omega_0) = \bar{V}_n \end{cases}$$


In analysis, we
assume to study
HARMONIC OSCILLATORS
($v(t)$ is sinusoidal)
i.e. high Q factor*

harmonic balance with
 n -harmonics (HB)

↓

$$\bar{I}_1 \cdot Z(\omega_0) = \bar{V}_1 ;$$
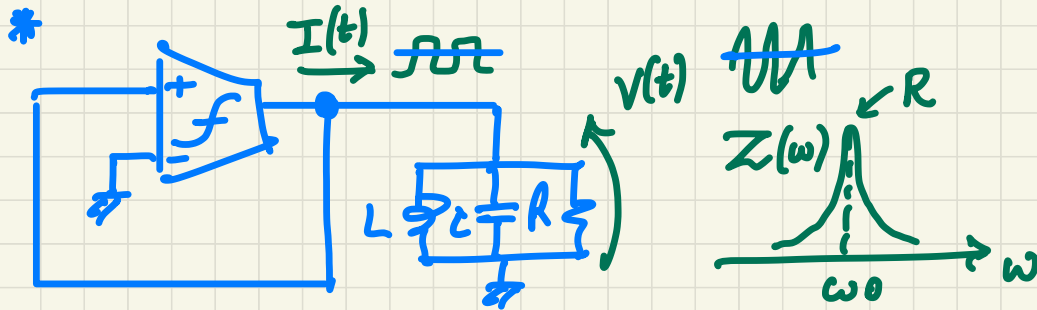
$$Z(\omega_0) = \frac{\bar{V}_1}{\bar{I}_1}$$



$$Z(j\omega_0) = \frac{\bar{V}_1}{\bar{I}_1}$$

\Downarrow


$$Z(j\omega_0) = \frac{1}{G_{mh}}$$

\Downarrow

$$G_{mh} \cdot Z(j\omega_0) = L G_h(j\omega_0) = 1$$

\uparrow


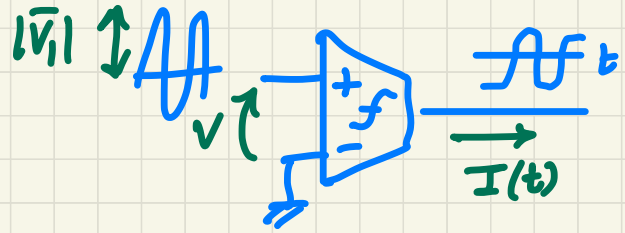
We replaced the small-signal G_m with
a harmonic G_m (method of Descriptive Function)



$$\frac{\bar{I}_1}{\bar{V}_1} \triangleq G_{mh}$$


HARMONIC transconduct.
(effective)

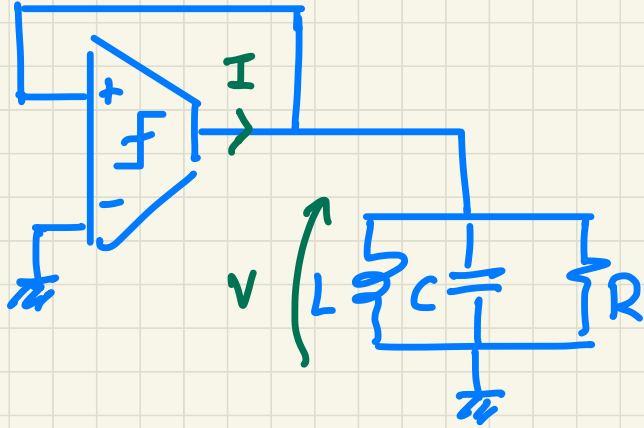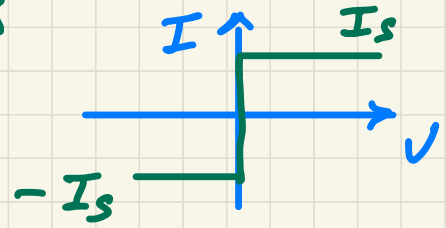case : $I(v) = I_s \cdot \text{sgn} \{V(t)\}$



Hyp: $V(t) = A_0 \cos \omega_0 t$

$\Rightarrow \bar{V}_1 = A_0$


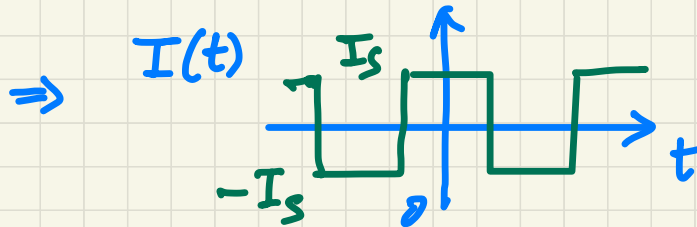


$\Rightarrow \bar{I}_1 = \frac{4}{\pi} \cdot I_s$

$LG_h(j\omega_0) = 1 \Rightarrow \begin{cases} G_{mh} \cdot R = 1 \text{ where } G_{mh} = \frac{\frac{4}{\pi} I_s}{A_0} \\ \omega_0 = \frac{1}{\sqrt{LC}} \end{cases}$

$$\underbrace{\frac{4}{\pi} \frac{I_s}{A_0}}_{G_{mh}} \cdot R = 1 \quad ; \quad A_0^* = \frac{4}{\pi} \cdot I_s \cdot R$$
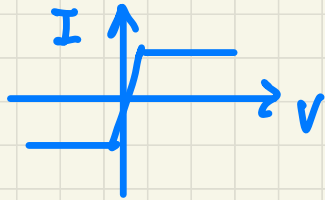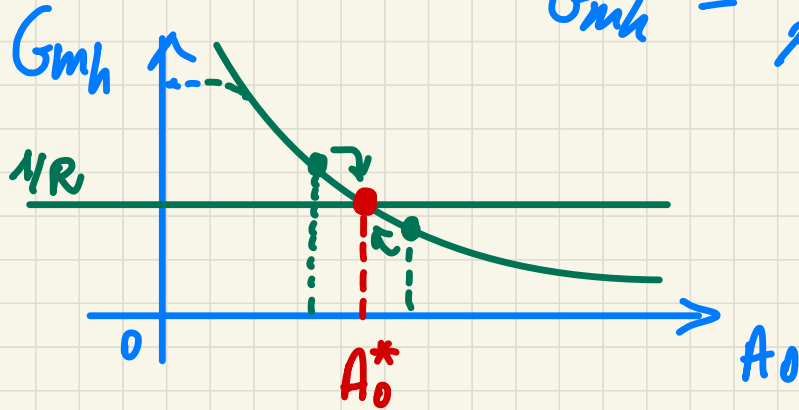
$$G_{mh} = \frac{1}{R} \quad \text{oscillation condition}$$



• if $A_0 > A_0^*$:


$$G_{mh} \cdot R < 1$$

poles into LHP

$\rightarrow A_0 \downarrow$

• if $A_0 < A_0^*$:
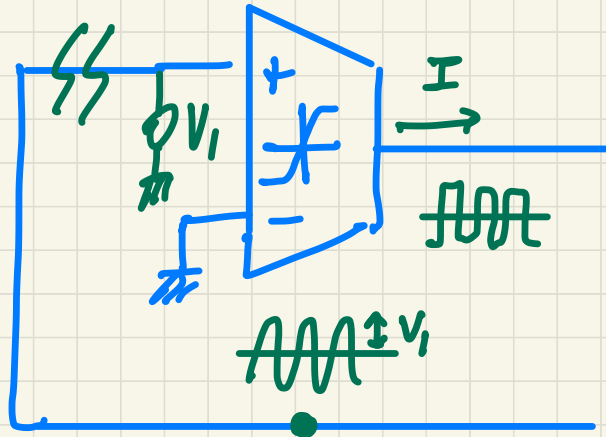
$$G_{mh} R > 1 \rightarrow A_0 \uparrow$$



Hyp. $V(t)$ sinusoidal
at ω_0





$$V_1 = I_1 \cdot Z(j\omega_0)$$

consistency equation



$$LG_h = \underbrace{\frac{I_1}{V_1}}_{\text{harmonic Gm}} \cdot Z(j\omega_0) = 1$$


harmonic Gm

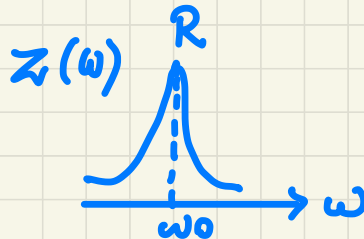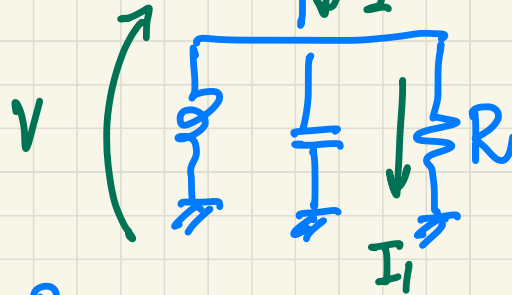

Ex. of real oscillators

- Differential oscillator

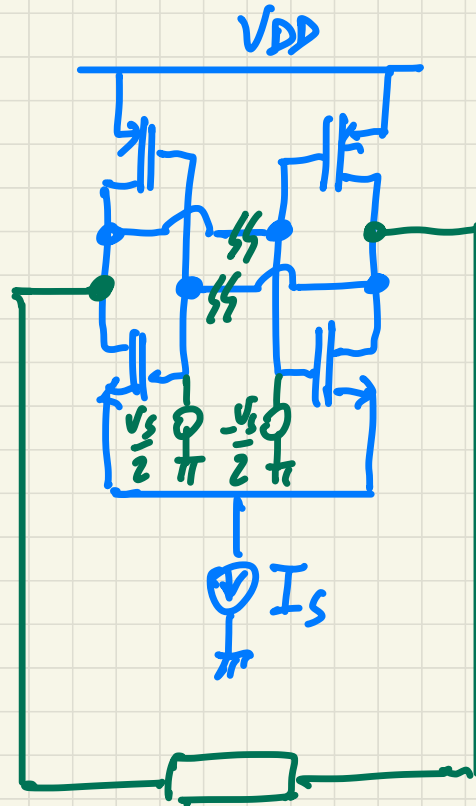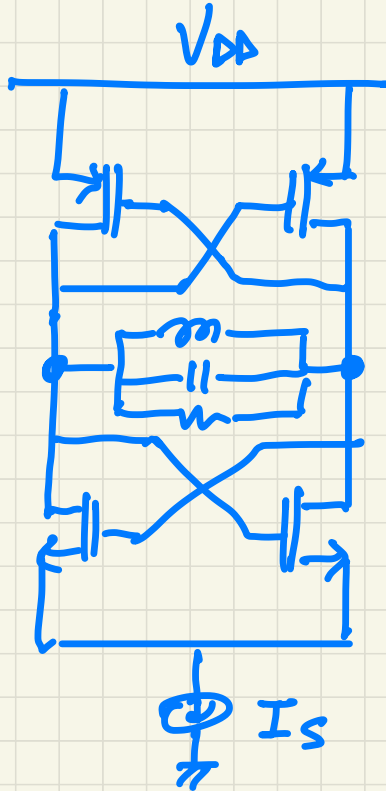

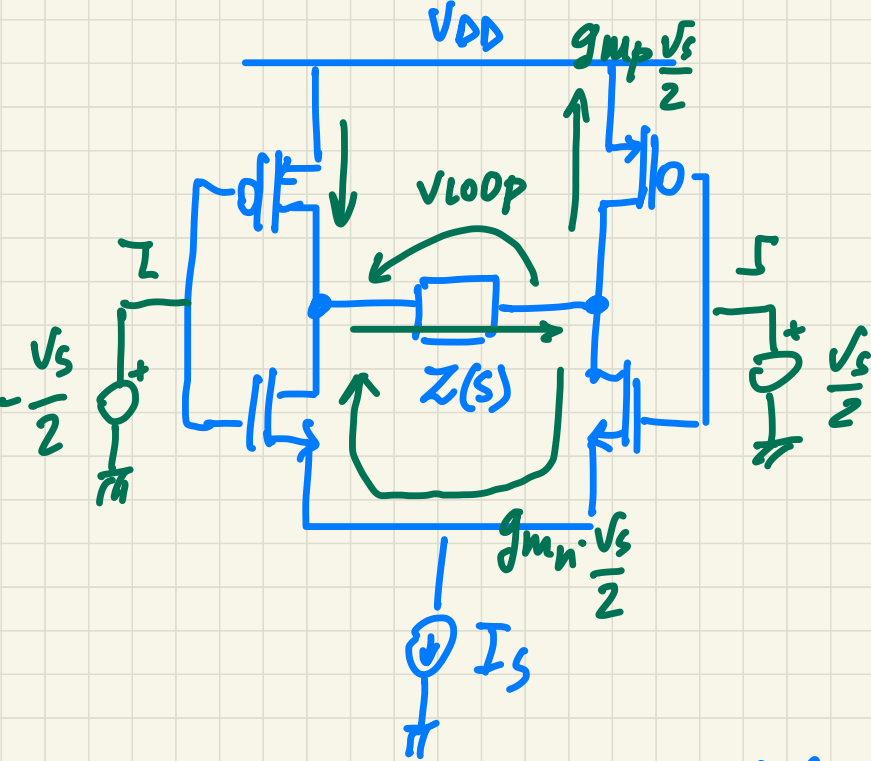

Differential mode

$$LG(s) = \frac{V_{loop}}{V_s} =$$

$$= Z(s) \cdot \underbrace{\frac{g_{mn} + g_{mp}}{2}}_{\text{small-signal } G_m}$$

Oscillation condition


$$LG(j\omega_0) = 1 :$$

$$\bullet \quad \angle LG(j\omega_0) = 0 ; \quad \angle Z(j\omega_0) = 0 ;$$

$$\omega_0 = \omega_r = \frac{1}{\sqrt{LC}}$$



$$\bullet \quad |LG(j\omega_0)| = 1 ; \quad \frac{g_{mn} + g_{mp}}{2} \cdot R = 1$$

Oscillator design :



- Startup condition : $LG(j\omega_0) > 1$ 

Startup margin $LG(j\omega_0) = \underset{\text{excess gain}}{EG} > 1$

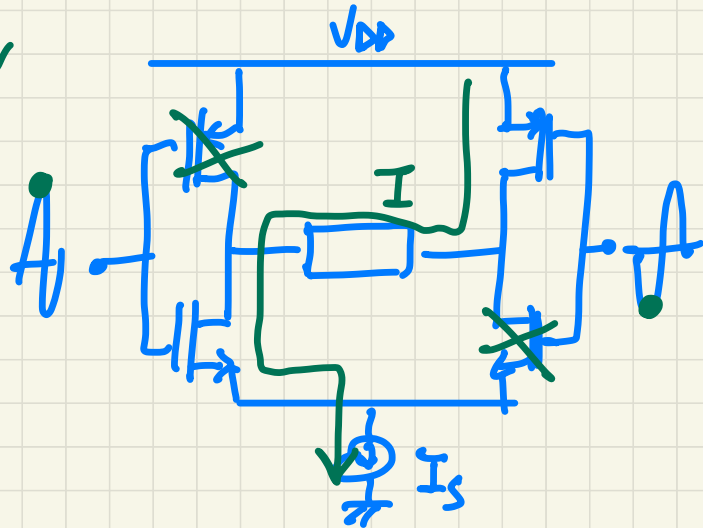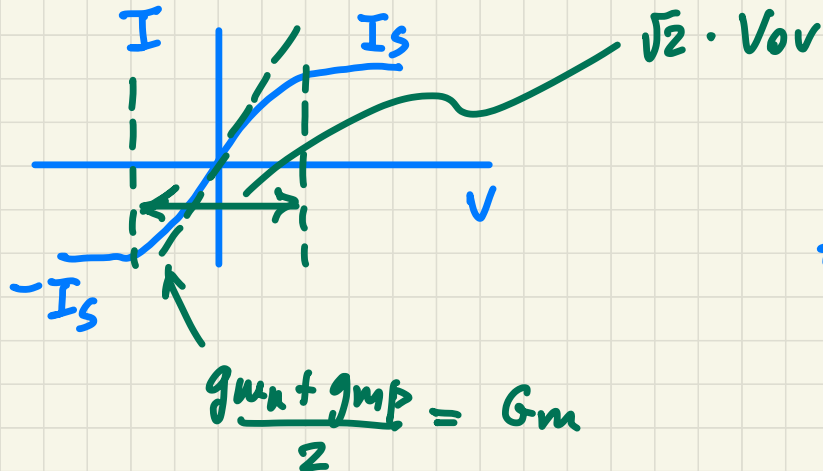- Oscillation amplitude : $LG_h(j\omega_0) = 1$





$$A_0^* \gg \sqrt{2} \cdot V_{ov}$$

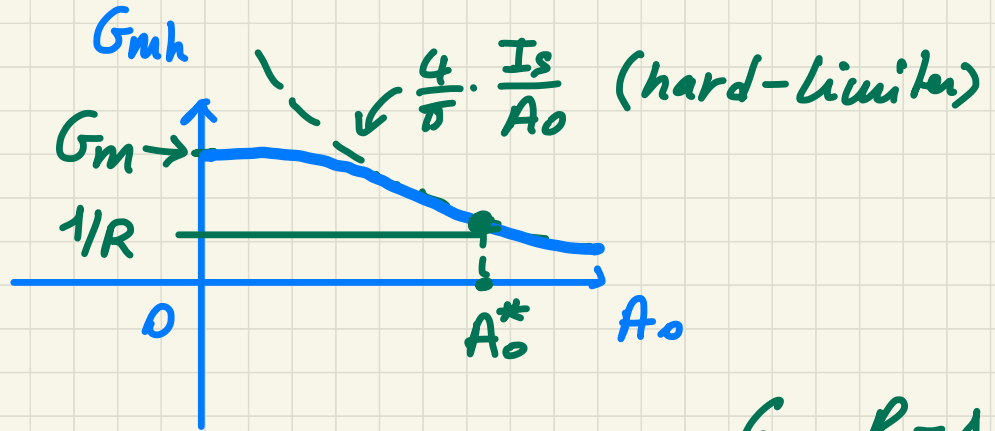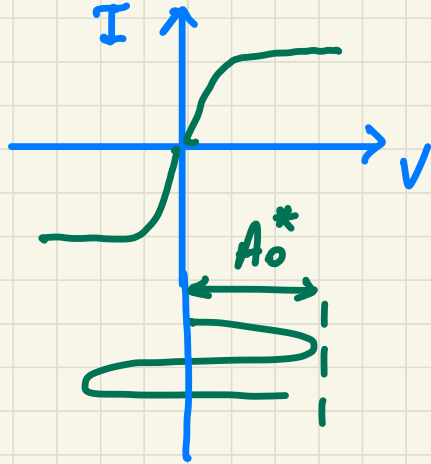


$$A_0^* \approx \frac{4}{\pi} I_s \cdot R$$

$$\Leftarrow G_{mh} \cdot R = 1$$


- Single-transistor oscillators

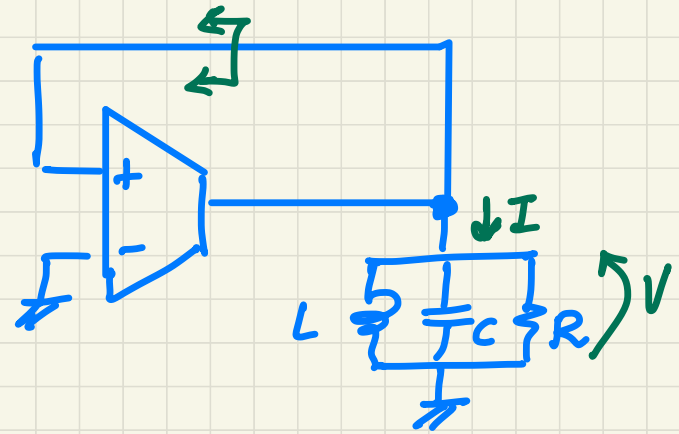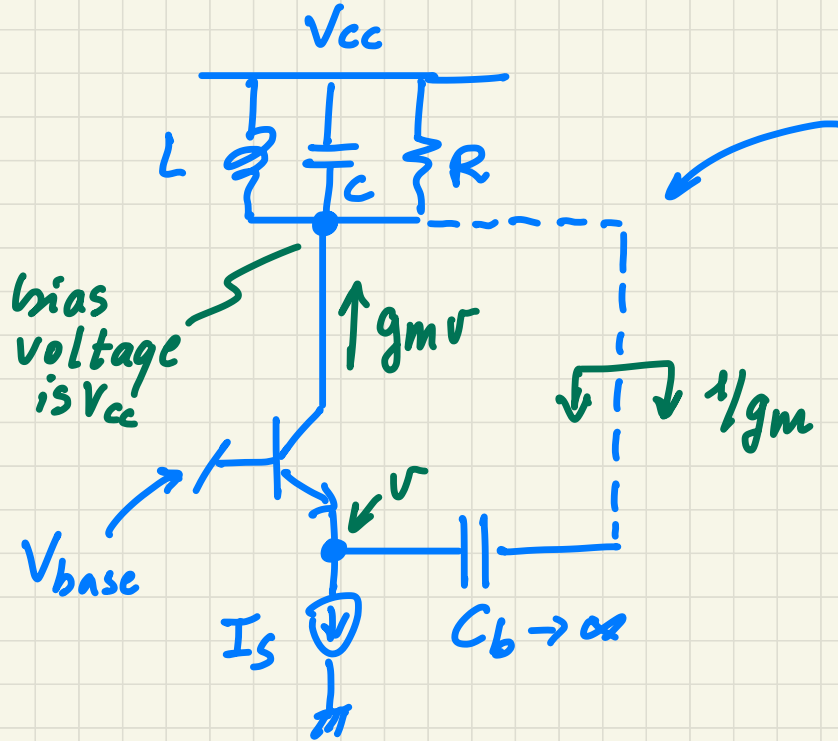


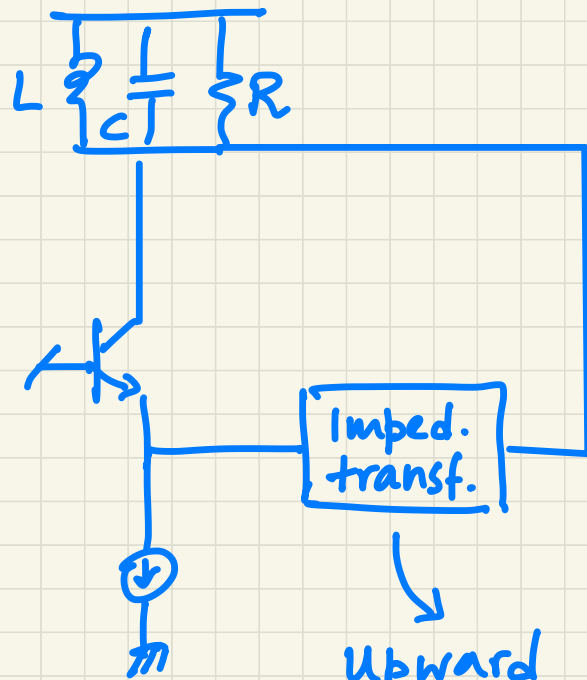we cannot connect the emitter to the resonator without spoiling the resonator's Q ?




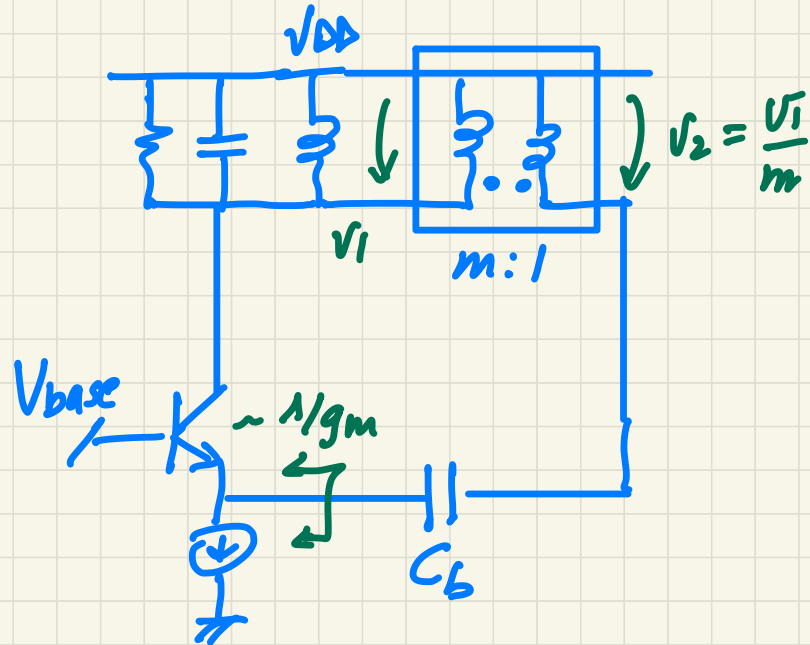upward :
voltage attenuation $\Rightarrow m > 1$



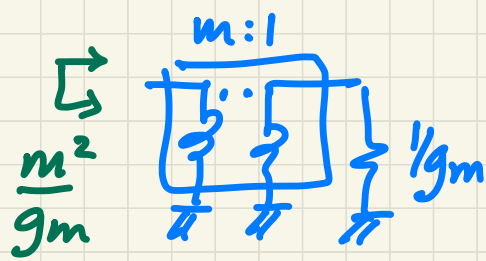

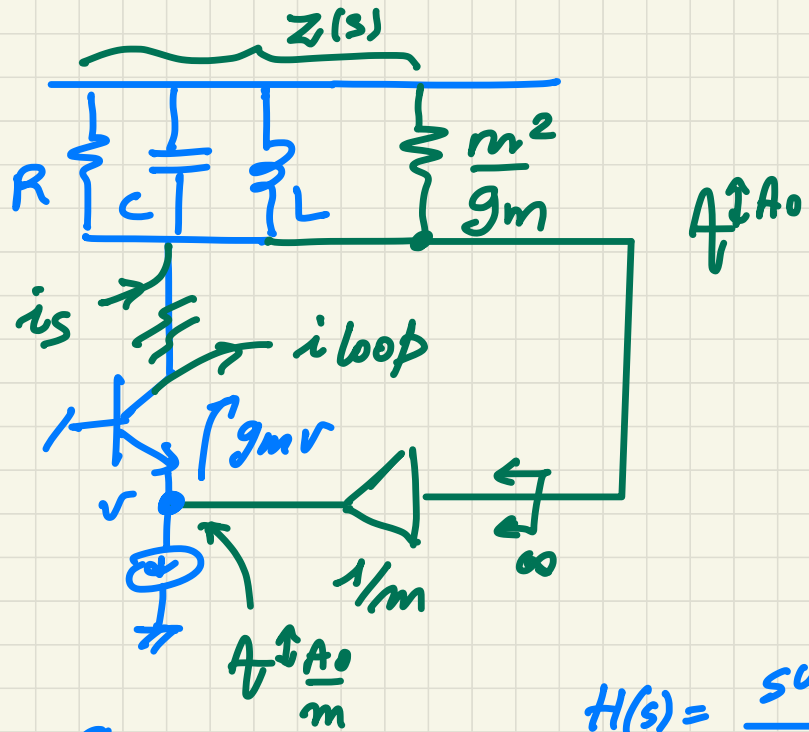Equivalent circuit
to compute
the loop gain



$$LG(s) = \frac{i_{loop}}{i_s} = Z(s) \cdot \frac{g_m}{m}$$

$$H(s) = \frac{s\omega_n/Q}{s^2 + s\frac{\omega_n}{Q} + \omega_n^2}$$

$$Z(s) = R_T \cdot H(s)$$

$$R_T = \frac{R \cdot \frac{m^2}{g_m}}{R + \frac{m^2}{g_m}} = \frac{m^2 \cdot R}{m^2 + g_m R}$$

$$LG(s) = \frac{g_m}{m} Z(s)$$

$$Z(s) = R_T \cdot H(s)$$

oscillation condition $LG(j\omega_0) = 1$:

$$LG(j\omega_0) = \frac{g_m}{m} \cdot R_T \cdot H(j\omega_0) = 1$$

$$\nexists LG(j\omega_0) = 0 : \underline{\omega_0 = \omega_c} \qquad |LG(j\omega_0)| = \frac{g_m}{m} \cdot R_T = 1$$

$$\frac{g_m}{m} \cdot \frac{\omega^2 R}{\omega^2 + g_m R} = 1 \quad \dots$$

$$\Rightarrow \underline{g_m R = \frac{m}{1 - 1/m}}$$


$$g_m R = \frac{m}{1 - 1/m}$$

At large m :

$g_m R \nearrow$

At small m :

$g_m R \nearrow$

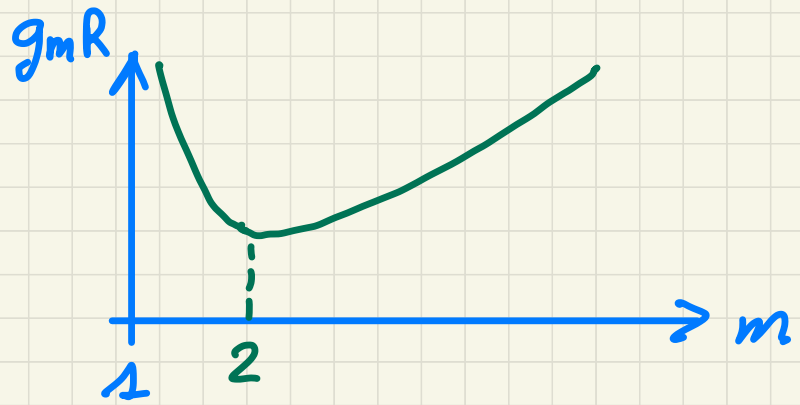


min. gain $g_m R = \frac{2}{1 - 1/2} = 4$
is obtained for $m=2$

trade-off in the choice of m


$m=2$: startup condition $g_m R > 4$

Oscillation amplitude

Large-signal

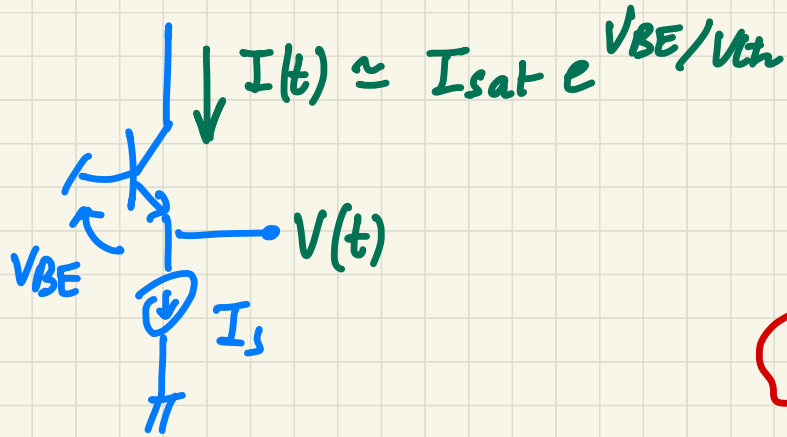

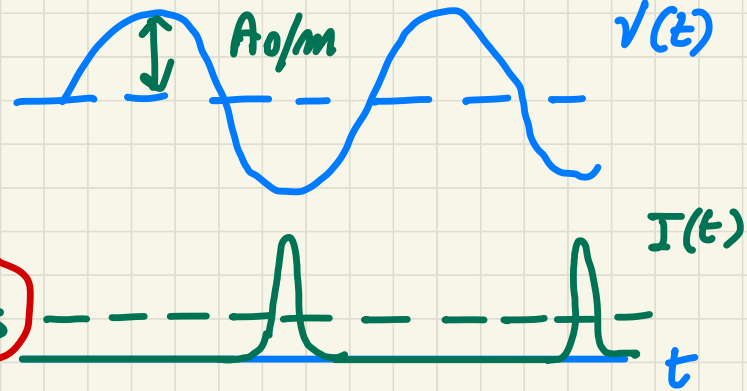
$$I(t) \approx I_{sat} e^{V_{BE}/V_{th}}$$



Approximation

$$\frac{A_0}{m} \gg \frac{kT}{q} = V_{th}$$
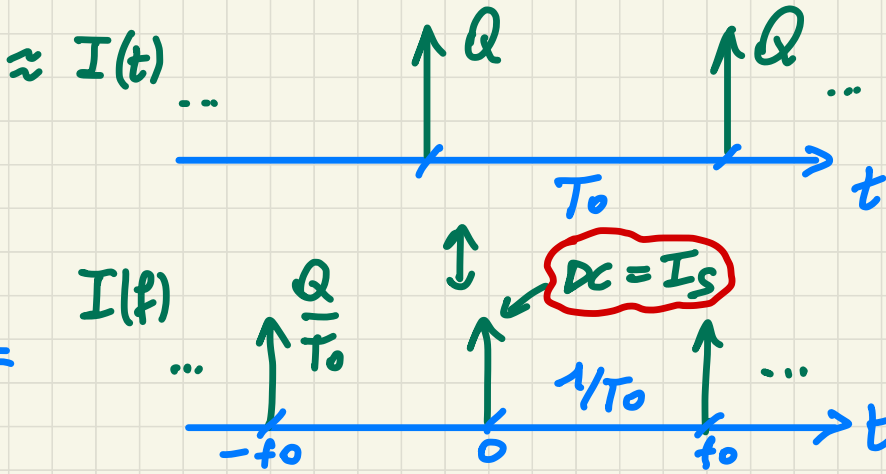
$$I(t) \approx Q \cdot \sum \delta(t - kT_0) = \frac{Q}{T_0} \cdot \sum e^{-jk\omega_0 t}$$



harmonic g_m

$$I_1 = 2 \cdot Q/T_0$$

$$g_{mh} = \frac{\overline{I_1}}{\overline{V_1}} = \frac{2 Q/T_0}{A_0/m} = \frac{2 I_s}{A_0/m}$$

Oscillation condition (large signal)

$$LG_h(j\omega_0) = 1 \quad \Leftrightarrow \quad \underbrace{g_{mh} R}_{\substack{\uparrow \\ \text{we replace} \\ \text{small-signal } g_m}} = \frac{m}{1 - \frac{1}{m}} ;$$

$$\frac{2 I_s}{A_0} \cancel{m} \cdot R = \frac{\cancel{m}}{1 - \frac{1}{m}} ; \quad A_0 = 2 I_s R \cdot \left(1 - \frac{1}{m}\right)$$

$$m = 2 : A_0 = 2 I_s R \cdot \frac{1}{2} = I_s R$$

$\swarrow m=1$
0 $\searrow m \rightarrow \infty$
2 $I_s R$