
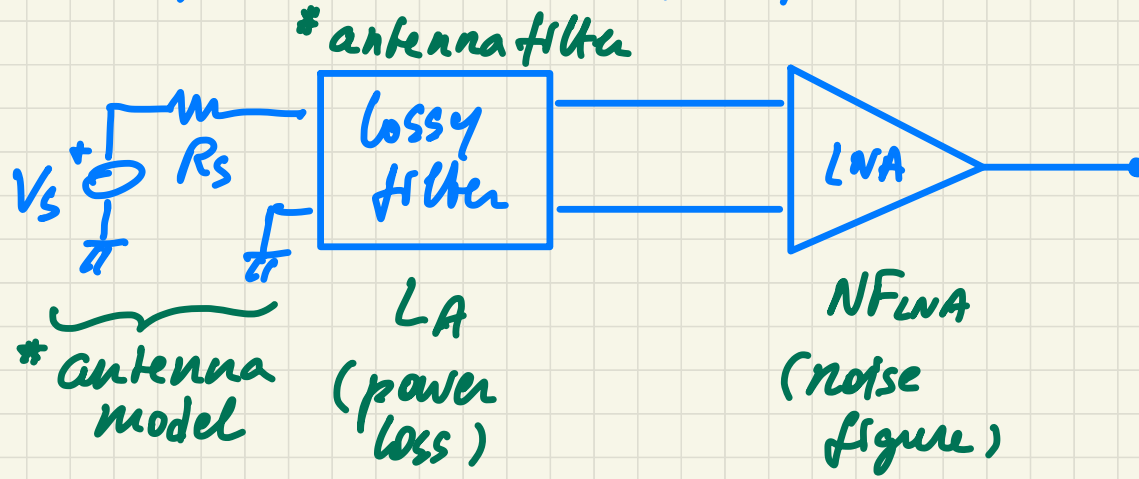


RF Circuit Design

L17



Example of NF of filter + LNA cascade



Total noise figure :


$$\begin{aligned}
 NF &= NF_{\text{filter}} + \frac{NF_{LNA} - 1}{\underbrace{1/LA}_{\text{ar. power gain of stage 1}}} = \\
 &= LA + LA(NF_{LNA} - 1) = \\
 &= LA \cdot NF_{LNA}
 \end{aligned}$$

$$\overset{\text{dB}}{\Rightarrow} NF_{\text{dB}} = L_{A,\text{dB}} + NF_{\text{LNA},\text{dB}}$$

$$\begin{aligned} \text{e.g. } L_A &= 2 \text{ dB} \\ NF_{\text{LNA}} &= 1.6 \text{ dB} \end{aligned} \Rightarrow NF = 3.6 \text{ dB}$$

Noise figure of the LNA is amplified by the losses of the previous passive filter

Noise matching

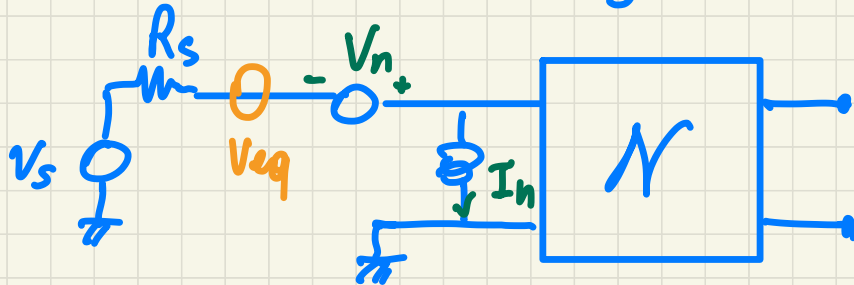

V_n, I_n input-ref. noise sources of N



correlated (origin from the same physical noise source)

$$NF = 1 + \frac{\text{Network noise in } V_{eq}}{\text{source noise in } V_{eq}} =$$


$$= 1 + \frac{(V_n + I_n R_s)^2}{4kTR_s}$$

$$\approx 1 + \frac{\overline{V_n^2} + \overline{I_n^2} R_s^2}{4kTR_s}$$

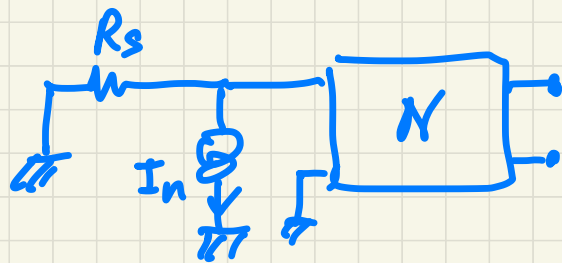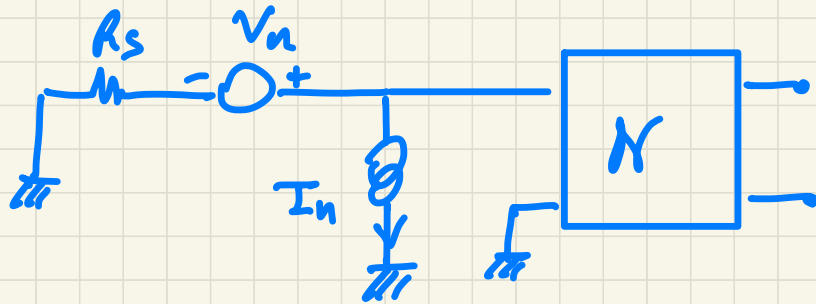Hyp. V_n, I_n uncorrelated
(approximation)



\equiv

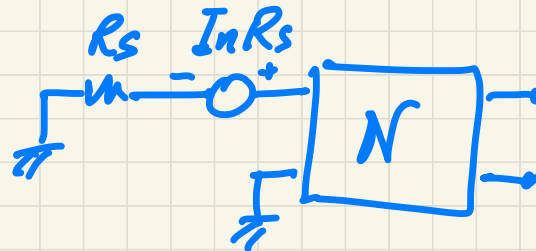

$$\Rightarrow NF = 1 + \frac{\overline{V_n^2}}{4kTR_s} + \frac{\overline{I_n^2}}{4kT/R_s}$$

Network voltage noise (points to $\overline{V_n^2}$)
 source voltage noise (points to $4kTR_s$)
 Network current noise (points to $\overline{I_n^2}$)
 Source current noise (points to $4kT/R_s$)


NF has a term decreasing with R_s
 and a term increasing with R_s

\Rightarrow an NF_{min} exists for an opt. R_s

$$\frac{\partial NF}{\partial R_s} = 0 \Rightarrow R_{s,opt} = \sqrt{\frac{\overline{V_n^2}}{\overline{I_n^2}}}$$

RX sensitivity and Dynamic Range

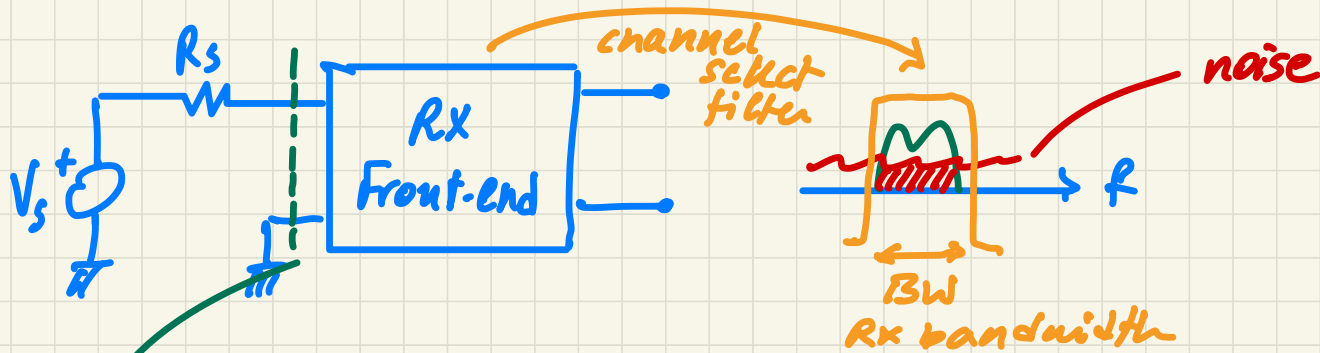
RX sensitivity = min. detectable signal ($SNR = SNR_{min}$)



$P_{s,av(min)}$ sensitivity

$$SNR_{min} = \frac{P_{s,av(min)}}{P_{n,av}}$$
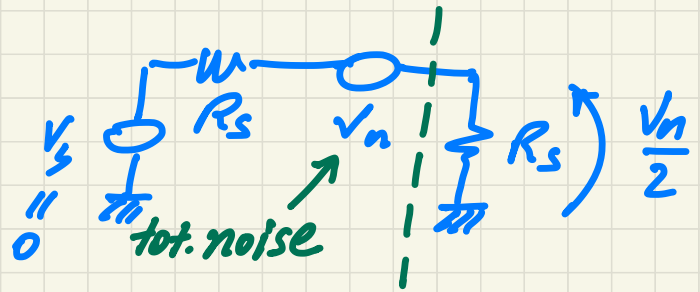
$$\frac{P_{n,av}}{\Delta f} = \frac{\frac{\overline{V_n^2}}{R_s} \cdot \frac{1}{4}}{\Delta f} =$$



$$= \frac{\cancel{4kTR_s} \cdot N_{F_{Rx}}}{\cancel{R_s}} = \Leftarrow \frac{\overline{V_n^2}}{\Delta f} = 4kTR_s \cdot N_{F_{Rx}}$$

$$= \underbrace{KT}_{\text{available power density of the source noise}} \cdot N_{F_{Rx}}$$

available power density
of the source noise

$$\Rightarrow P_{n,av} = KT \cdot N_{F_{Rx}} \cdot BW \Rightarrow SNR = \frac{P_{s,avmin}}{KT \cdot N_{F_{Rx}} \cdot BW}$$

$$\Rightarrow P_{s,armin} = \underbrace{KT} \cdot N F_{rx} \cdot SNR_{min} \cdot BW$$

$$KT \simeq 4 \cdot 10^{-21} \text{ J at } 25^\circ \text{ temperature}$$

$$\Rightarrow 10 \log_{10} KT = -204 \text{ dBW/Hz} =$$

$$= -174 \text{ dBm/Hz}$$

dB
→

$P_{s,armin}$
sensitivity
in dBm

$$= -174 \frac{\text{dBm}}{\text{Hz}} + N F_{rx}|_{\text{dB}} + SNR_{min}|_{\text{dB}} +$$

$$+ 10 \log(BW)$$




e.g. GSM handset :

- sensitivity $P_S = -100 \text{ dBm}$
- $BW = 200 \text{ KHz}$
- $SNR_{min} = 9 \text{ dB}$

$$\Rightarrow NFR_x = P_S + 174 - SNR_{min} - 10 \log(BW) =$$
$$= -100 + 174 - 9 - 53 =$$
$$= -162 + 174 = 12 \text{ dB}$$

$2 \cdot 10^5 \Rightarrow 3 + 50$


Dynamic Range

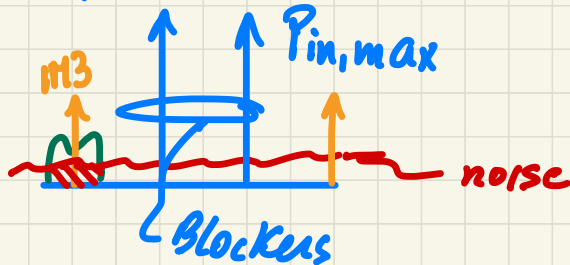

SFDR spurious free dynamic range

$$SFDR_{dB} = \underbrace{P_{in,max}}_{\substack{\text{input power of} \\ \text{the two tones such} \\ \text{that } IM3 \text{ power equals} \\ \text{noise power}}} - \underbrace{P_{in,min}}_{\substack{\text{sensitivity} \\ \text{level}}}$$
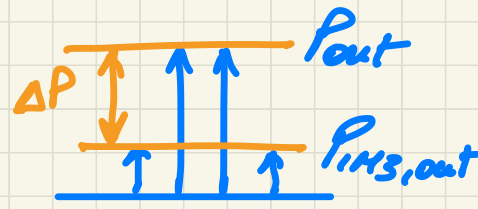
$$P_{11P3 \text{ dBm}} = P_{in} + \frac{\Delta P}{2}$$



$$G_{dB} = P_{out} - P_{in}$$

$$P_{11P3} = P_{in} + \frac{P_{out} - P_{1M3,out}}{2} =$$

$$= P_{in} + \frac{P_{in} + \cancel{GA} - (P_{1M3,in} + \cancel{GA})}{2} =$$

$$= \frac{3}{2} P_{in} - \frac{1}{2} P_{1M3,in}$$

input-referred
level of 1M3
products

$$P_{11P3} = \frac{3}{2} P_{in, \text{max}} - \frac{1}{2} P_n$$

1M3 = noise level

input-referred
level of noise

$$\Rightarrow P_{in, max} (dBm) = \frac{2 P_{11} P_3 + P_n}{3}$$


$$SFDR = P_{in, max} - P_{in, min} = \quad \swarrow \quad SNR_{min} = P_{in, min} - P_n$$

$$= \frac{2}{3} P_{11} P_3 + \frac{1}{3} P_n - (P_n + SNR_{min}) =$$

$$= \frac{2}{3} P_{11} P_3 - \frac{2}{3} P_n - SNR_{min} =$$

$$= \frac{2}{3} (P_{11} P_3 - P_n) - SNR_{min}$$

Scattering Parameters or S-parameters

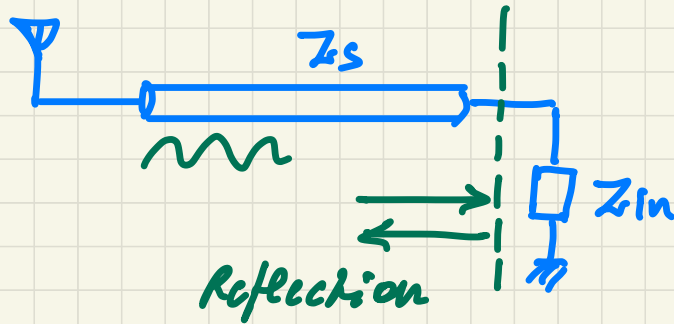

Reflection coefficient

$$\Gamma = \frac{P_{\text{reflected}}}{P_{\text{incident}}}$$


$$\Gamma = \left| \frac{Z_{in} - Z_s}{Z_{in} + Z_s} \right|^2$$

only if $Z_{in} = Z_s$: $\Gamma = 0$
no reflection ("termination" is
matched to the characteristic
impedance of the line)

↙

$$P_{\text{ref}} = \Gamma \cdot P_{\text{inc}}$$

Extension to 2-port networks

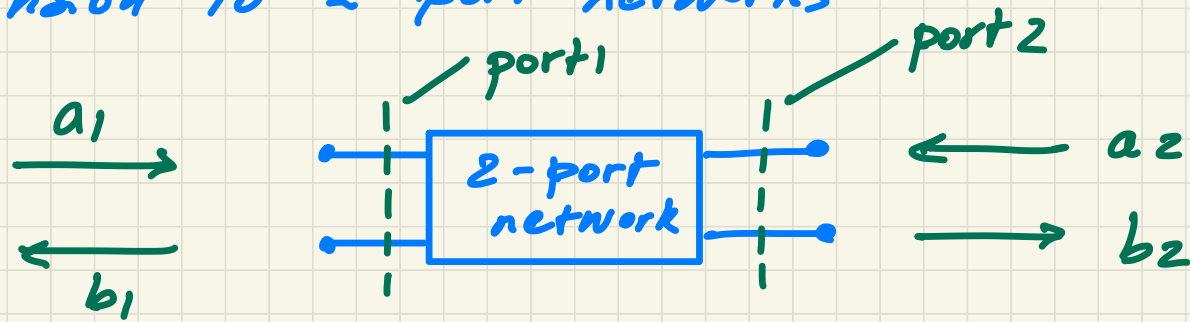

a_1 is incident power wave at port 1

b_1 is reflected power wave " " "

$$\begin{cases} b_1 = S_{11} \cdot a_1 + S_{12} a_2 \\ b_2 = S_{21} a_1 + S_{22} a_2 \end{cases}$$

scattering or S param
 $\begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix}$

$$S_{11} = \frac{b_1}{a_1}$$

capital "S"



\uparrow
 small "s"

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{\underbrace{V_2^+ = 0}_{\text{matched load at port 2}}} \Rightarrow S_{11} \text{ is the reflection coefficient at port 1 with matched port 2}$$


Input return loss : $RL_{in} = 10 \log_{10} \frac{1}{|S_{11}|^2} =$

Output return loss : $= -20 \log_{10} \{ |S_{11}| \}$

$$RL_{out} = -20 \log_{10} \{ |S_{22}| \}$$

Forward gain $20 \cdot \log \{s_{21}\}$


Reverse isolation $-20 \log \{s_{12}\}$

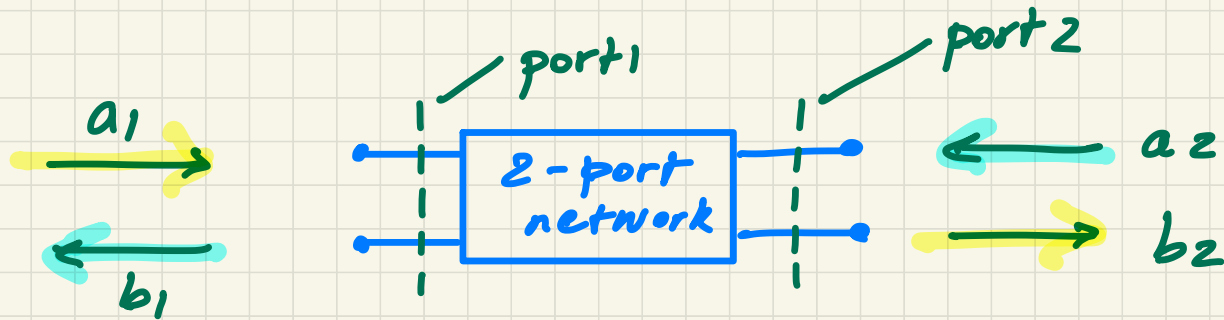

$$s_{21} = \frac{b_2}{a_1}$$


$$s_{12} = \frac{b_1}{a_2}$$

↑
capital "s"

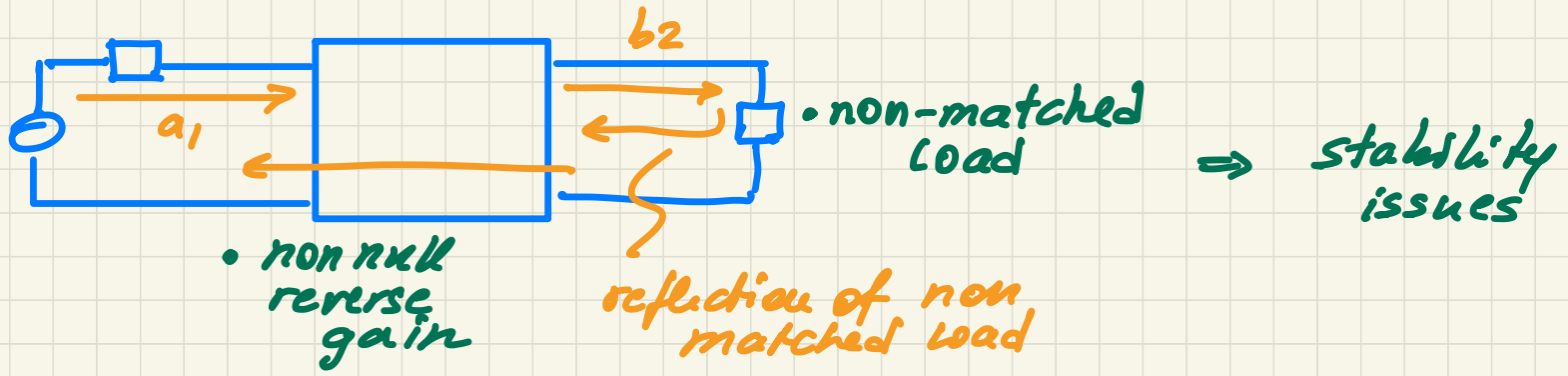

Low - Noise Amplifiers (LNAs)

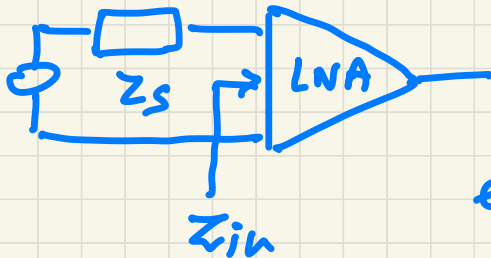- low noise (NF noise figure)
- large gain (G_A or S_{21} power gain)
- input matching (Return loss $1/S_{11}$)



$$S_{11} = \left| \frac{Z_{in} - Z_s}{Z_{in} + Z_s} \right|^2$$

e.g. $Z_s = 50 \Omega$
 $Z_{in} = 40 \Omega$


typ. $S_{11} = -10 \text{ dB}$
is acceptable

$$\Rightarrow S_{11} = 20 \log \left| \frac{40 - 50}{40 + 50} \right| = -20 \text{ dB}$$

$P_{ref} = 0.1 \cdot P_{inc}$ (loss of 10%)


- linearity (1IP3 intercept point) because of blocking

Common - gate topology

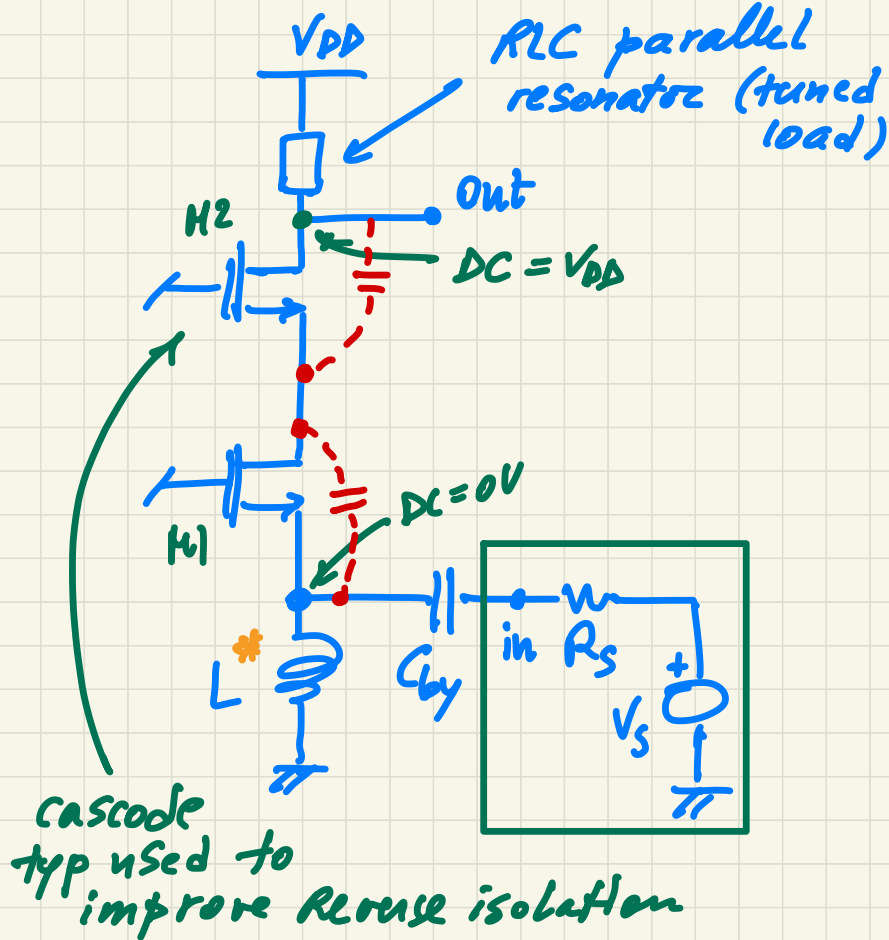

* choke inductor

$$\frac{di_L}{dt} = \frac{V_L}{L}$$

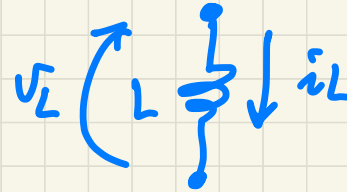


$$L \rightarrow \infty$$

$$\Rightarrow \frac{di_L}{dt} \rightarrow 0$$

$$\Rightarrow i_L \rightarrow \text{constant}$$

Sufficiently large ind. is used as a current generator

at center frequency
to A

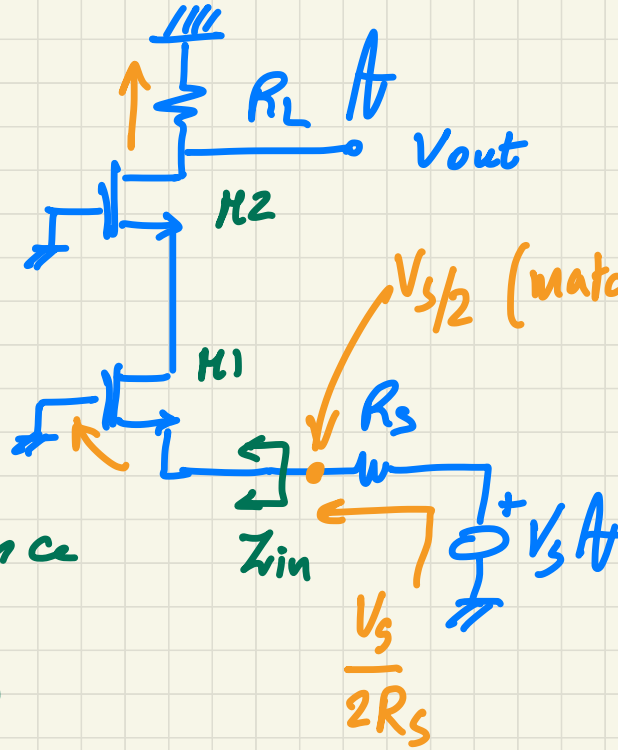

input impedance

$$Z_{in} \approx \frac{1}{g_{m1}}$$

neglecting r_{o1}
neglecting C_{gs1} , C_{ds1} , C_{sb1}

• Matching condition


$$g_{m1} = \frac{1}{R_s}$$

$$R_s = 50 \Omega :$$

$$g_m = 20 \text{ mS}$$

• Voltage gain
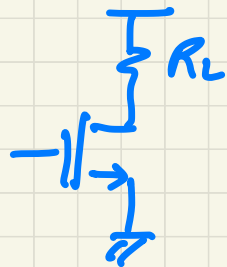
$$A_o = \frac{V_{out}}{V_s} \stackrel{\text{match}}{=} \frac{V_s/2R_s \cdot R_L}{V_s} = \frac{R_L}{2R_s}$$




$$g_m R_L = \frac{2I}{V_{ov}} \cdot R_L = 2 \frac{V_{RL}}{V_{ov}}$$

e.g. $f_0 = 1 \text{ GHz}$ $L = 1 \text{ nH}$

$$Q = 10$$

$$\Rightarrow R_L = 62.8 \Omega$$

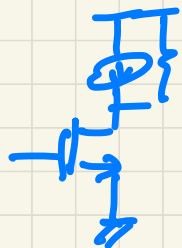


$$g_m r_o = \dots$$

$$R_s = 50 \Omega$$

$$\Rightarrow A_0 = \frac{R_L}{2R_s} = 1 \div 10$$

↓

$$0 \div 20 \text{ dB}$$

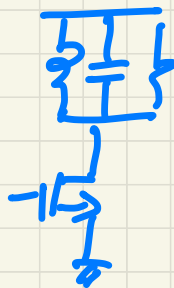

$$R_L = \omega_0 L Q$$

$$Q = \frac{R_L}{\omega_0 L}$$

$$g_m R_L$$

at RF

$$R_L \approx 100 \div 1000 \Omega$$