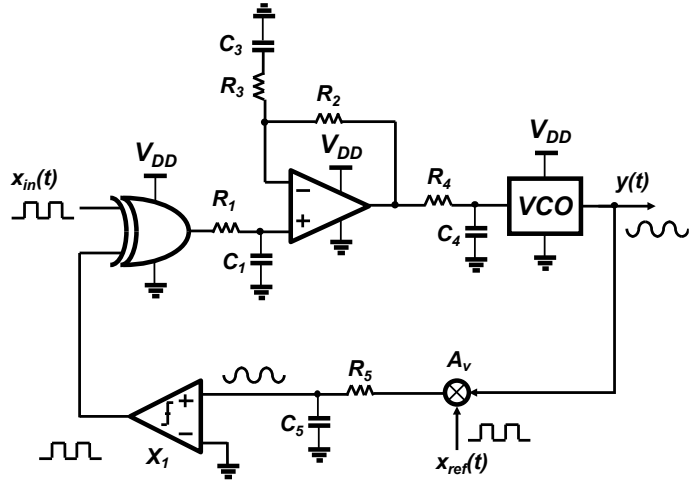


RF Circuit Design**Prof. Salvatore Levantino**Available time: 120 minutes

Jul. 22, 2021

Problem #1


Let $R_1=10\text{k}\Omega$, $R_3=R_4=R_5=1\text{k}\Omega$, $C_1=100\text{nF}$, $C_3=10\text{nF}$, $C_4=2\text{nF}$, $C_5=200\text{pF}$, $V_{dd} = 1.8\text{V}$. The signals $x_{in}(t)$ and the $x_{ref}(t)$ are 50%- duty-cycle square-waves with 1.5MHz and 21.5MHz frequency, respectively. The VCO has 1V output amplitude and linear tuning range centered at 20MHz with 500kHz span over the 0- V_{dd} range of V_{tune} . Let the OpAmp be ideal, and the mixer conversion gain be $A_v=0.5$. The block X_1 acts as a level-shifting comparator, convertin eg a sinusoid to a 0- V_{dd} square-wave.



- Derive the **continuous-time model** of the system and write the expression of the **loop gain**.
- Calculate R_2 that sets the unity-gain frequency to 8kHz and evaluate the **phase margin** in degrees.
- What are the **frequencies of the main spurs** in the spectrum of $y(t)$? Calculate the **level (in dBc)** of the two main spurs at the output.

Problem #2

In the mixer in figure, let $V_{lo,p}(t)$ and $V_{lo,n}(t)$ be out-of-phase 5GHz sinusoids with dc voltage of 1V and zero-peak amplitude of 0.1V. Let $V_{rf}(t)$ be a 5GHz sinusoid modulated with 1MHz bandwidth and with 0.6V dc value. Let $V_{dd} = 1.4\text{V}$, $V_{bias} = 0.7\text{V}$, $R = 500\Omega$, $C_1 = 300\text{fF}$. For the FETs: $|V_t| = 0.3\text{V}$, $I/2\mu_n C_{ox} = 200\mu\text{A/V}^2$, $\mu_p/\mu_n = 0.5$, $(\gamma/\alpha) = 0.8$, $(W/L)_{M1} = 222$, $(W/L)_{M2,3} = 128$, $(W/L)_{M4} = 188$.

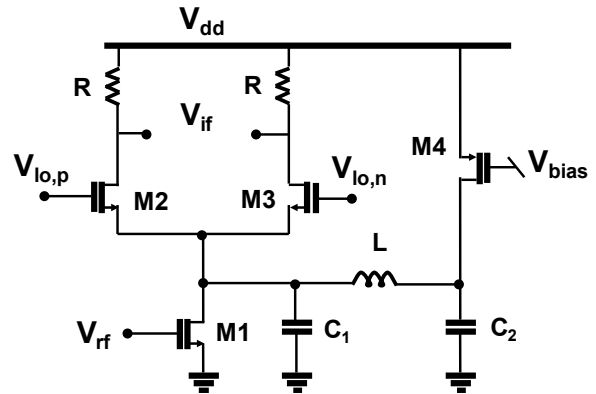

- Neglecting L and C_2 (i.e. $L = 0$, $C_2 = 0$) but considering C_1 , calculate the value of the **conversion gain (in dB)** of the mixer (from RF to IF), and the **noise figure (in dB)** with respect to an input impedance of 50Ω (calculate first the contribution of each noise source).
- Considering now $L = 3.38\text{nH}$ and $C_2 = 10\text{pF}$, calculate the new values for the **conversion gain** and the **noise figure** (calculate first the contribution of each noise source).
- Let us assume the M2-M3 pair has an input-referred offset voltage of 10 mV. Calculate the value of the **output differential voltage at DC** (using the abrupt-switching approximation). Through what mechanism can this offset voltage degrade the **SNR at the output of the mixer in a zero-IF receiver in the presence of interferers**? (Justify your answer and quantify the impact of the offset voltage on the output SNR).