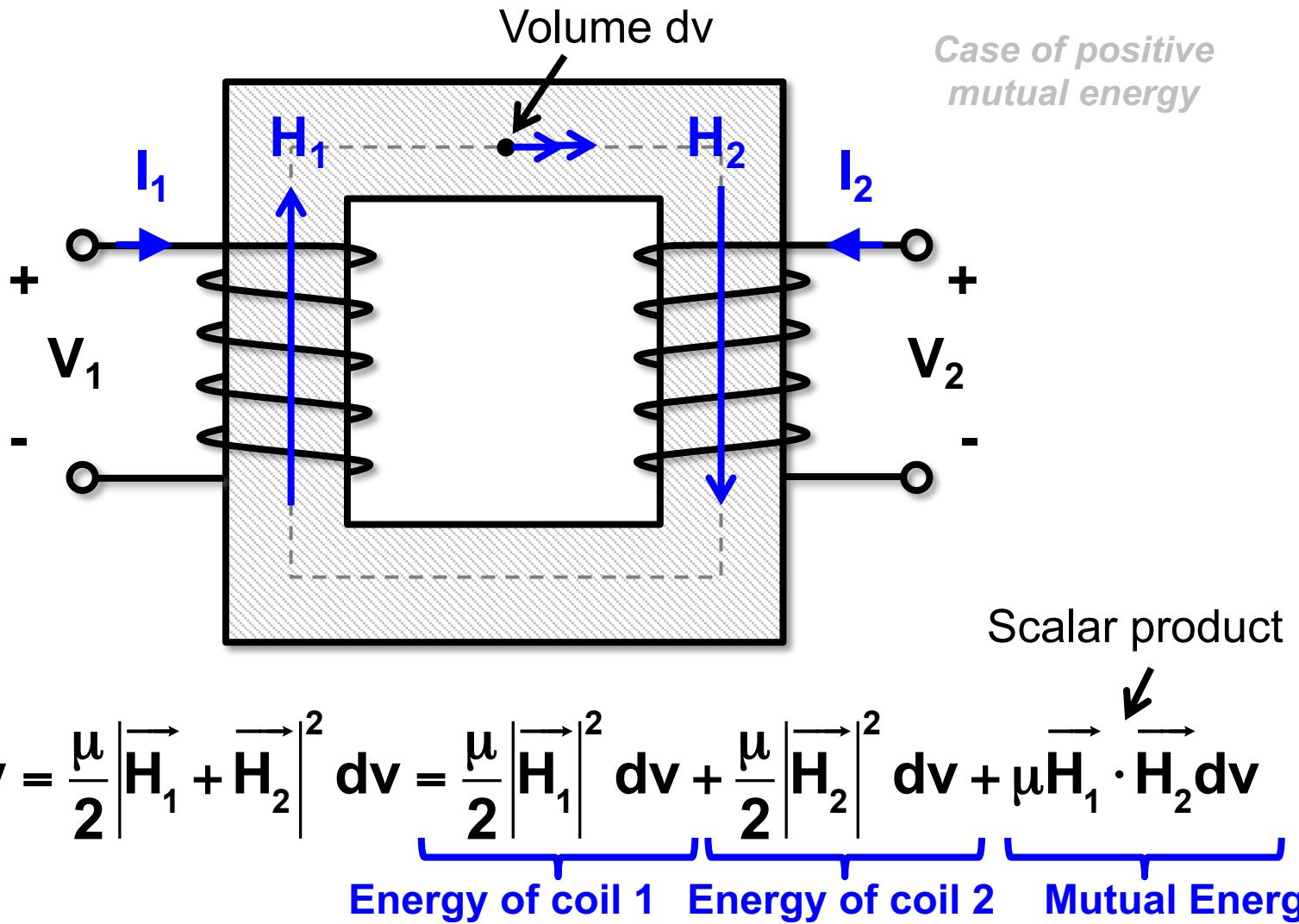


# RF Circuit Design



T6



# Transformers: Physical View



# Transformers: Circuit View

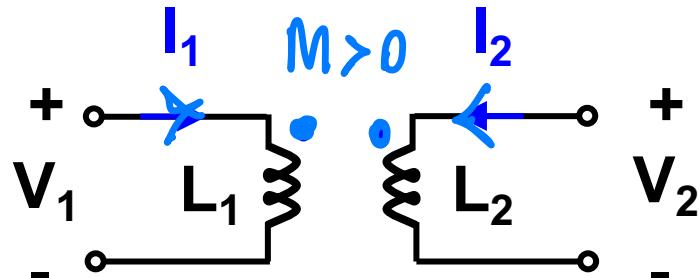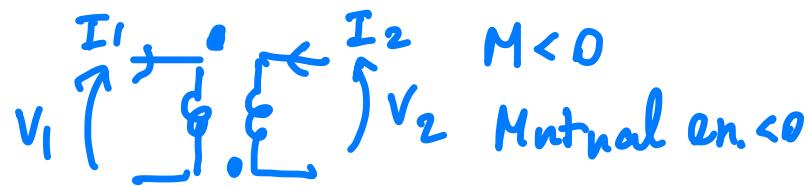

*Case of positive mutual energy*

$$\begin{cases} \phi_1 = L_1 I_1 + M I_2 \\ \phi_2 = M I_1 + L_2 I_2 \end{cases}$$

$$\begin{cases} V_1 = \dot{\phi}_1 \\ V_2 = \dot{\phi}_2 \end{cases}$$


*Passive sign convention*

$$\text{Energy} = \int_0^t (V_1 I_1 + V_2 I_2) dt' = \underbrace{\frac{1}{2} L_1 I_1^2(t)}_{\text{Energy of coil 1}} + \underbrace{\frac{1}{2} L_2 I_2^2(t)}_{\text{Energy of coil 2}} + \underbrace{M \cdot I_1(t) I_2(t)}_{\text{Mutual Energy}}$$

- **Sign of mutual energy depends on the sign of  $M$  and on the sign of  $I_1 I_2$**
- **Dot convention:  $M$  is positive if both currents enter or leave the dotted terminal**


# Transformers: More on dot convention

---

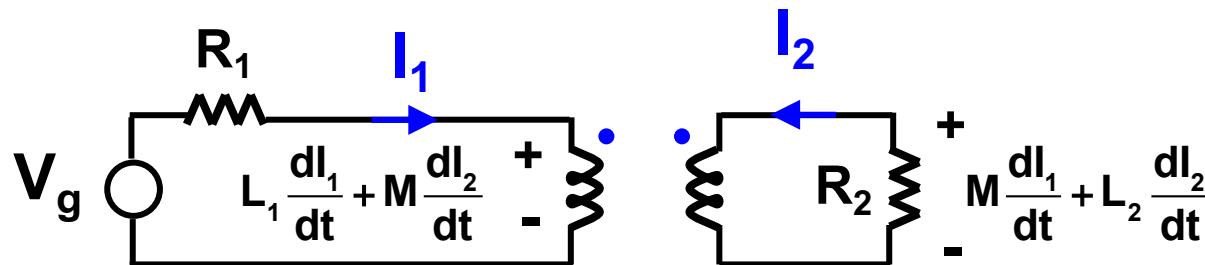

- If a current **enters** the dotted terminal of a coil, the reference polarity of the voltage induced in the other coil is **positive** at its dotted terminal.
- If a current **leaves** the dotted terminal of a coil, the reference polarity of the voltage induced in the other coil is **negative** at its dotted terminal.

# Coupling Coefficient

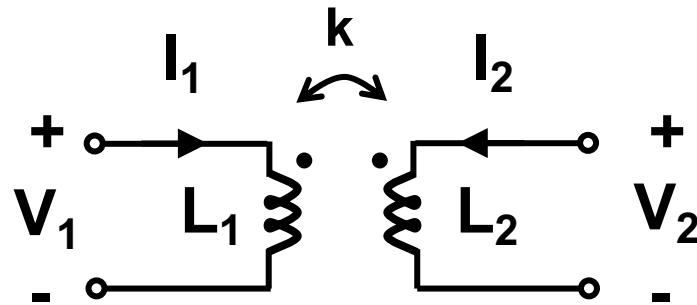

$$\begin{cases} \phi_1 = L_1 I_1 + M I_2 \\ \phi_2 = M I_1 + L_2 I_2 \end{cases}$$

Mutual Inductance  
Self-Inductance


- Definition of coupling coefficient

$$k = \frac{|M|}{\sqrt{L_1 L_2}}$$

- Conservation of energy implies that

$$0 \leq k \leq 1$$

Examples : Series of coupled inductors

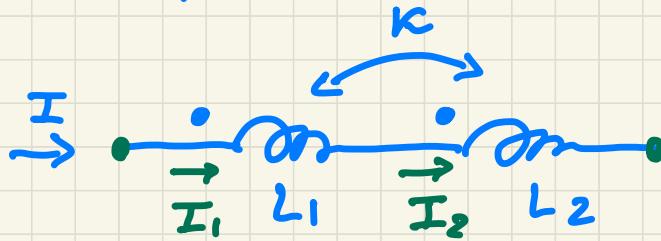


$$I = I_1 = I_2$$

- This is the case of Positive  $M$  (mutual energy) because  $I_1$  and  $I_2$  enter the dotted terminal
- Total inductance  $L_{TOT}$ :


$$\phi = \phi_1 + \phi_2 = \underbrace{L_1 I_1 + M I_2}_{\phi_1} +$$

flux
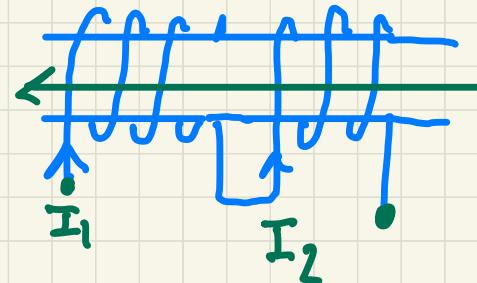
$$+ \underbrace{M I_1 + L_2 I_2}_{\phi_2} = (\underbrace{L_1 + L_2 + 2M}_{L_{TOT}}) \cdot I$$




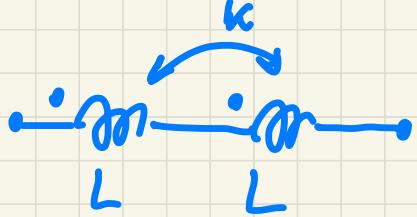
$$L_{TOT} = L_1 + L_2 + 2M = L + L + 2 \cdot K \cdot L = 2(1+K) \cdot L$$



- case:  $L_1 = L_2 = L$

$$|M| = K \cdot \sqrt{L_1 L_2} = K \cdot L$$

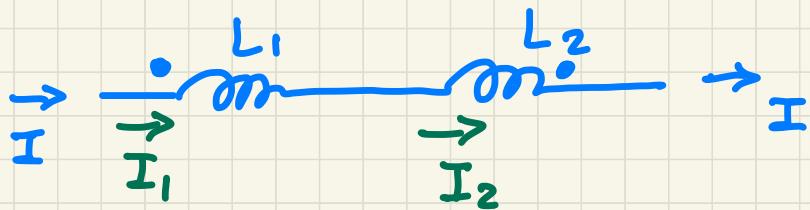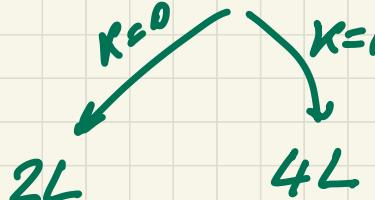


NEGATIVE  $M$  ( $M < 0$ )



$$\begin{aligned}\phi = \phi_1 + \phi_2 &= L_1 I_1 - |M| I_2 - |M| I_1 + L_2 I_2 = \\ &= \underbrace{(L_1 + L_2 - 2|M|)}_{\text{total inductance } L_{TOT}} I\end{aligned}$$

- case  $L_1 = L_2 = L$  :

$$L_{TOT} = 2 \cdot (1-K) \cdot L$$

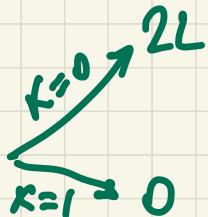
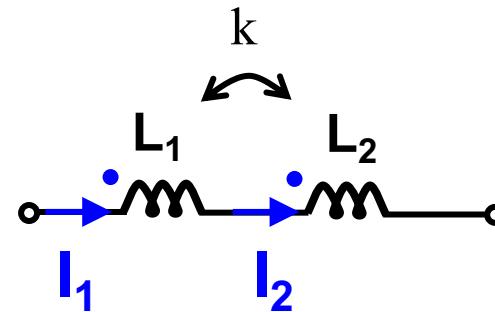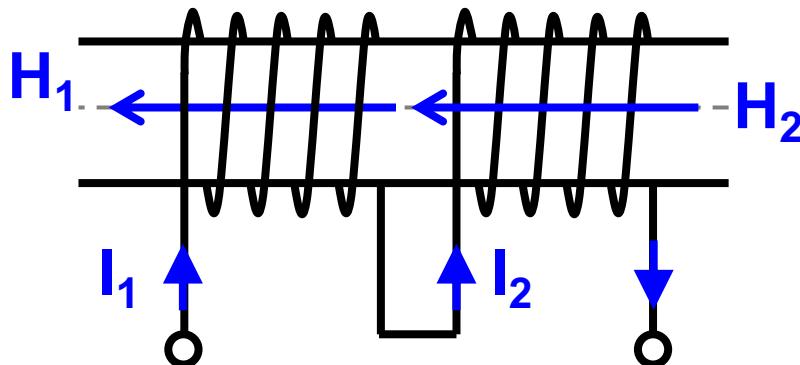
# *Example: Series of Two Coupled Inductors (I)*



*Case of positive mutual energy  
(M is positive)*



$$\phi = \phi_1 + \phi_2 = L_1 I_1 + M I_2 + M I_1 + L_2 I_2 = \underbrace{(L_1 + L_2 + 2M)}_{\text{Total Inductance } L_{\text{tot}}} I$$

**Total Inductance  $L_{\text{tot}}$**

- If  $L_1 = L_2 = L$ :

$$L_{\text{tot}} = 2(1+k)L$$
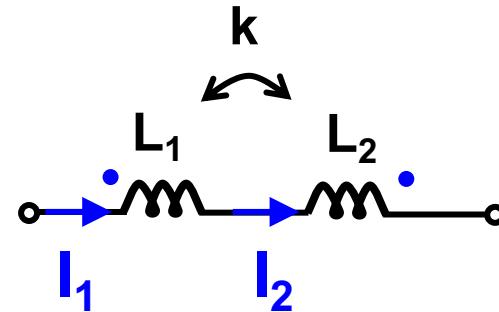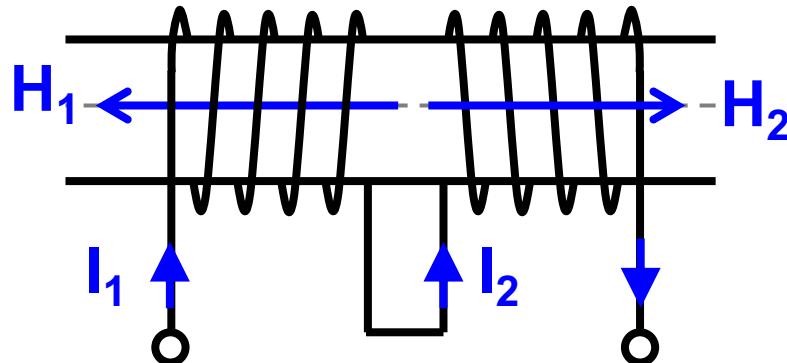
## *Example: Series of Two Coupled Inductors (II)*



*Case of negative mutual energy  
(M is negative)*

$$\phi = \phi_1 + \phi_2 = L_1 I_1 - |M| I_2 - |M| I_1 + L_2 I_2 = \underbrace{(L_1 + L_2 - 2|M|)}_{\text{Total Inductance } L_{\text{tot}}} I$$

**Total Inductance  $L_{\text{tot}}$**


- If  $L_1 = L_2 = L$ :

$$L_{\text{tot}} = 2(1-k)L$$

## Model of coupled inductors :

- model based on ideal transformer
- T-circuit model

Ideal transformer

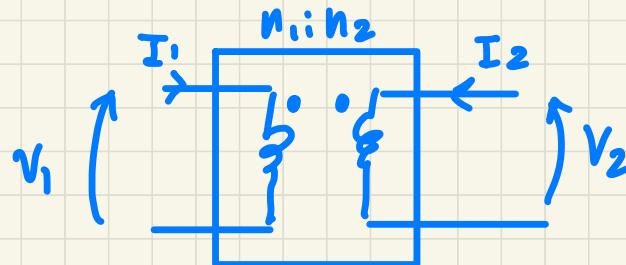

e.g. 1:n ideal transf.

$$V_2 = V_1 \cdot n$$

voltage amplification

i) No flux dispersion  
( $k=1$ )

$$\Phi_1 = n_1 \phi \quad \begin{matrix} \text{flux of a single} \\ \text{turn} \end{matrix}$$

$$\Phi_2 = n_2 \phi$$

$$\frac{V_1}{V_2} = \frac{n_1}{n_2}$$

2) infinite self-inductance ( $L_1, L_2 \rightarrow \infty$ )

HOPKINSON  
LAW

$$\text{m. m. f.} = \frac{\Phi \cdot R}{\Lambda} = \frac{\Phi}{\Lambda} \xrightarrow[\text{flux}]{\text{Reluctance } (\text{H}^{-1})} \xrightarrow[0]{\text{Permeance}} \infty$$

↑      ↑

magnetomotive  
force

$$\text{m. m. f.} \rightarrow 0$$


AMPERE'S  
LAW

$$\text{m. m. f.} = n_1 I_1 + n_2 I_2$$

$$0 \leftarrow$$




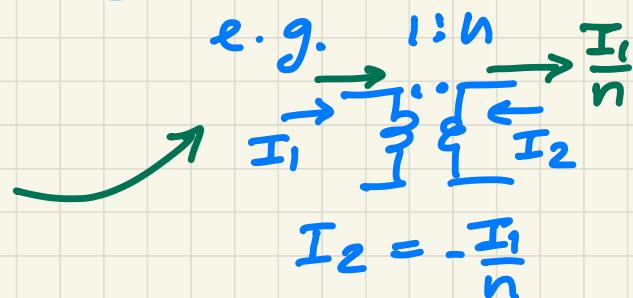
$$\boxed{\frac{I_1}{I_2} = -\frac{n_2}{n_1}}$$



$$\frac{V_1 \cdot I_1}{V_2 \cdot I_2} = \frac{n_1}{n_2} \cdot \left( -\frac{n_2}{n_1} \right) = -1 \Rightarrow V_1 I_1 + V_2 I_2 = 0 \Rightarrow \text{LOSSLESS}$$

# Equivalent model of coupled inductors

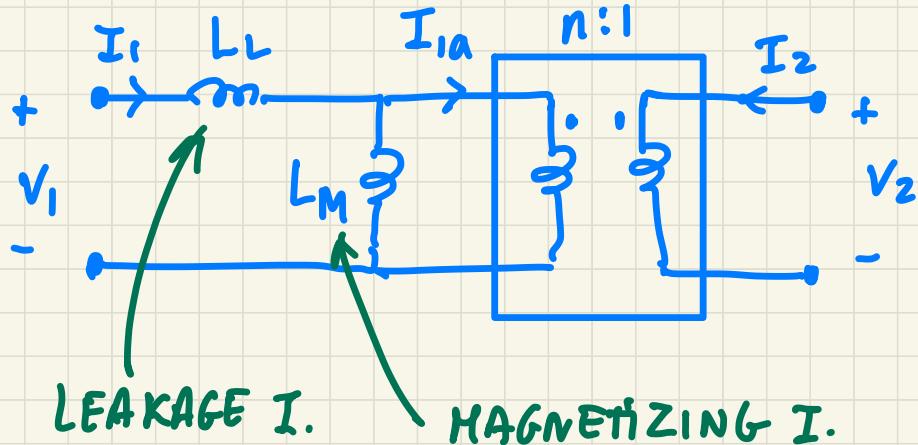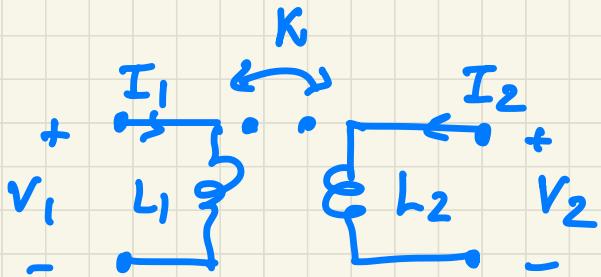

$$\left\{ \begin{array}{l} L_L = (1 - K^2) L_1 \\ L_M = K^2 \cdot L_1 \\ n = K \cdot \sqrt{\frac{L_1}{L_2}} \end{array} \right.$$


verification:

$$\Phi_1 = L_1 I_1 + M I_2$$


$$L_1 = \left. \frac{\Phi_1}{I_1} \right|_{I_2=0} = L_L + L_M$$

$$I_2 = 0 \Rightarrow I_{1a} = 0 \Rightarrow \Phi_1 = (L_L + L_M) \cdot I_1$$

# T-circuit model of coupled inductors

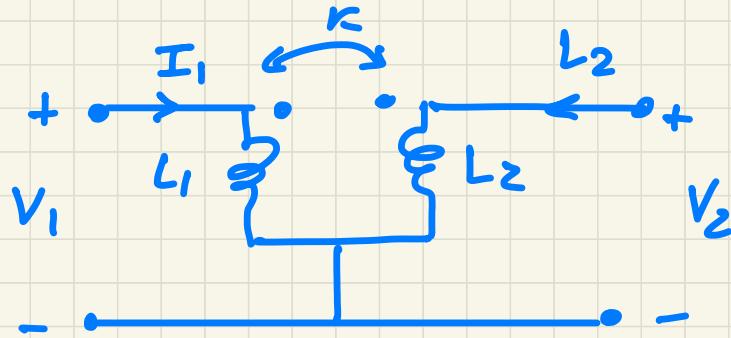


$$L_1 = \left. \frac{\Phi_1}{I_1} \right|_{I_2=0} = L_A + L_C$$

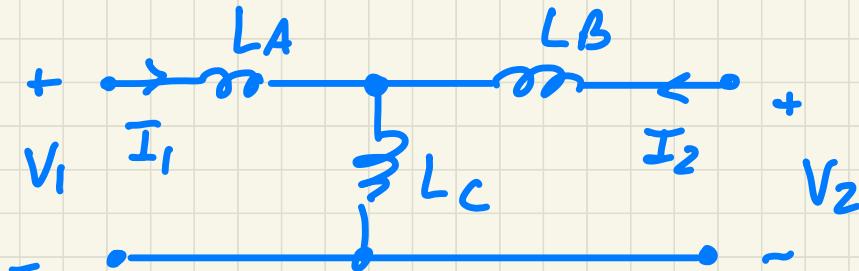


$$L_2 = \left. \frac{\Phi_2}{I_2} \right|_{I_1=0} = L_B + L_C$$

⋮

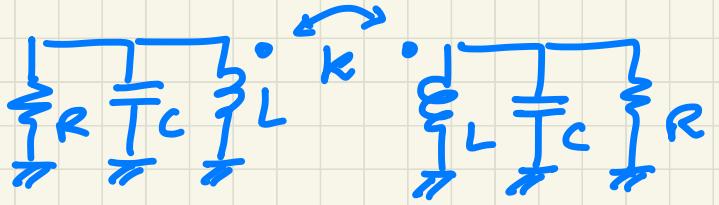
$$\begin{cases} L_A = L_1 - M \\ L_B = L_2 - M \\ L_C = M \end{cases}$$



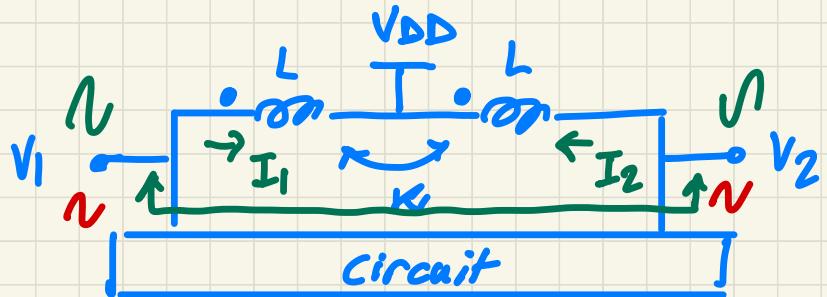
- How many resonant frequencies has this circ?



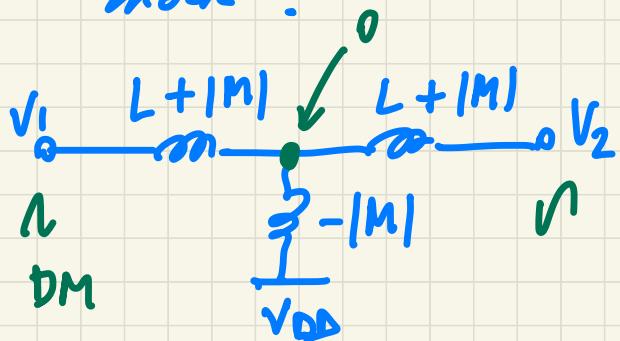- What is the load imped. in common mode and in differential mode ?




$$K=1 : \quad Z_{CM} \rightarrow 0$$

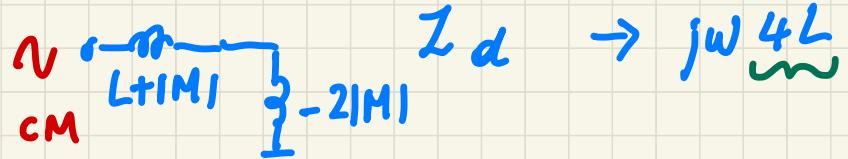
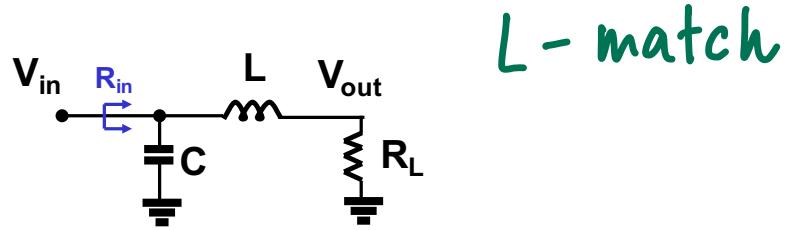
## Tutorial T6


**T6.1** Let us consider the L-match network in figure, where  $R_L=50\Omega$ .



- Size L and C in order to obtain  $R_{in}=100\Omega$  at 5 GHz. What is the Q of the network?
- Driving the input port of the network with a current source, evaluate the complex transimpedance  $V_{out}/I_{in}$  at 5GHz.


[Solution: a.  $C = 318fF$ ,  $L = 1.59nH$ ; b.  $V_{out}/|I_{in}| = 50\Omega - j50\Omega$ ]

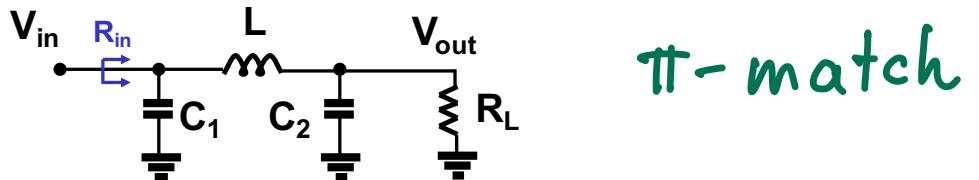**T6.2** Let us consider the  $\pi$ -match network in figure, where  $R_L=50\Omega$ . Size L,  $C_1$  and  $C_2$  in order to obtain  $R_{in}=100\Omega$  at 5GHz, and a quality factor of the resulting network equal to  $Q=5$ .



[Solution: a.  $C_1 = 955fF$ ,  $C_2 = 1.274fF$ ,  $L = 1.59nH$ ]


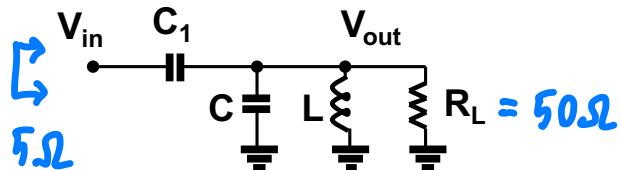
**T6.3** Let us consider the impedance transformation network in figure. Assuming  $R_L=50\Omega$  and  $C=2pF$ , size L and  $C_1$  to obtain an equivalent input impedance of  $5\Omega$  at 5GHz. What is the quality factor of the network?



[Solution:  $L = 258pH$ ,  $C_1 = 2.12pH$ ,  $Q = 3$ ]

T6.1

$$f_0 = 5 \text{ GHz}$$

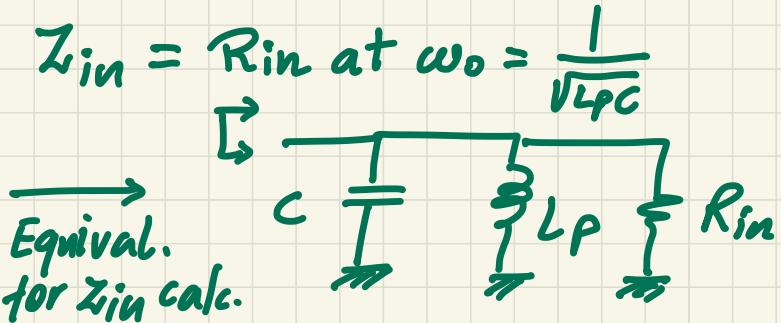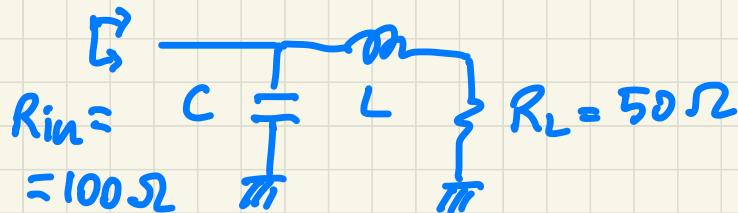

a.

- $R_{in} = R_L \cdot (1 + Q_L^2) \quad \text{where} \quad Q_L = \frac{\omega_0 L}{R_L}$

$\omega_0 = \frac{1}{\sqrt{L_P C}} \quad \text{where} \quad L_P = L \cdot \left(1 + \frac{1}{Q_L^2}\right)$


$\Rightarrow Q_L = \sqrt{\frac{R_{in}}{R_L} - 1} = \sqrt{\frac{100}{50} - 1} = 1$

$$L_P = L \cdot (1+1) = 2L$$

$$L = \frac{Q_L \cdot R_L}{\omega_0} = \frac{1 \cdot 50}{2\pi \cdot 5 \cdot 10^9} = 1.59 \text{ nH}$$

$$\left. \Rightarrow C = \frac{1}{\omega_0^2 L_P} = 318.6 \text{ fF} \right\}$$

b.

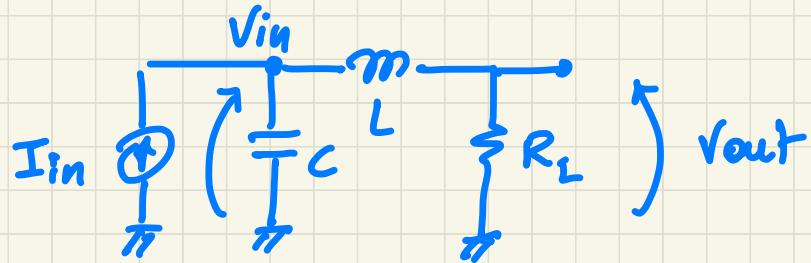

$$\frac{V_{out}}{I_{in}} \text{ at } f_0 = 5 \text{ GHz}$$

$$\frac{V_{out}}{I_{in}} = \underbrace{\frac{V_{in}}{I_{in}}}_{Z_{in}} .$$

$$\frac{V_{out}}{V_{in}} = R_{in} \cdot \frac{\cancel{R_L}^1}{(\cancel{R_L} + j\omega L) \cancel{R_L} Q_L} = \\ = R_{in} \cdot \frac{1}{1 + jQ_L} =$$

$$= 100 \cdot \frac{j}{1 + j} =$$

$$= 100 \cdot \frac{1-j}{1+j} = 50\Omega - j50\Omega$$

\*\*\*\*\*  
\*\*\* MacSpice  
\*\*\* Coco  
\*\*\* Date  
\*\*\*\*\*

### MacSpice Console

Get MacSpice

Some use

source <  
run  
edit  
display  
plot <pl  
applehel  
set  
rusage a  
quit

MacSpice

Circuit:

MacSpice


Circuit:

MacSpice

### Plot 5 [ac2] Lmatch.cir

real(imp)


Re{Zin}

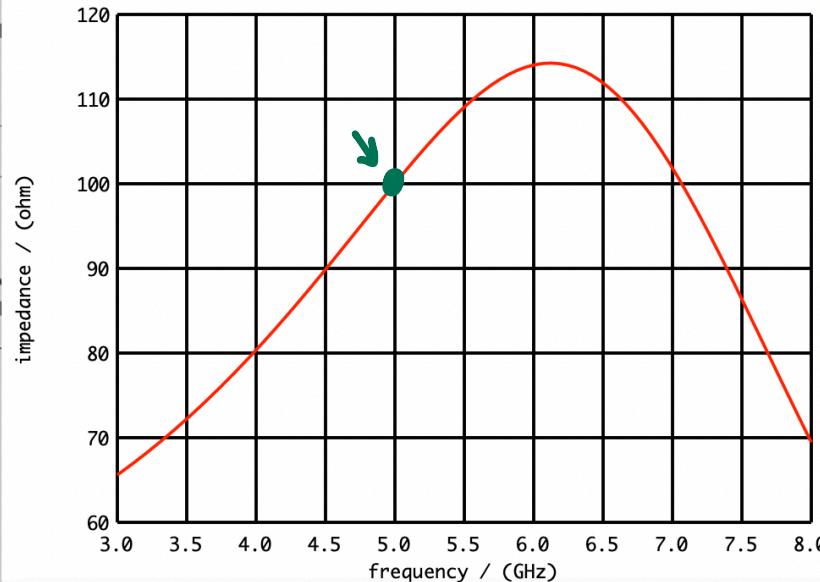

### Plot 7 [ac2] Lmatch.cir

mag(transimp)


|Vout/Iin|

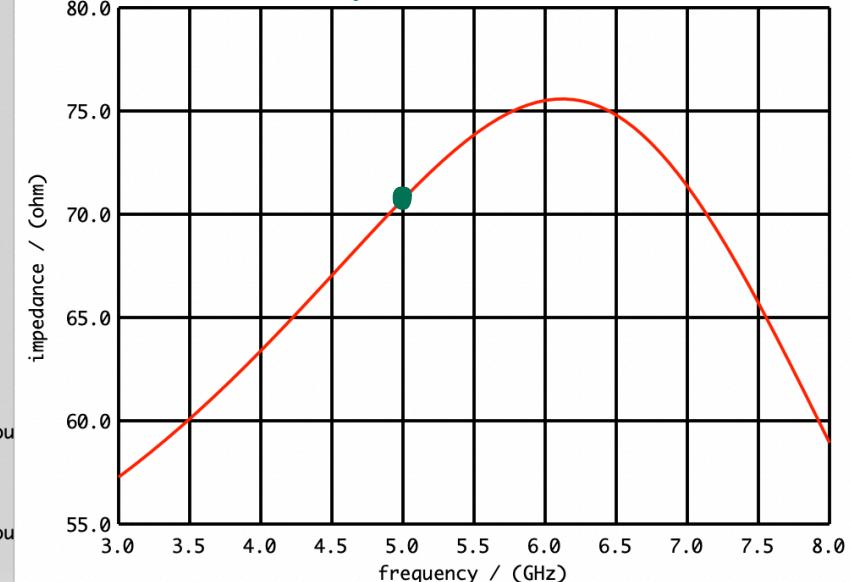

### Plot 6 [ac2] Lmatch.cir

imag(imp)


Im{Zin}

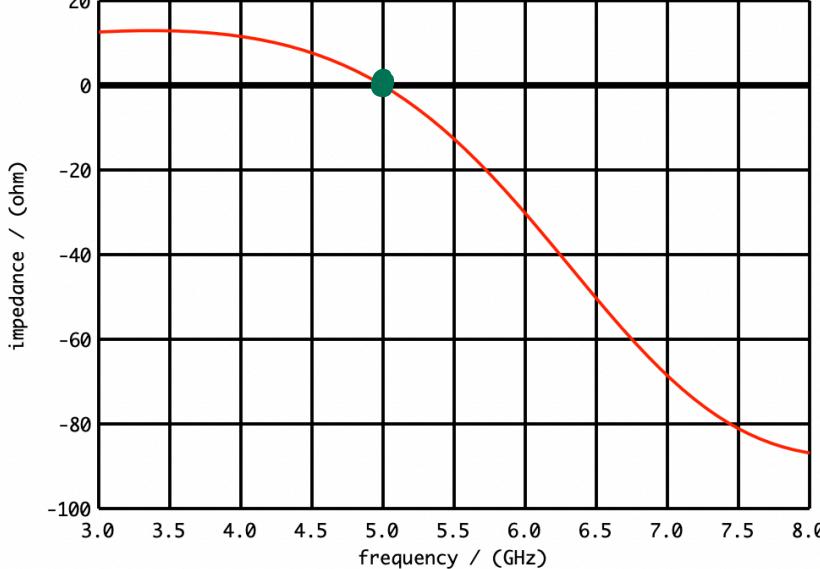


### Plot 8 [ac2] Lmatch.cir

phase(transimp)

∠ Vout/Iin

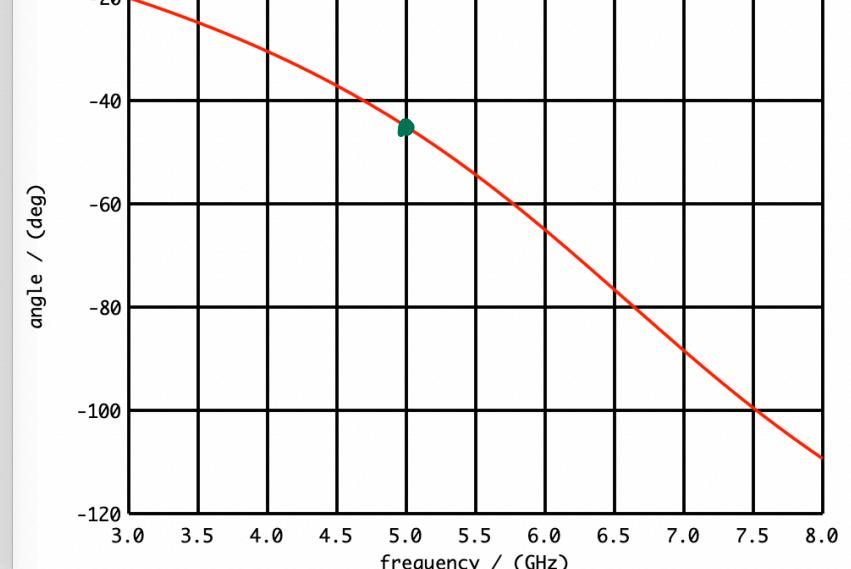

T6.2

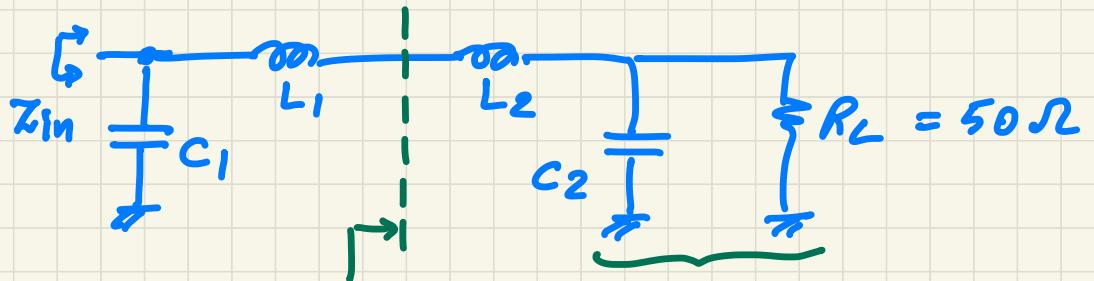

$$Q_2 = \frac{\omega_0 L_2}{R_s}$$

$$R_s = \frac{R_L}{1 + Q_2^2}$$


$$C_{2s} = C_2 \cdot \left( 1 + \frac{1}{Q_2^2} \right)$$

$$\underline{\omega_0 = \frac{1}{\sqrt{L_2 C_{2s}}}}$$

$$R_{in} = R_s \cdot (1 + Q_1^2)$$

$$Q_1 = \frac{\omega_0 L_1}{R_s}$$
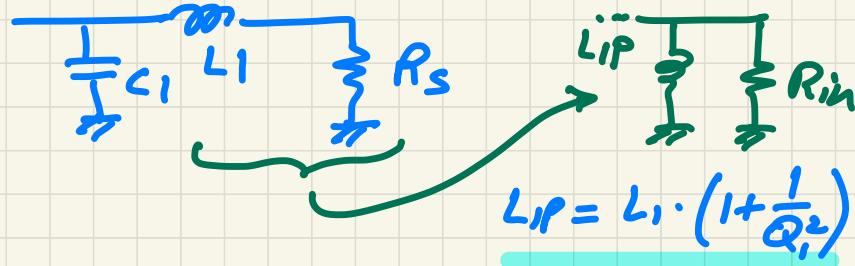
$$\underline{a_b = \frac{1}{\sqrt{L_{IP} C_1}}}$$



$$\underline{L_{IP} = L_1 \cdot \left( 1 + \frac{1}{Q_1^2} \right)}$$

$$\Rightarrow \left\{ \begin{array}{l} R_{in} = R_L \cdot \frac{1+Q_1^2}{1+Q_2^2} = R_L \cdot \frac{1+Q_1^2}{1+(Q-Q_1)^2} \\ Q = Q_1 + Q_2 ; \quad Q_2 = Q - Q_1 \end{array} \right.$$

Known

$$\frac{100}{50} = 2 = \frac{1+9}{1+4} = \frac{10}{5}$$

$$\left\{ \begin{array}{l} Q_1 = 3 \\ Q_2 = 2 \end{array} \right.$$

$$R_s = \frac{R_{in}}{1+Q_1^2} = \frac{100}{1+9} = 10 \Omega$$

$$\left. \begin{array}{l} L_1 = \frac{Q_1 R_s}{\omega_0} = \frac{3 \cdot 50}{2\pi \cdot 50} = 955 \text{ pH} \\ L_2 = \frac{Q_2 R_s}{\omega_0} = 637 \text{ pH} \end{array} \right\} L = L_1 + L_2 = 1.59 \text{ nH}$$

$$C_1 = \frac{1}{\omega_0^2 L_1 \left(1 + \frac{1}{Q_1^2}\right)} = 955 \text{ fF}$$

$$C_2 = \frac{1}{\omega_0^2 L_2 \cdot \left(1 + \frac{1}{Q_2^2}\right)} = 1.273 \text{ pF}$$

```
*****
*** MacSpice - 3f5 v3.1.24
*** Cocoa
*** Date 08/20/2013
```

Get MacSpice

Some useful

```
source <f
run
edit
display
plot <plot>
applehelp
set
rusage al
quit
```

MacSpice

Circuit:

MacSpice

Circuit:

MacSpice 3 --&gt; close all

Error: No

MacSpice 4

Error: No

MacSpice 5

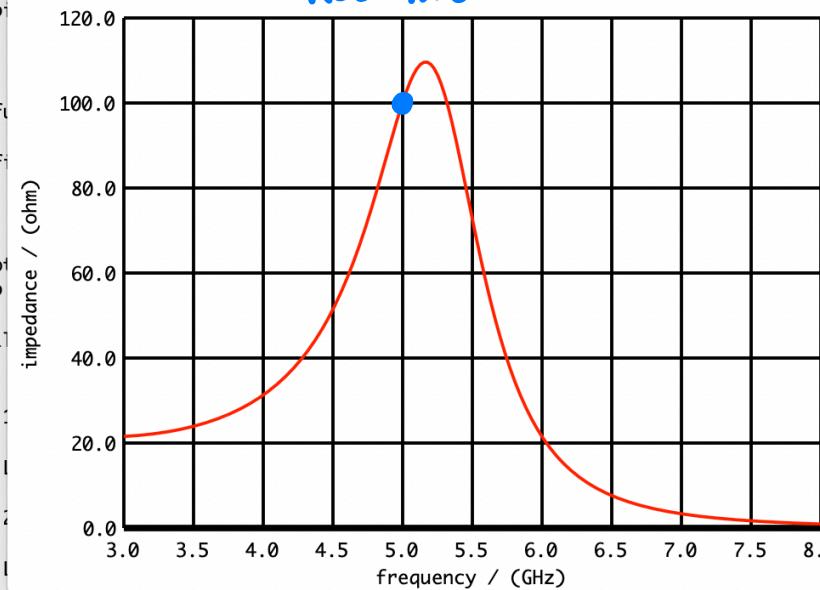
Circuit:

MacSpice 6

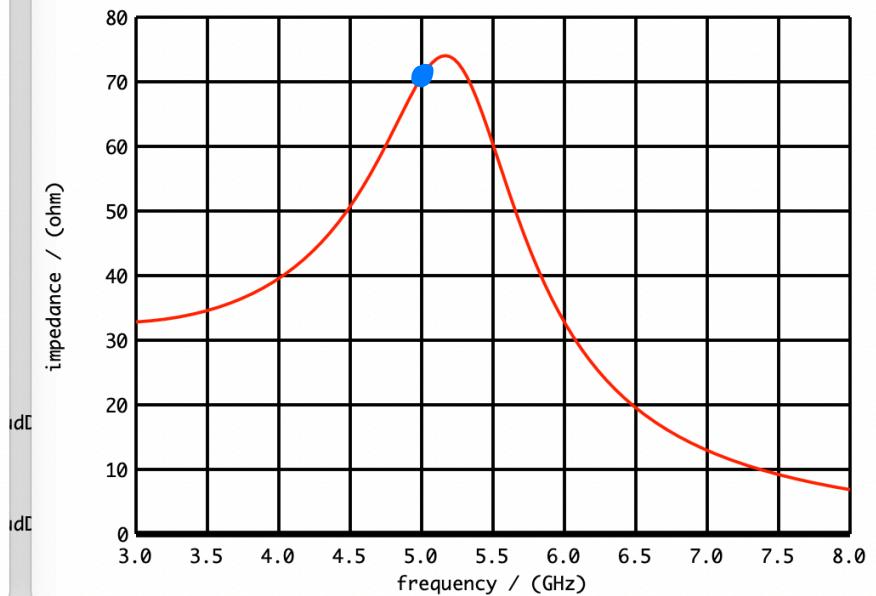
Circuit:

MacSpice 7


Plot 12 [ac4] Pmatch.cir

 $\text{Re}\{\text{Zin}\}$ 


Plot 14 [ac4] Pmatch.cir

 $\text{mag}(\text{transimp})$ 

Plot 13 [ac4] Pmatch.cir

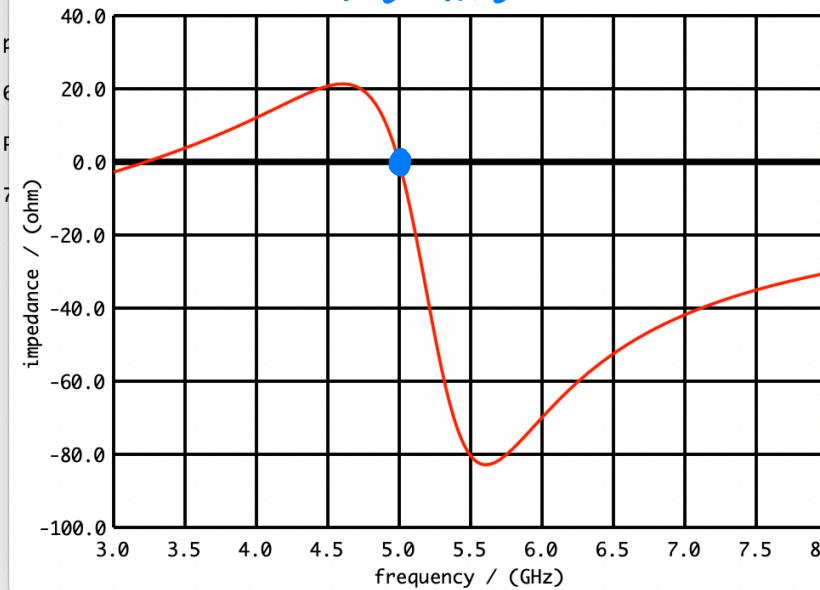
 $\text{Im}\{\text{Zin}\}$ 

Plot 15 [ac4] Pmatch.cir

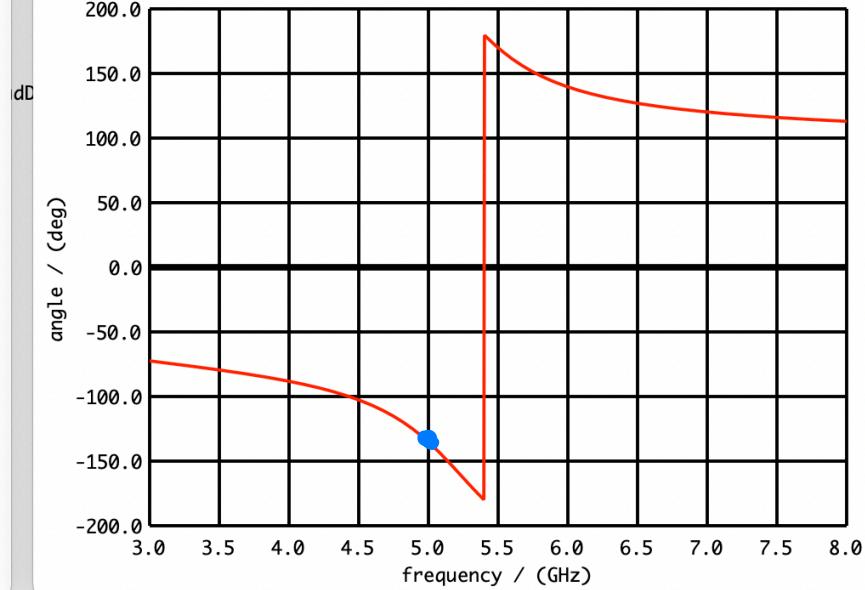
 $\text{phase}(\text{transimp})$ 

T6.3


$$C = z \cdot f \cdot F$$

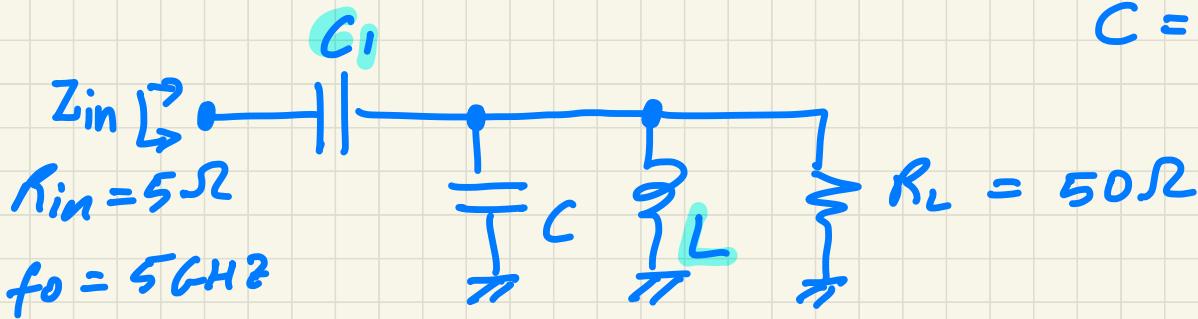

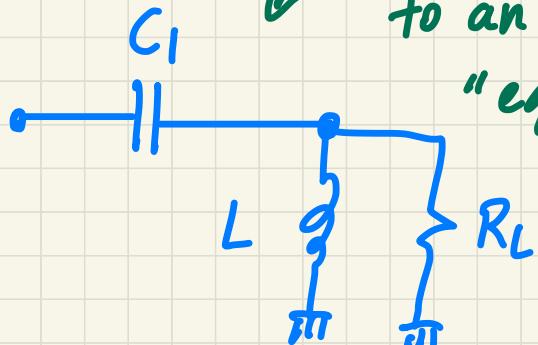How can we get  
to an L-match  
"equivalent"  
case?





L-match

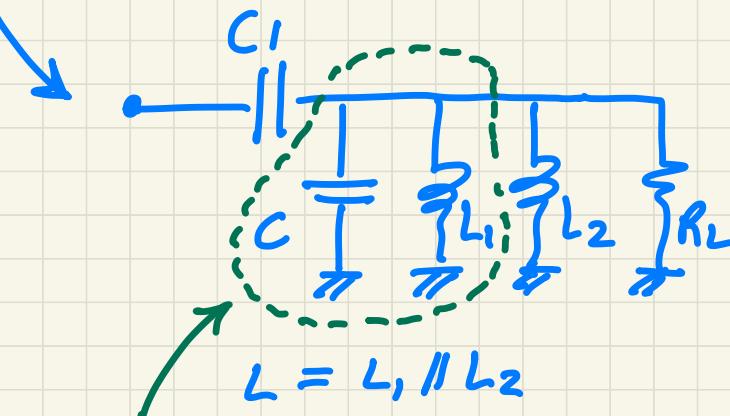

Resonance :
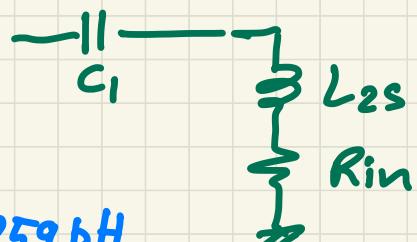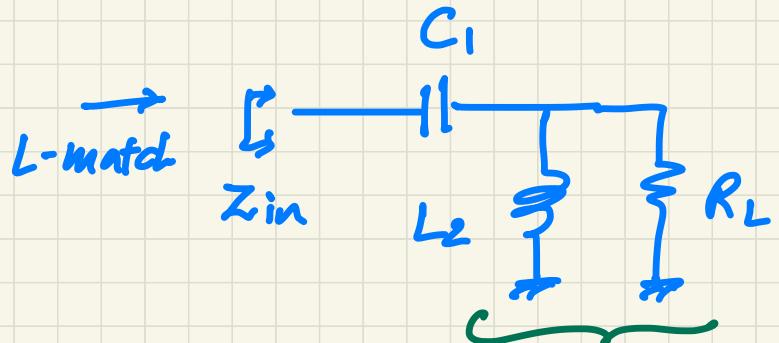
$$L_1 = \frac{1}{\omega_0^2 \cdot C} = 507 \mu\text{H}$$



$$L = L_1 \parallel L_2 = 259 \text{ pH}$$

$$(1) \quad Z_{in} = \frac{R_L}{1 + Q_{L2}^2} = R_{in}$$

$$(2) \quad Q_{L2} = \frac{R_L}{\omega_0 L_2}$$

$$(3) \quad \omega_0 = \frac{1}{\sqrt{C_1 L_{2s}}} =$$

$$= \frac{1}{\sqrt{C_1 \frac{L_2}{1 + 1/Q_{L2}^2}}}$$

(1)


$$Q_{L2} = \sqrt{\frac{R_L}{R_{in}}} - 1 = \sqrt{\frac{50}{5}} - 1 = 3$$

(2)

$$L_2 = \frac{\omega_0 Q_{L2}}{R_L} = 531 \text{ pH}$$

$$(3) \quad C_1 = 2,12 \text{ pF}$$

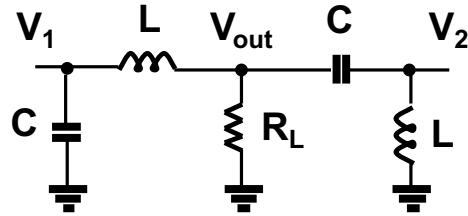
**T6.4** We want to design a differential to single-ended signal converter Let us consider the circuit in figure, where  $R_L=50\Omega$ .



- a) Find the values of L and C to have a gain  $|V_{out}|/(|V_1 - V_2|) = 1$  at 5GHz.
- b) Evaluate the differential impedance between  $V_1$  and  $V_2$  at 5GHz.


[Solution: a.  $L=1.59\text{nH}$ ,  $C=637\text{fF}$ ; b.  $R_{diff}=50\Omega$ ]

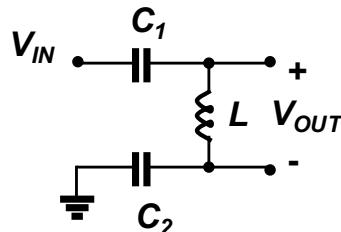**T6.5** We want to design a single-ended-to-differential converter of a sinusoidal signal from  $V_{IN}$  to  $V_{OUT}$ , using the circuit in figure. Assuming a  $50\Omega$  source resistance for  $V_{IN}$ , set  $C_1$ ,  $C_2$ , and  $L$  to achieve differential output and  $V_{OUT}/V_{IN} = 3$  at 5GHz.



[Solution:  $C_1 = C_2 = 424\text{fF}$ ,  $L = 4.78\text{nH}$ ]

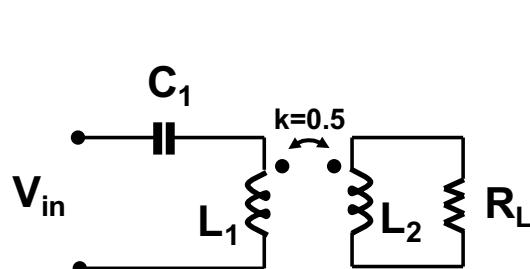**T6.6** Let us consider the impedance-matching network in figure, based on a real transformer. Given a coupling factor  $k=0.5$  between primary and secondary windings,  $L_2 = 1.59\text{nH}$  and  $R_L=50\Omega$ , size  $L_1$  and  $C_1$  to obtain an equivalent input impedance of  $5\Omega$  at 5GHz. What is the Q of the resulting network?




[Solution:  $L_1 = 1.237\text{nH}$ ,  $C_1 = 909.5\text{fF}$ ,  $Q=7$ ]

Differential - to - single-ended converter


is a "Bal Un": balanced - to - unbalanced converter

1.

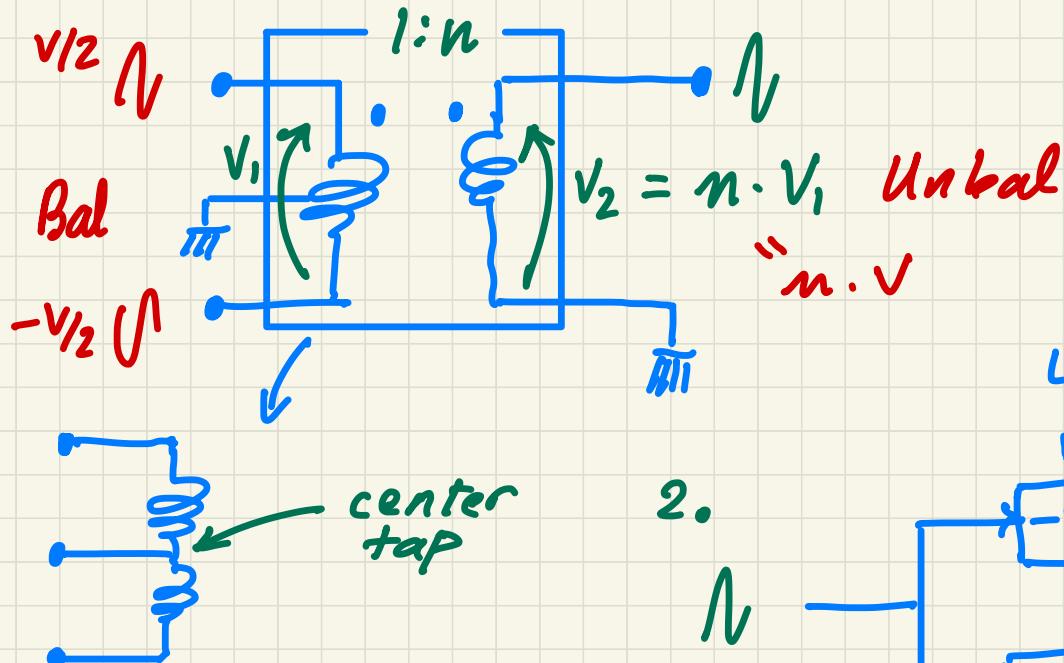


possible implementation  
of Balun  
based on  
transformers

LC network

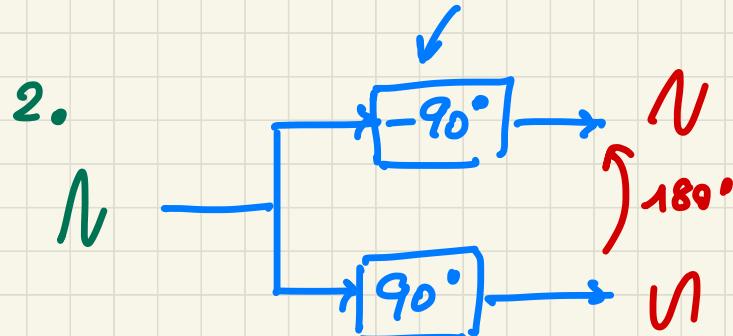

T6.6

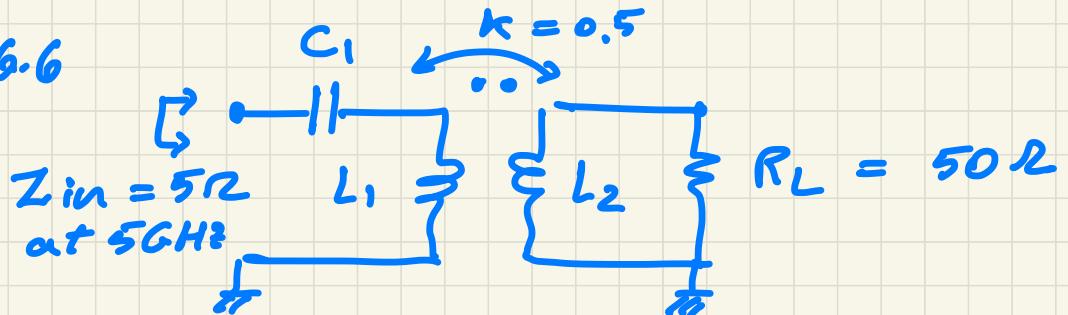

use equiv. model of coupled inductors

