

# RF Circuit Design

---


T36

---

---


---

---


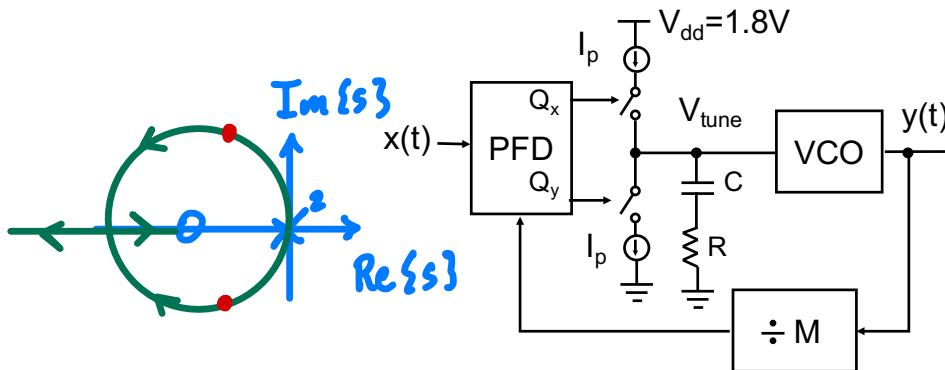
## Tutorial T3

**T3.1.** In the PLL in figure, the VCO has a free-running frequency of 3 GHz and a sensitivity of 300 MHz/V, with  $M = 100$  and  $I_p = 0.1$  mA.




*second-order  
type-II  
PLL*

- Derive the linear equivalent model of the PLL and the values of  $R$  and  $C$  to have closed-loop poles at 10 kHz and at 45 degrees on the Gauss plane.
- What is the contribution of the thermal noise of the resistor  $R$  to the phase noise  $\mathcal{L}_y(f)$  at the output  $y(t)$  at 1 MHz? (Please provide the value in dBc/Hz)
- Taking into account the contributions of (i) a white phase noise  $\mathcal{L}_x(f)$  of -140dBc/Hz, affecting the reference  $x(t)$ , and (ii) the thermal noise of  $R$ , plot the phase noise  $\mathcal{L}_y(f)$  at the output  $y(t)$  (Please provide the relevant values on the x and y axes).

[Solution: a.  $R = 296 \Omega$ ,  $C = 76$  nF; b.  $\mathcal{L}_y(1\text{MHz}) = -126.7$  dBc/Hz; c. Spectrum has  $\mathcal{L}_y(0) = -100$  dBc/Hz, zero at 3 kHz, two poles at 10 kHz, with peak  $\mathcal{L}_y(10 \text{ kHz}) = -89.6$  dBc/Hz]

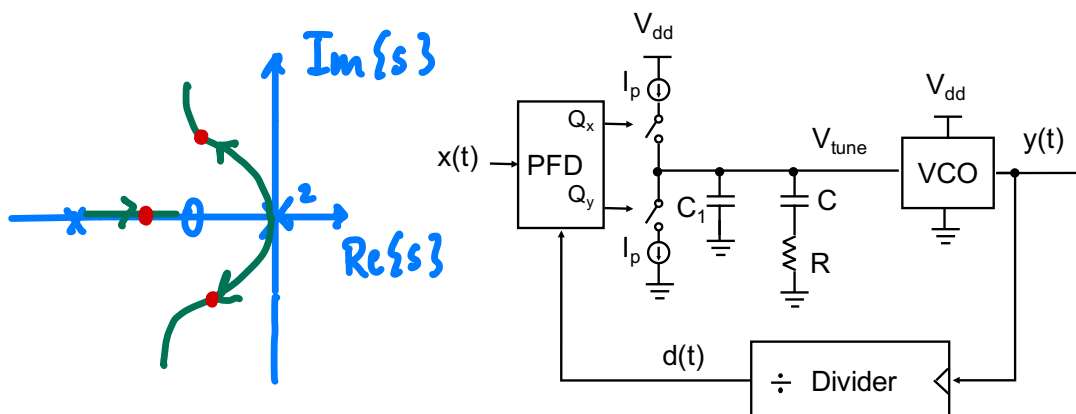**T3.2.** In the PLL in figure,  $V_{dd} = 3\text{V}$ ,  $R = 1.6$  k $\Omega$ ,  $C = 100$  nF. The PLL should synthesize all the frequencies from 1900 to 2100 MHz in steps of 1 MHz.




*3rd-order  
type-II  
PLL*

- Describe the behavior of the circuit in the case of a constant current drained from the VCO input and describe the steady state condition of the PLL.
- If this leakage current is 100 nA (assuming it is much smaller than the charge-pump current), set the value of  $C_1$  to limit the spur in the output spectrum to -50 dBc, and derive the minimum  $K_{VCO}$  to cover the whole frequency range with the given supply voltage.
- Calculate the cross-over frequency of the loop gain that maximizes the phase margin. Derive the value of the maximum phase margin and the charge-pump current  $I_p$ .

[Sol. a.  $M = 2000$ ,  $t_e/T_x = I_L/I_p$ ; b.  $K_{VCO} = 418.7 \text{ Mrad/(Vs)}$ ,  $C_1 = 336 \text{ pF}$ ,  $f_z = 1 \text{ kHz}$ ,  $f_p = 296 \text{ kHz}$ ; c.  $f_u = 17.2 \text{ kHz}$ ,  $PM = 83 \text{ deg}$ ,  $I_p = 2 \text{ mA}$ .]

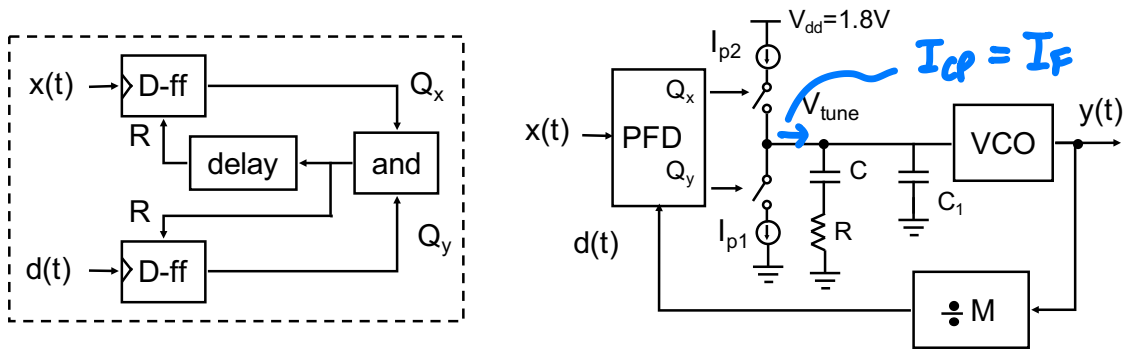
**T3.3.** In the PLL in figure, we are using a *modified* PFD schematic which is shown inside the dashed box. Unlike a conventional PFD, the block “delay” after the “and” gate introduces a delay  $t_d$  in the reset signal of just one of the two D-type flip-flops.



- Derive and plot the input-output characteristic of the PFD (i.e. input phase vs. output average voltage), drawing the voltage waveforms of all PFD nodes ( $x$ ,  $d$ ,  $Q_x$ ,  $Q_y$ ,  $R$ ) for both positive and negative input phase delays. Explain whether the PFD acts as a phase and frequency detector.
- Using the PFD in the PLL in figure, where  $K_{VCO}/2\pi = 20 \text{ MHz/V}$ ,  $I_p = 8 \text{ mA}$ ,  $f_x = 2 \text{ MHz}$ ,  $t_d = 2 \text{ ns}$ ,  $M = 1024$ , calculate the time delay between  $x(t)$  and  $d(t)$  at steady state.
- Set the values of  $R$ ,  $C$ , and  $C_1$  to have (i) a maximum spurious tone at  $y$  output with -70 dBc level, (ii) a cross-over frequency of the loop gain at 20 kHz and (iii) phase margin of 60 degrees.
- Keeping the same values of  $K_{VCO}$ ,  $I_p$ ,  $f_x$ ,  $t_d$ ,  $M$  and the same stability margin, which one of the design parameters you would modify to reduce the level of the reference spur? Illustrate the inherent drawbacks of your choice.

[Sol. a. The PFD/CP block has time offset  $-t_d$  and current  $I_p t_d f_x$  at  $t_e = 0$ ; b.  $t_e = -2 \text{ ns}$ ; c.  $C_1 = 2 \text{ nF}$ ,  $R = 804 \Omega$ ,  $C = 28.7 \text{ nF}$ ; d. After some manipulation, SFDR can be re-written as a function of the unity-gain frequency:  $\text{SFDR} = (M\omega_u\omega_p t_d^2)^2$ . Thus, the only free parameters are  $\omega_u$  and  $\omega_p$ . Reducing both of them, I would trade the loop bandwidth with the level of the spur.]

T3.2

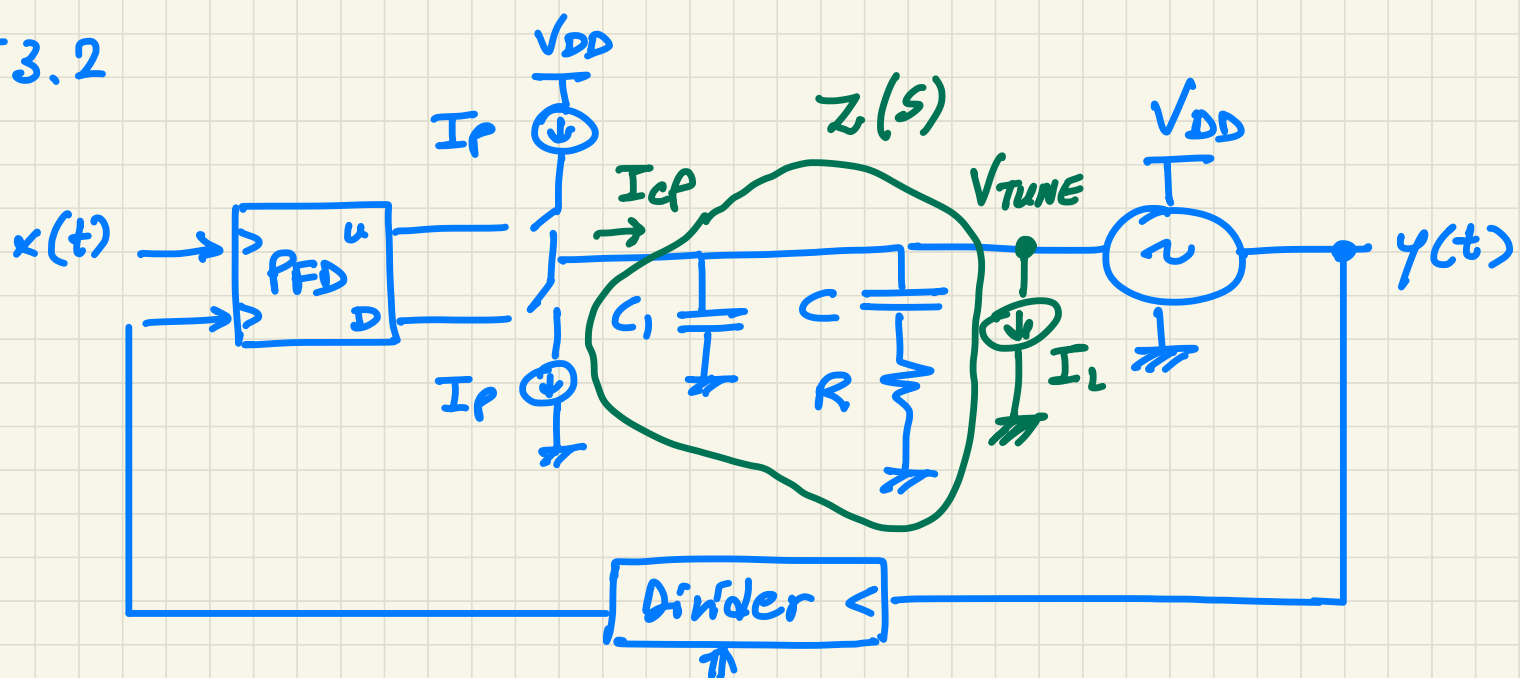

$$V_{DD} = 3V$$

$$R = 1.6 \text{ K}\Omega$$

$$C = 100 \text{ nF}$$

$$f_y = 1900 \div 2100 \text{ MHz (TR)}$$

$$\Delta f_y = 1 \text{ MHz (resolution)}$$




$$\hookrightarrow f_x = 1 \text{ MHz} \quad N = 1900 \div 2100$$

a. Describe behaviour and steady state with  $I_L$


b.  $I_L = 100 \text{ nA} \ll I_P$   
 $L_{spur} < -50 \text{ dBc}$   
 $C_1, K_{VCO}$  unknown

c.  $\max \phi_m$ :  $f_u$ ;  $\phi_m, I_P$  unknown


PHD

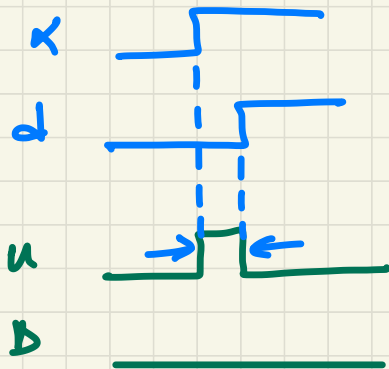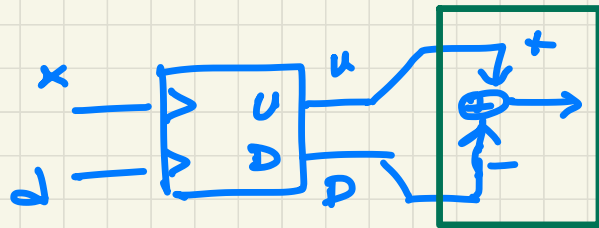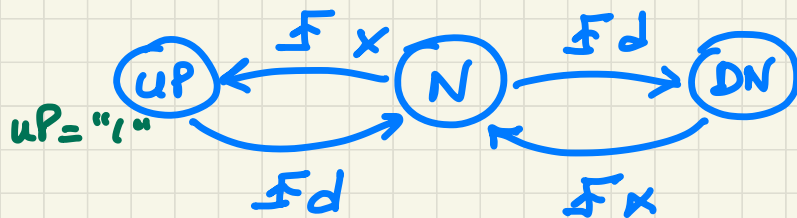

$t_s > 0$

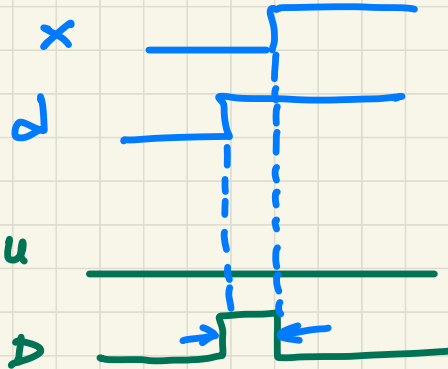


$t_s < 0$

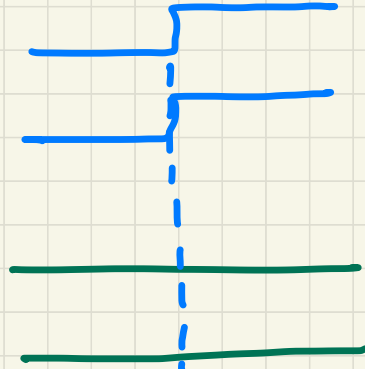

$t_s = 0$


Integer-N PLL

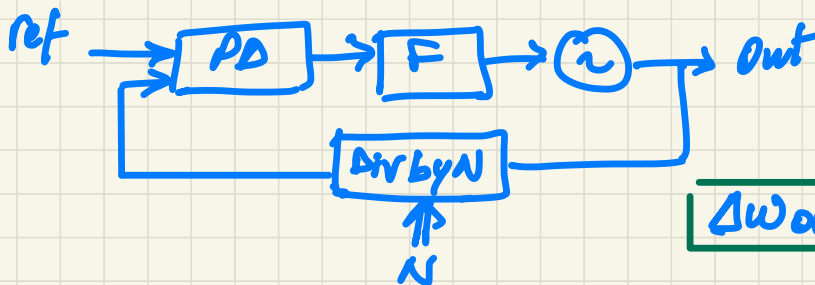$\omega_{out} = N \cdot \omega_{ref}$   
(in lock)



$\Delta N = 1$   
 $\downarrow$

$\Delta \omega_{out} = \omega_{ref}$

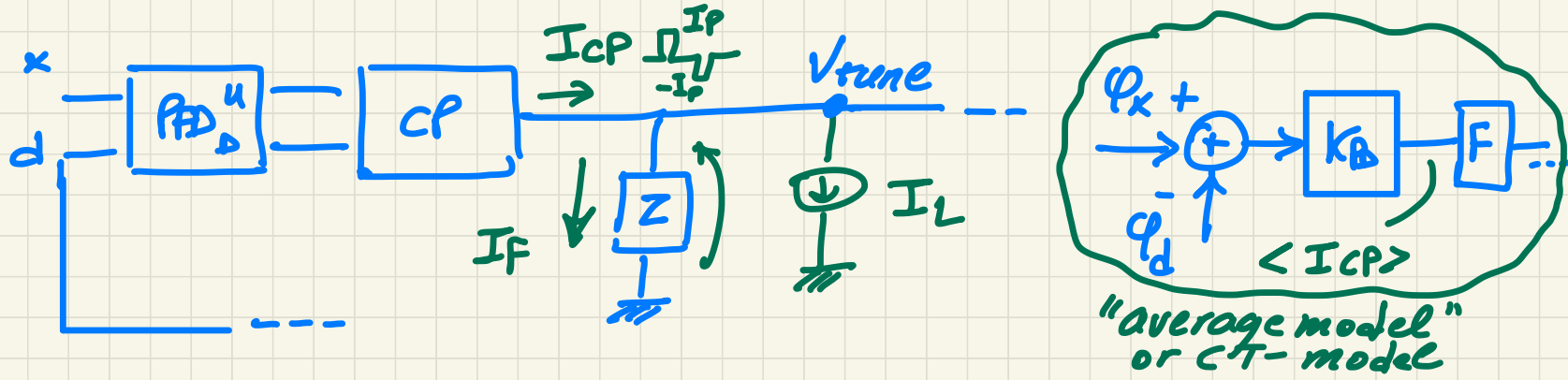


- $I_L = 0$  : at steady state :  $\omega_y = N \cdot \omega_x$



$\Rightarrow V_{tune} = \text{constant}$

$$I(0) \rightarrow \infty \Rightarrow \boxed{\langle I_F \rangle = 0}$$
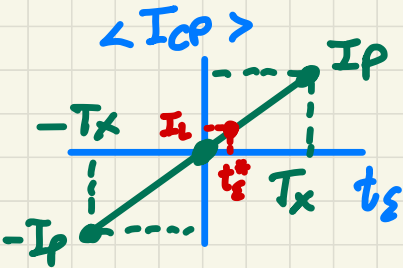
$$\Rightarrow \langle I_{CP} \rangle = 0 \Rightarrow t_E = 0 \quad \text{PFD in "N"}$$




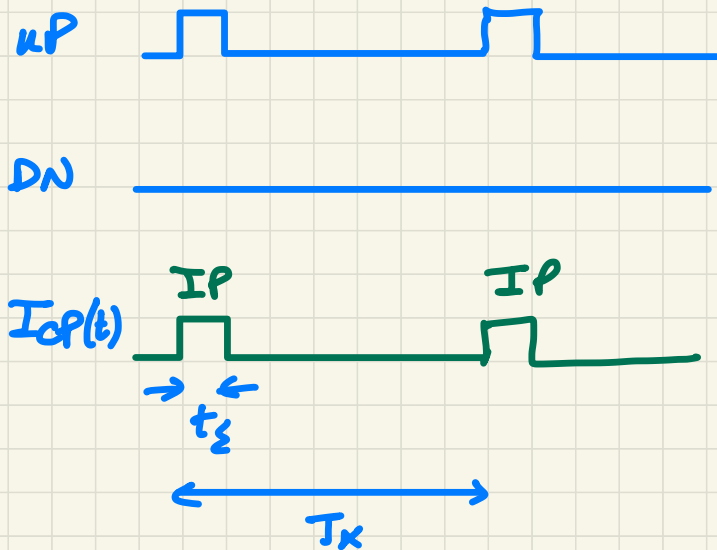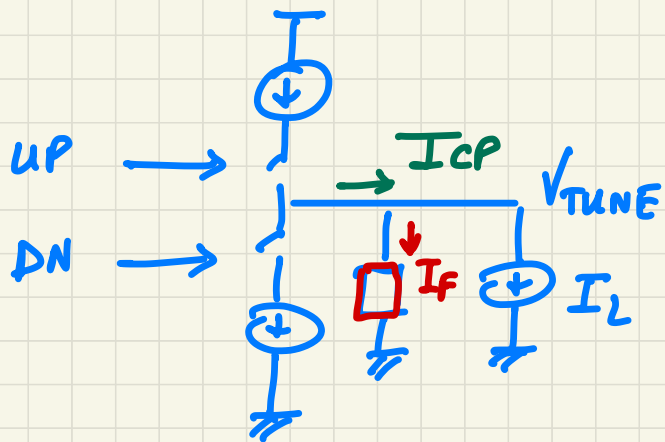- $I_L \neq 0$  : at steady state :  $\langle I_{CP} \rangle = I_L$   
from PFD/CP charact.  $\Rightarrow t_E^* = \frac{I_L}{I_P} \cdot T_x$



$$\underbrace{I_L \cdot T_X}_{\text{leakage charge}} = \underbrace{I_P \cdot t_E^*}_{\text{charge-pump charge}}$$

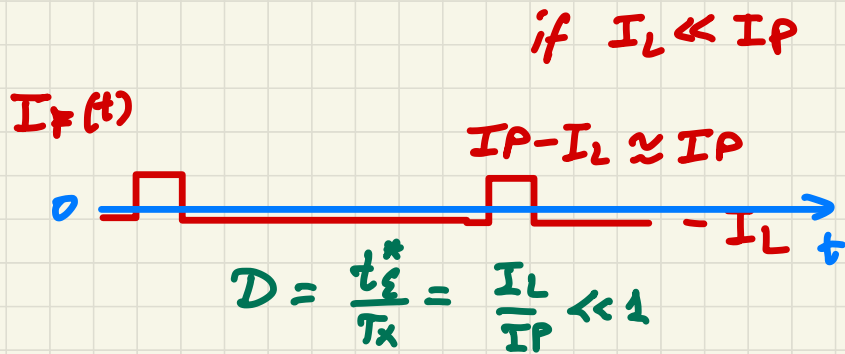
$$\Rightarrow t_E^* = \frac{I_L}{I_P} \cdot T_X$$




\*\*\* Gardner's limit : CT model is valid if  
 $PLL\ BW < f_{ref}/10$  or  $f_{ref}/20$   
 (rule of thumb)

Reference Spur

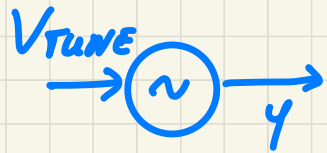$I_F(t)$  is  $T_x$  - periodic  $\Rightarrow V_{TUNE}$  is  $T_x$  - periodic




periodic FM modulation

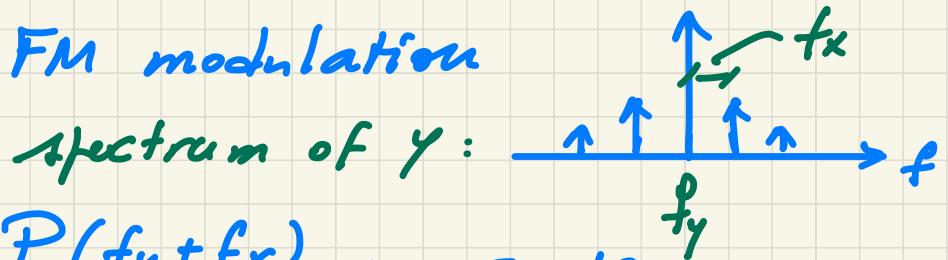

$$L(\Delta f = f_x) = 10 \log_{10} \frac{P(f_y + f_x)}{P(f_y)} \leq -50 \text{ dBc}$$
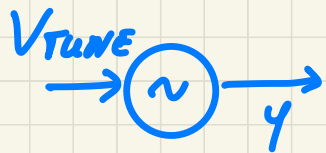
$$L = \frac{S_{\gamma\gamma}}{2} \Rightarrow L_{\text{dBc}} = S_{\gamma\gamma_{\text{dBc}}} - 3 \text{ dB} \Rightarrow S_{\gamma\gamma} \leq -47 \text{ dBc}$$






$$V_{TUNE} = V_{TUNE0} + \underbrace{V_{TUNE}^{(1)}}_{\text{amplitude of the 1st harm.}} \cos \omega_x t + \dots$$



$$\omega_y = \omega_{fr} + K_{VCO} V_{TUNE}$$
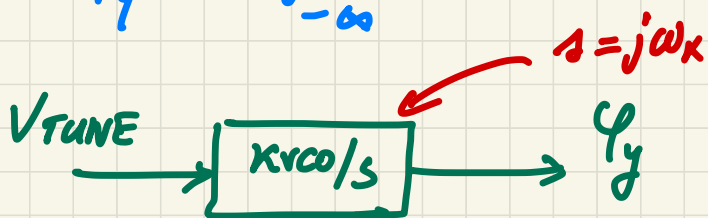
$$\phi_y = \int_{-\infty}^t \omega_y(t') dt'$$




$$\phi_y = \phi_y^{(1)} \sin \omega_x t + \dots$$

$$\phi_y^{(1)} = \frac{K_{VCO}}{j\omega_x} \cdot V_{TUNE}^{(1)}$$



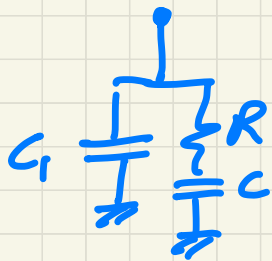
$$S_{\phi_y} = \frac{K_{VCO}^2}{\omega_x^2} \cdot S_{V_{TUNE}}$$



$$Z(s) = \frac{1}{s(C_1 + C)} \cdot \frac{1 + s\tau_2}{1 + s\tau_p}$$

$$\tau_2 = \frac{1}{\omega_2}$$

$$\tau_p = \frac{1}{\omega_p}$$

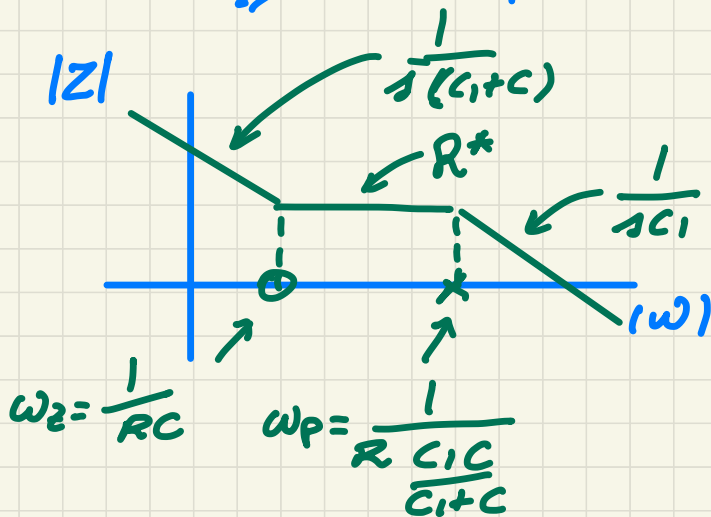


$$\bullet \omega \rightarrow 0 : \frac{1}{j\omega C} \rightarrow \infty$$

$$\approx C_1 \parallel \left( R \parallel \frac{1}{sC} \right) \quad Z \approx \frac{1}{s(C_1 + C)}$$



$$\bullet \omega \rightarrow \infty : \frac{1}{j\omega C} \rightarrow 0$$

$$\approx \frac{1}{sC_1} \quad Z \approx \frac{1}{sC_1}$$
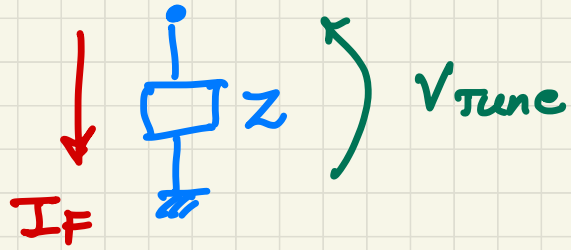
$$\bullet R^* = \frac{1}{\frac{1}{RC} \cdot (C_1 + C)} = R \cdot \frac{C}{C_1 + C}$$



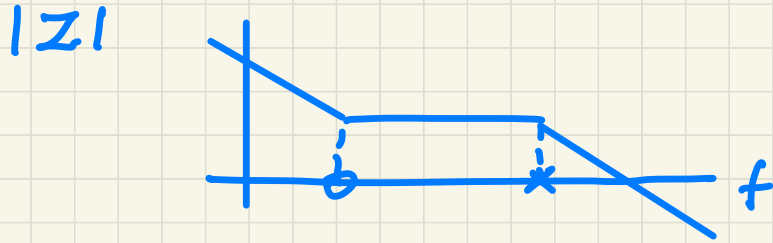
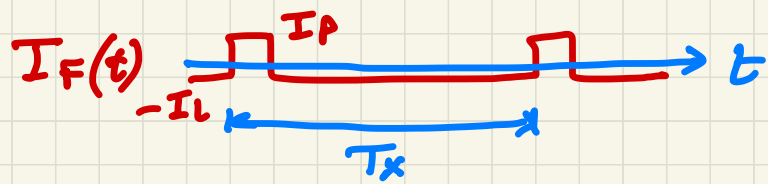
How to determine  
the 1st harmonic  
of  $V_{TUNE}$ ?



- calculate 1st harm. of  $I_F$  :  $I_F^{(1)}$

- $V_{TUNE}^{(1)} = I_F^{(1)} \cdot |Z(j\omega_x)| \Rightarrow S_{V_{TUNE}}(\omega_x) = |Z(j\omega_x)|^2 \cdot S_{I_F}(\omega_x)$
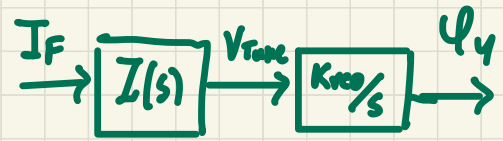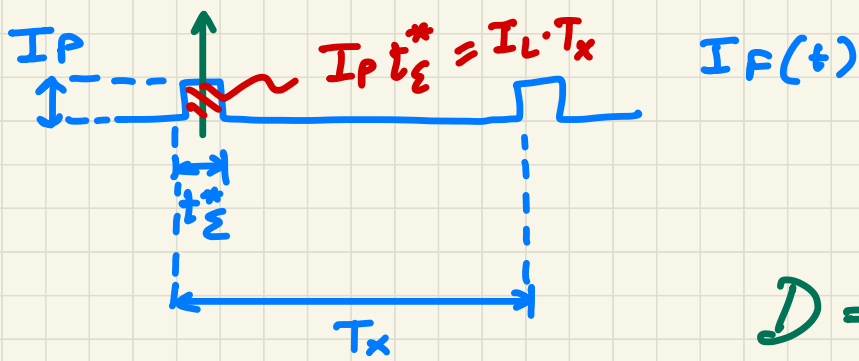
$$S_{y_y}(\omega_x) = \frac{K_{VCO}^2}{\omega_x^2} \cdot S_{V_{TUNE}}(\omega_x)$$



$$D = \frac{t_\epsilon}{T_x}$$

$$\text{sinc}(x) = \frac{\sin \pi x}{\pi x}$$

Graph of a single pulse  $I_{rect}$  with peak  $I_P$  and width  $t_\epsilon$ . The equation is:

$$I_P \cdot t_\epsilon \cdot \text{sinc}(t_\epsilon \cdot f) = \mathcal{F}\{I_{rect}\}$$

Equation for the first harmonic of  $I_F(t)$ :

$$\frac{I_F^{(1)}}{2} = \frac{1}{T_x} \cdot I_P \cdot t_\epsilon \cdot \text{sinc}\left(\frac{t_\epsilon}{T_x}\right) = I_P \cdot D \cdot \text{sinc}(D)$$

First harmonic of  $I_F(t)$

Equation for the output power spectrum  $S_{\psi_y}(\omega_x)$ :

$$\Rightarrow S_{\psi_y}(\omega_x) = \frac{K_{VCO}^2}{\omega_x^2} \cdot |Z(j\omega_x)|^2 \cdot \left[ \frac{I_F^{(1)}}{2} \right]^2 \leftarrow S_{I_F}$$




$$K_{VCO} = 2\pi \cdot \Delta f_{VCO} / V_{DD} = 419 \frac{\text{Mrad}}{\text{Vs}}$$


$$\Rightarrow C_1 = \frac{K_{VCO}}{\omega_x^2} \cdot \frac{\sqrt{2} \cdot I_L}{\sqrt{S_{qy}}} = \frac{419 \cdot 10^6}{(2\pi)^2 \cdot 10^{12}} \cdot \frac{\sqrt{2} \cdot 10^{-7}}{4.5 \cdot 10^{-3}} = 3.34 \cdot 10^{-10} \text{ F} = 334 \text{ pF}$$

100 nA

$\sqrt{10^{-4.7}}$

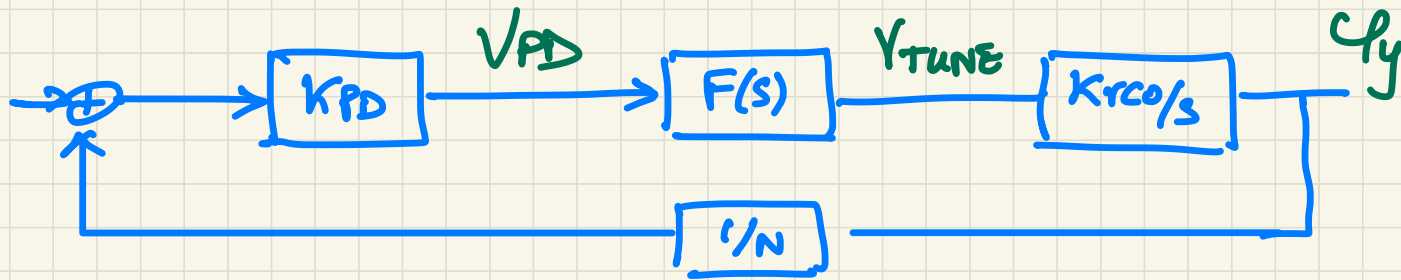

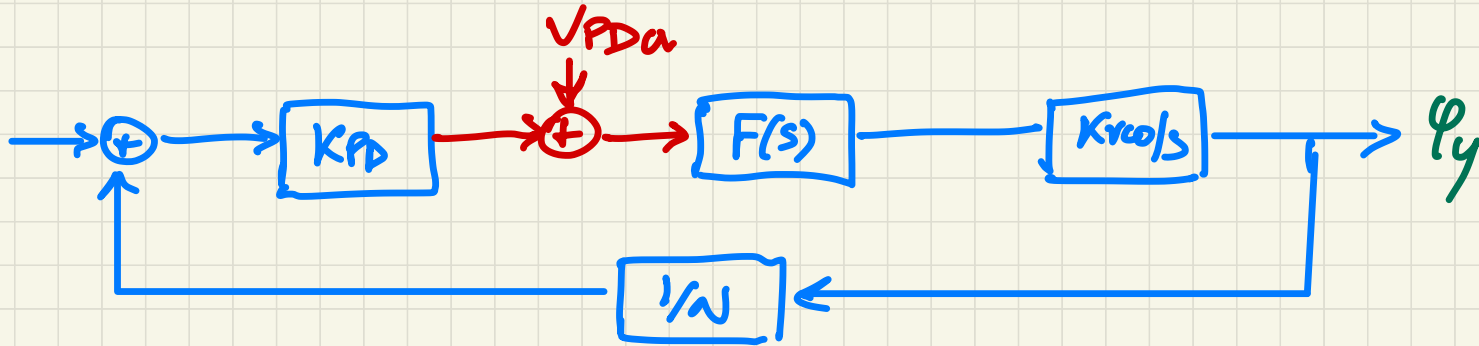
$$\phi_y = \frac{K_{vcw}}{s} \cdot F(s) \cdot V_{PD}(s)$$




$$\phi_y = \frac{K_{vcw}/s \cdot F(s)}{1 + LG(s)} \cdot V_{PDa}(s)$$

c.

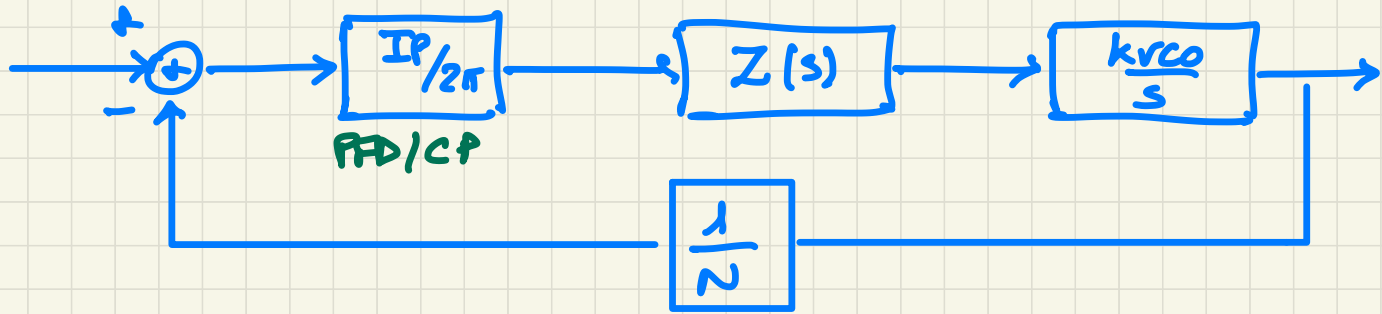

$$LG(j\omega) = \frac{I_P}{2\pi} \cdot \frac{krco}{N} \cdot \frac{1}{j\omega} \cdot \underbrace{\frac{1}{s(c_1+c)}}_{Z(j\omega_k) = R \cdot \frac{C}{c_1+c}} \cdot \frac{1+s\tau_z}{1+s\tau_p} \Big|_{s=j\omega}$$

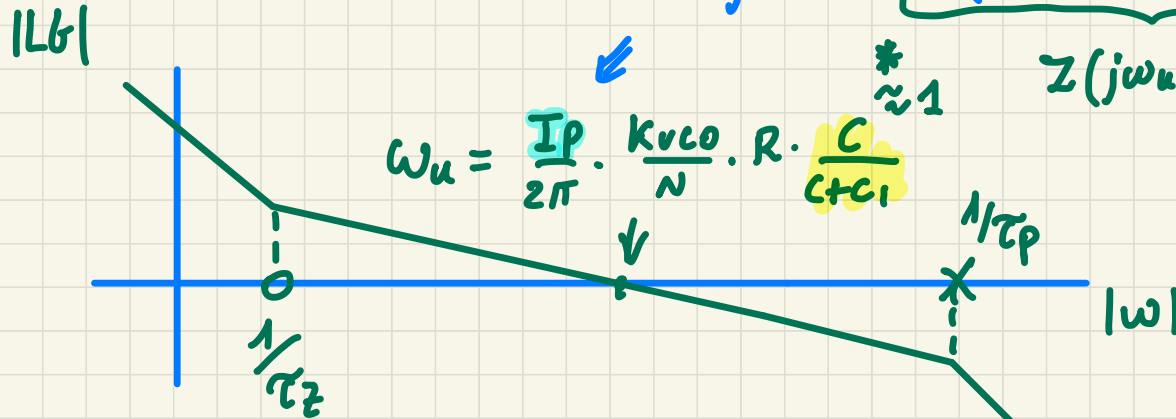

$$\omega_u = \frac{I_P}{2\pi} \cdot \frac{krco}{N} \cdot R \cdot \frac{C}{c_1+c_1} \quad \begin{matrix} * \\ \approx 1 \end{matrix}$$

$$Z(j\omega_k) = R \cdot \frac{C}{c_1+c}$$


$$\begin{aligned} \tau_z &= RC \\ \tau_p &= R \frac{CC_1}{C+c_1} \end{aligned}$$

Asymptotic approximation ( $\omega_u \gg 1/\tau_z$ ,  $\omega_u \ll 1/\tau_p$ )  $\begin{matrix} * \\ 1/\tau_z \ll 1/\tau_p \end{matrix}$



$$\varphi_m = \arctan\left(\frac{\omega_u}{\omega_z}\right) - \arctan\left(\frac{\omega_u}{\omega_p}\right)$$

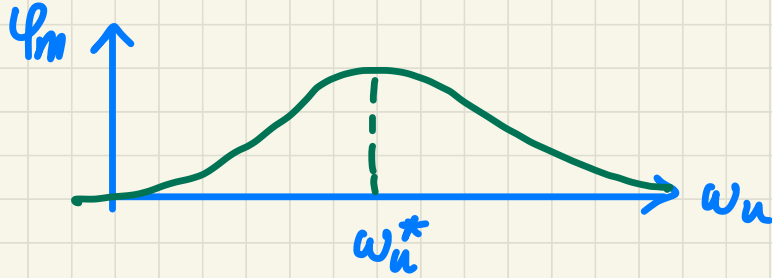max.  $\varphi_m$  as a function of  $\omega_u$



$$C_1 = 334 \text{ pF}$$

$$C = 100 \text{ nF}$$



$$R = 1.6 \text{ k}\Omega$$

$$\frac{d\varphi_m}{d\omega_u} = \frac{1}{\omega_z} \cdot \frac{1}{1 + \left(\frac{\omega_u}{\omega_z}\right)^2} - \frac{1}{\omega_p} \cdot \frac{1}{1 + \left(\frac{\omega_u}{\omega_p}\right)^2} = 0 \Rightarrow \dots \Rightarrow$$


$$\Rightarrow \boxed{\omega_u = \sqrt{\omega_z \cdot \omega_p}}$$

$$f_u = 17.3 \text{ kHz} \leftarrow$$
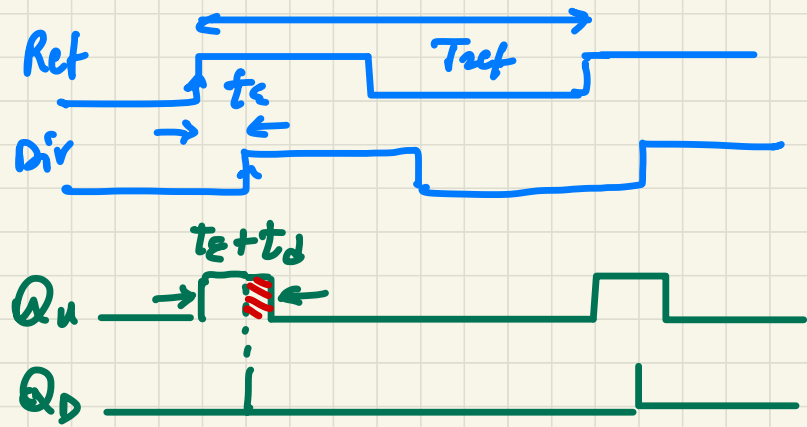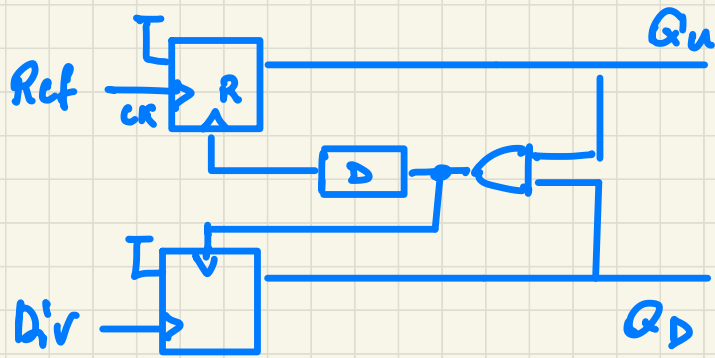
$$\begin{cases} f_z = \frac{1}{2\pi RC} = \sim 1 \text{ kHz} \\ f_p \approx \frac{1}{2\pi RC_1} = \sim 300 \text{ kHz} \end{cases}$$




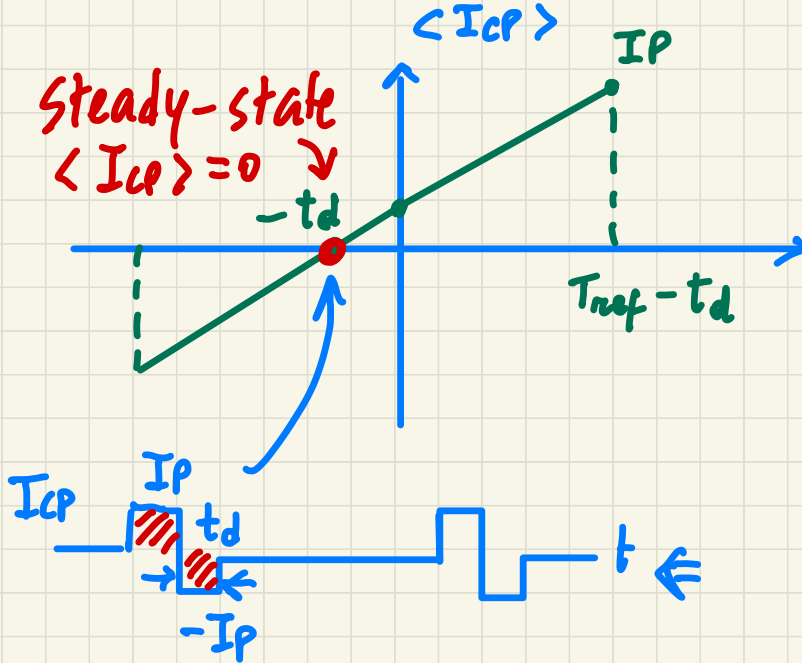Steady-state  
 $\langle I_{cp} \rangle = 0$




•  $t_{\varepsilon} = 0$  :

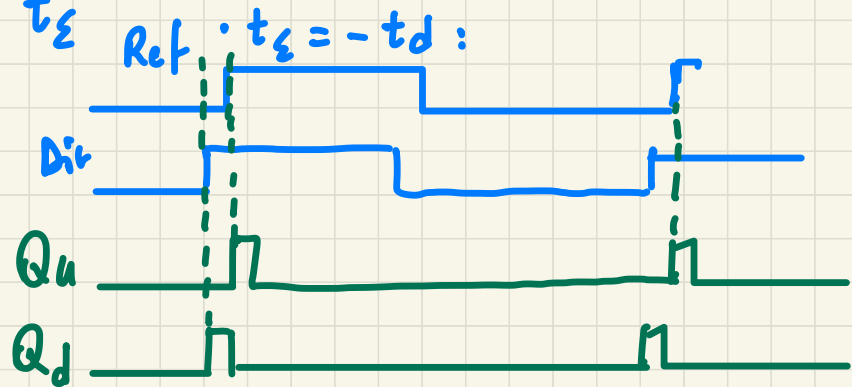
$$\langle I_{cp} \rangle = I_p \cdot \frac{t_d}{T_{ref}}$$



$$I_{CP} = I_F(t)$$

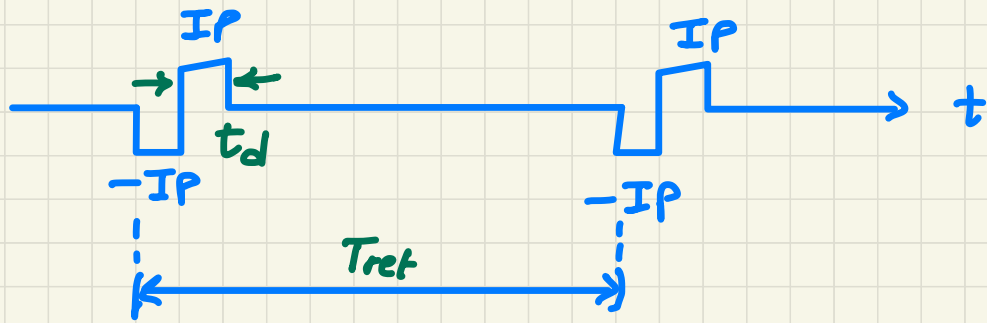


$$e^x \approx 1+x$$

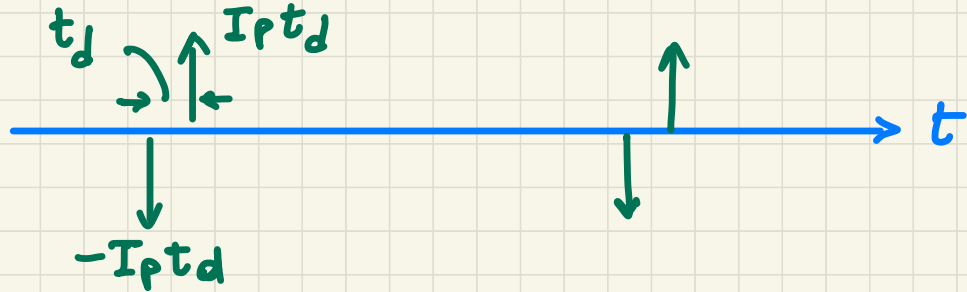

$$I_F(t) \approx -Q \cdot \sum \delta(t - nT_{ref}) + Q \sum \delta(t - nT_{ref} - t_d)$$

$$\begin{aligned} \mathcal{F}\{I_F(t)\} &= \frac{Q}{T_{ref}} \cdot \sum \delta\left(f - \frac{n}{T_{ref}}\right) \left[ \underbrace{-1 + e^{-j2\pi f t_d}}_{\approx j \cdot 2\pi f \cdot t_d} \right]_{f = \frac{n}{T_{ref}}} \\ &= \sum \frac{I_P \cdot t_d}{T_{ref}} \cdot j \cdot 2\pi n \frac{t_d}{T_{ref}} \cdot \delta\left(f - \frac{n}{T_{ref}}\right) \end{aligned}$$
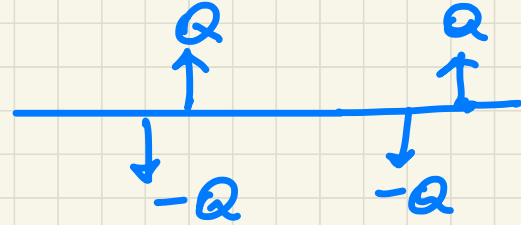
$$I_F^{(1)} = 2 \cdot \underbrace{\frac{I_p \cdot t_d}{T_{ref}}}_{\frac{Q}{T_{ref}}} \cdot \underbrace{2\pi \cdot \frac{t_d}{T_{ref}}}_{\omega_{ref} \cdot t_d} =$$



$$= 2 \cdot I_p \cdot 2\pi \cdot \left( \frac{t_d}{T_{ref}} \right)^2$$

\*\* with single pulse train  
 $2 I_p \cdot D \cdot \underbrace{\sin D}_{\approx 1}$

$$\mathcal{L}(\omega_{ref}) = \frac{S_4}{2} = \frac{1}{2} \left( \frac{K_{vco}}{\omega_{ref}} \right)^2 \cdot \left( \frac{1}{\omega_{ref} C_1} \right)^2 \cdot \frac{[I_F^{(1)}]^2}{2}$$

$\Downarrow$   
 $C_1$

# Real charge pump : Dead zone

