
Phase-Locked Loop Design

Part 1


RF Circuit Design
Prof. Salvatore Levantino
2020/2021

Outline


- **Type-I PLL with Analog Multiplier**
 - **Type-I PLL with XNOR**
-

Type-I PLL with Analog Multiplier

PLL with Analog Multiplier

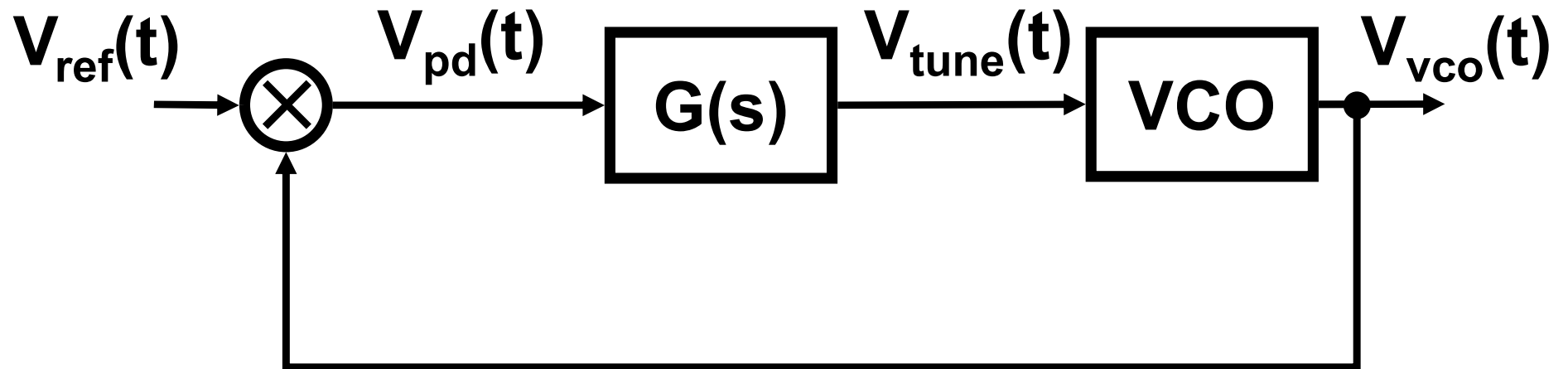

Linear Continuous-Time (CT) Model

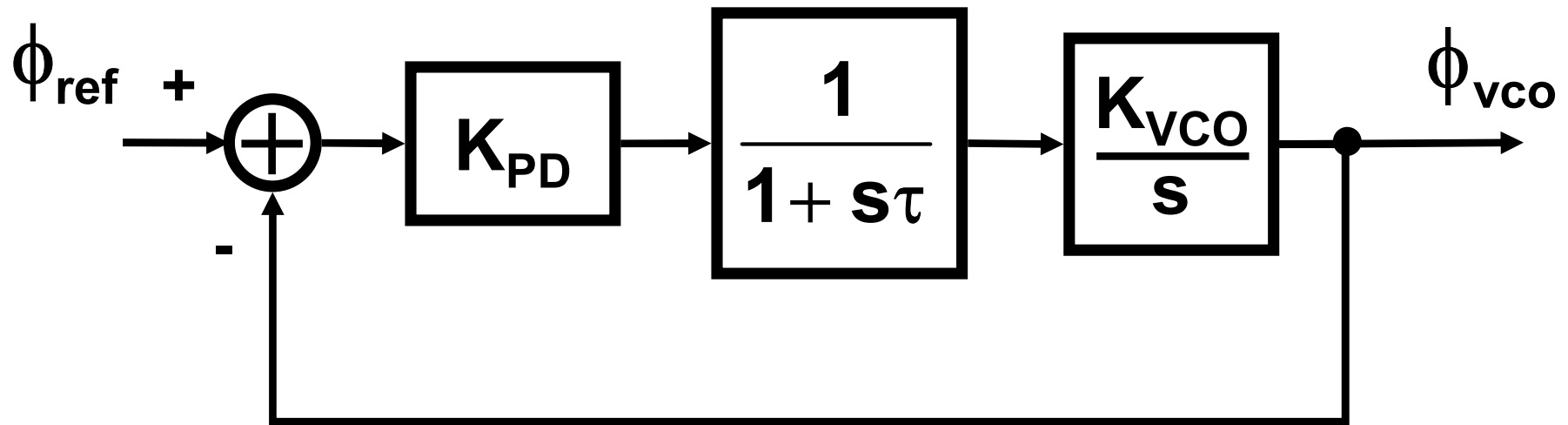


$$\frac{\Phi_{VCO}(s)}{\Phi_{ref}} = \frac{k/\tau}{s^2 + s/\tau + k/\tau}$$

$$\rightarrow H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\rightarrow \begin{cases} \omega_n = \sqrt{k/\tau} \\ \zeta = \frac{1}{2\sqrt{k\tau}} \end{cases}$$

Loop dynamics: Step response of 2nd ord system
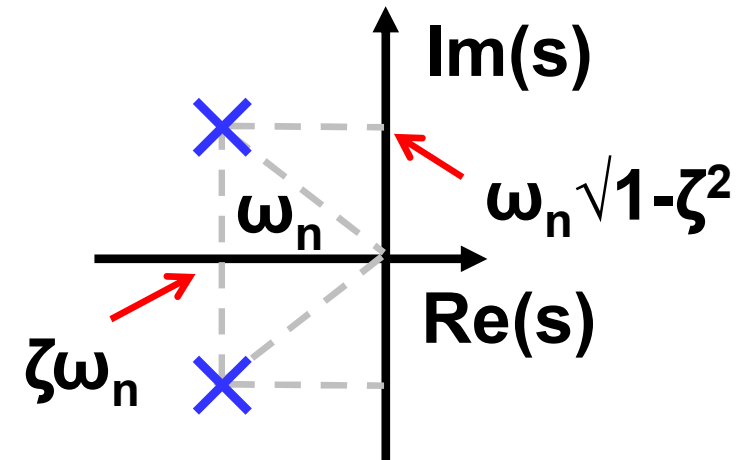
$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$




$\zeta < 1$:

Error w.r.t. final values


$$y(t) = \left[1 - \frac{1}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_n t} \sin\left(\omega_n \sqrt{1-\zeta^2} t + \psi\right) \right] \cdot u(t)$$

$$\psi = \arcsin \sqrt{1-\zeta^2}$$

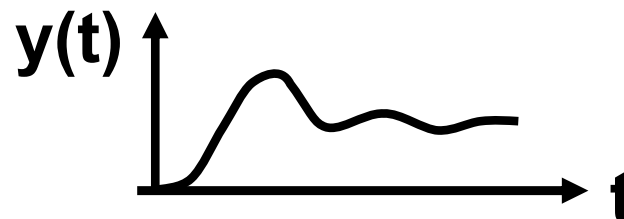

Unit Step Function

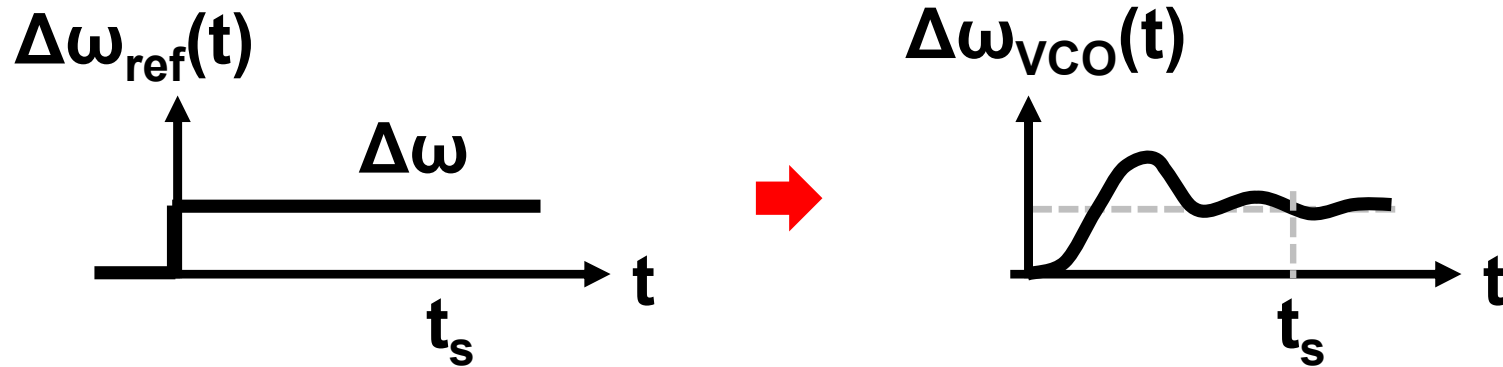Loop dynamics: *Settling time of 2nd ord. system*



$$\omega_{\text{err}} \leq \Delta\omega \cdot \frac{1}{\sqrt{1-\zeta^2}} \cdot e^{-\zeta\omega_n t_s}$$

→

$$t_s = \frac{1}{\zeta\omega_n} \cdot \ln \left(\frac{\Delta\omega}{\omega_{\text{err}} \sqrt{1-\zeta^2}} \right)$$

Parameter Set

$$\frac{\Phi_{\text{VCO}}(s)}{\Phi_{\text{ref}}} = \frac{k/\tau}{s^2 + s/\tau + k/\tau}$$

$$\begin{cases} \omega_n = \sqrt{k/\tau} \\ \zeta = \frac{1}{2\sqrt{k\tau}} \end{cases}$$


$$\zeta = \frac{\sqrt{2}}{2}$$




$$\begin{cases} \tau = \frac{1}{2k} \\ \omega_n = k\sqrt{2} \end{cases}$$

Critical damping

Linear CT Model (Simulink)

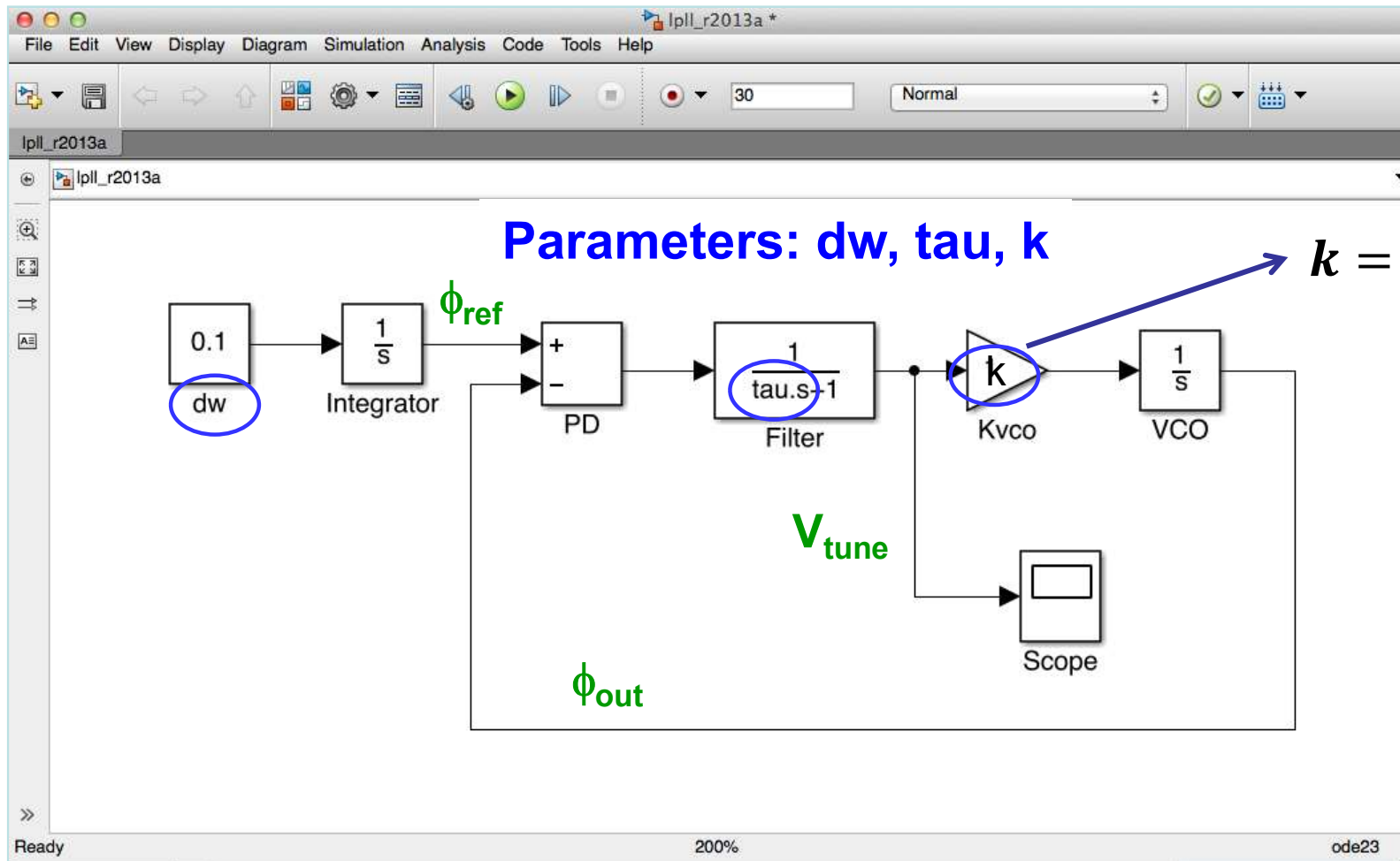

Simulation Parameters (Simulink)

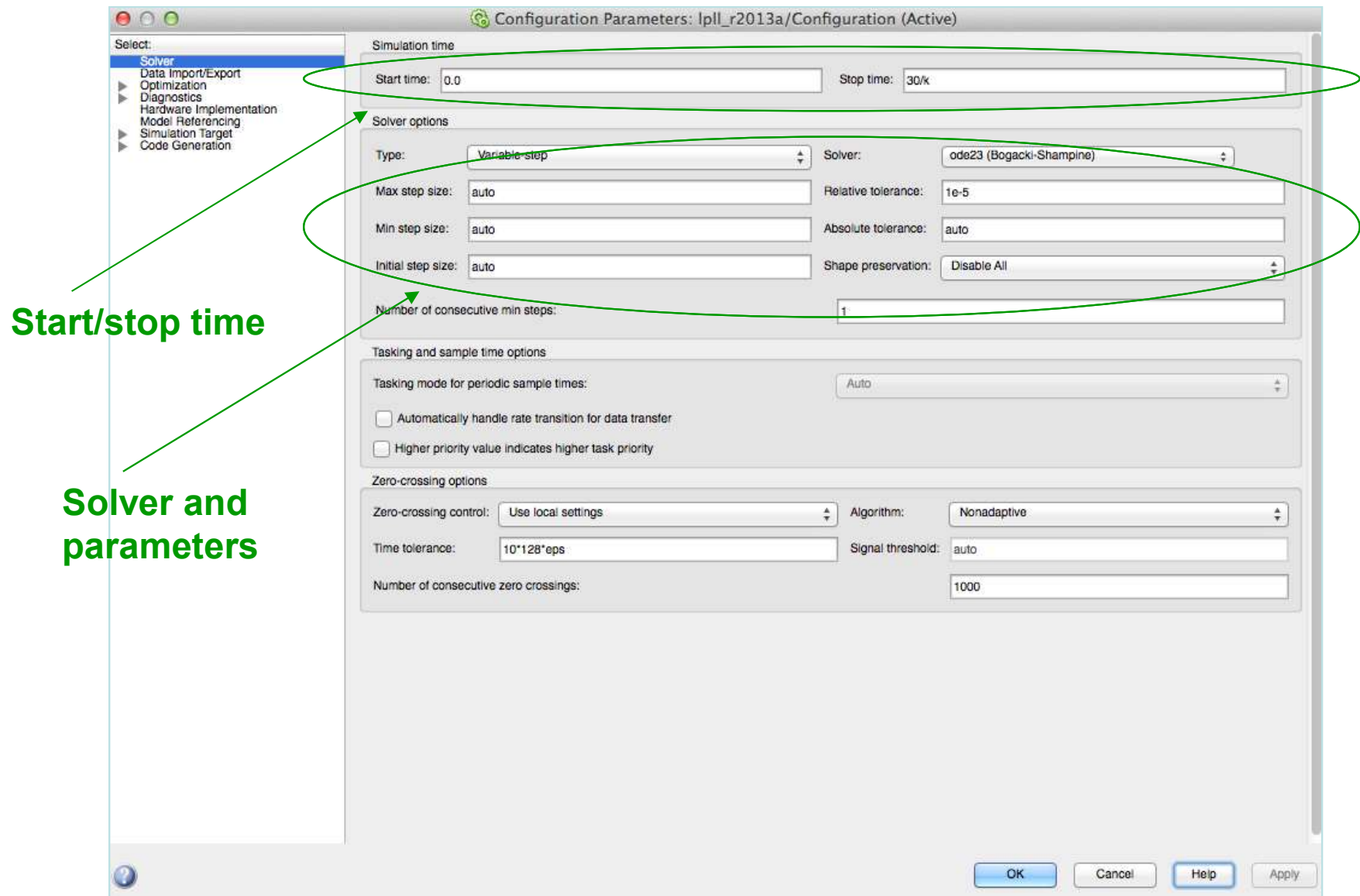

Parameter Set (Simulink)

$$\begin{cases} \omega_n = \sqrt{k/\tau} \\ \zeta = \frac{1}{2\sqrt{k\tau}} \end{cases}$$

$$\zeta = \frac{\sqrt{2}}{2}$$




$$\begin{cases} \tau = \frac{1}{2k} \\ \omega_n = k\sqrt{2} \end{cases}$$

Critical damping

Parameter set:

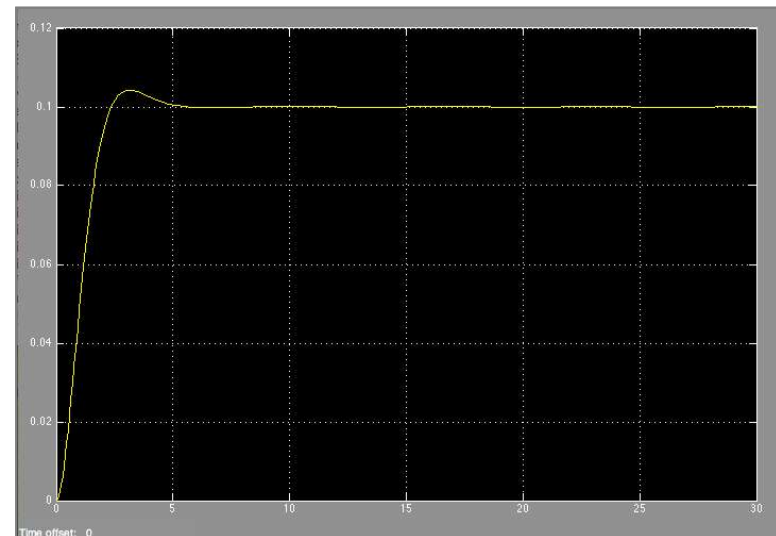
- **$k = 1$**
- **$\tau = 0.5$**
- **$t_{\text{stop}} = 30$**
- **$dw = 0.1$**



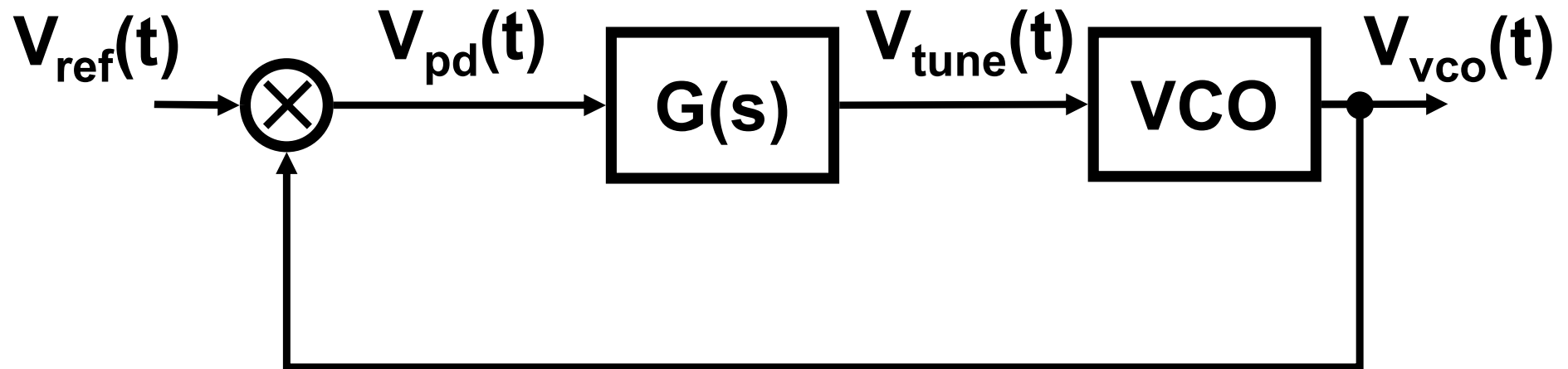Exercise #1


- **Estimate the settling time of the PLL linear model** to make a frequency step $\Delta\omega$ with an error ω_e such that $\omega_e/\Delta\omega = 1\%$ from theory and simulation.
- **Change the parameter settings** to halve the damping factor while keeping the same PLL bandwidth value. Plot again the step transient and comment the result.

PLL with Analog Multiplier: Nonlinear Equations




$$\left\{ \begin{array}{l} \mathbf{V}_{\text{ref}}(\mathbf{t}) = \sin\left[(\omega_0 + \Delta\omega)\mathbf{t}\right] \\ \mathbf{V}_{\text{vco}}(\mathbf{t}) = \cos\left[\omega_0\mathbf{t} + \mathbf{K}_{\text{vco}}\int_0^{\mathbf{t}} \mathbf{V}_{\text{tune}}(\mathbf{t}')\mathbf{d}\mathbf{t}'\right] \\ \mathbf{V}_{\text{pd}}(\mathbf{t}) = 2\mathbf{V}_{\text{ref}}(\mathbf{t}) \cdot \mathbf{V}_{\text{vco}}(\mathbf{t}) \\ \mathbf{V}_{\text{tune}}(\mathbf{t}) = \mathbf{V}_{\text{pd}}(\mathbf{t}) * \mathbf{g}(\mathbf{t}) \end{array} \right.$$

PLL with Analog Multiplier (Simulink)

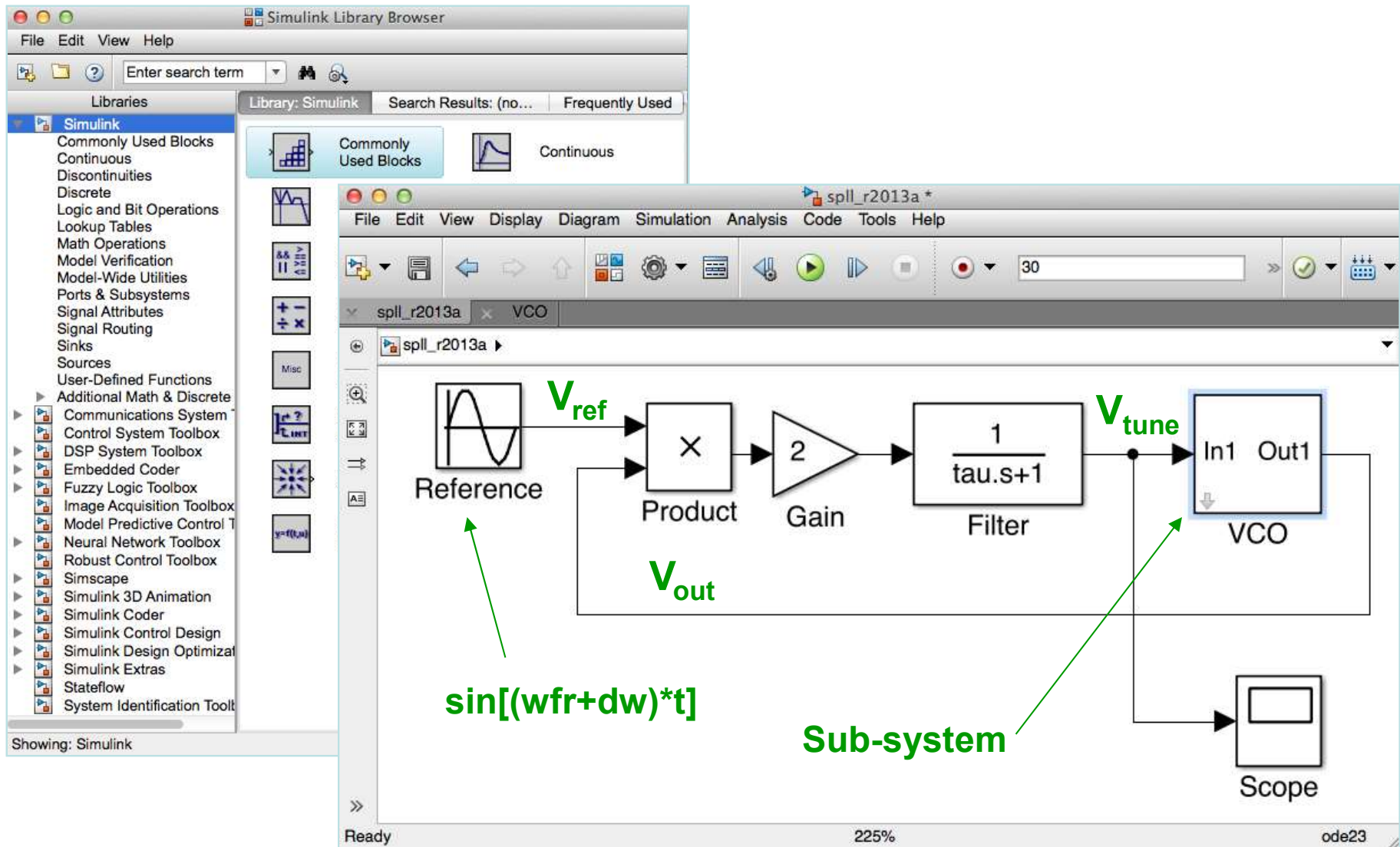

VCO Model (Simulink)

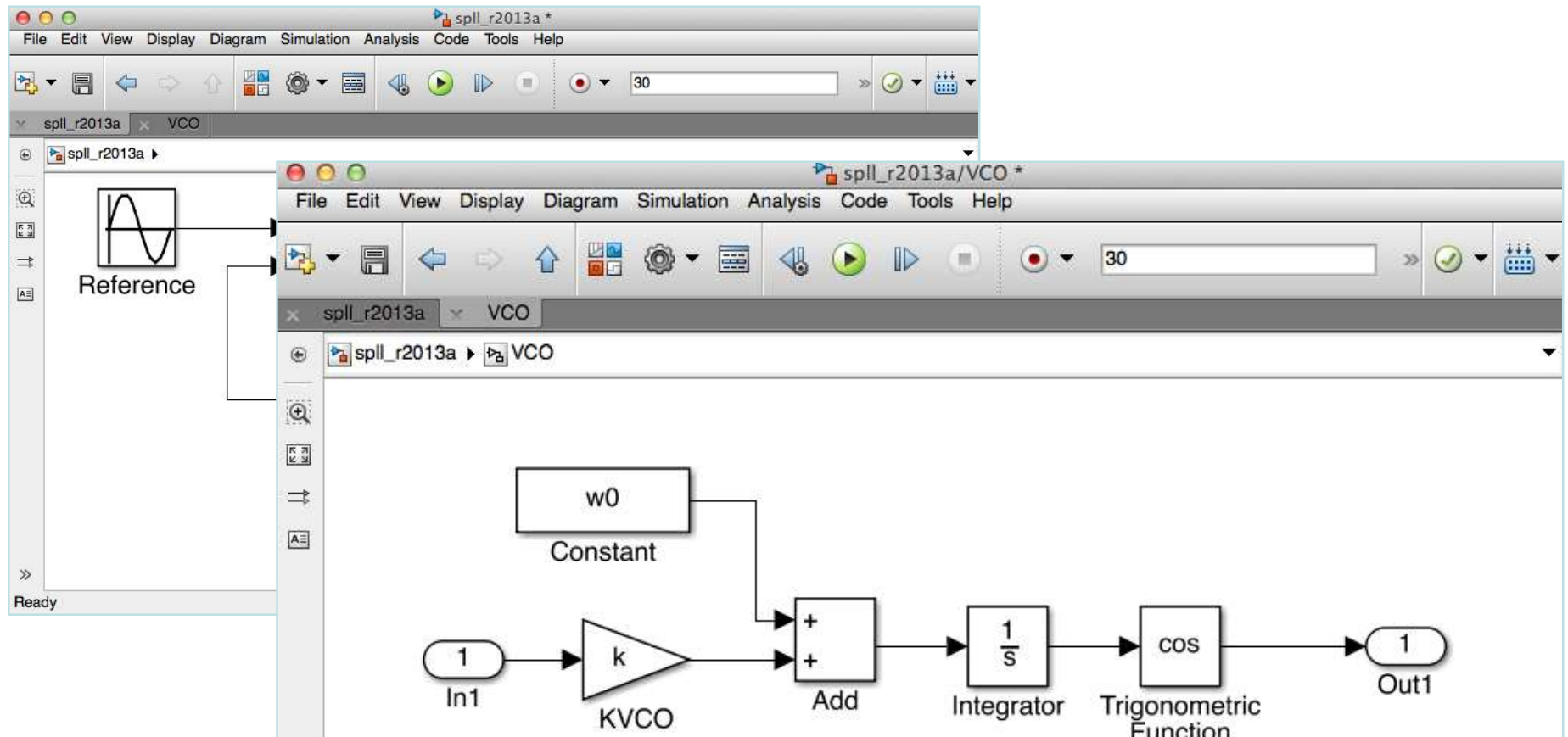

Parameters: w_0 , k

$$V_{VCO}(t) = \cos[\omega_0 t + k \int_0^t V_{\text{tune}}(t') dt']$$

Parameter Set

$$\begin{cases} \omega_n = \sqrt{k/\tau} \\ \zeta = \frac{1}{2\sqrt{k\tau}} \end{cases}$$

Critical damping


$$\zeta = \frac{\sqrt{2}}{2}$$




$$\begin{cases} \tau = \frac{1}{2k} \\ \omega_n = k\sqrt{2} \end{cases}$$

Parameter set:

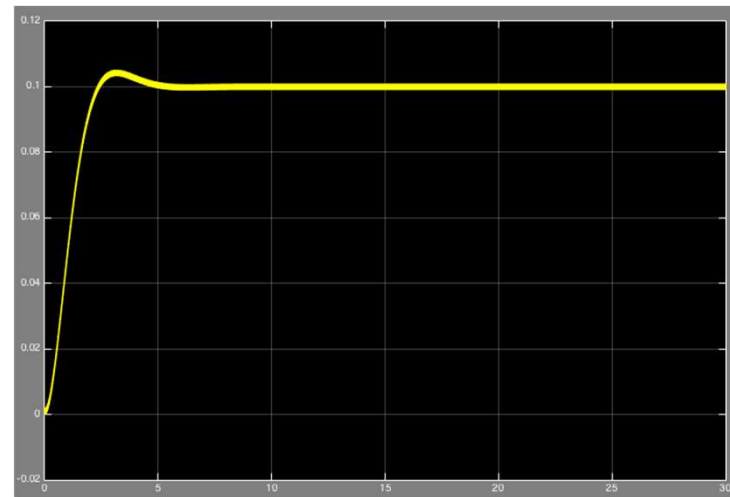
- $k = 1$
- $\tau = 0.5$
- $t_{\text{stop}} = 30$
- $w_0 = 1e3$
- $dw = 0.1$



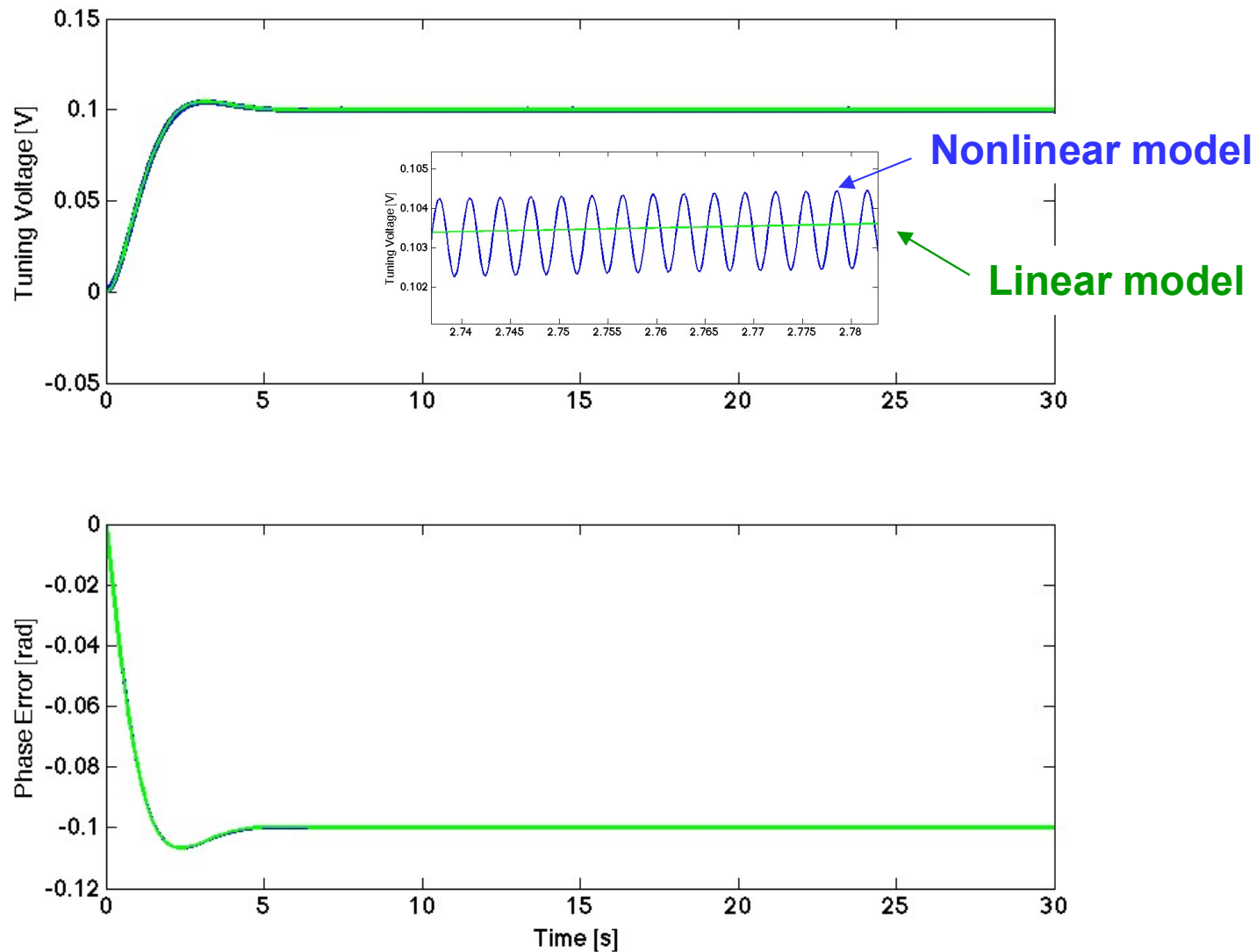
Nonlinear vs Linear (Maximum Flat Response)



Nonlinear vs Linear (Underdamped)

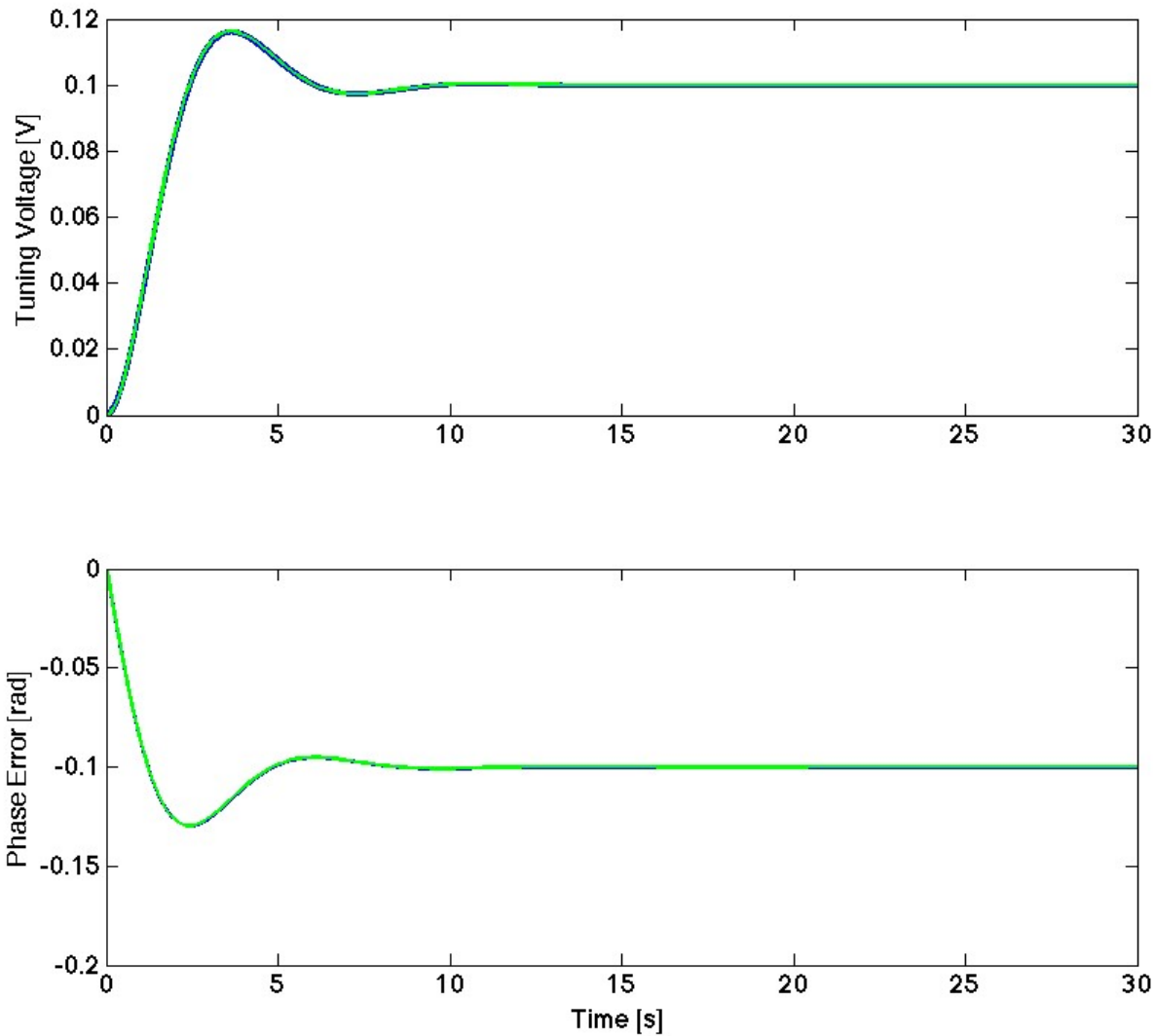

Nonlinear vs Linear (Out of Lock Range)

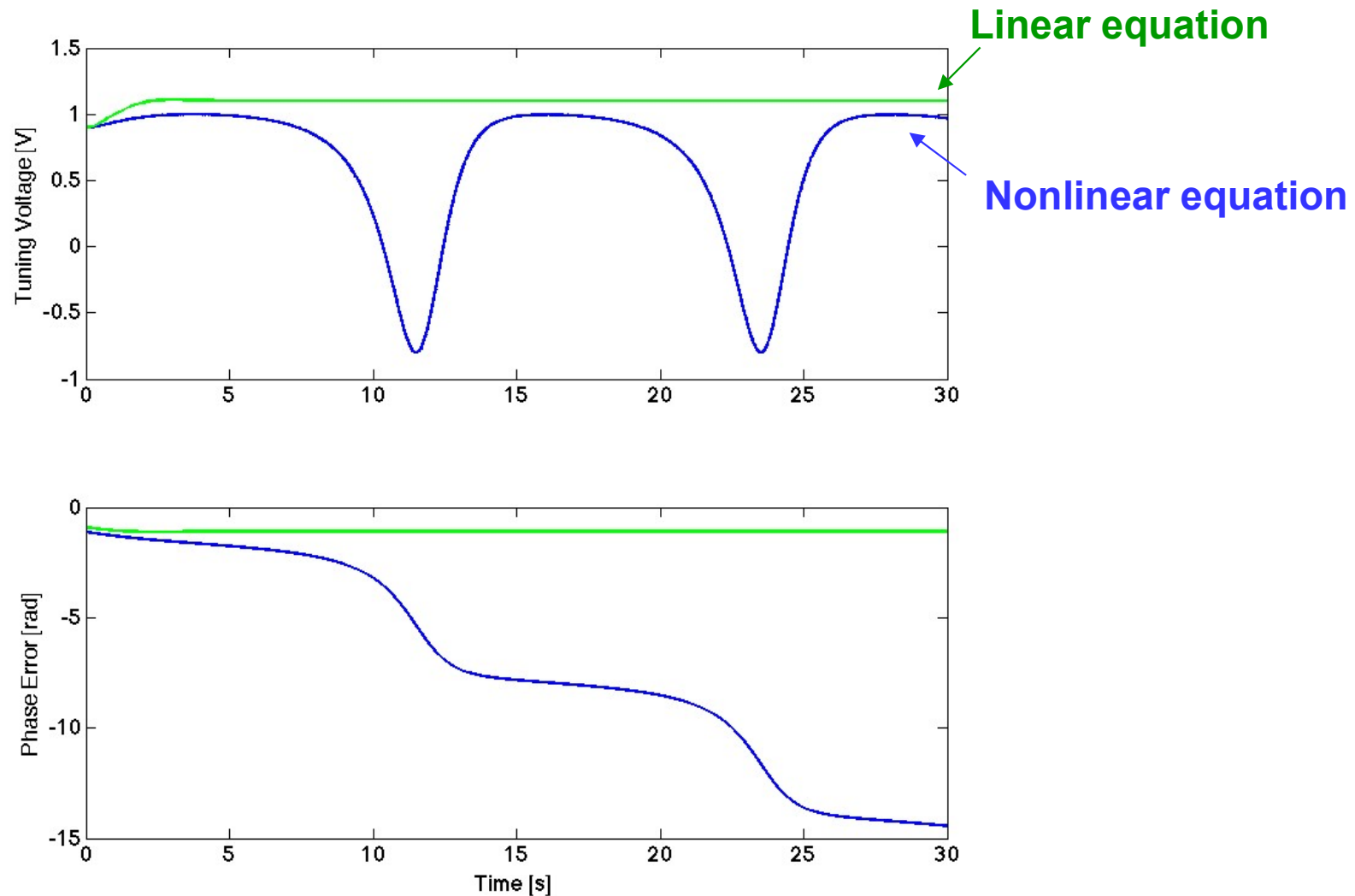


Exercise #2


- **Estimate the ripple amplitude and frequency of the tuning voltage (in critical damping and underdamped case) from theory and simulation.**
- **Estimate the lock range and the capture range of the PLL (in critical and underdamped case) from theory and simulation.**

Type-I PLL with XNOR


Type-I PLL with XNOR

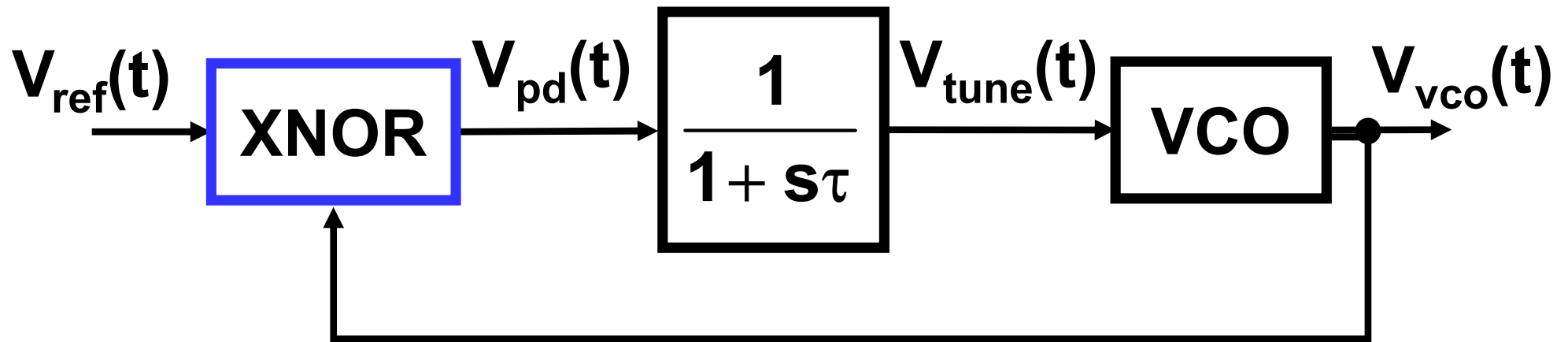


Type-I PLL with XNOR (Simulink)

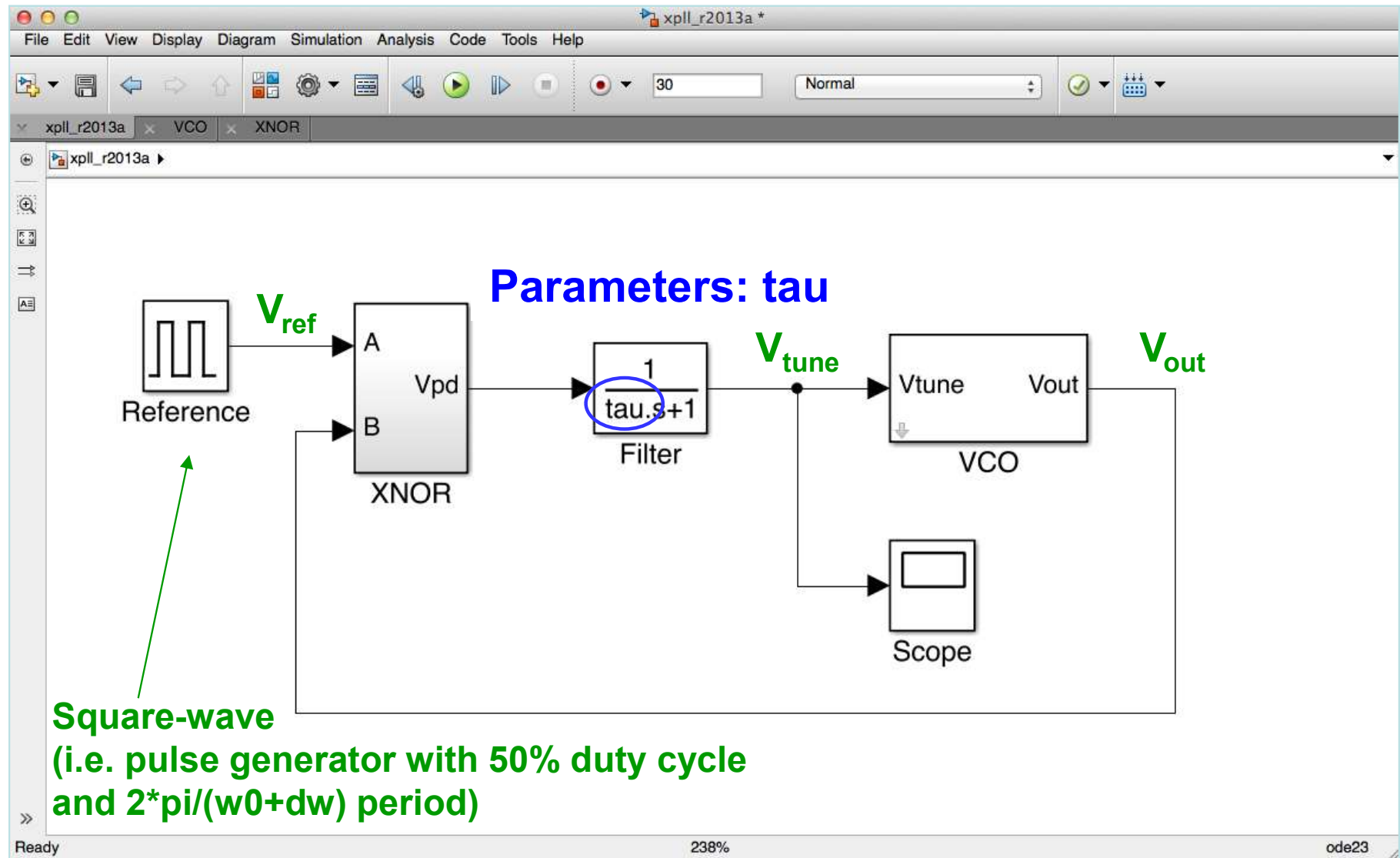


Reference Signal (Simulink)

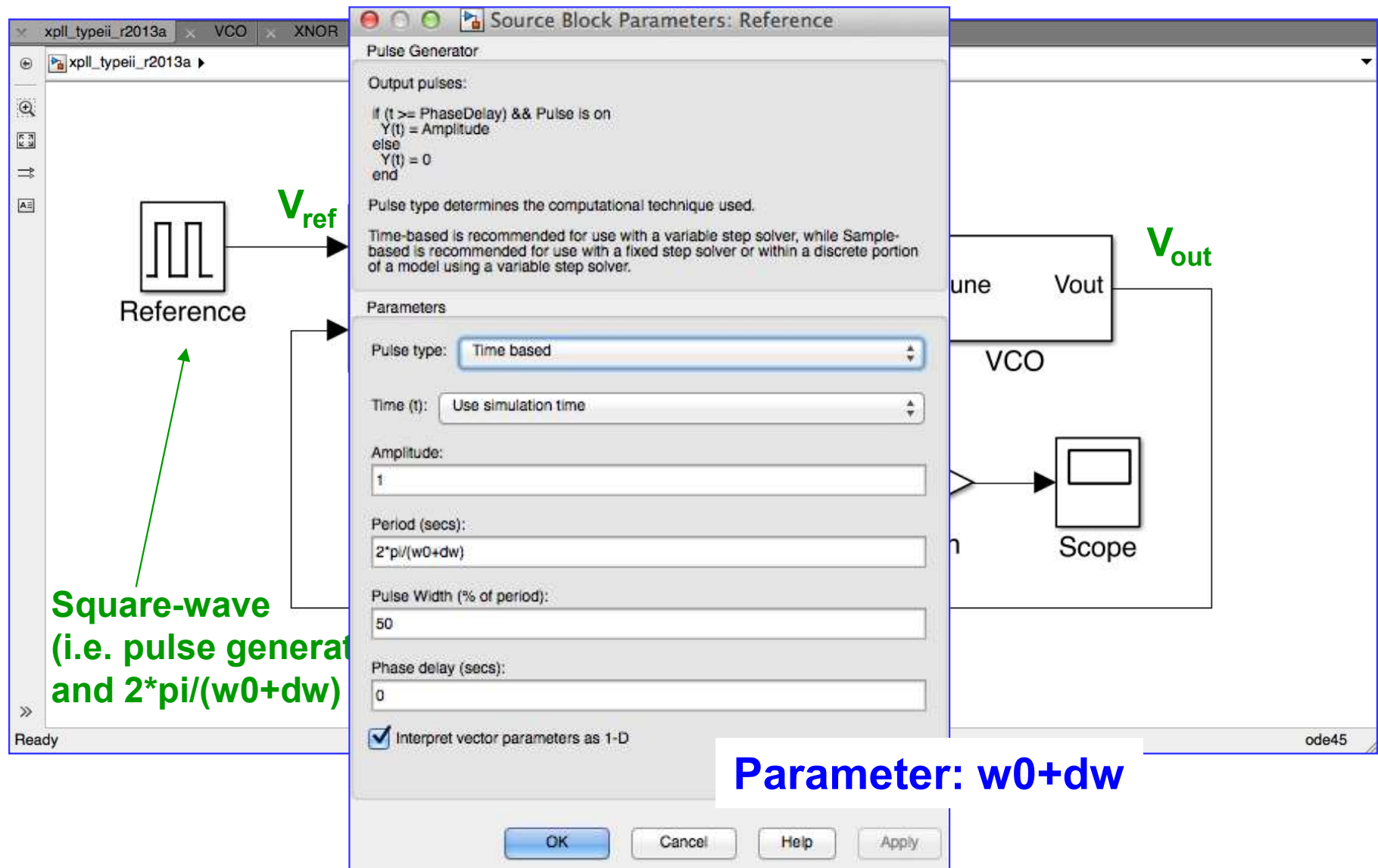


XNOR Block (Simulink)

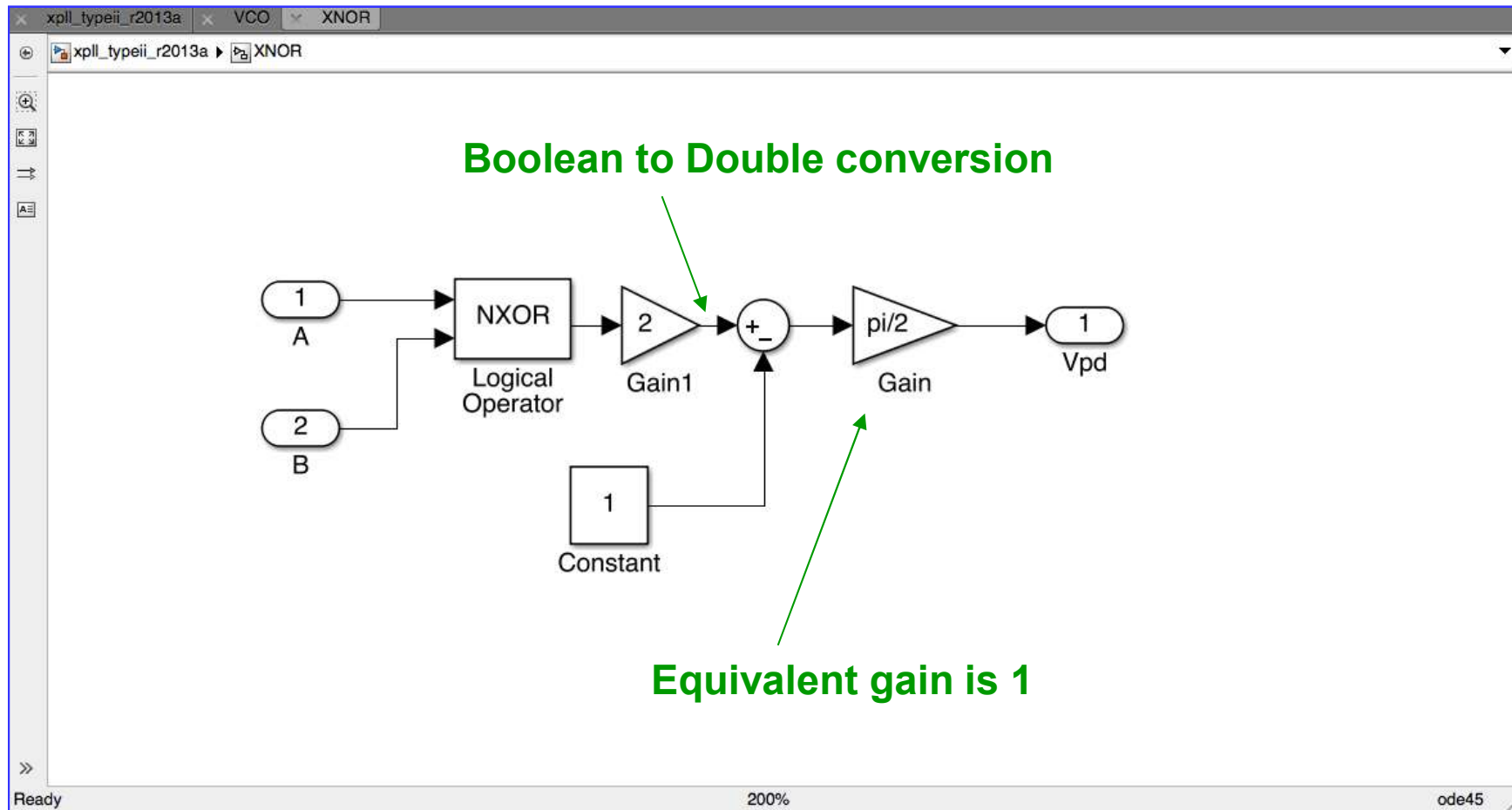

VCO (Simulink)

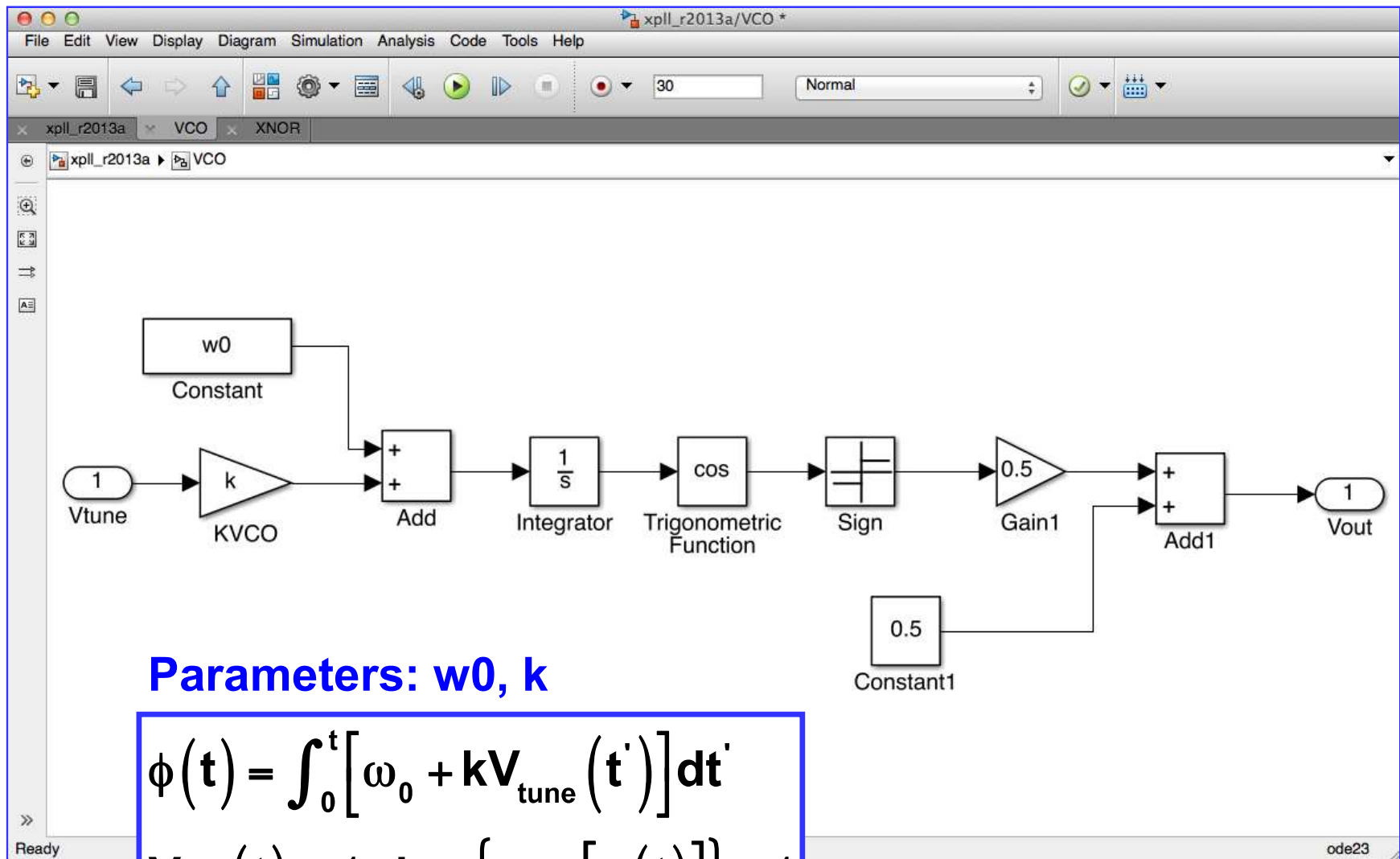

Nonlinear vs Linear

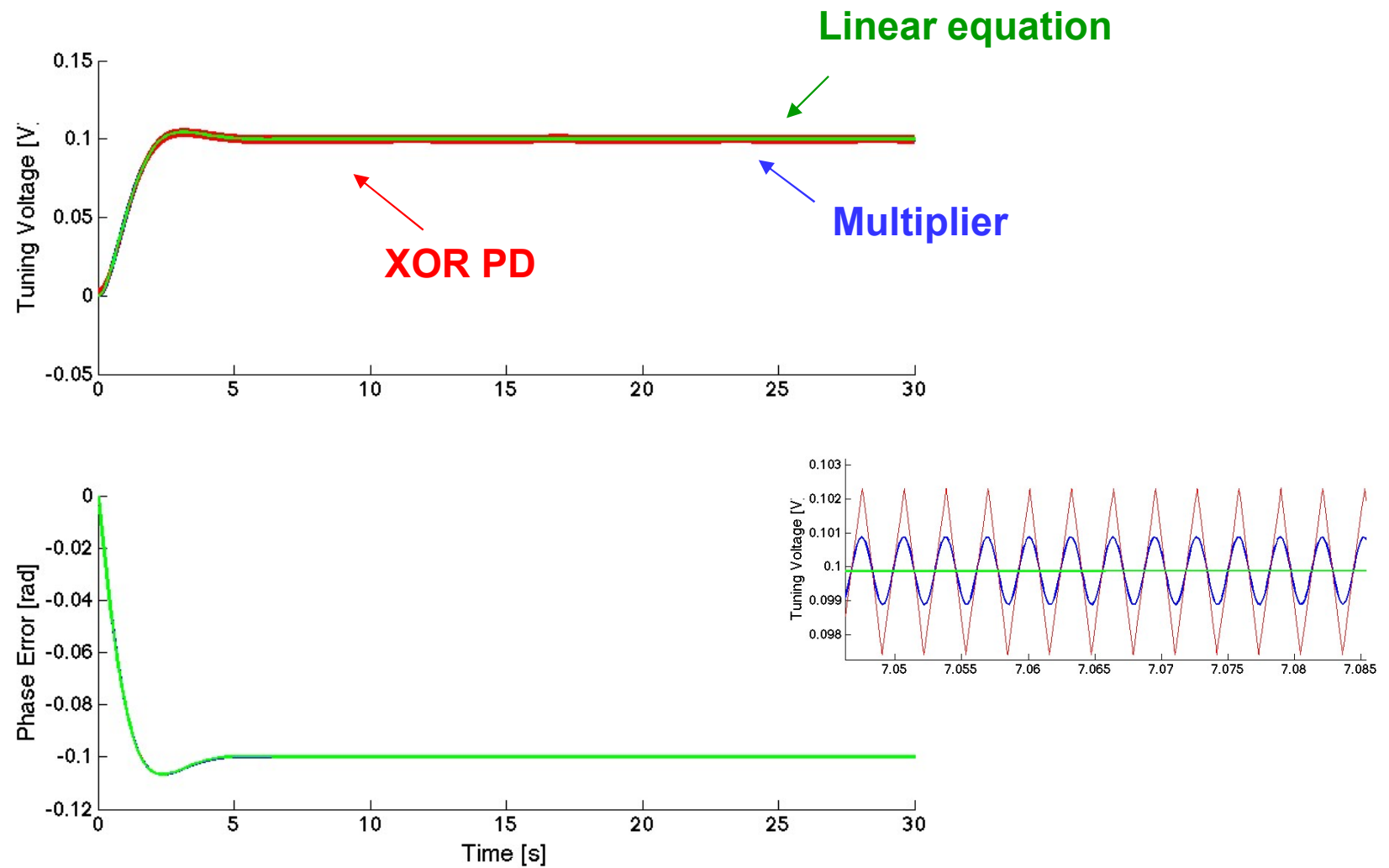

Exercise #3

- **Estimate the ripple amplitude and frequency of the tuning voltage (in critical damping and underdamped case) from simulation.**
- **Try to theoretically justify the previous empirical result**