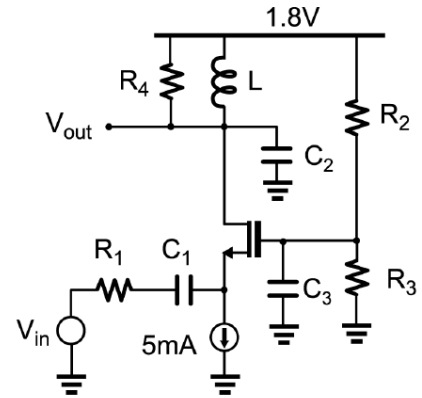


## Tutorial T10

**T10.1** Let us consider the LNA in figure, where  $R_1 = 50\Omega$ ,  $C_1 = 1\text{nF}$ ,  $L = 1\text{nH}$ ,  $R_2 = 2\text{k}\Omega$ ,  $R_3 = 8\text{k}\Omega$  and the MOSFET has threshold  $V_T = 0.5\text{V}$ ,  $\frac{1}{2}\mu C_{OX} = 0.2\text{mA/V}^2$  and  $\frac{\gamma}{\alpha} = \frac{2}{3}$ .


- Derive the bias point of the circuit. Considering an operating frequency  $f_0 = 3.3\text{GHz}$  and  $C_3 = 30\text{pF}$ , size  $R_4$ ,  $C_2$  and  $\left(\frac{W}{L}\right)$  of the transistor to guarantee: (i) input matching, (ii) maximum gain and (iii) noise figure of 2.7dB.
- Please modify the circuit by connecting  $C_2$  between the output node and gate of the transistor. Find the new values for  $C_2$ ,  $C_3$  and  $\left(\frac{W}{L}\right)$  to obtain a noise figure of 1.2dB at  $f_0 = 3.3\text{GHz}$ , while still guaranteeing input matching.
- Evaluate the “transducer power gain” of the stage in dB.



[Sol. a)  $(W/L) = 100$ ,  $C_2 = 2.33\text{pF}$ ,  $R_4 = 1024\Omega$ ; b)  $(W/L) = 434$ ,  $C_2 = 2.4\text{pF}$ ,  $C_3 = 89.6\text{pF}$ ; c)  $G_p = 13\text{dB}$ ]


**T10.2** Let us consider the LNA in figure, where  $C = 1\text{nF}$  and the MOSFETs have threshold  $V_T = 0.5\text{V}$ ,  $\frac{1}{2}\mu C_{OX} = 0.1\text{mA/V}^2$  and  $\frac{\gamma}{\alpha} = 2$ .

- Neglecting the unknown component (marked by the “?” sign), and assuming the transformer to be ideal, size  $\left(\frac{W}{L}\right)_1$  to obtain input matching to  $50\Omega$  at  $f_0 = 2.5\text{GHz}$ .
- Evaluate the noise figure NF referred to a source resistance of  $50\Omega$ , at  $f_0 = 2.5\text{GHz}$  and considering all noise sources.
- Assuming the transformer to be non-ideal with coupling coefficient  $k = 1$ , and  $L_{11} = 1\text{nH}$ ,  $L_{22} = 9\text{nH}$  the inductances of the primary and secondary winding, respectively. Choose the unknown component (marked by the “?” sign) which maintains input matching to  $50\Omega$ ?

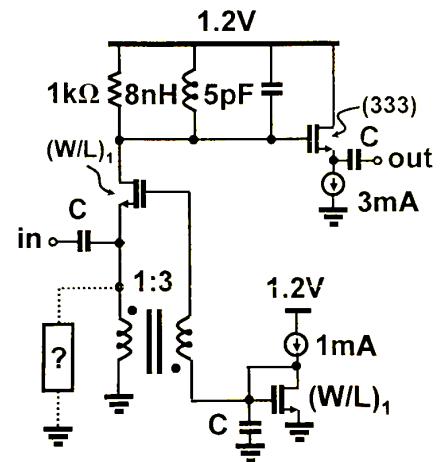

[Sol. a)  $g_{m1} = 5\text{mS}$ ,  $(W/L)_1 = 62.5$ ; b)  $\text{NF} = 2.35\text{dB}$ ; c)  $C_2 = 4\text{pF}$ ]

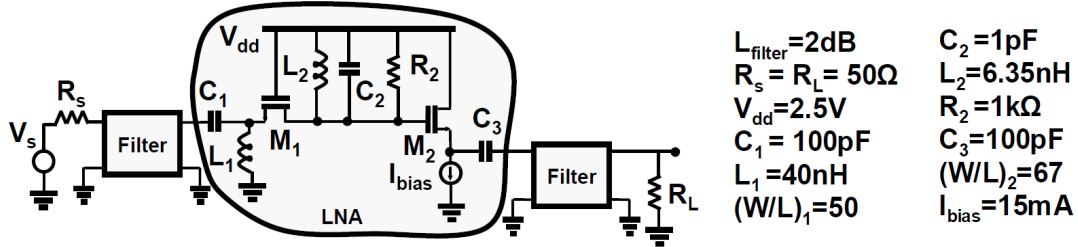- 9.3. Let us consider the circuit in figure, where the MOSFETs have threshold  $V_T = 0.5V$ ,  $\frac{1}{2}\mu C_{OX} = 0.1mA/V^2$ ,  $\frac{\gamma}{\alpha} = \frac{2}{3}$ .



- Derive the bias point of the circuit. Evaluate “available power gain”  $G_A$  and noise figure  $NF_{\text{LNA}}$  for the LNA section.
- Calculate the power delivered to the load  $R_L$ , assuming: (i) input available power  $P_s = -90\text{dBm}$ , (ii) available power loss of the filters  $L = 2\text{dB}$  at  $2\text{GHz}$ , and (iii)  $50\Omega$  input and output impedance of the filters at  $2\text{GHz}$ .
- Compute the overall  $NF_{\text{TOT}}$  at  $2\text{GHz}$ .

[Sol. a)  $g_{m1} = 20\text{mS}$ ,  $g_{m2} = 20\text{mS}$ ,  $G_A = 20\text{dB}$ ,  $NF_{\text{LNA}} = 2.72\text{dB}$ ; b)  $P_{\text{out}} = -74\text{dBm}$ ; c)  $NF_{\text{TOT}} = 4.74\text{dB}$ ]