


RF Circuit Design

L13




Variants in Oscillator topologies


①

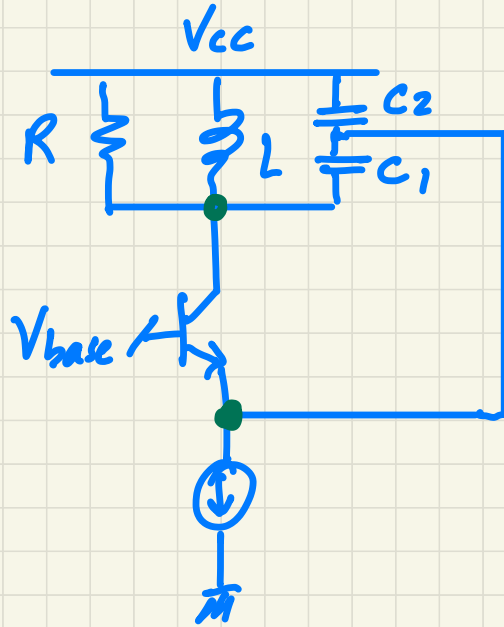

Colpitts Oscillator


small
signal

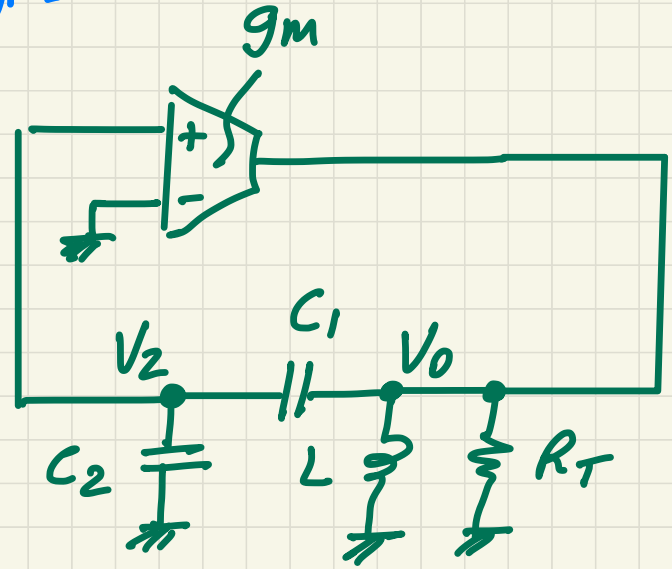

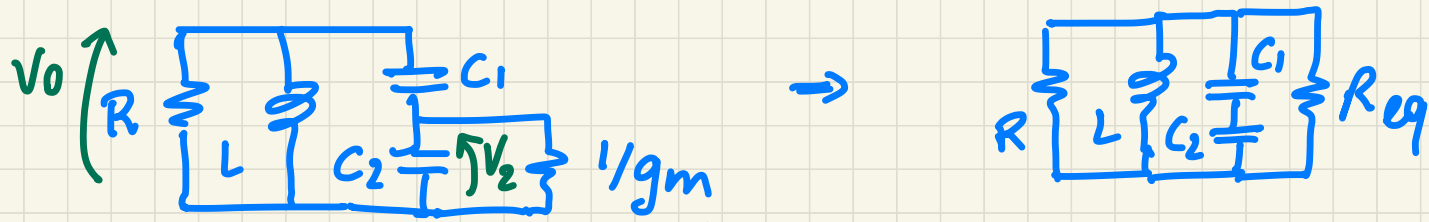

Hyp. low-loss approx. $\underbrace{\frac{1}{g_m} \gg \frac{1}{\omega_0 C_2}}_{Q_c \gg 1} : V_2 \approx \underbrace{\frac{C_1}{C_1 + C_2}}_{n < 1} \cdot V_0$

$$\Rightarrow R_{eq} \approx \frac{1}{g_m} \cdot \frac{1}{\left| \frac{V_2}{V_0} \right|^2} = \frac{1}{n^2 \cdot g_m}$$

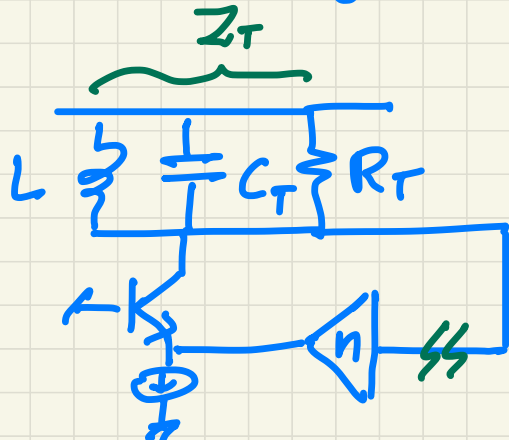

$$R_T = R \parallel R_{eq} = R \parallel \frac{1}{n^2 g_m}$$

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

$$LG(s) = n \cdot g_m \cdot Z_T(s)$$

Oscillation condition (small-signal) :

$$LG(j\omega_0) = 1 \quad \Leftrightarrow$$


$$\begin{cases} g_m R_T n = 1 \\ \omega_0 = \frac{1}{\sqrt{LC_T}} \end{cases}$$

$$\frac{R \cdot \frac{1}{n^2 g_m}}{R + \frac{1}{n^2 g_m}}$$


$$\Leftrightarrow g_m R = \frac{1}{n(1-n)}$$

equivalent to the general case where $m = 1/n$

②

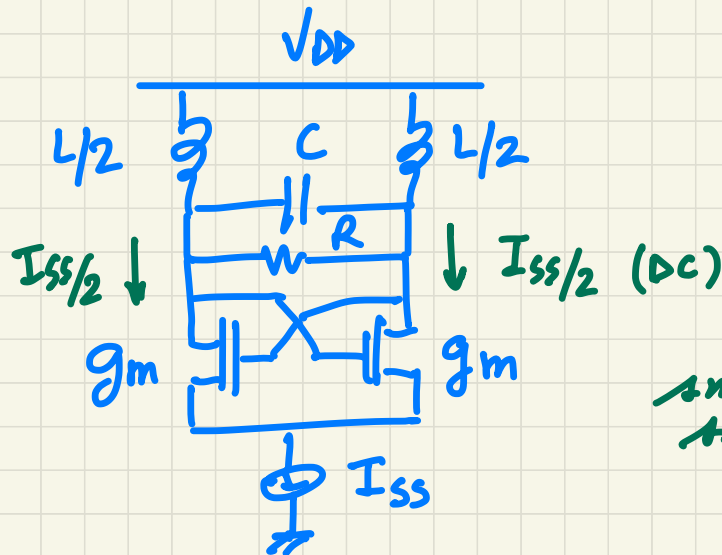


small-signal

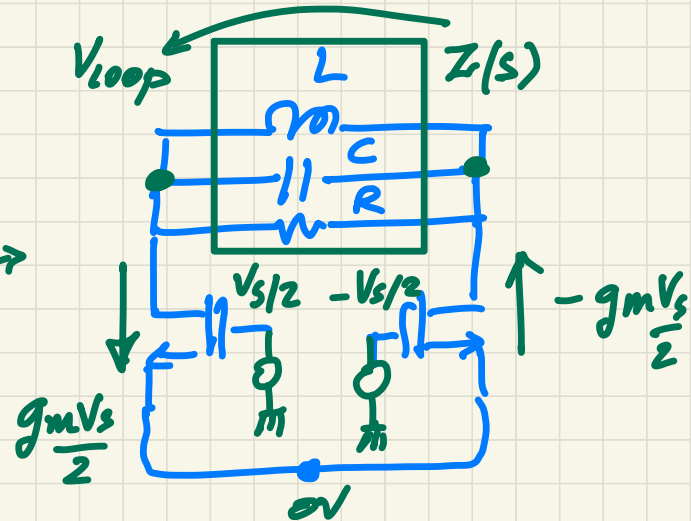


$$\begin{aligned} \Rightarrow LG(s) &= \frac{V_{loop}}{V_s} = \frac{g_m v_{s/2} \cdot Z(s)}{V_s} = \\ &= \underbrace{\frac{g_m}{2}}_{G_{nu}} \cdot Z(s) \end{aligned}$$

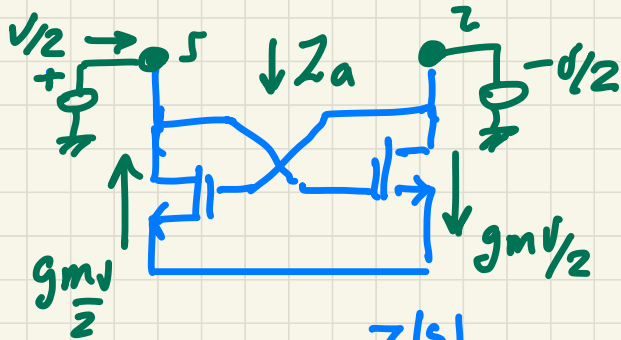Oscillation condition: $LG(j\omega_0) = 1 \Rightarrow \begin{cases} \omega_0 = \frac{1}{\sqrt{LC}} \\ \underline{\frac{g_m}{2} R = 1} \end{cases}$



alternative:
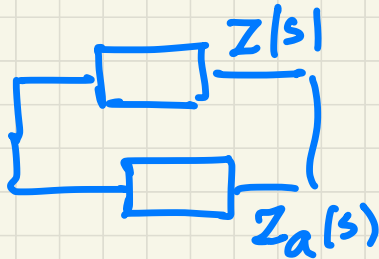
$$Z_a(s) = \frac{v}{-g_m \frac{v}{2}} = -\frac{2}{g_m}$$



Oscillation condition $-Z_a(s) = Z(s)$

$$\Leftrightarrow \underline{+\frac{2}{g_m} = R} \text{ and } \omega_0 = \frac{1}{\sqrt{LC}}$$

Large signal

Hyp: assuming full switching
(hard limiting $I(V)$)

$$A_0 \gg \sqrt{2} \cdot V_{ov}$$

assuming MOSFET in sat. when on

Oscillation condition

$$|G_{mh}| \cdot R = 1$$

$$G_{mh} = \frac{\overline{I_1}}{\overline{V_1}} = \frac{\frac{2}{\pi} \cdot I_{SS}}{A_0}$$


First harmonic
of $I(t)$



First harmonic
of $V(t)$



$$A_0 = \frac{2}{\pi} \cdot I_{SS} \cdot R$$

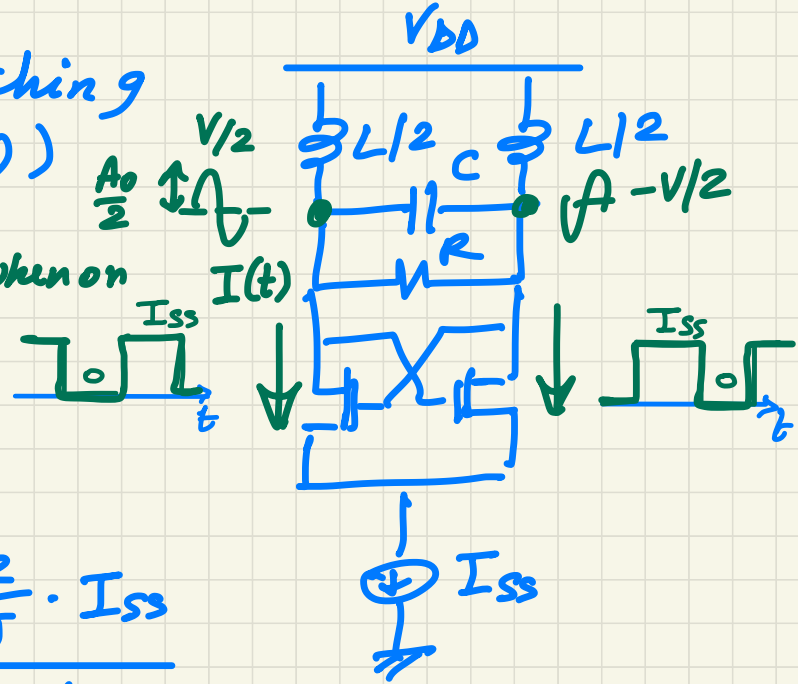
also valid if MOSFET are
in triode when on



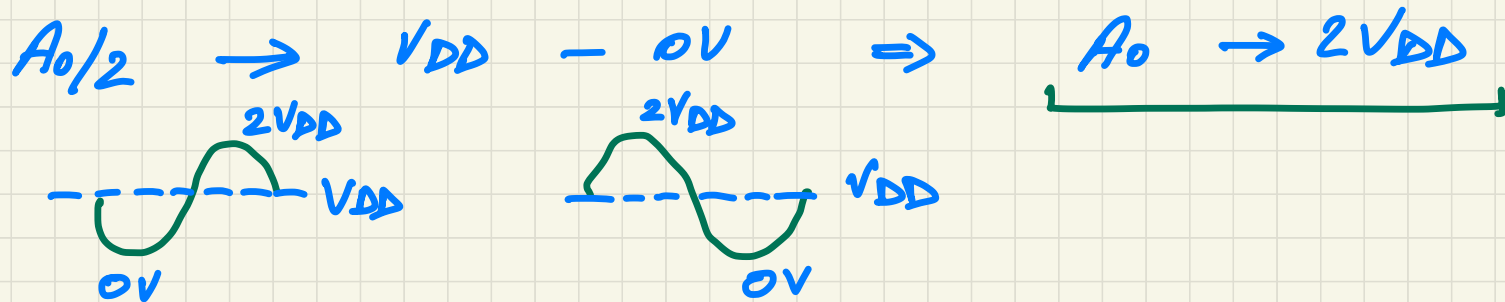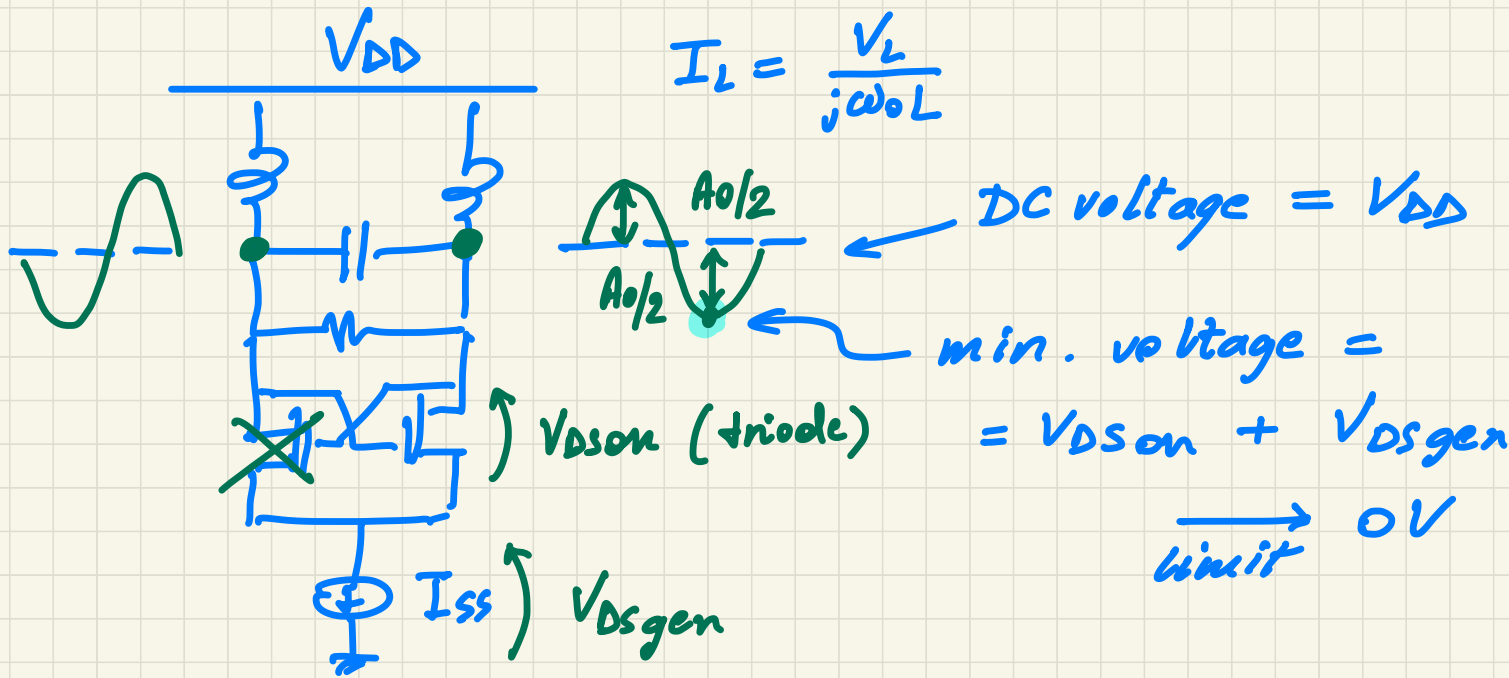

Frequency Stability

φ is an extra delay
in the loop

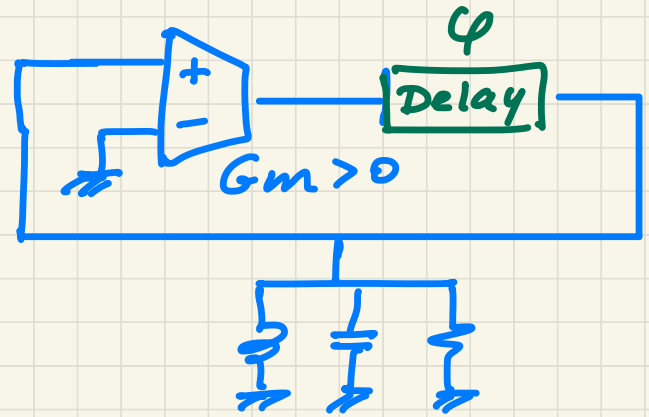

Oscillation condition :

$$\angle LG(j\omega_0) = 0$$


\Downarrow

$$-\varphi + \angle Z(j\omega_0) = 0$$


$$-\varphi + \frac{\pi}{2} - \arctan \left\{ \frac{\omega_0 \omega_z / Q}{\omega_z^2 - \omega_0^2} \right\} = 0 ;$$

$$\arctan \left\{ \frac{\omega_z^2 - \omega_0^2}{\omega_0 \omega_z / Q} \right\} = \varphi$$
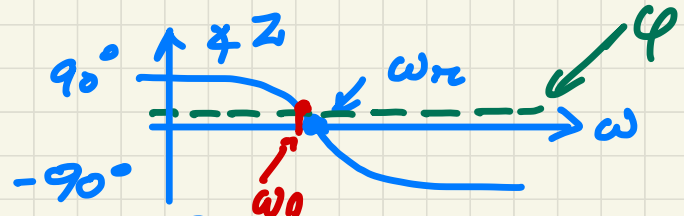
$$LG(j\omega) = G_m e^{-j\varphi} \cdot Z(j\omega)$$


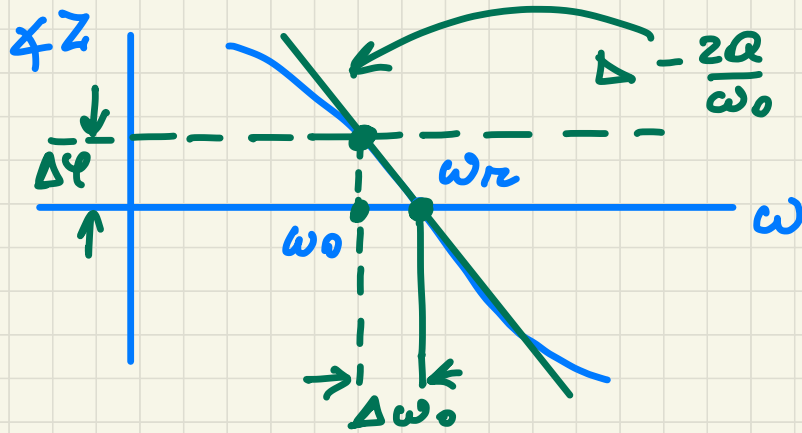
$$\frac{\pi}{2} - \arctan\{x\} = \arctan\left\{\frac{1}{x}\right\}$$



$$\frac{d}{dx} \arctan(x) = \frac{1}{1+x^2}$$

$$\Delta Z = \arctan \underbrace{\frac{\omega_r^2 - \omega_0^2}{\omega_0 \omega_r Q}}_x$$

$$\begin{aligned} \Delta \omega_0 &\approx \frac{\Delta \varphi}{\left. \frac{d \Delta Z}{d \omega_0} \right|_{\omega_0 = \omega_r}} = \Delta \varphi \cdot \frac{1}{\left. \frac{1}{1 + \left(\underbrace{Q \cdot \frac{\omega_r^2 - \omega_0^2}{\omega_0 \omega_r}}_x \right)^2} \cdot \frac{Q}{\omega_r} \cdot \frac{-2\omega_0^2 - (\omega_r^2 - \omega_0^2)}{\omega_0^2} \right|_{\omega_0 = \omega_r}} \\ &= \frac{\Delta \varphi}{-2Q/\omega_0} \end{aligned}$$

$$\Rightarrow \frac{\Delta \omega_0}{\omega_0} = - \frac{\Delta \varphi}{2Q}$$

Relative frequency variation induced by an extra delay φ is INVERSELY PROPORTIONAL TO Q


$$\text{Frequency stability Factor} \triangleq \frac{\Delta \omega_0 / \omega_0}{\Delta \varphi} = - \frac{1}{2Q}$$

for the basic LC oscillator.


Exercise : Compute frequency stability factor for a ring oscillator ?


Voltage - Controlled Oscillators (VCOs)

→ use of variable capacitors (VARACTORS)

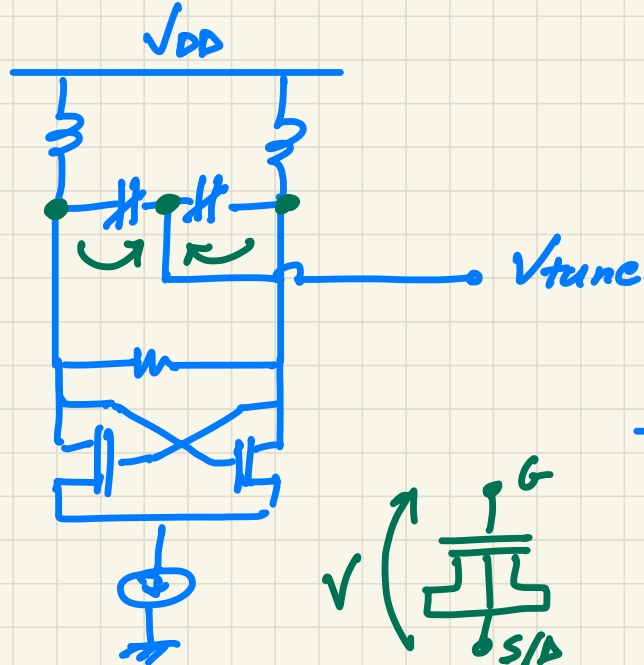

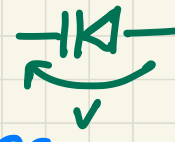

2 main options:


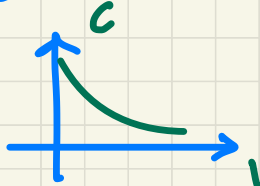
a) pn junction  in reverse biasing



$$C = \frac{C_{j0}}{\left(1 + \frac{V}{V_{j0}}\right)^m}$$

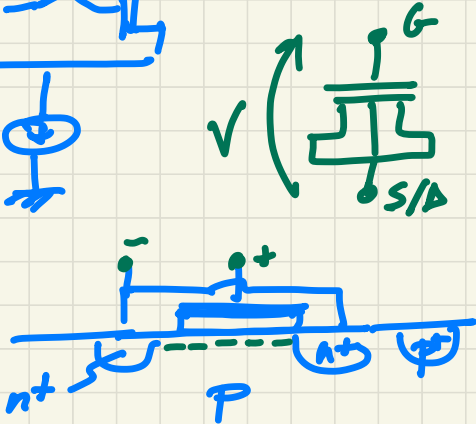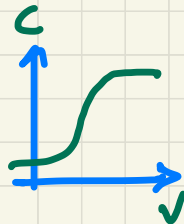
b) MOS junctions

- 1 - from inversion - to depletion  
- 2 - from accumulation to depletion




Phase Noise 2 mechanisms :

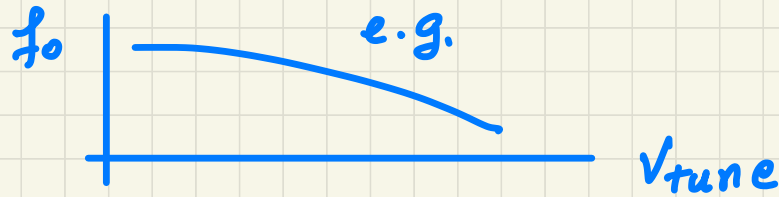- Indirect : AM-to-FM conversion :
upconversion of low-frequency noise



$$K_{VCO} = 2\pi \cdot \frac{\partial f_0}{\partial V_{tune}}$$

VCO sensitivity or gain

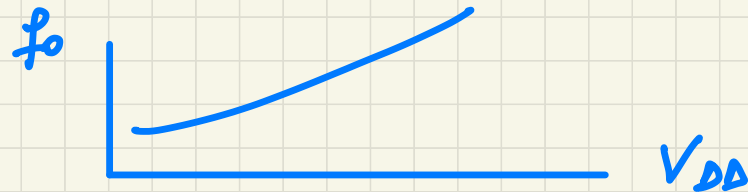

$$K_{VDD} = 2\pi \frac{\partial f_0}{\partial V_{DD}}$$

VCO supply pushing

Low frequency noise in

V_{tune} PSD $S_{V_{tune}}(\omega)$

$$\Rightarrow_{FM} S_{\omega_0}(\omega) = K_{VCO}^2 \cdot S_{V_{tune}}(\omega) \Rightarrow_{PM} S_{\phi}(\omega) = \frac{K_{VCO}^2 S_{V_{tune}}}{\omega^2}$$