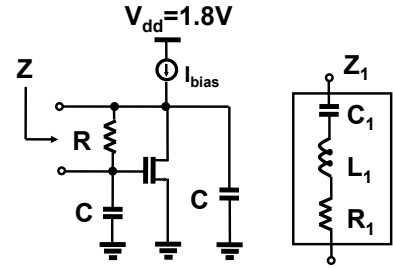


## Tutorial T7

**T7.1** Let us consider the crystal oscillator in figure, where  $L_1 = 4.4$  mH,  $C_1 = 3.6$  fF,  $R_1 = 30$   $\Omega$ ,  $C = 1$  pF,  $R \rightarrow \infty$ ,  $V_t = 0.5$  V,  $K = \frac{1}{2} \mu C_{OX} \left( \frac{W}{L} \right) = 2$   $\mu A/V^2$  and  $Z_1$  represents the equivalent impedance of an XTAL.


- Derive the expression for  $Z(\omega)$  as a function of the circuit parameters.
- Evaluate oscillation frequency when the XTAL is connected in parallel to the previously evaluated impedance.
- What is the minimum  $I_{bias}$  to guarantee start-up of the oscillation?



**[Sol. a)**  $Z(j\omega) = \frac{2}{j\omega C} - \frac{g_m}{\omega^2 C^2}$ ; **b)**  $f_{osc} = 40$  MHz; **c)**  $I_{bias} = 0.45$   $\mu A$ ]

**T7.2** Let us consider the oscillator in the figure, where  $V_{dd} = V_{ss} = 1.25$  V,  $V_t = 0.5$  V,  $K = \frac{1}{2} \mu C_{OX} \left( \frac{W}{L} \right) = 10$  mA/V<sup>2</sup>,  $L = 4$  nH,  $C_1 = 0.5$  pF,  $C_2 = 0.5$  pF,  $R_1 = 1$  k $\Omega$ ,  $R_2 = 2$  k $\Omega$  and  $I_{bias} = 3$  mA.

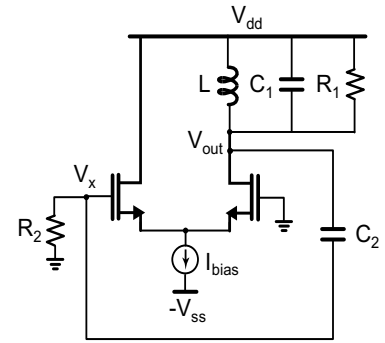
- Making the necessary simplifications, derive the oscillation frequency and check the start-up condition.
- Assuming full-switching of the differential stage, evaluate the oscillation amplitude at the output node,  $V_{out}$ .
- Plot  $V_{out}$  and  $V_x$  over one period and check the operating region of the transistors.



**[Sol. a)**  $f_{osc} = 3.56$  GHz,  $|LG(f_{osc})| = g_m(R_1 || R_2)/2 = 2.58 > 1$ ; **b)**  $|V_{out}| = 1.27$  V; **c)**  $V_{out} = 1.25$  V +  $1.27$  V  $\cdot \cos(\omega_{osc} t)$ ,  $V_x = 1.27$  V  $\cdot \cos(\omega_{osc} t)$ ]

**T7.3** Let us consider the circuit in figure, where  $V_t = 0.5$  V,  $\frac{1}{2} \mu C_{OX} = 0.1$  mA/V<sup>2</sup> and  $\gamma/\alpha = 2/3$ .

- Evaluate the resonant frequency of the differential load and find the values of  $(W/L)_1$  and  $(W/L)_2$  to obtain: (i) differential gain at resonance  $(V_{out}^+ - V_{out}^-)/(V_{in}^+ - V_{in}^-)$  equal to 5 dB and (ii) a -3 dB bandwidth of the gain equal to 270 MHz.
- Considering both transistor and resistor noise, evaluate the output noise voltage spectral density at resonance.
- Is there any limit on the choice of  $(W/L)_2$ ? If so, explain why.

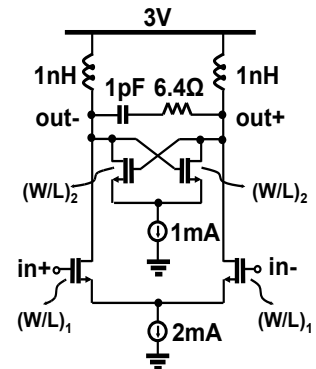

**[Sol. a)**  $f_0 = 3.56$  GHz,  $g_{m1} = 6$  mS,  $(W/L)_1 = 90$ ,  $g_{m2} = 2.9$  mS,  $(W/L)_2 = 41$ ; **b)**  $S_{V_{out}}^{(SSB)}(f_0) = (6.1 \text{ nV}/\sqrt{\text{Hz}})^2$ ; **c)**  $(W/L)_{2,max} = 205$ , to prevent oscillation.]