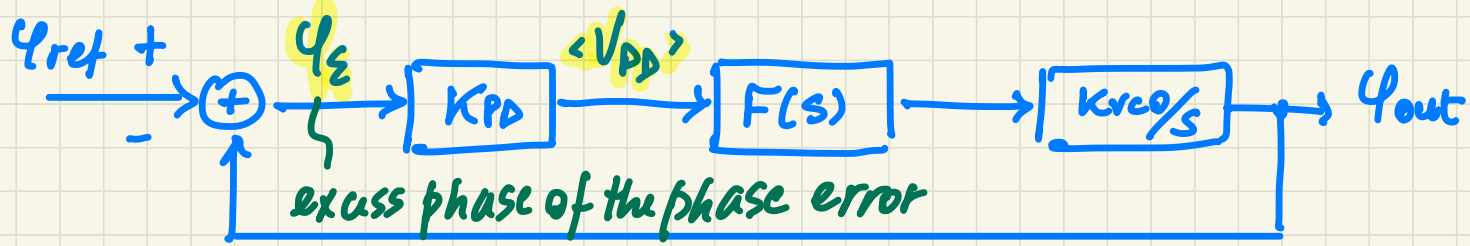


RF Circuit Design

T2







Linear "CT" equivalent model

$$F(s) = \frac{R + 1/sC}{R_1} =$$
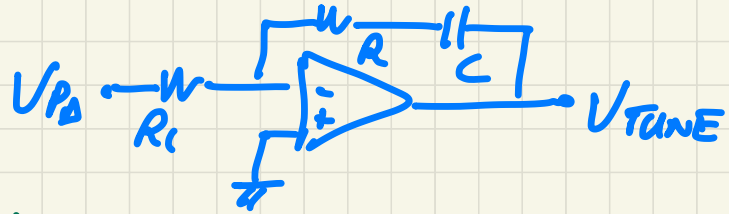
$$= \frac{1 + \underbrace{sRC}_{\tau_z}}{\underbrace{sR_1C}_{\tau_0}} = \frac{1 + \tau_z s}{\tau_0 s}$$




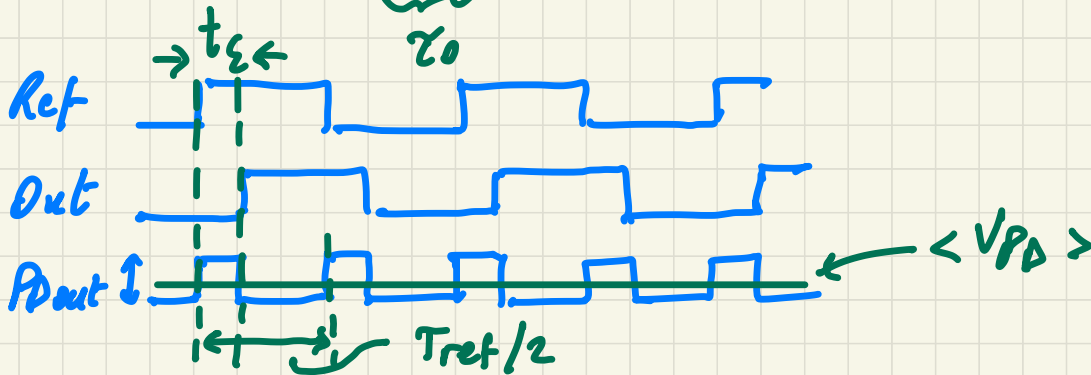
$$\varphi_\varepsilon = \omega_{ref} \cdot t_\varepsilon$$




Ref	Out	Pout
0	0	0
0	1	1
1	0	0
1	1	1
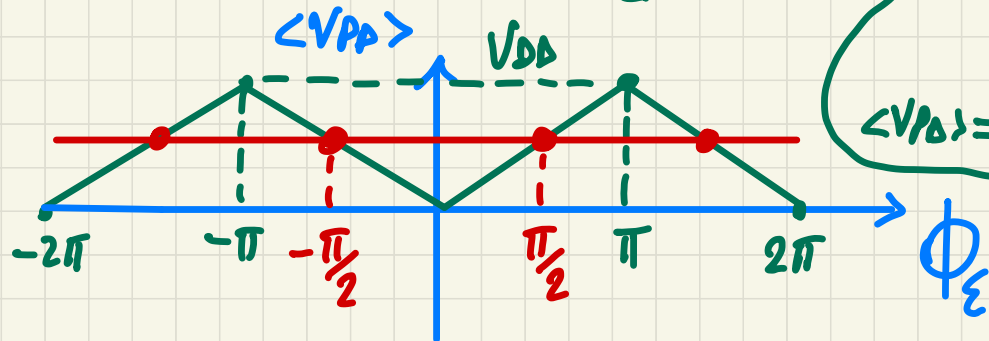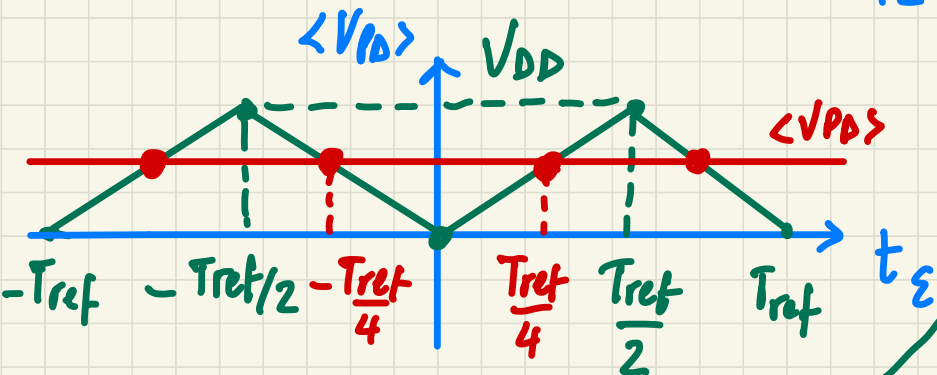
$$\langle V_{PD} \rangle = D \cdot V_{DD} = \frac{t_{\varepsilon}}{T_{ref}/2} \cdot V_{DD} = \frac{2}{T_{ref}} \cdot V_{DD} \cdot t_{\varepsilon}$$


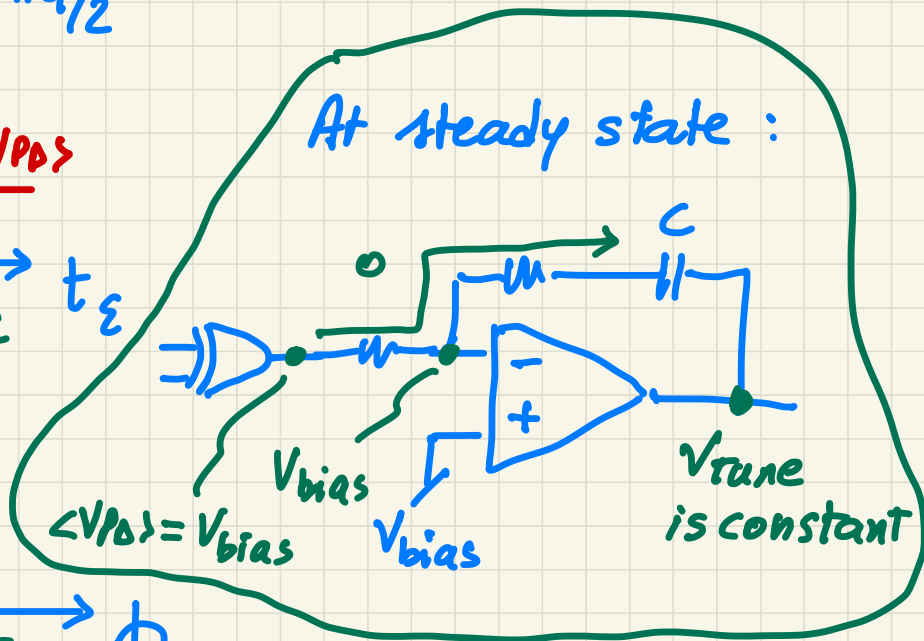
$$\Rightarrow K_{PD} = \frac{\langle V_{PD} \rangle}{\phi_{\varepsilon}} = \frac{V_{DD}}{\pi}$$



$$V_{bias} = V_{DD}/2$$


$$\Rightarrow \langle V_{PD} \rangle = V_{DD}/2$$

i. $I_{PD,max} = 1 \text{ mA}$

$V_{PD,max} = V_{DD}$


$I_{PD,max} = \frac{V_{DD} - V_{DD}/2}{R_1}$

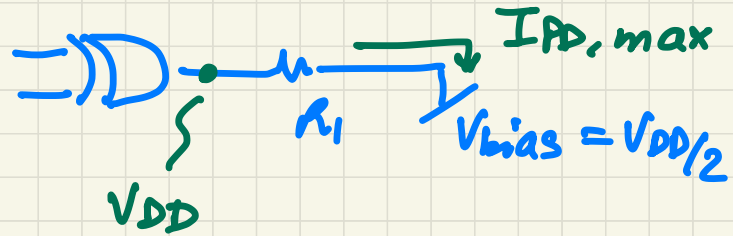$= 1 \text{ mA} ; R_1 = \frac{1.65 \text{ V}}{1 \text{ mA}} = 1.65 \text{ k}\Omega$



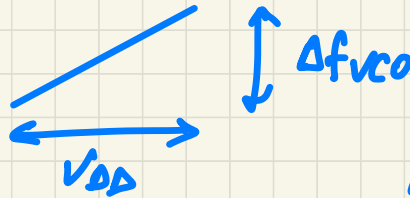ii. $\Delta f_{VCO} = 50 \text{ kHz}$

$K_{VCO} \triangleq \frac{\partial \omega_{out}}{\partial V_{TUNE}}$



$K_{VCO} = \frac{2\pi \cdot 50 \text{ K}}{3.3} = 95.2 \frac{\text{Krad}}{3.3 \text{ V}}$

iii. iv. $\varphi_m = 60 \text{ deg}$

$f_u = 1 \text{ kHz}$


$LG(s) = K_{PD} \frac{K_{VCO}}{s} F(s) = K_{PD} \cdot K_{VCO} \frac{1}{s} \cdot \frac{1 + s\tau_z}{s\tau_o}$

$\tau_z = RC \quad \tau_o = R_i C$

" TYPE-II PLL "

- $|LG(\omega_u)| = 1$;
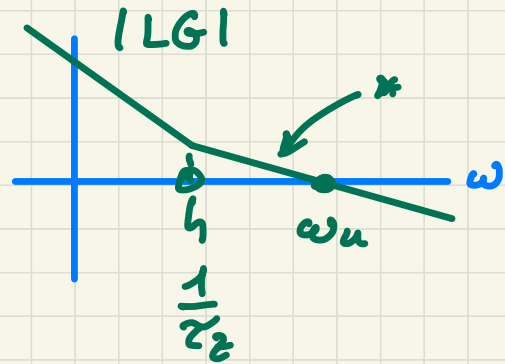
$$(1) \frac{K_{PD} \cdot K_{VCO}}{\omega_u^2 \cdot \tau_0} \cdot \sqrt{1 + \omega_u^2 \tau_z^2} = 1$$



* Asymptotic approx. $LG(j\omega) \approx \frac{K_{PD} K_{VCO}}{j\omega} \cdot \frac{\tau_z}{\tau_0}$

- $\varphi_m = \cancel{180^\circ} - \cancel{90^\circ} - \cancel{90^\circ} + \arctan\left(\frac{\omega_u}{\omega_z}\right) = 60^\circ$

$$(2) \omega_z = \frac{\omega_u}{\tan(60)} = \frac{\omega_u}{\sqrt{3}}$$

$$\tau_z = RC$$

$$\omega_z = \frac{1}{\tau_z}$$

$$(1) \tau_0 = \frac{K_{PD} K_{VCO}}{\omega_u^2} \cdot \sqrt{1 + \frac{\omega_u^2}{\omega_z^2} \cdot 3} = \frac{K_{PD} K_{VCO}}{\omega_u^2} \cdot 2 =$$

$$= \frac{\cancel{V_{DD}}}{\pi} \cdot \frac{\cancel{2\pi} \cdot \cancel{\Delta f_{VCO}}}{\cancel{V_{DD}}} \cdot \frac{2}{(2\pi \cdot 10^3)^2} = \frac{4 \cdot 50 \text{ k}}{(2\pi)^2 \cdot 10^6} = 5.07 \text{ ms}$$

$$C = \frac{\tau_0}{R_1} = \frac{5.07 \text{ ms}}{1.65 \text{ k}\Omega} = 3.07 \mu\text{F} \quad (\text{with asymptotic approx. } 2.66 \mu\text{F})$$



$$R = \frac{\tau_z}{C} = \frac{1}{\frac{\omega_z}{\sqrt{3}} \cdot C} = \frac{\sqrt{3}}{2\pi \cdot 10^3 \cdot 3.07 \cdot 10^{-6}} = 89.8 \Omega$$


(with asymptotic approx. 103.7Ω)

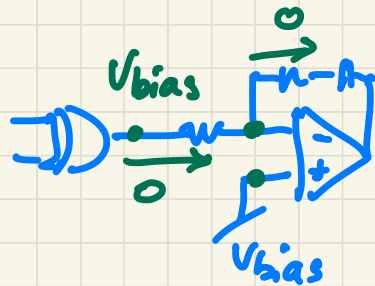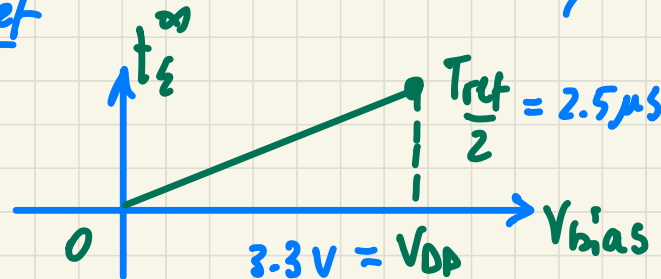b) Static time error t_ε vs. V_{bias}

$$\langle V_{PD} \rangle = V_{DD} \cdot \frac{t_\varepsilon}{T_{ref}/2} = V_{\text{bias}} \quad \text{at steady state}$$

$$t_\varepsilon^\infty = \frac{V_{\text{bias}}}{V_{DD}} \cdot \frac{T_{ref}}{2}$$




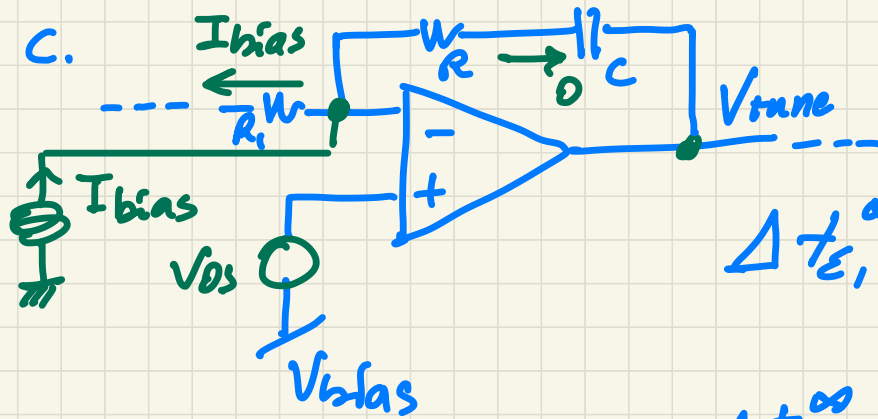

$$t_E^\infty = ?$$


$$\Delta t_{E1}^\infty = \frac{V_{os}}{V_{DD}} \cdot \frac{T_{ref}}{2}$$
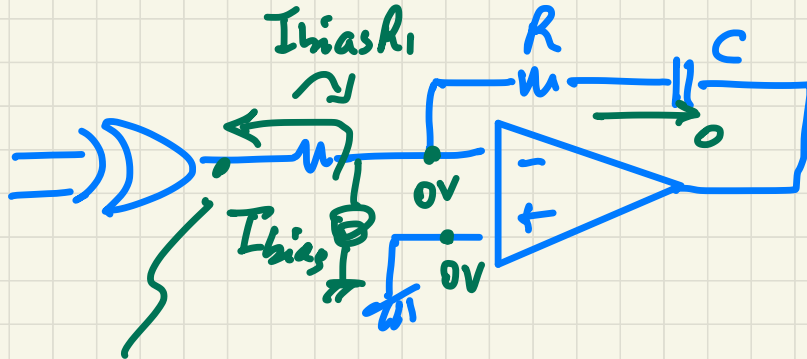
$$\Delta t_{E2}^\infty = \frac{-I_{bias} R_1}{V_{DD}} \cdot \frac{T_{ref}}{2}$$




$$\langle V_{pd} \rangle = -I_{bias} R_1$$


superposition principle

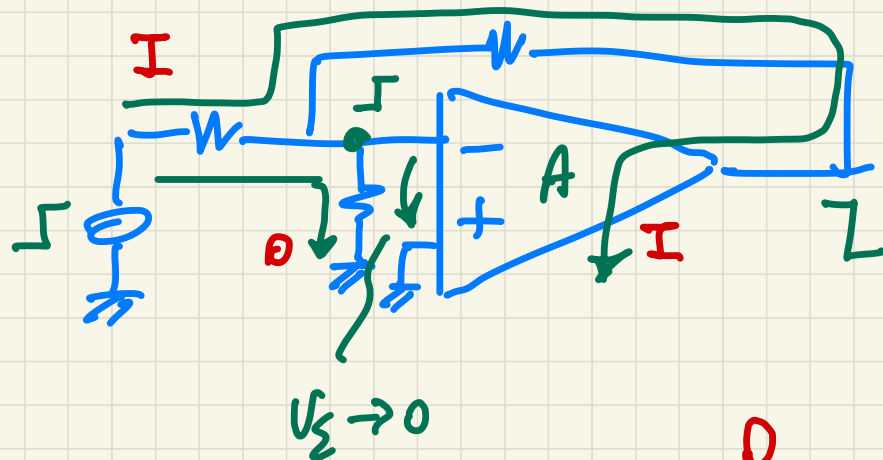

Feedback amplifier
analogy

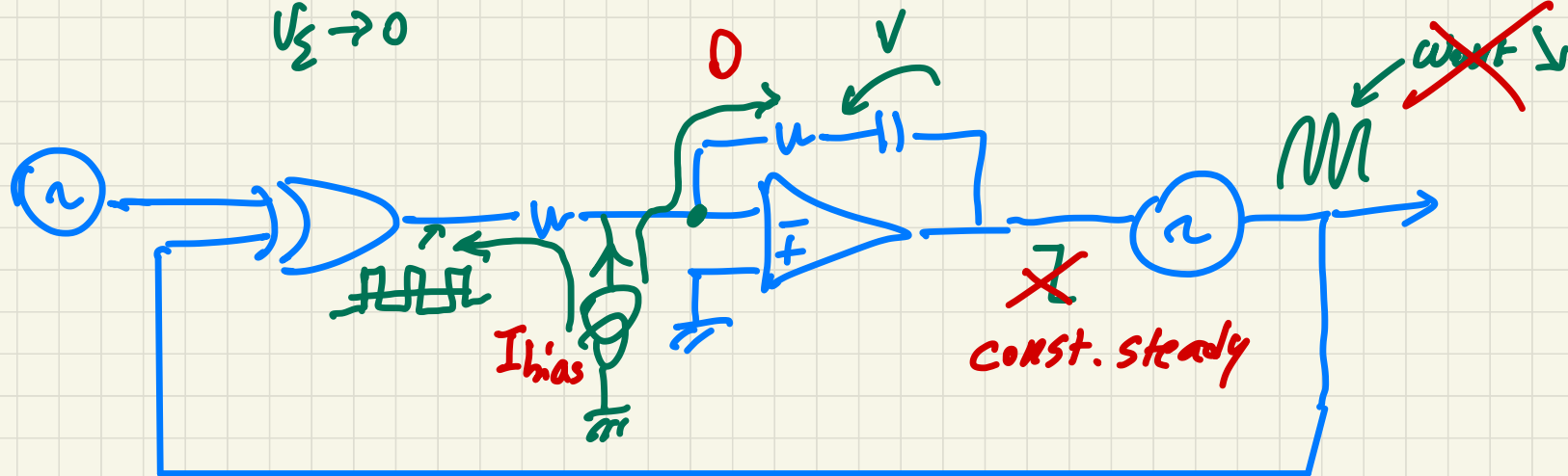


T.2.2

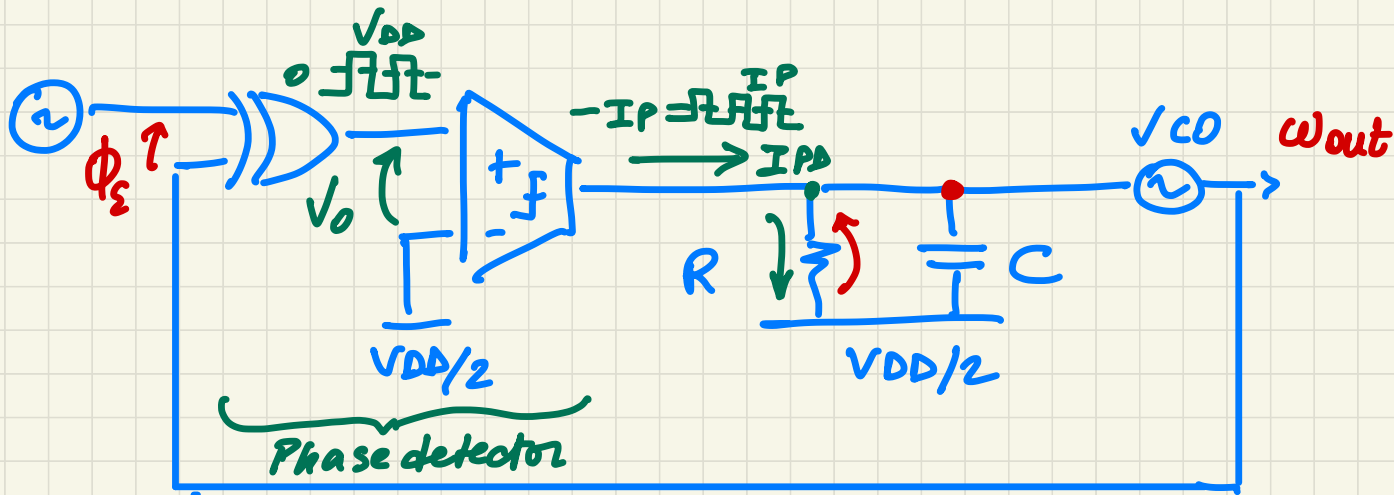



$$\left. \begin{array}{ll} V_o > 0 & I_{PD} = +I_P \\ V_o < 0 & I_{PD} = -I_P \end{array} \right\} \text{Charge pump}$$

• Equivalent model of PD :

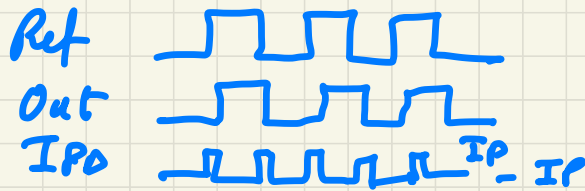
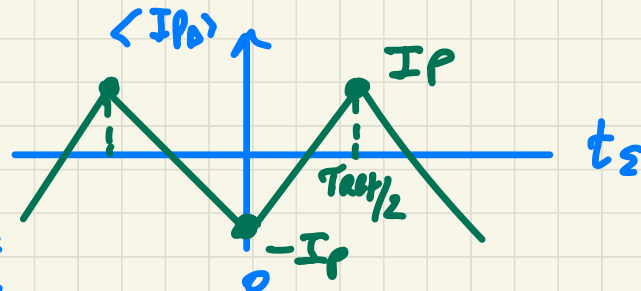
$$\begin{aligned} \langle I_{PD} \rangle &= 2I_P \cdot D = \\ &= 2I_P \cdot t_E / T_{REF/2} \end{aligned}$$




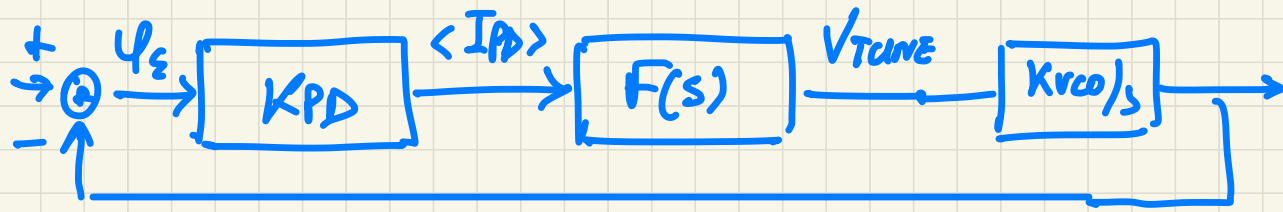


$$K_{PD} = \frac{\langle I_D \rangle}{\varphi_E} = \frac{2 I_P}{\pi}$$

$$\Leftarrow \langle I_D \rangle = 2 I_P \cdot \frac{\varphi_E}{\pi}$$
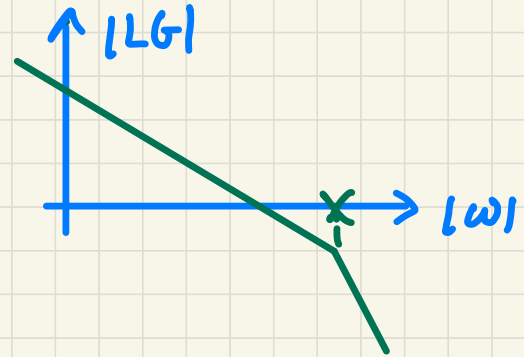
$$F(s) = R \parallel \frac{1}{sC} = \frac{R}{1 + sRC} = \frac{R}{1 + s \underbrace{RC}_{\tau_p}}$$



T2.3

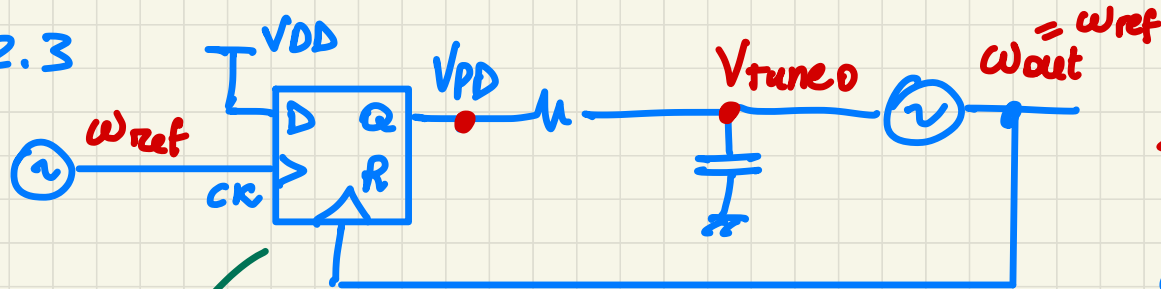

• Bias point
 $\langle V_{PD} \rangle = V_{tune0}$



• Equivalent model

D-type flip flop


CK \uparrow : $Q \rightarrow D = "1"$

R \uparrow : $Q \rightarrow "0"$

otherwise : Q is constant

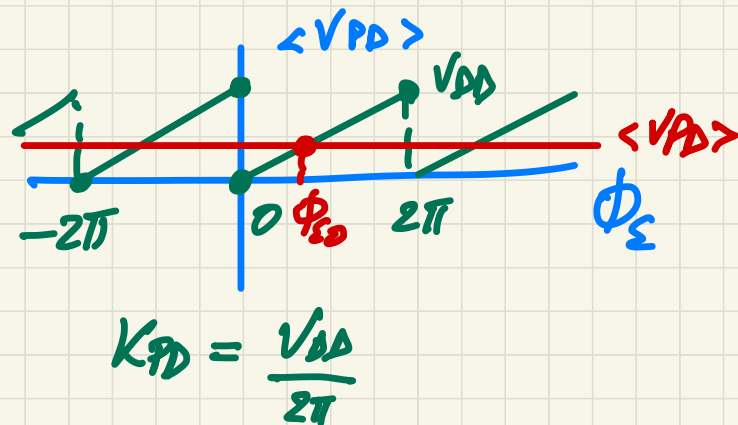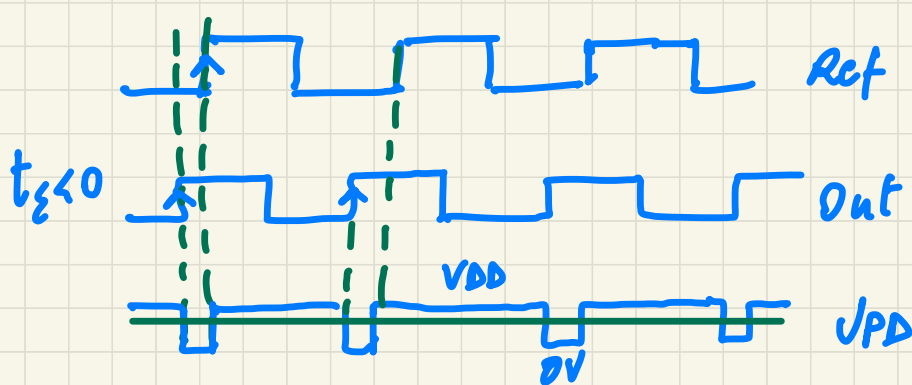


Integer-N PLLs

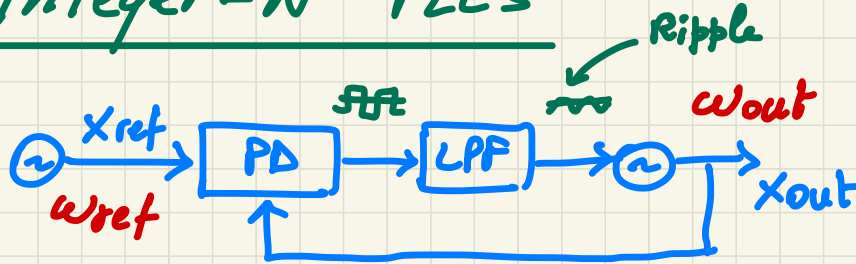


frequency follower


$\omega_{out} \rightarrow \omega_{ref}$

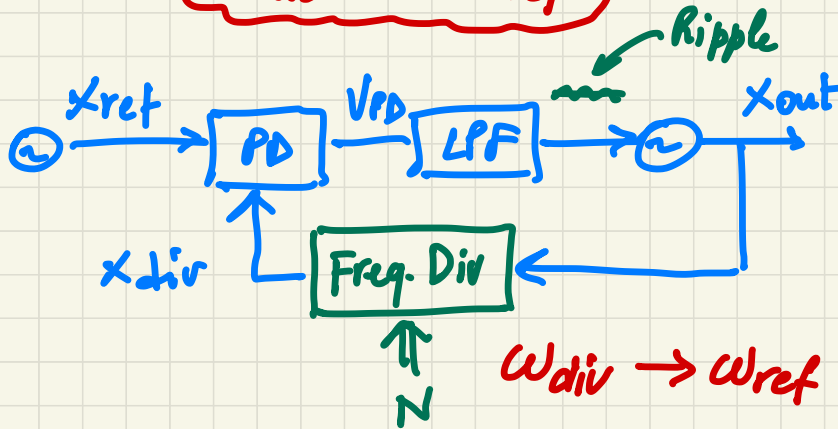

frequency multiplier

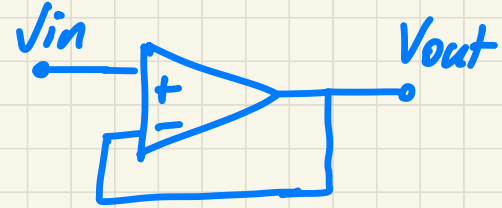



voltage follower

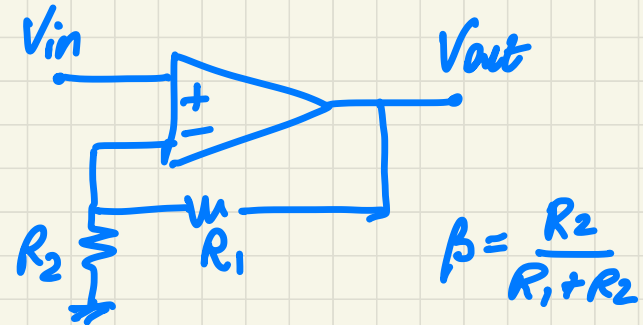


voltage amplifier

$$V_{out}/V_{in} = \frac{1}{\beta}$$


eg. Frequency divider by $N=2$

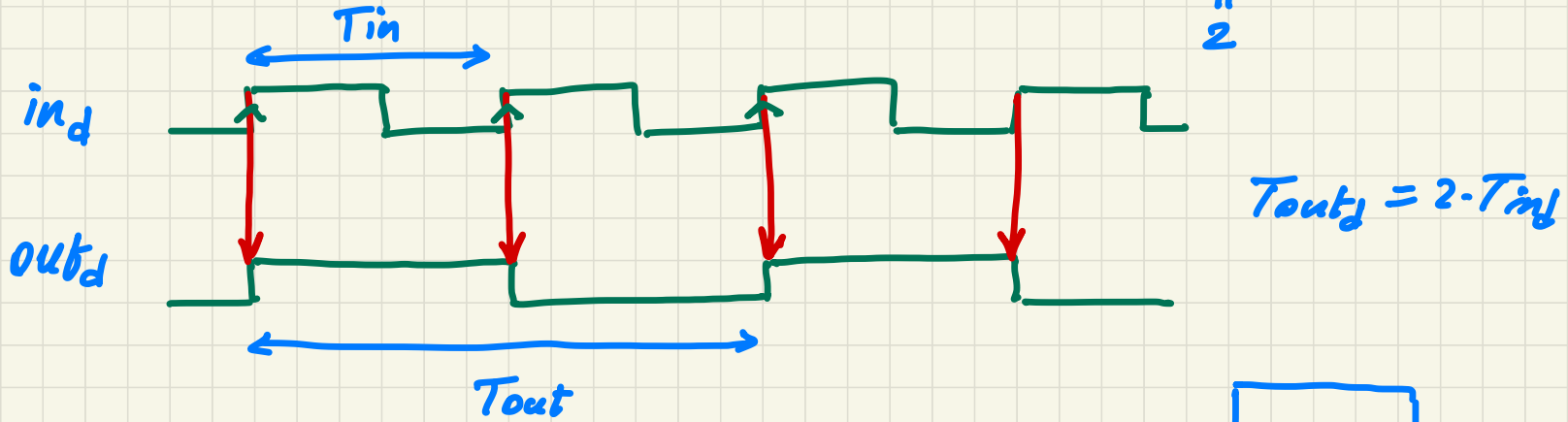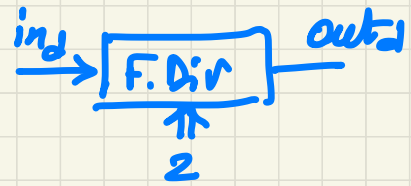

Module-2 counter (MSB output)

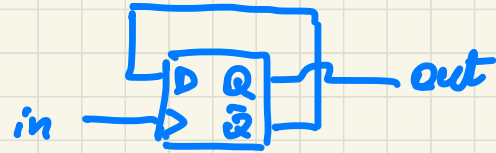

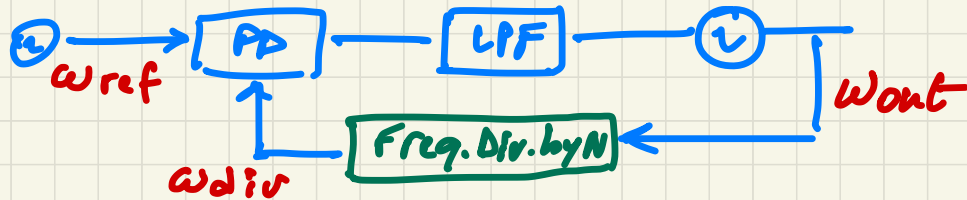
In gen. module N -counter as freq. div. by N



$$T_{div} = N \cdot T_{out}$$


$$\omega_{div} = \frac{\omega_{out}}{N} \Rightarrow \omega_{out} = N \omega_{div} \rightarrow \omega_{ref}$$

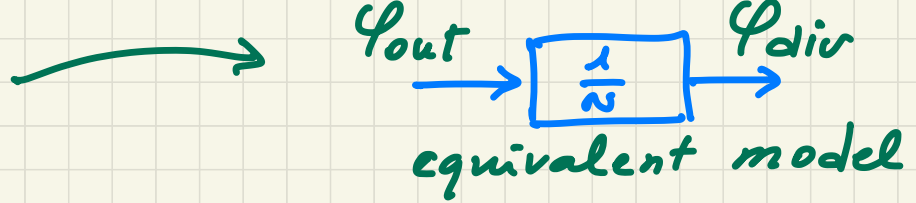- Equivalent model of the frequency divider



$$\omega_{div} = \frac{\omega_{out}}{N} \Rightarrow \phi_{div} = \frac{\phi_{out}}{N}$$


- Equivalent model of an integer- N PLL:

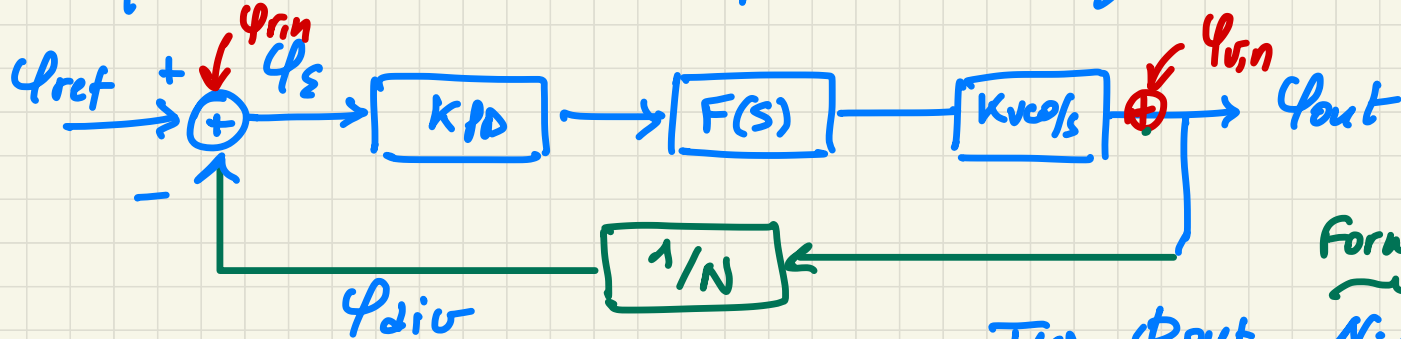

$$LG(s) = K_{PD} \cdot \frac{K_{VCO}}{s} \cdot F(s) \cdot \frac{1}{N}$$

Forward gain
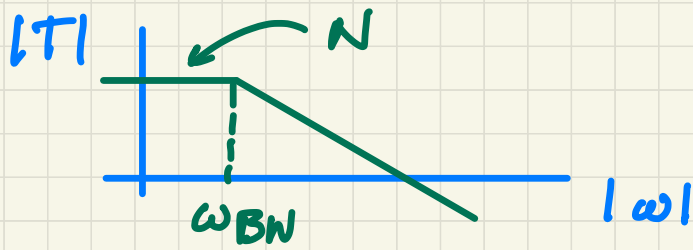
$$T(s) = \frac{\phi_{out}}{\phi_{ref}} = \frac{N \cdot LG(s)}{1 + LG(s)}$$




Int-N PLLs amplify the ref. phase noise by N^2 (within PLL BW)



Phase noise :




$$S_{\phi_{out}} = S_{\phi_{ref}} \cdot \underbrace{|T(f)|^2}_{(LPF) \ N^2 \text{ within } f_{BW}} + S_{\phi_{ref}} \cdot \underbrace{\left| \frac{1}{1 + LG(f)} \right|^2}_{(HPF) \text{ gain } 1 \text{ outside } f_{BW}}$$

Ripple and Reference Spur

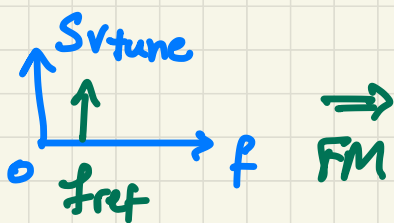

FM

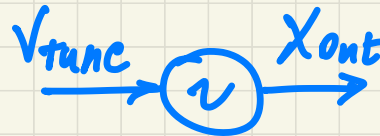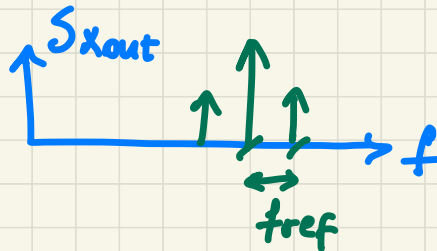

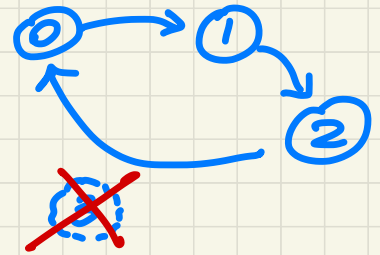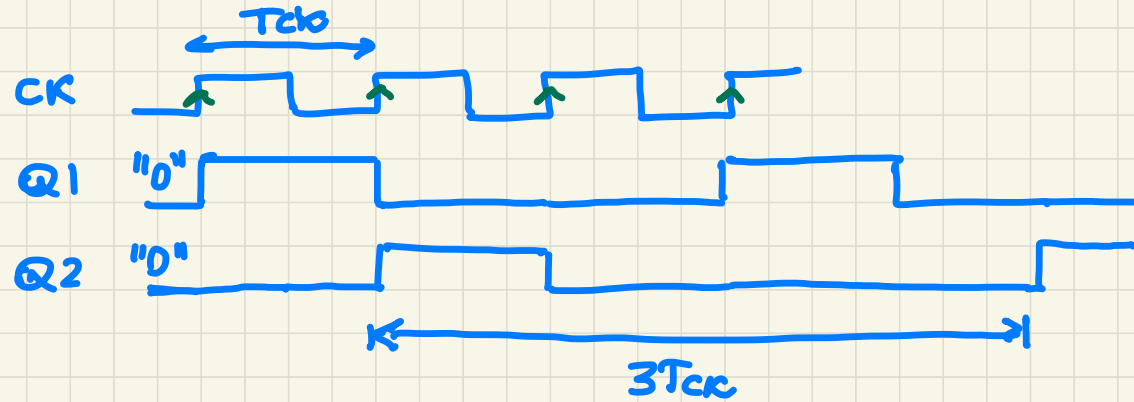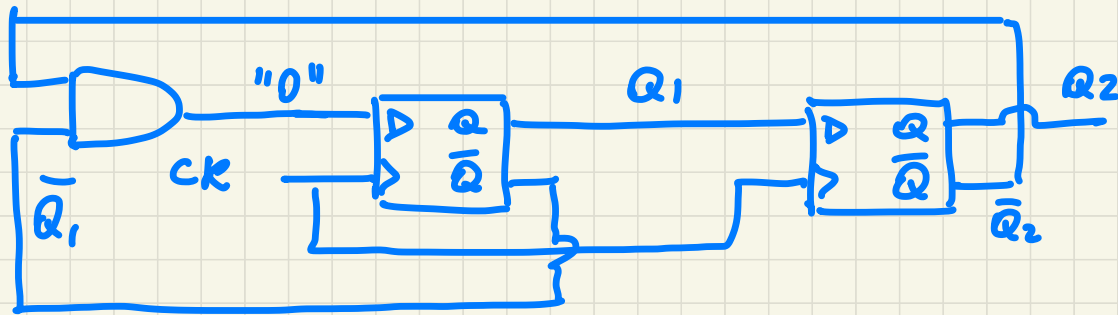

*Synchronous
Divider by 3*