

RF Circuit Design

L24


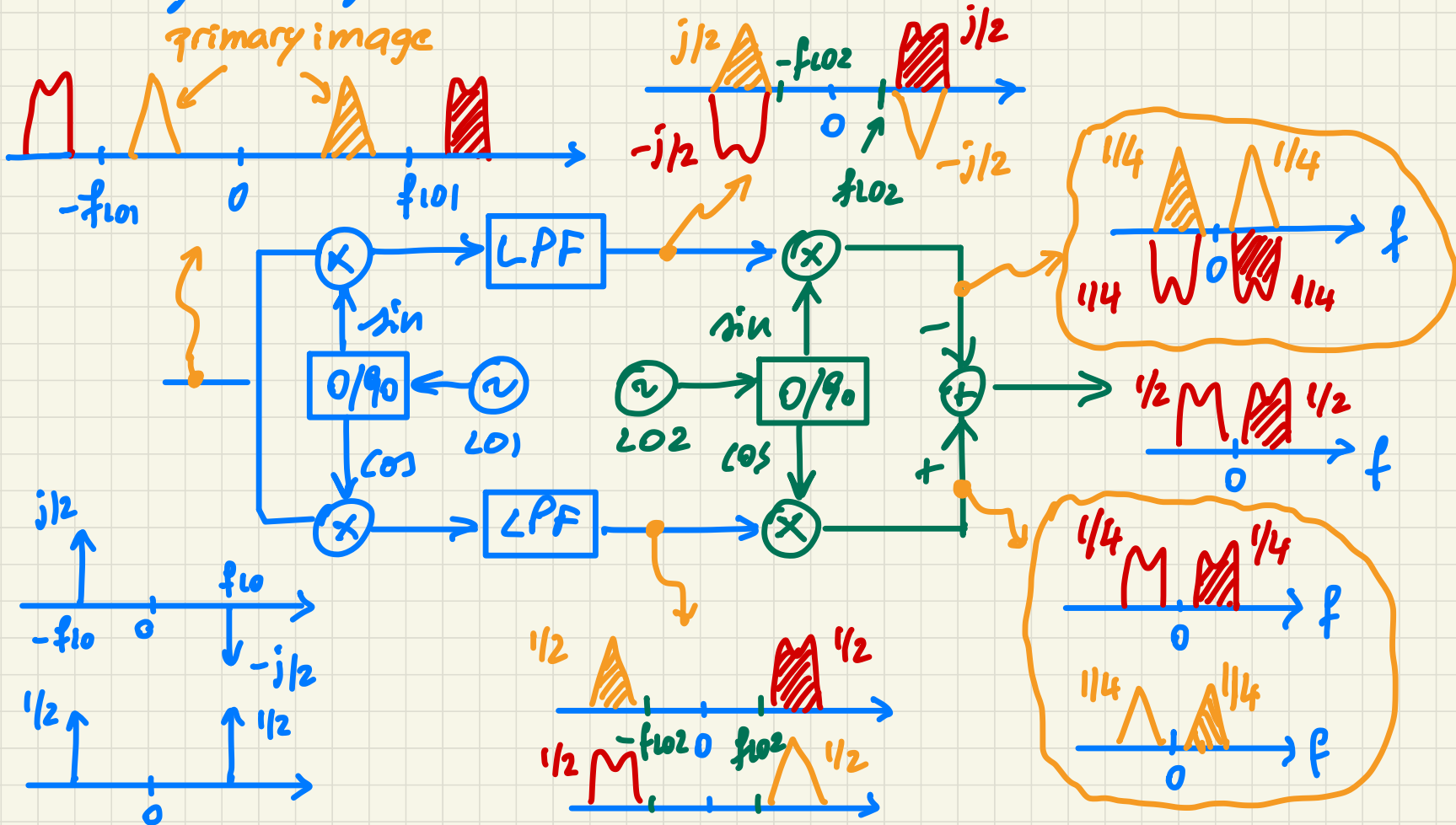
2020/21 



Image-reject Rx : Weaver architecture



Comparison of Hartley vs. Weaver arch.

- Hartley : phase shifter has limited BW
+ sensitive to RC absolute accuracy
⇒ limited IRR
phase shifter introduces thermal noise and power loss
- Weaver : problem of secondary image


Sol: $\pm 1R$ filter $\neq IF_2 = 0$

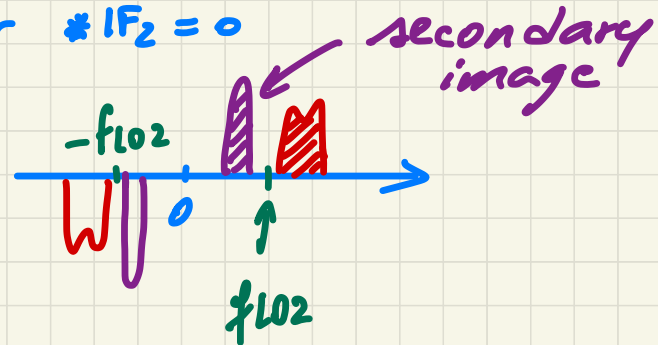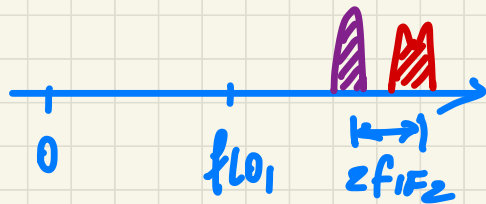

TRANSMITTER Architectures

ACPR : TX has to limit emissions

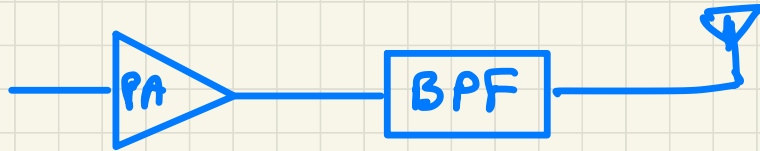↓
Linearity to avoid spectral regrowth
in non-constant
envelope modulations
Filter loss \leftrightarrow selectivity




$$L = \frac{P_{ANT}}{P_{PA}}$$

power loss degrades
efficiency of TX


e.g. $L = 2 \text{ dB}$

$$P_{ANT} = 1 \text{ W}$$
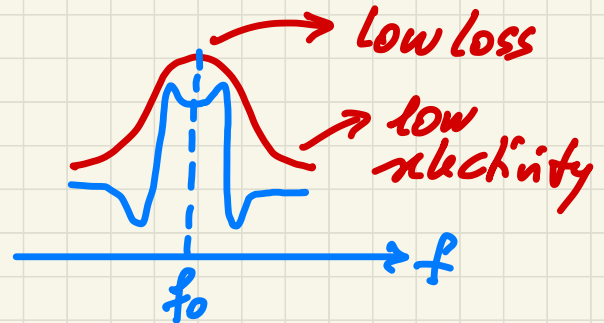
$$P_{diss} = 370 \text{ mW} \text{ (dissipated in the filter)}$$




• Direct-conversion TX

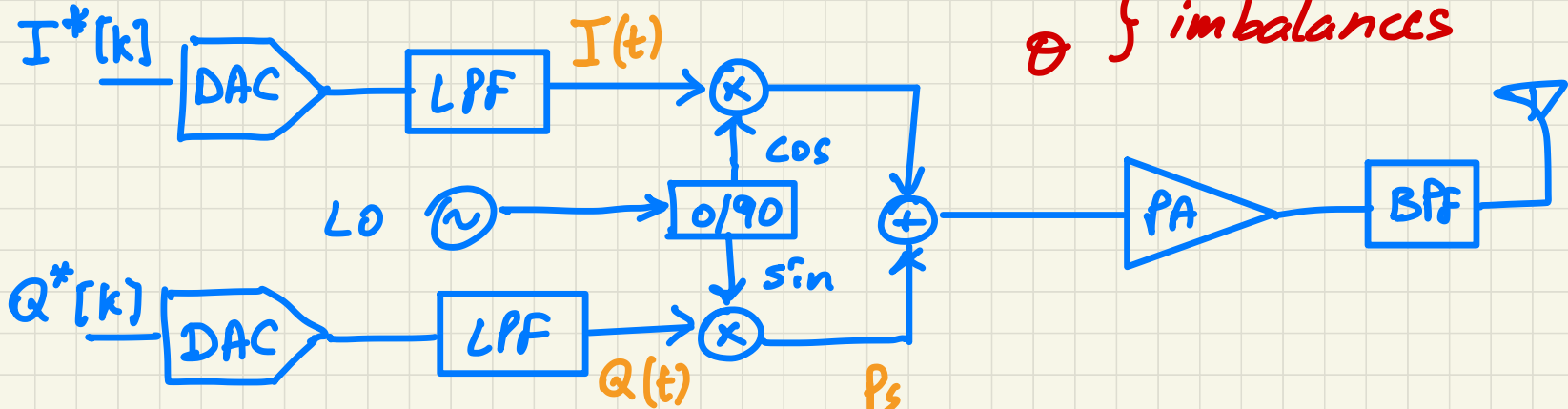

ϵ
 θ } imbalances



$$I(t) = \cos \omega_{bb} t$$

$$Q(t) = \sin \omega_{bb} t$$

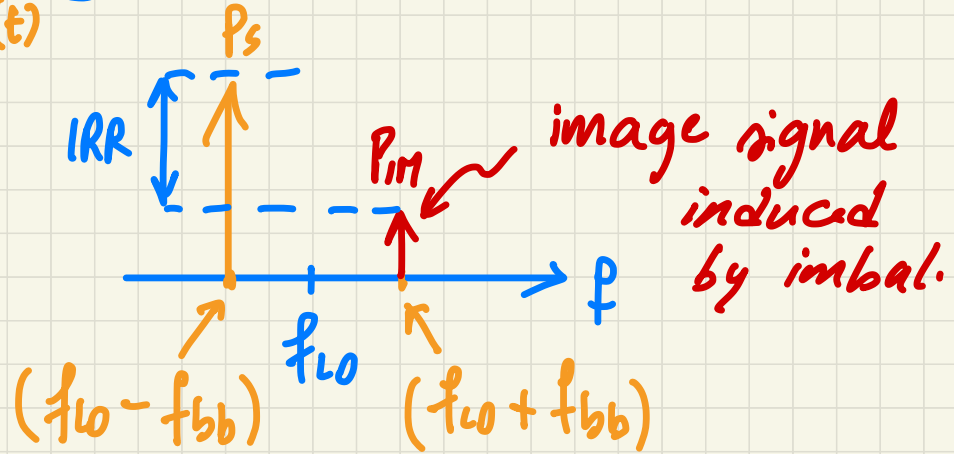


$$\cos \omega_{bb} t \cos \omega_{LO} t - \sin \omega_{bb} t \sin \omega_{LO} t = \cos (\omega_{LO} - \omega_{bb}) t$$

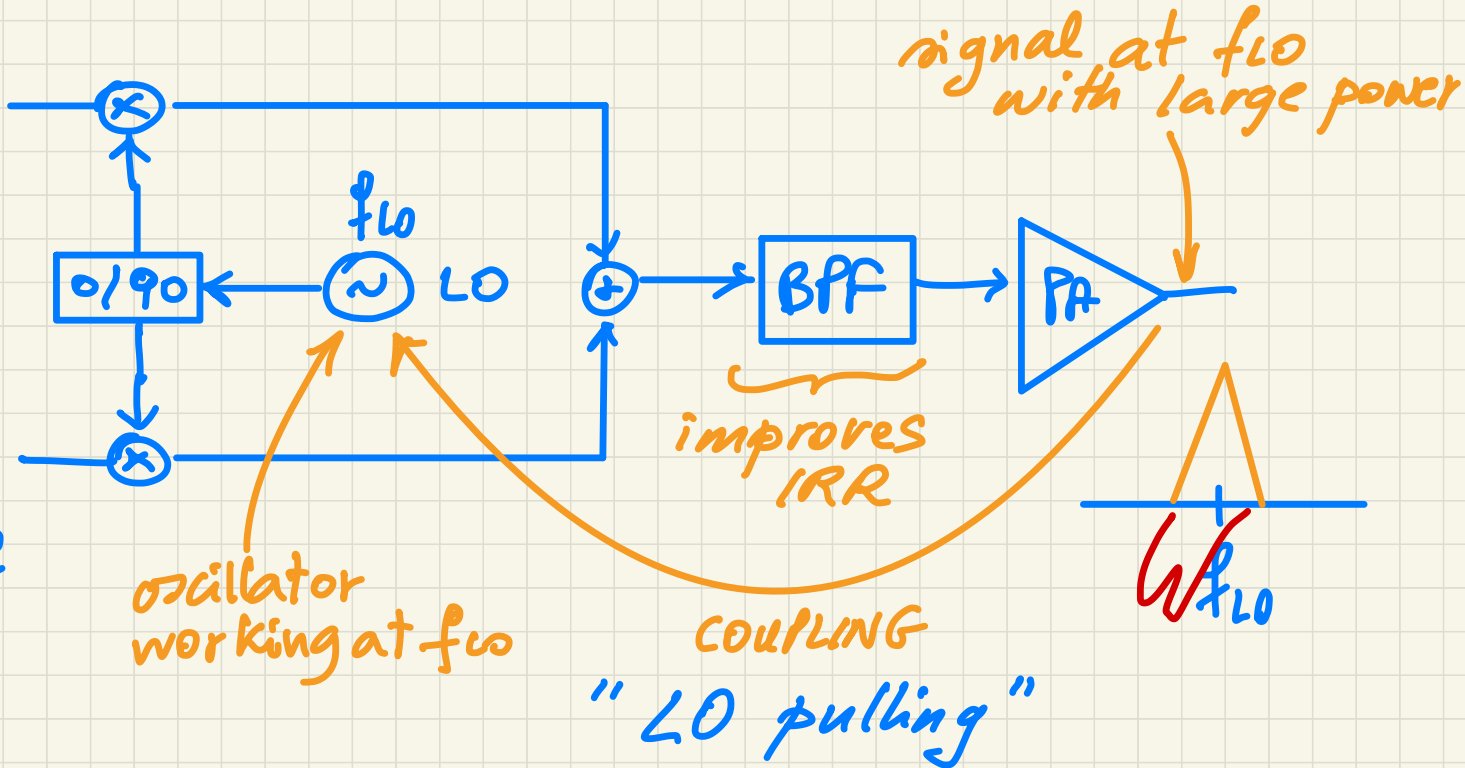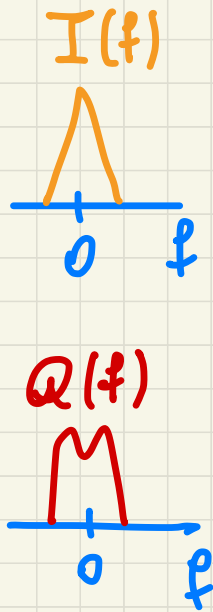
$$IRR = \frac{P_s}{P_{im}} = \frac{4}{\varepsilon^2 + \vartheta^2}$$



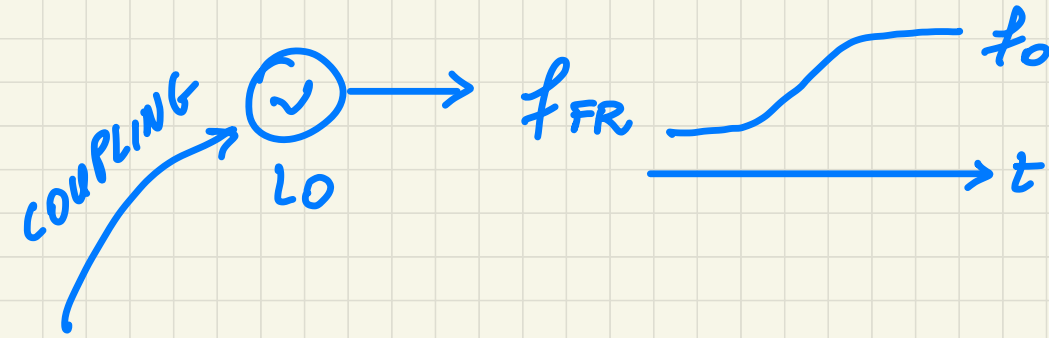Oscillators are subject to INJECTION LOCKING



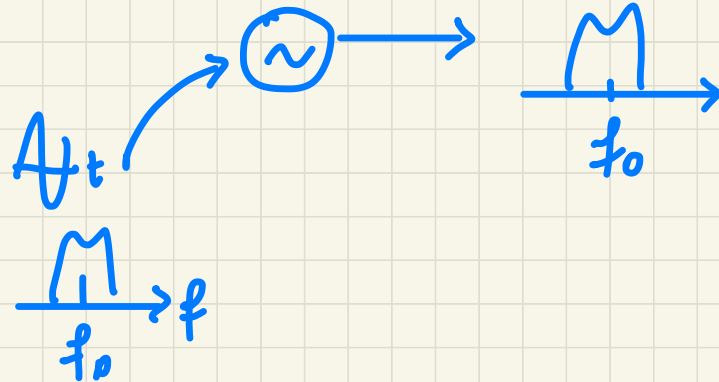oscillator
"locks" to
the injected
signal




oscillator (locked)
follows the input
phase/frequency
modulation



Solution : offsetting LO freq. w.r.t. PA frequency

- Two-step TX architecture :

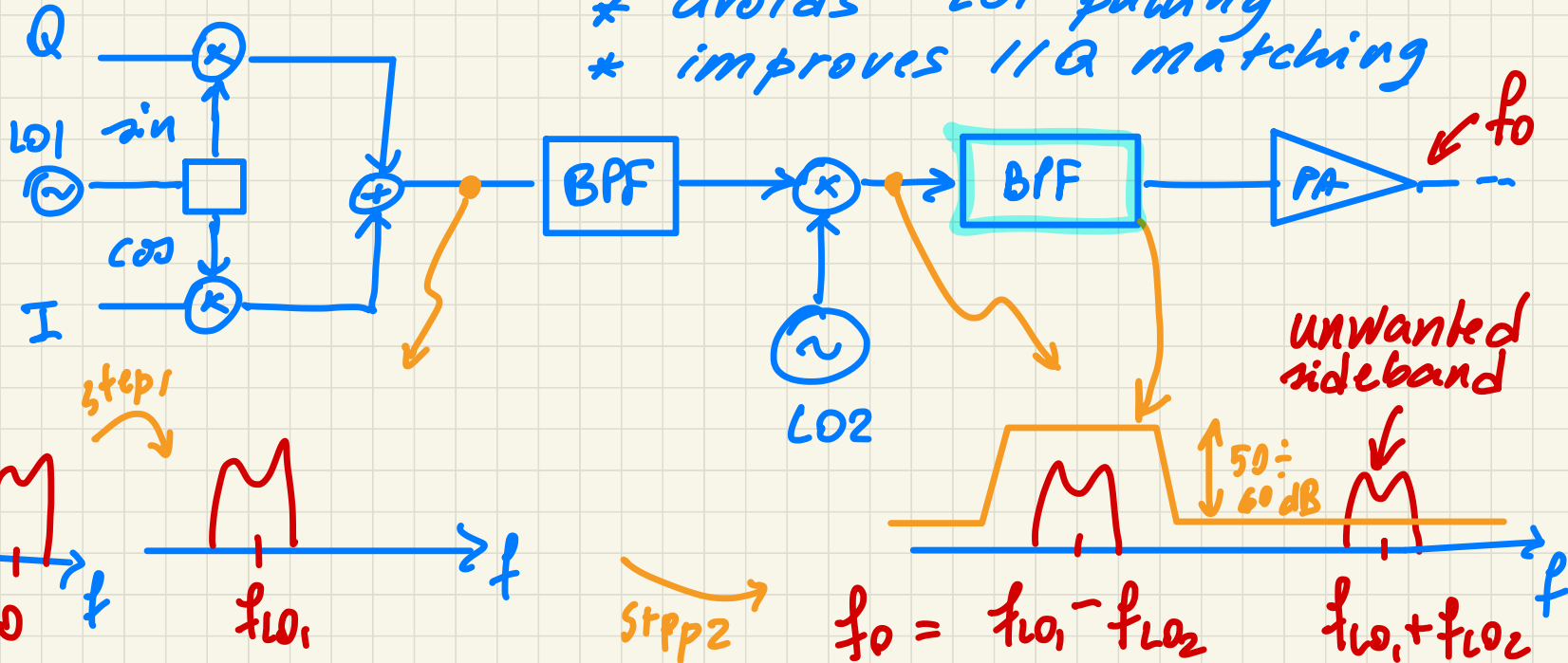* avoids LO pulling
* improves I/Q matching



Single-side band mixer (SSB mixer)

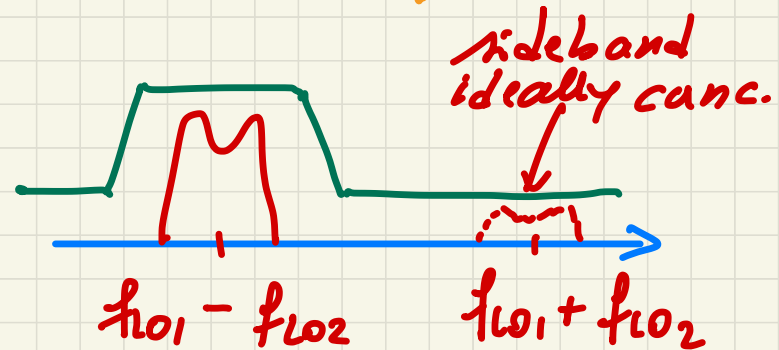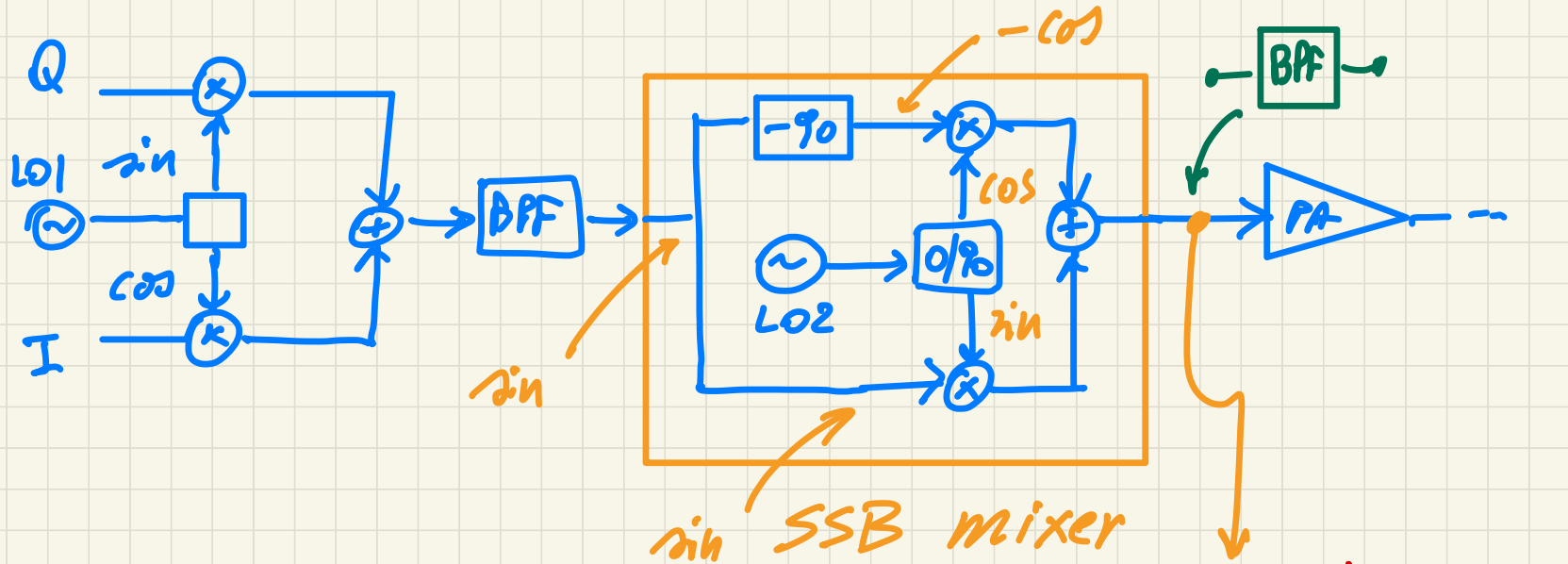

Examination :

— Written test

max. score 28+

— Oral test*

score

$0 \div 2$

1 single
question
out of
40

max. score 30+

• mid term test

• final⁺ test (June 14th)

or

• full test (June 14th, July 22nd,)

* I provide 40 questions to be published

Theses


- Sensors and microsystems
↳ electronics in
(3.3V) 0.35 μm CMOS
or 0.18 μm CMOS
(1.8V)
- In analog / RF circuit design
28 nm CMOS (1V) or 22 nm CMOS
or FinFET 16 nm CMOS

Communication System \rightarrow pushes operating frequency to have higher bit rates

→ mm waves $\lambda \approx 1 \div 10 \text{ mm}$
(wide BW available)

- enable high bit rate wireless ($1 \div 10 \text{ Gb/s}$)

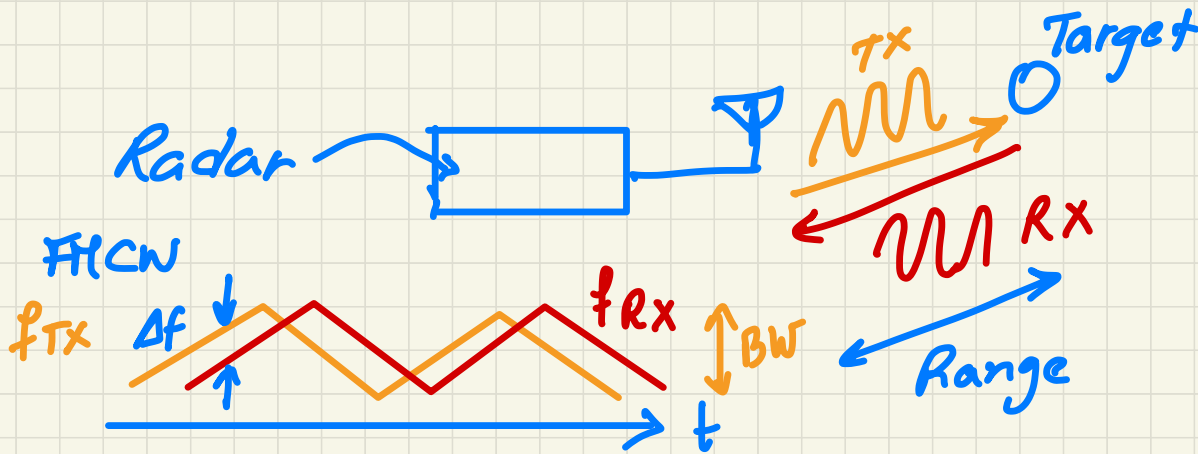- enable ranging applications with fine resolution (cm)




Chirp signal


Delay \div Range

$\Delta f \div$ Delay

Beam steering

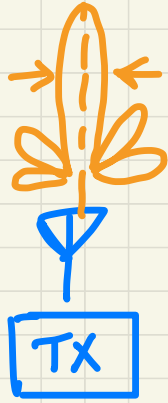

higher f
↓
narrower beam

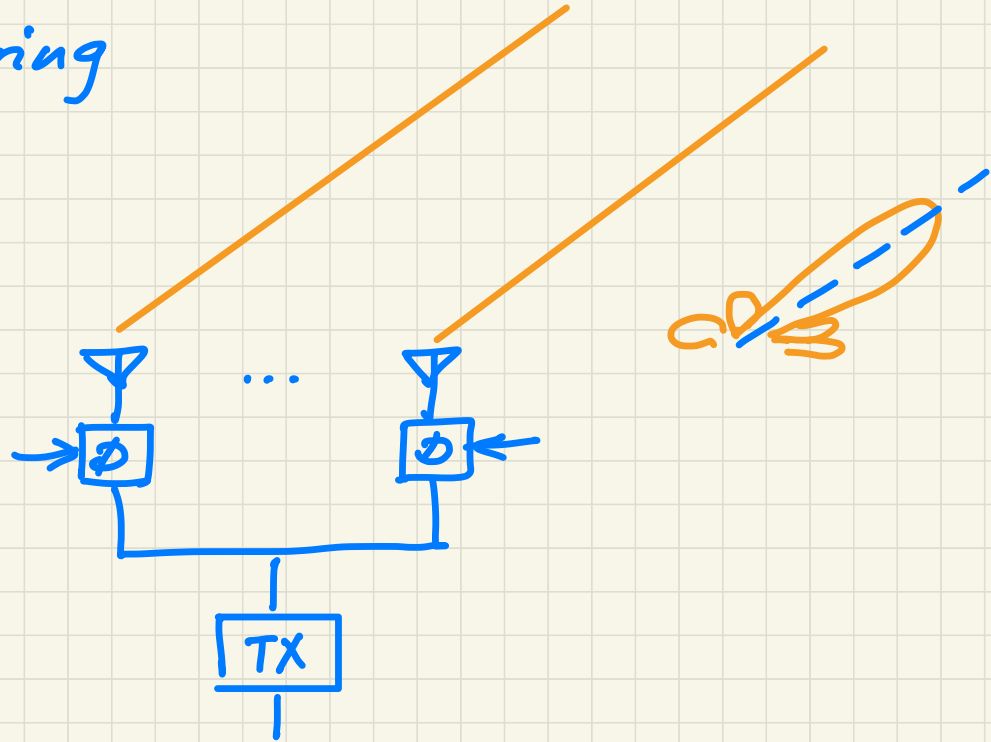


Digitally assisted analog design

- Topics :
- Frequency synthesizers in CMOS
 $10 \div 100 \text{ GHz}$ $28 \text{ nm} \rightarrow 22 \text{ nm}$
 - RF TX for beam steering in CMOS

- A/D converters for 5G commun.
 $\text{BW} \simeq 500 \div 800 \text{ MHz}$
 $\Rightarrow \text{GS/s ADCs}$
 $\rightarrow \text{Time-interleaving}$

ADC
 $\text{ENOB} > 10 \text{ bit}$

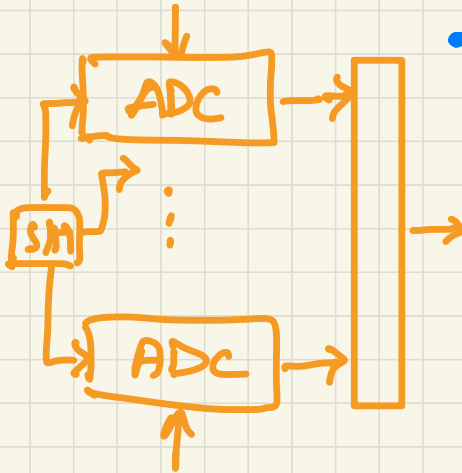

People :

- myself RF
- prof. Samorì ADC
- prof. Lacaita RF
- prof. Bonfanti ADC
- 10 PhD students

LO phase shifting

