

---

# ***Phase-Locked Loop Design*** ***Part 2***

**RF Circuit Design**  
***Prof. Salvatore Levantino***  
***2020/2021***

# ***Outline***

---

- **Type-II PLL with XNOR**
  - **Charge-Pump PLL**
-


---

# ***Type-II PLL with XNOR CT Model***


---

# *Type-II PLL with XNOR*

---

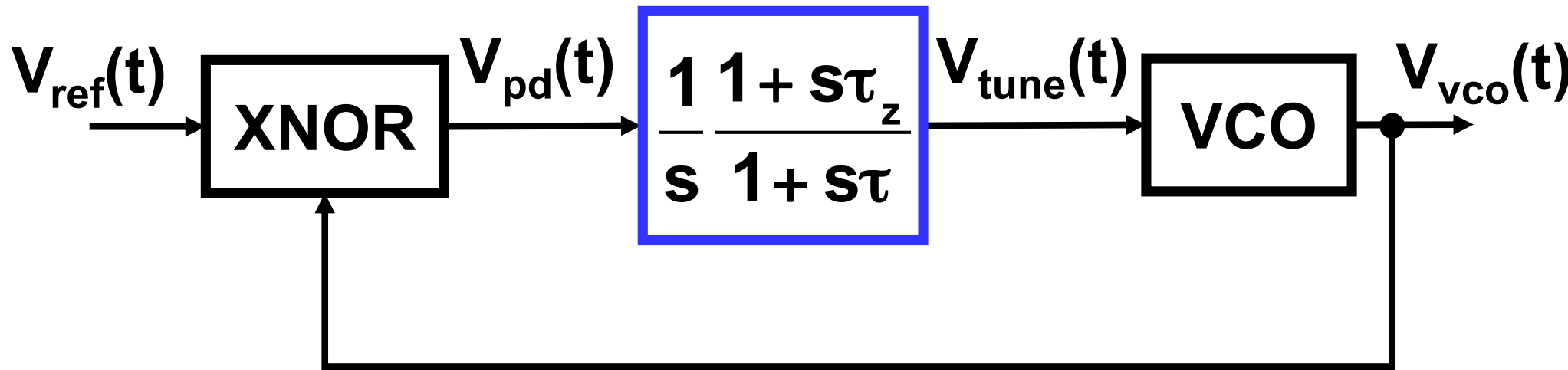

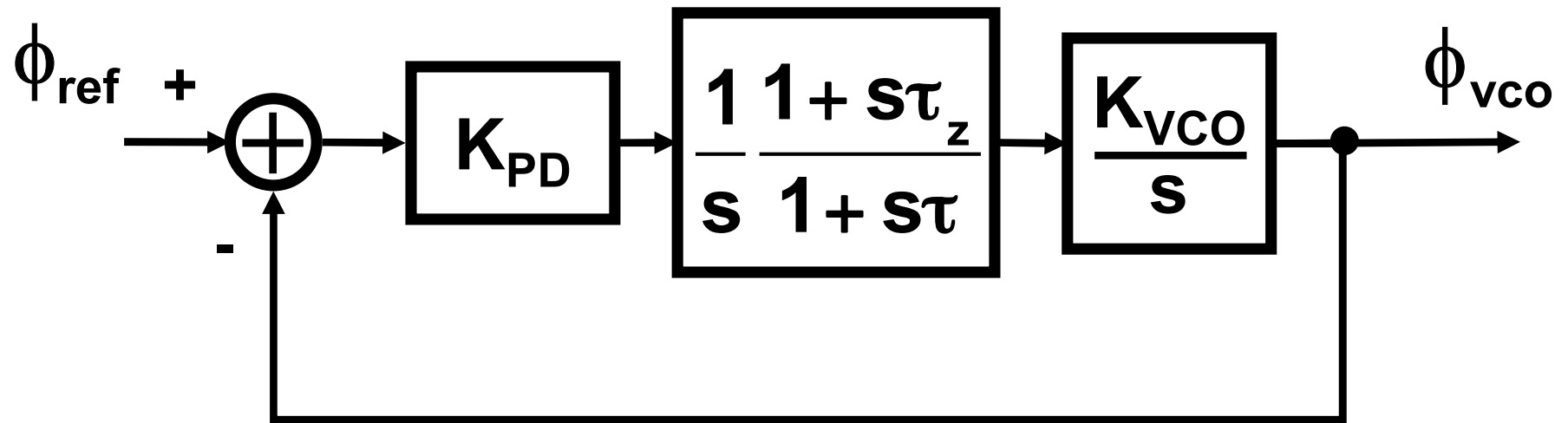
## Linear CT Model: *Third-Order Type-II*



$$\mathbf{G}_{\text{loop}}(s) = \frac{\mathbf{K}}{s^2} \cdot \frac{1 + s\tau_z}{1 + s\tau}$$

# Type I and Type II PLL: Root Loci

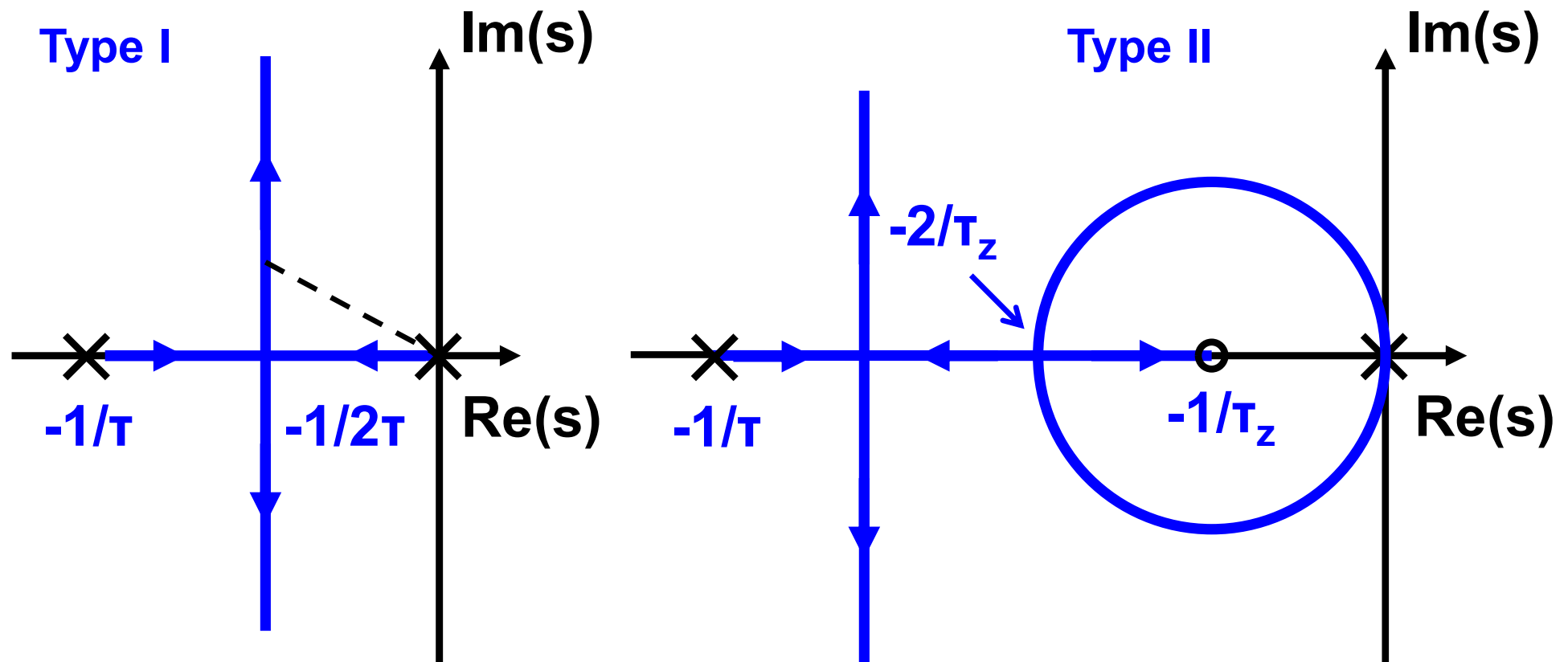


$$G_{\text{loop}}(s) = \frac{K}{s(1 + s\tau)}$$

$$G_{\text{loop}}(s) = \frac{K}{s^2} \cdot \frac{1 + s\tau_z}{1 + s\tau}$$
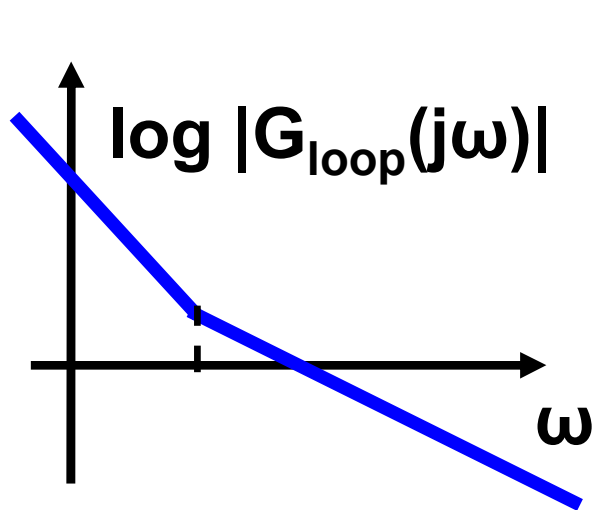
# Approximated *Second-Order* Analysis

$$\mathbf{G}_{\text{loop}}(\mathbf{s}) = \frac{\mathbf{K}}{\mathbf{s}^2} \cdot \frac{1 + \mathbf{s}\tau_z}{1 + \mathbf{s}\tau} \approx \frac{\mathbf{K} \cdot (1 + \mathbf{s}\tau_z)}{\mathbf{s}^2} \quad \text{if } \mathbf{s}\tau \ll 1$$



↓

$$\mathbf{H}(\mathbf{s}) = \frac{\mathbf{G}_{\text{loop}}}{1 + \mathbf{G}_{\text{loop}}} = \frac{\mathbf{K}(1 + \mathbf{s}\tau_z)}{\mathbf{s}^2 + \underbrace{\mathbf{sK}\tau_z}_{2\zeta\omega_n} + \underbrace{\mathbf{K}}_{\omega_n^2}}$$

→

$$\omega_n = \sqrt{\mathbf{K}} \quad \zeta = \frac{\tau_z \sqrt{\mathbf{K}}}{2}$$

# Approximated *Second-Order* Analysis (II)

---

$$\omega_n = \sqrt{K} \quad \zeta = \frac{\tau_z \sqrt{K}}{2}$$

BW can be increased  
if K is increased,  
until CT approximation  
breaks down

$$\zeta = \frac{\sqrt{2}}{2} \quad \rightarrow \quad \tau_z = \sqrt{\frac{2}{K}}$$

Parameter set:

$w_0 = 1e3$ ;  $dw = 0.1$ ;  $k = 1e-2$ ;  
 $\tau_{uz} = \text{sqrt}(2/k)$ ;  $\tau_u = 1$ ;

Frequency of third pole is  
much higher than bandwidth  $\omega_n$




# Root Locus (Matlab)


Matlab Code:

```
s = tf( 's' );  
Gloop = k / s ^ 2 * ( 1 + s * tauz ) / ( 1 + s * tau );  
rlocus( Gloop );  
hold on;  
rlocus( Gloop, 1, '*')
```

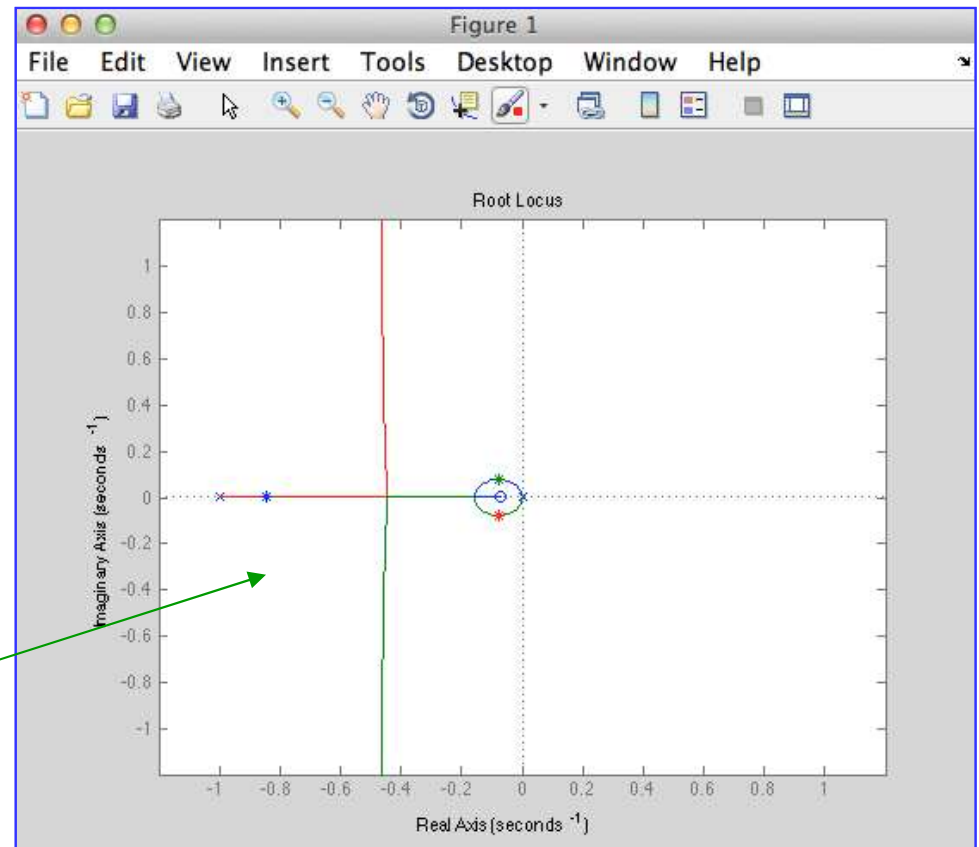
Two complex poles at  $45^\circ$   
and one much faster third pole




# Linear CT Model (Simulink)

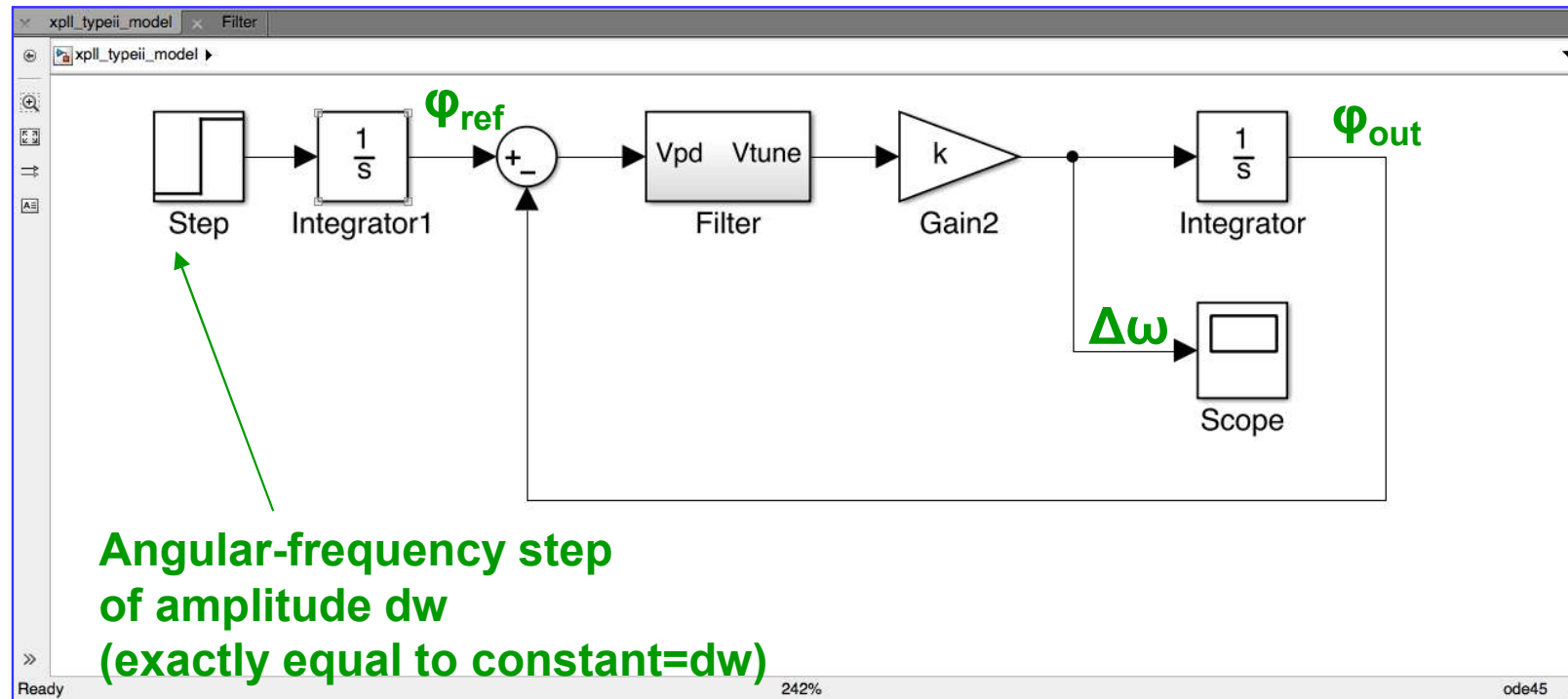

# Loop Filter (Simulink)

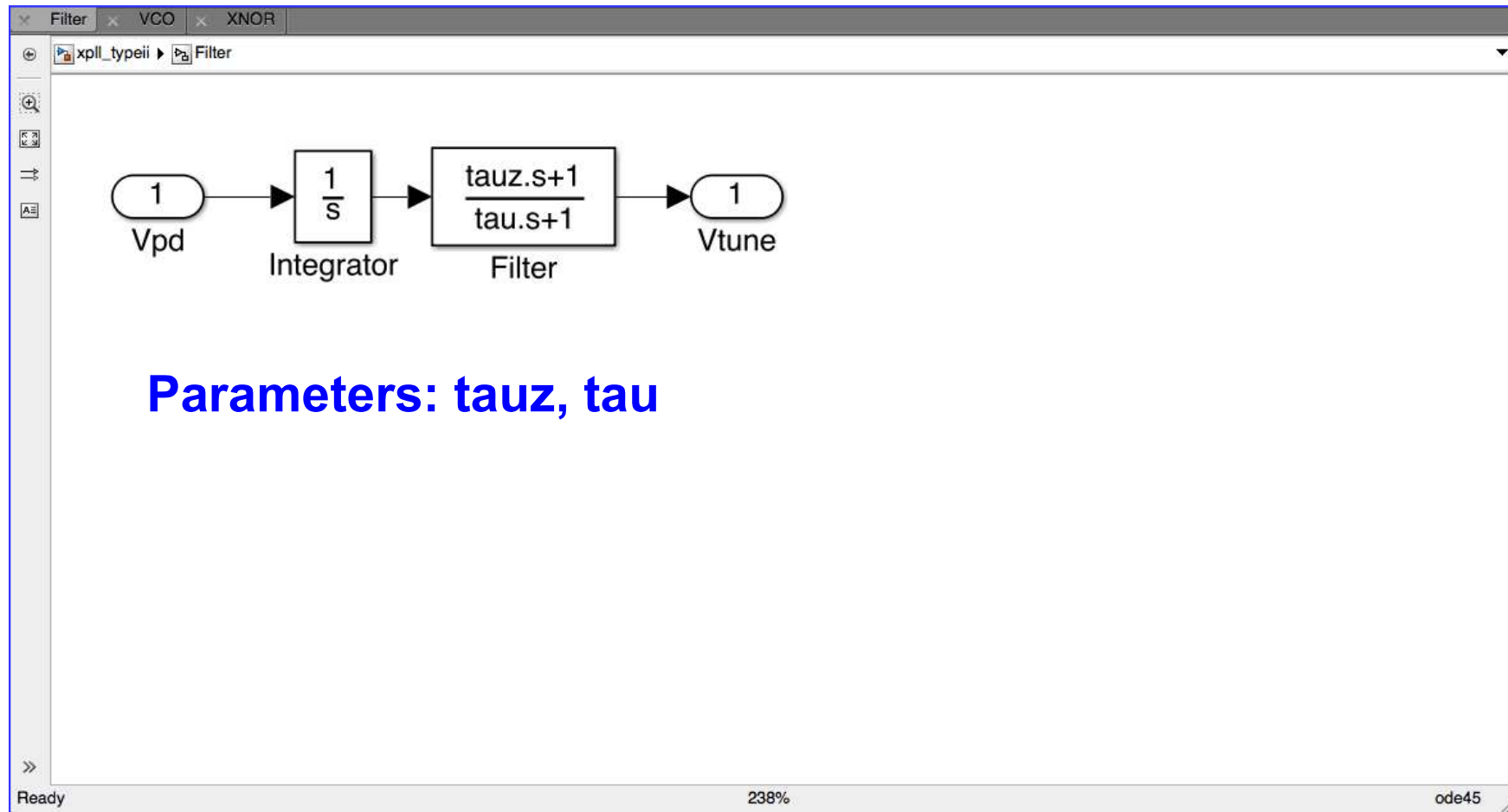

# Simulation Parameters (Simulink)

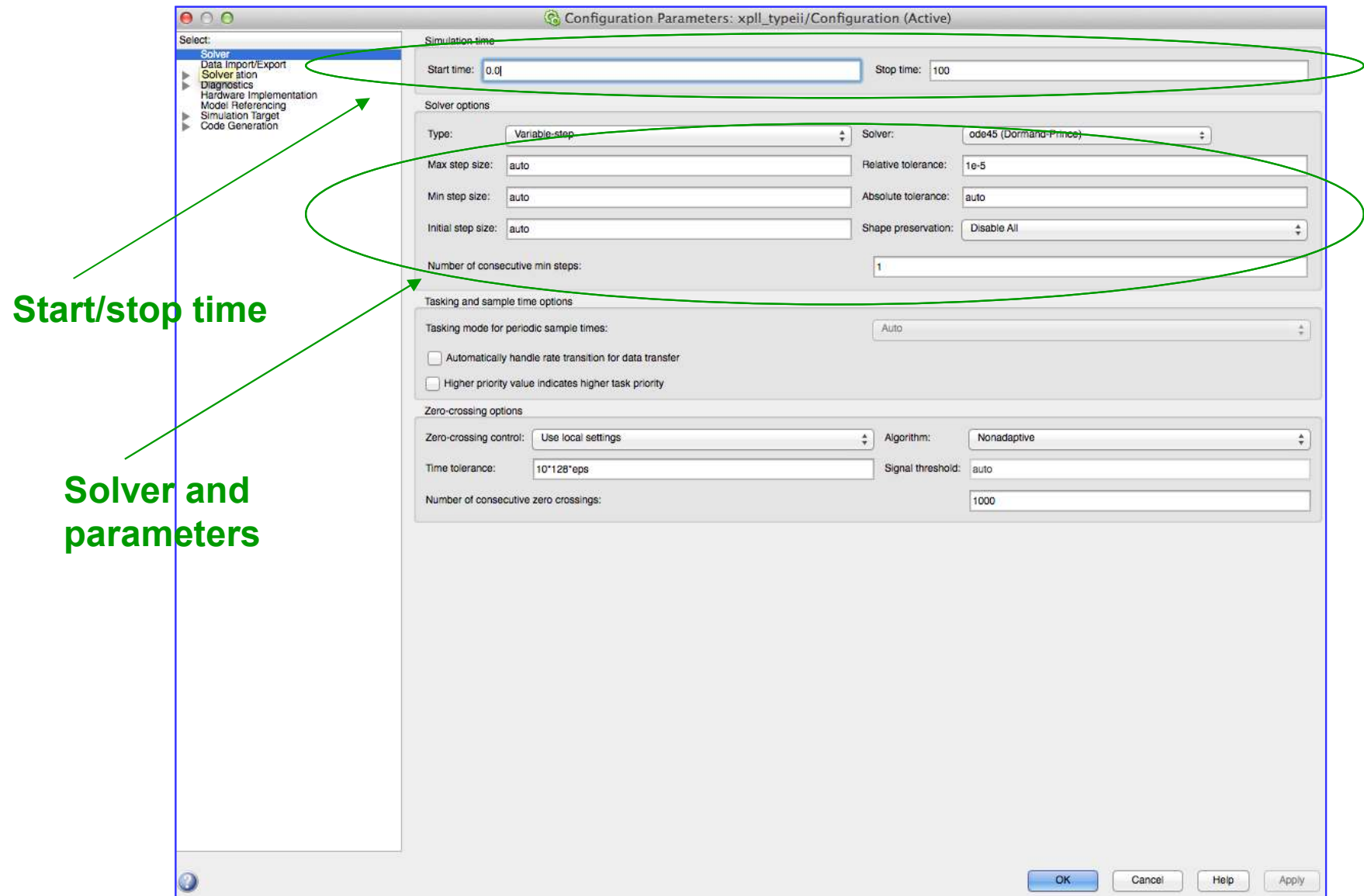

# Exercises

---


- By means of the **root locus**, compute the **position of the three closed-loop poles** and compare their values with the target ones.
- Plot the **response of the output frequency to an input frequency step**
- Plot the **phase error vs time** after the application of the input frequency step

---

***Type-II PLL with XNOR  
Behavioral Model***

---
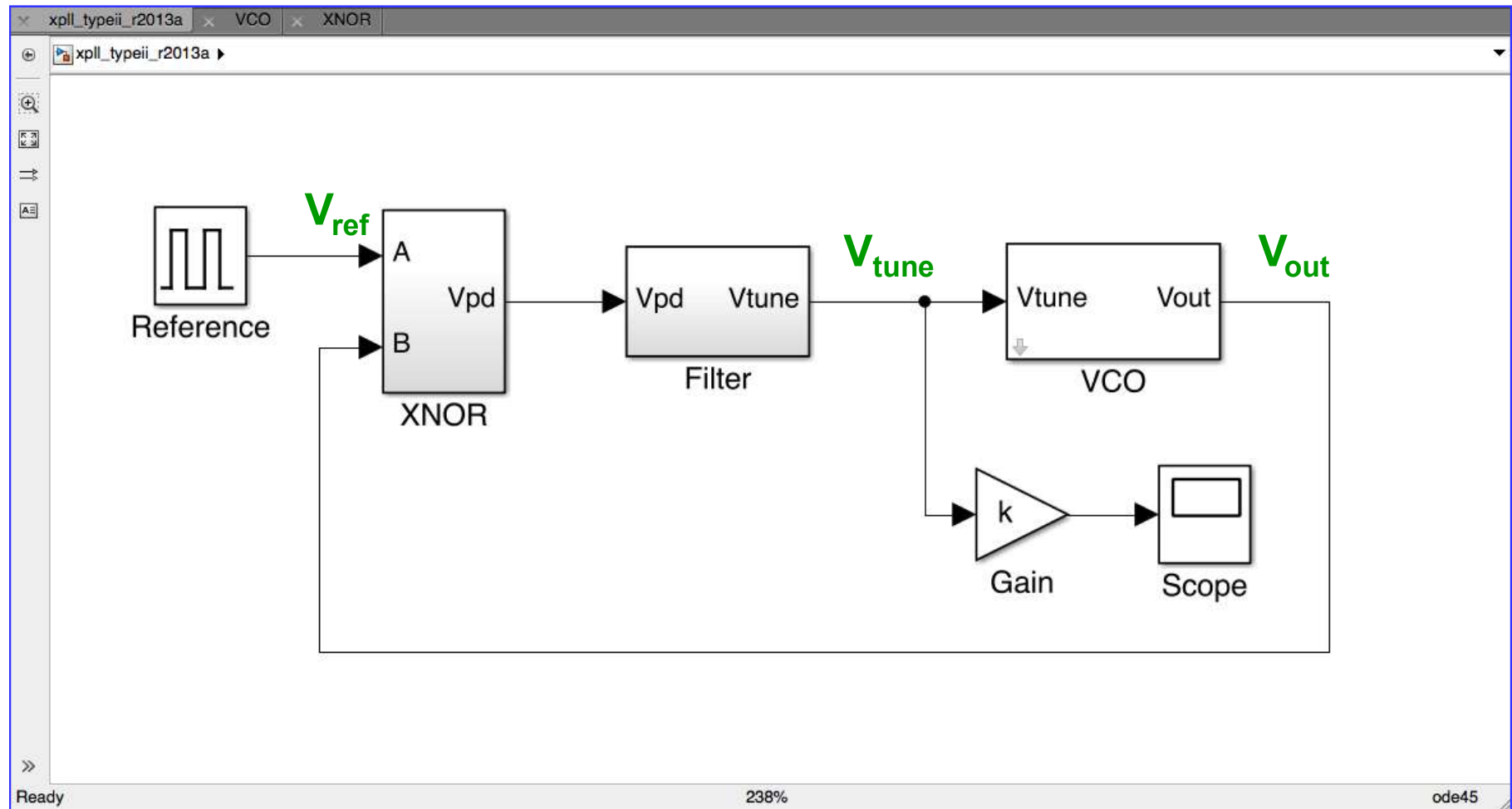
# Nonlinear Type-II PLL with XNOR (Simulink)



# Exercises

---

- Plot the **response of the output frequency to an input frequency step**, at different initial delays of the reference. Justify the result.
- Estimate the **residual ripple** of oscillator frequency from simulation
- Discuss what happens to the output frequency when **k is increased by 1000x** and why.
- Starting from the original parameter set, make the **time constant of the third pole 10 times smaller** and estimate the **residual ripple** again. Can you justify the change in ripple value?




---

# ***Charge-Pump PLL***



---

# Third-Order Type-II Charge-Pump PLL


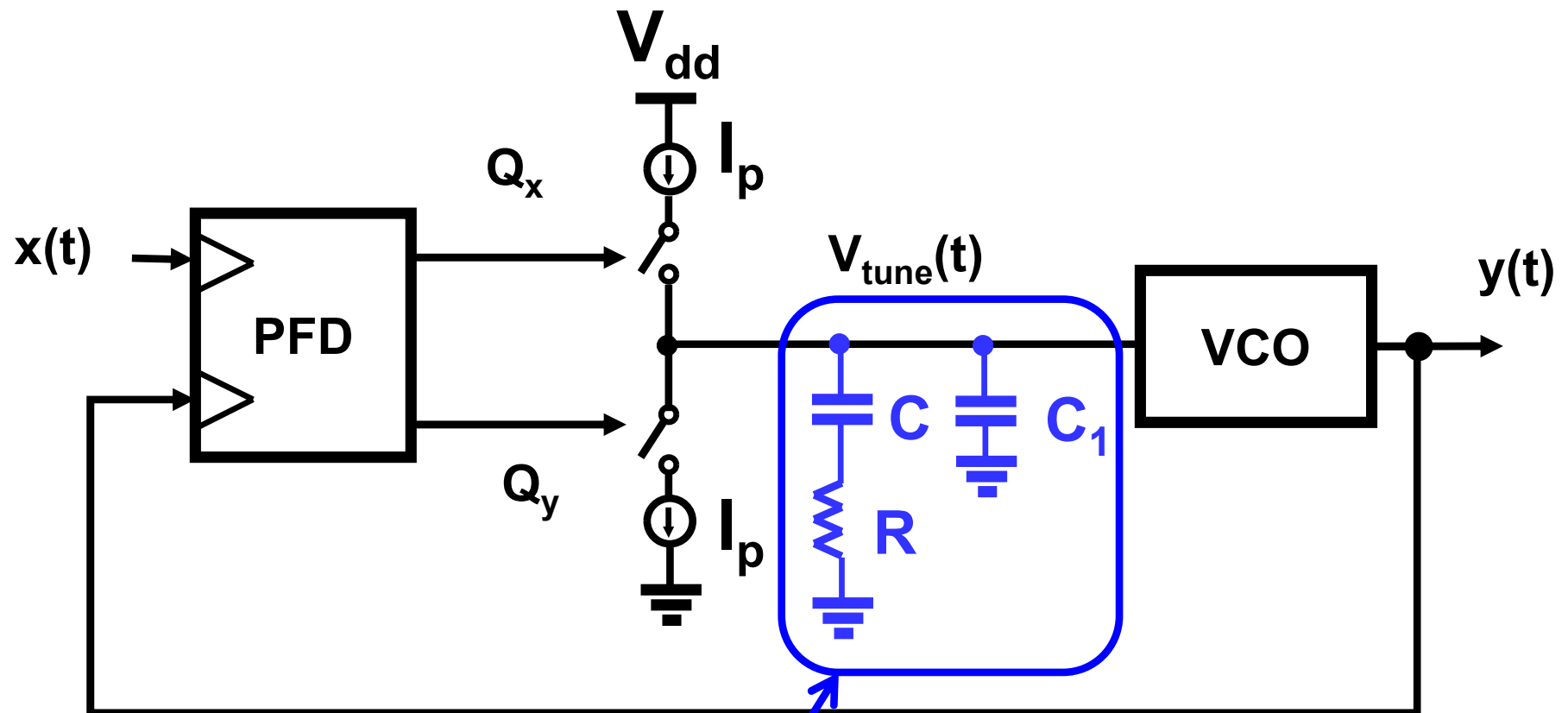


$$Z(s) = \frac{1}{sC_{\text{tot}}} \frac{1 + s\tau_z}{1 + s\tau}$$

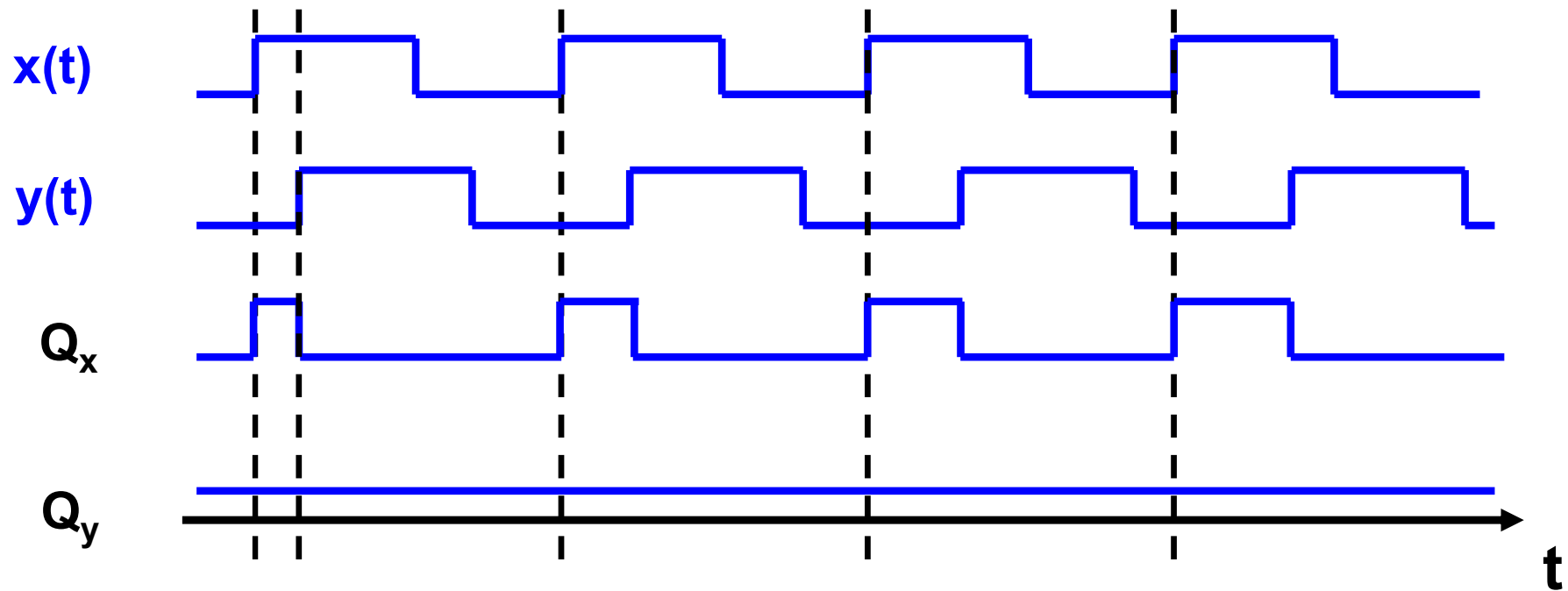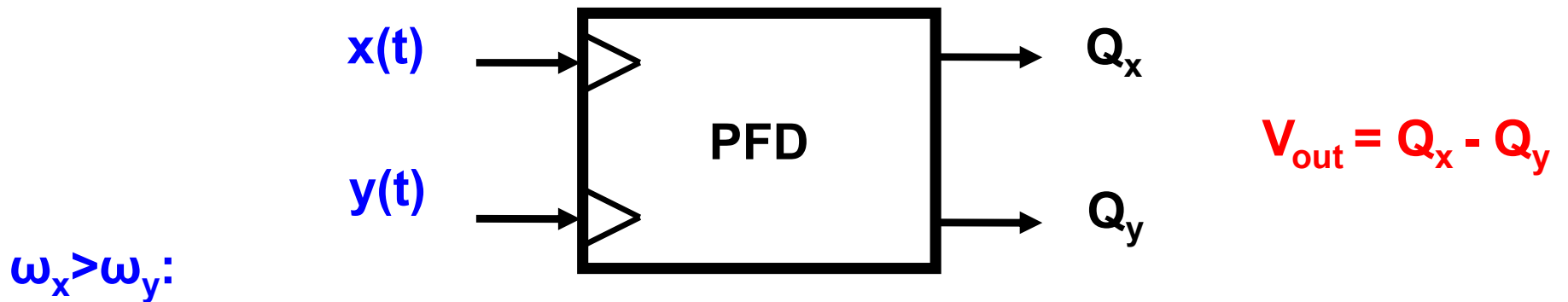
# Phase/Frequency Detector (PFD): $\omega_x > \omega_y$


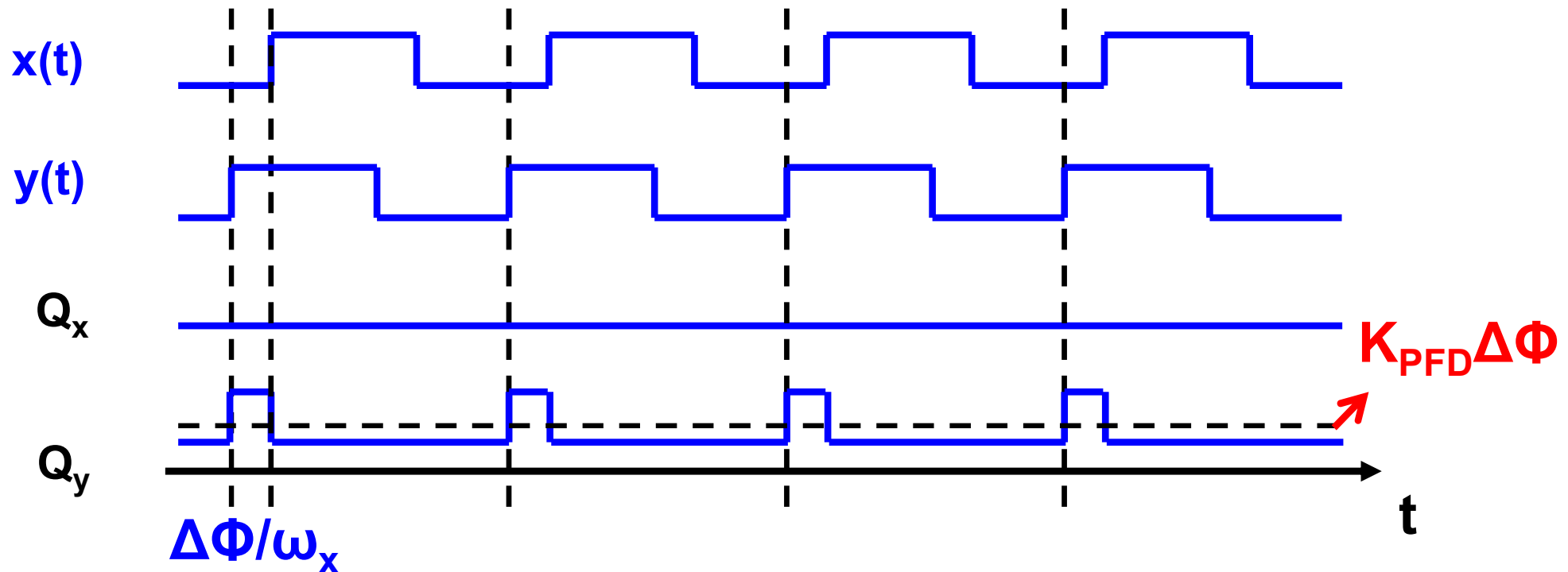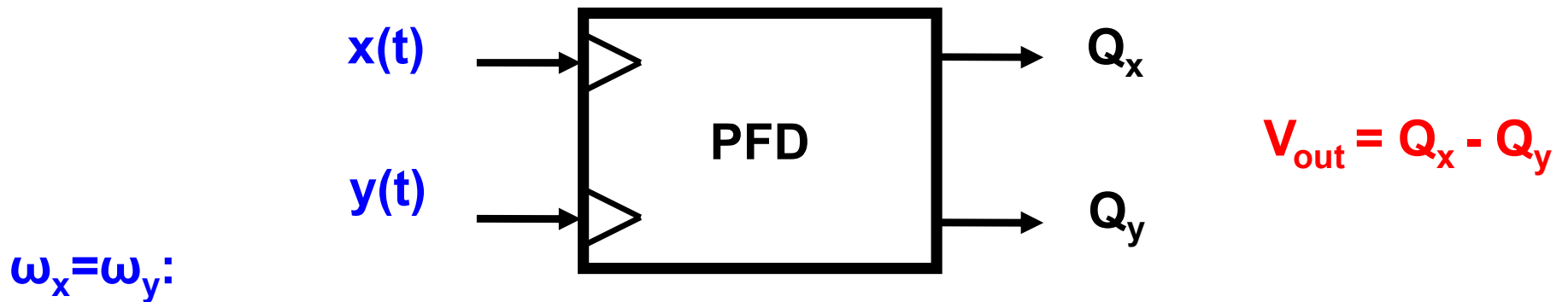
# Phase/Frequency Detector (PFD): $\omega_x = \omega_y$




# PFD State Diagram

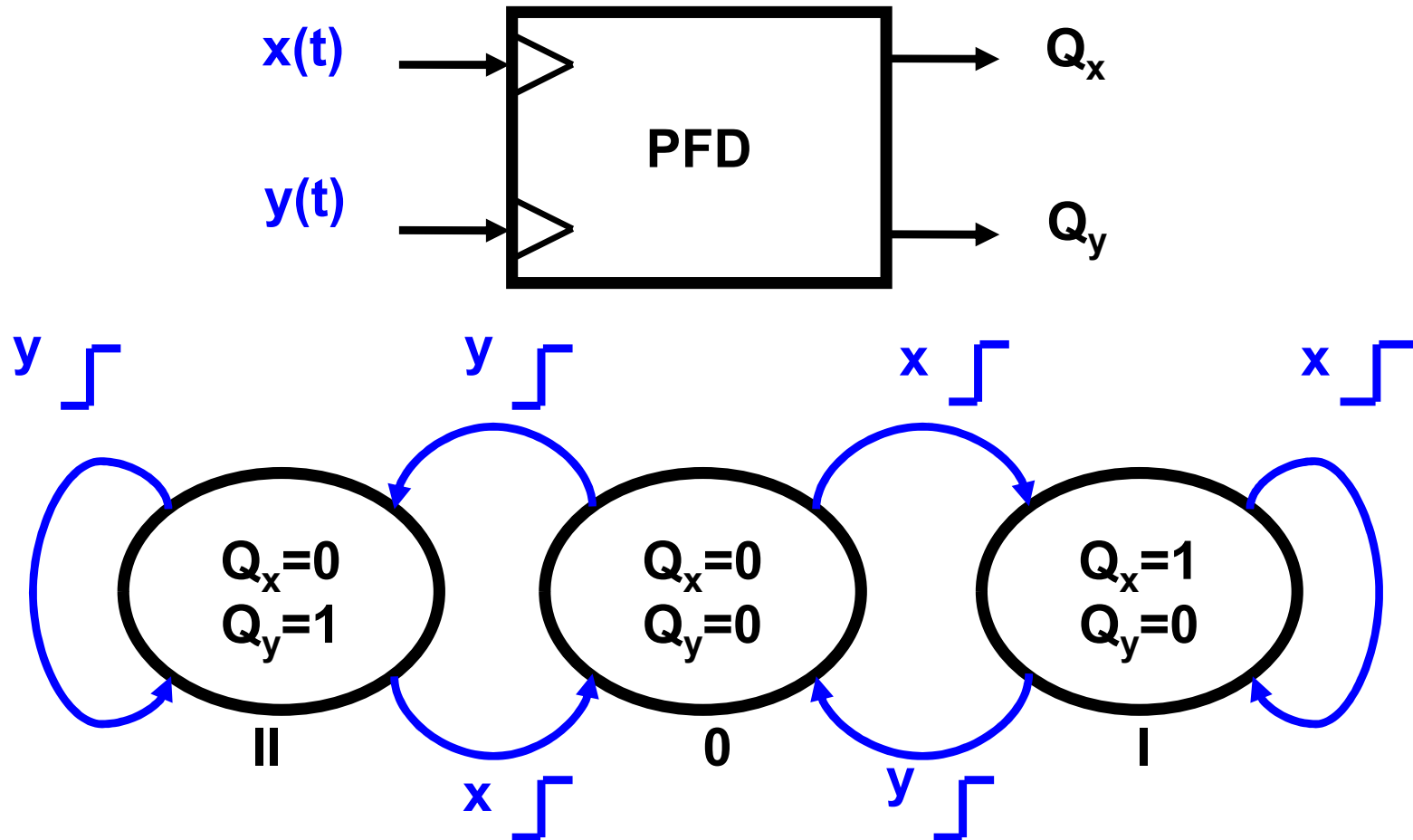


If  $\omega_x > \omega_y$ : even starting from state II, it will leave that state

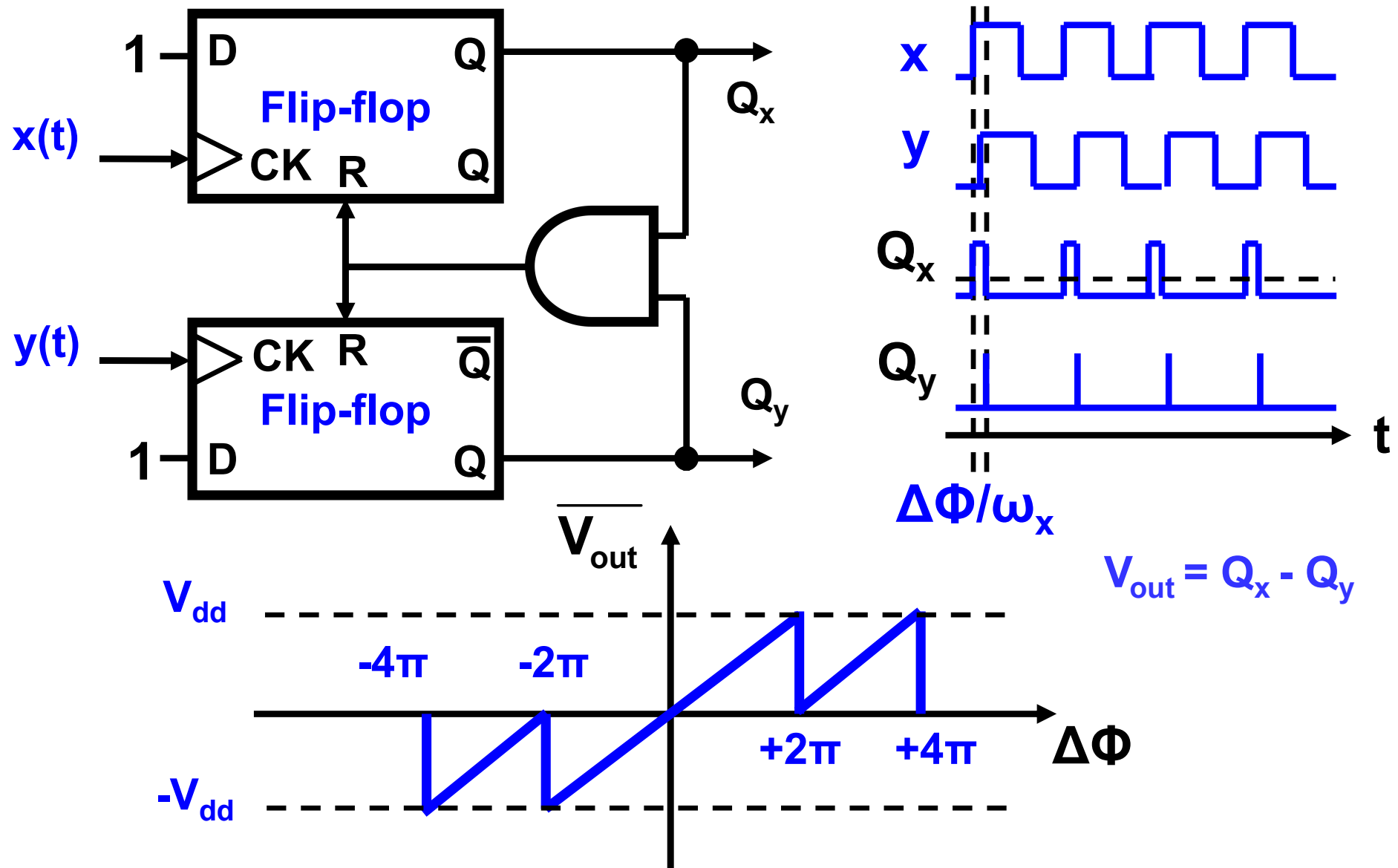
# PFD Implementation and Static Characteristic



# Charge Pump

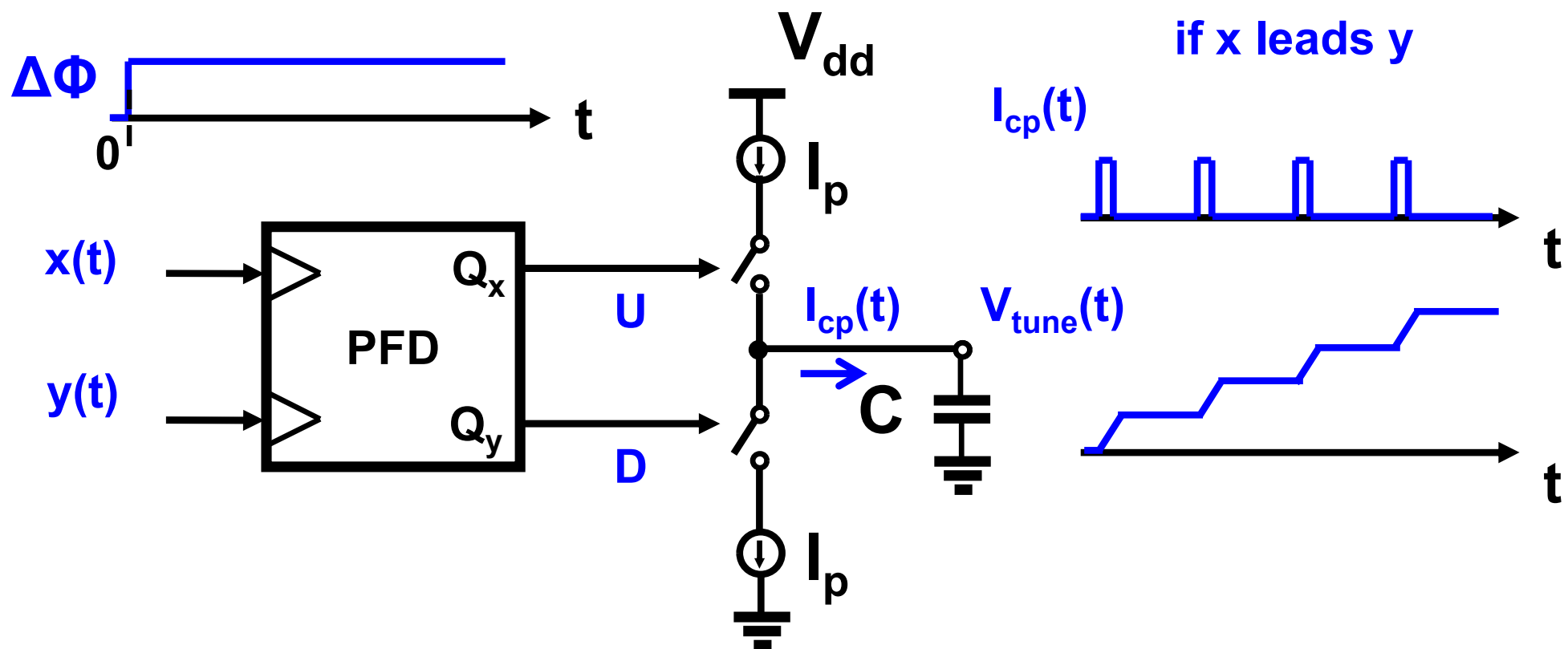

# Linear CT Model of PFD/CP/Filter

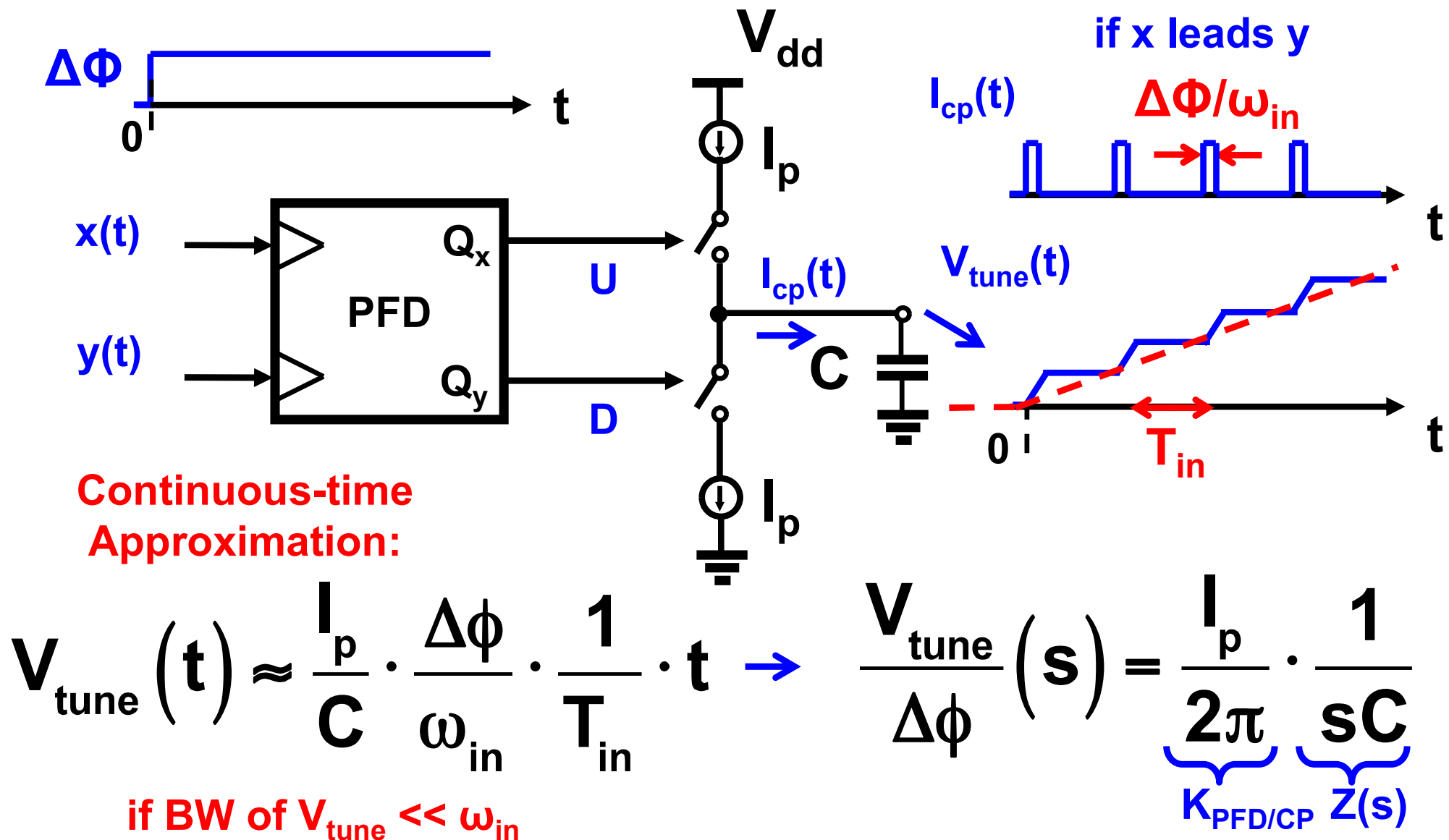




# Approximated *Second-Order* Analysis

$$\mathbf{G}_{\text{loop}}(s) = \underbrace{\left( \frac{I_p}{2\pi} \frac{K_{\text{vco}}}{C_{\text{tot}}} \right)}_{K \text{ [rad/s]}^2} \cdot \frac{1}{s^2} \cdot \frac{1+s\tau_z}{1+s\tau}$$

if  $s\tau \ll 1$

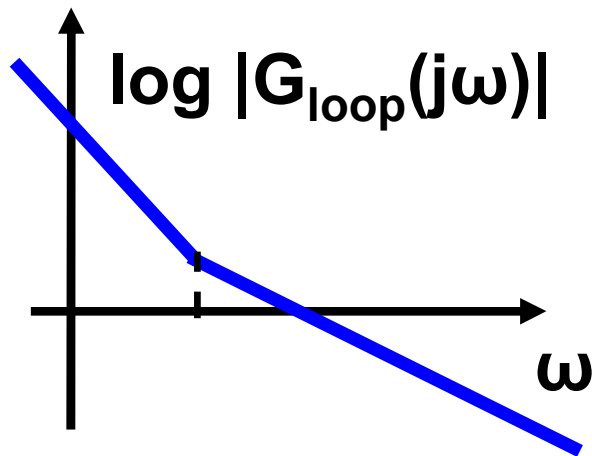

$$\mathbf{H}(s) = \frac{\mathbf{G}_{\text{loop}}}{1 + \mathbf{G}_{\text{loop}}} = \frac{K(1 + s\tau_z)}{s^2 + sK\tau_z + K}$$


$$\xi = \frac{\sqrt{2}}{2}$$




$$\tau_z = \sqrt{\frac{2}{K}}$$

$$\omega_n = \sqrt{K}$$

# Nonlinear CP-PLL (Simulink)

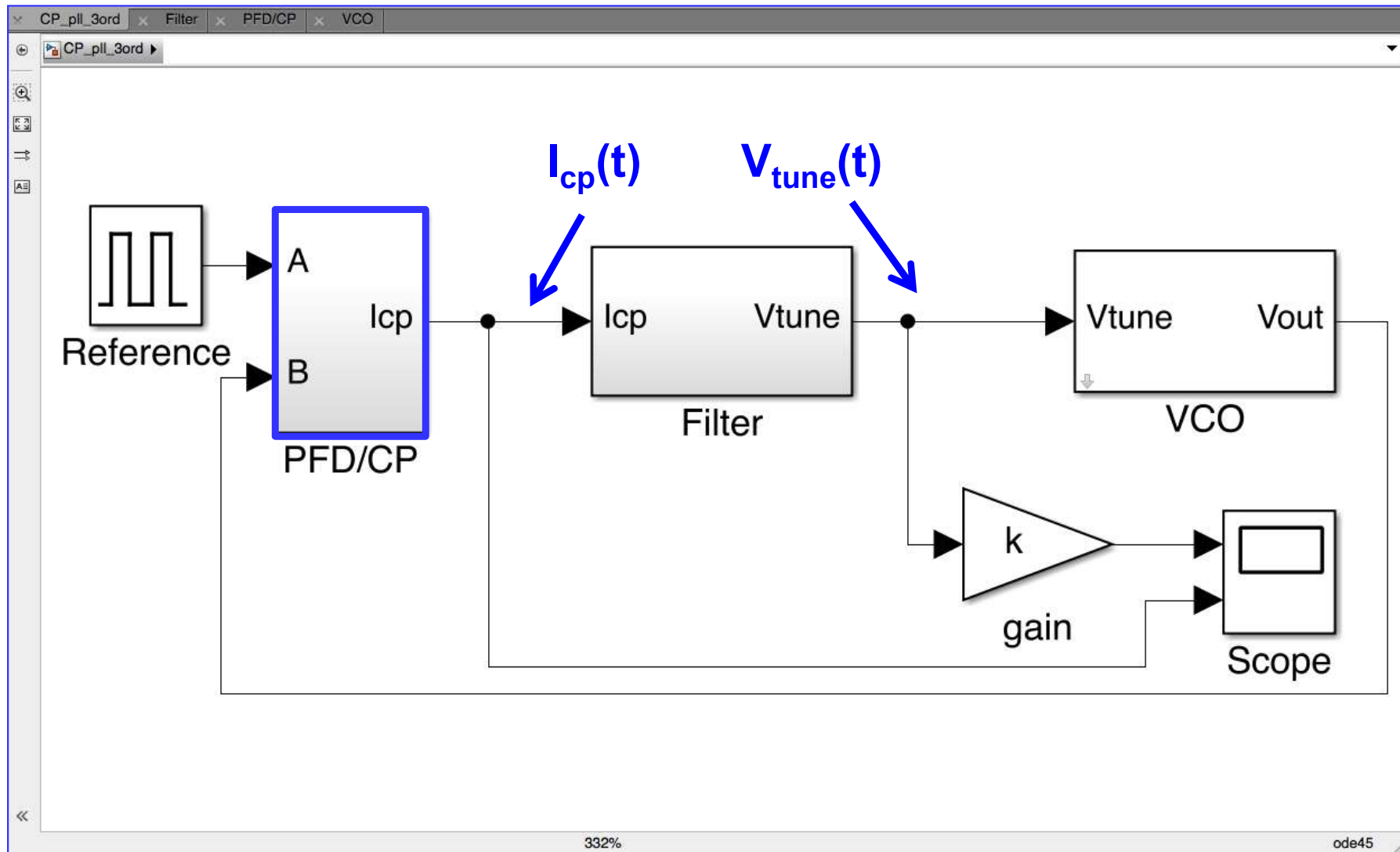


# PFD/CP Block (Simulink)

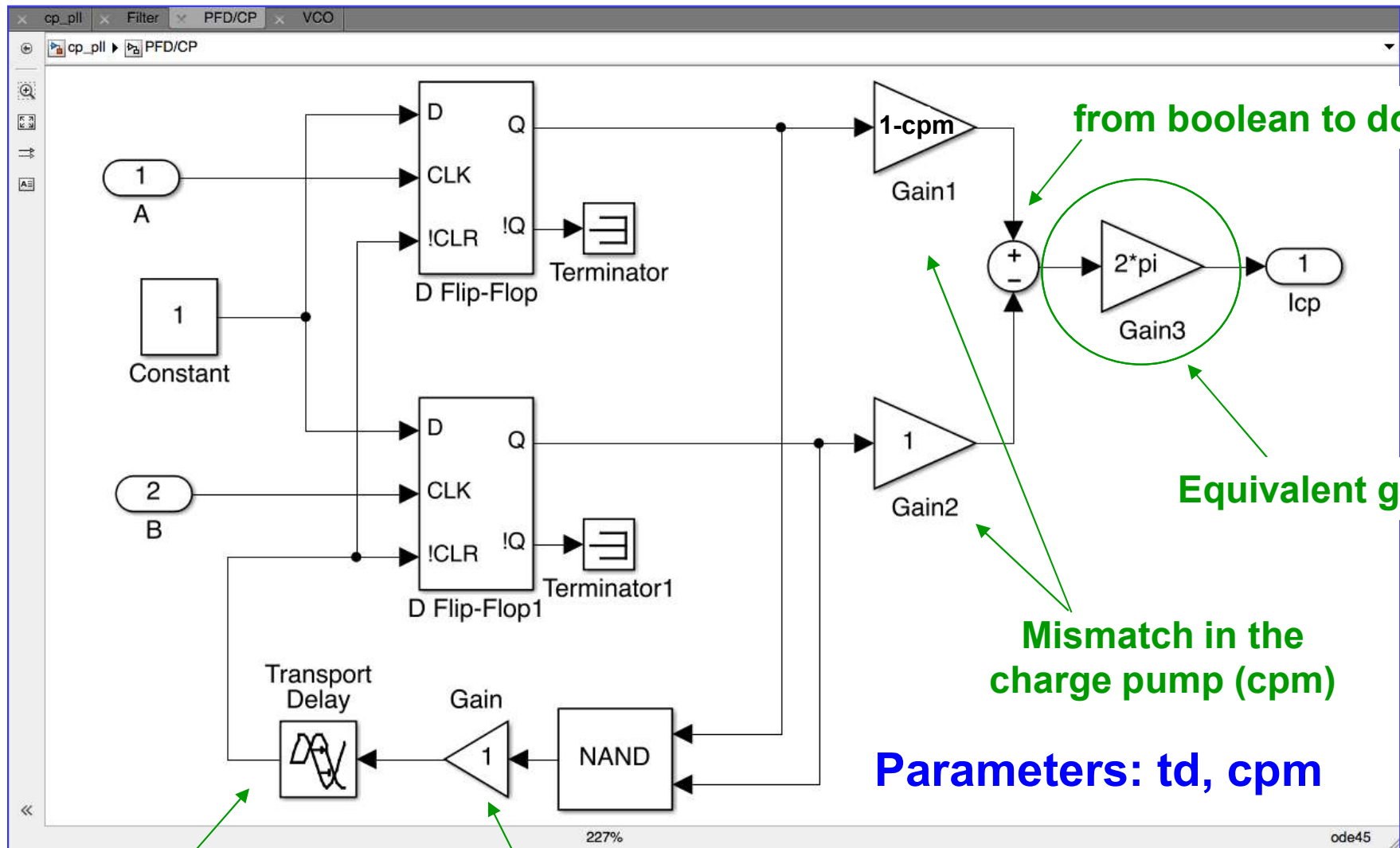


Reset delay in the PFD (td)

For data type conversion (from boolean to double)

# Loop Filter (Simulink)

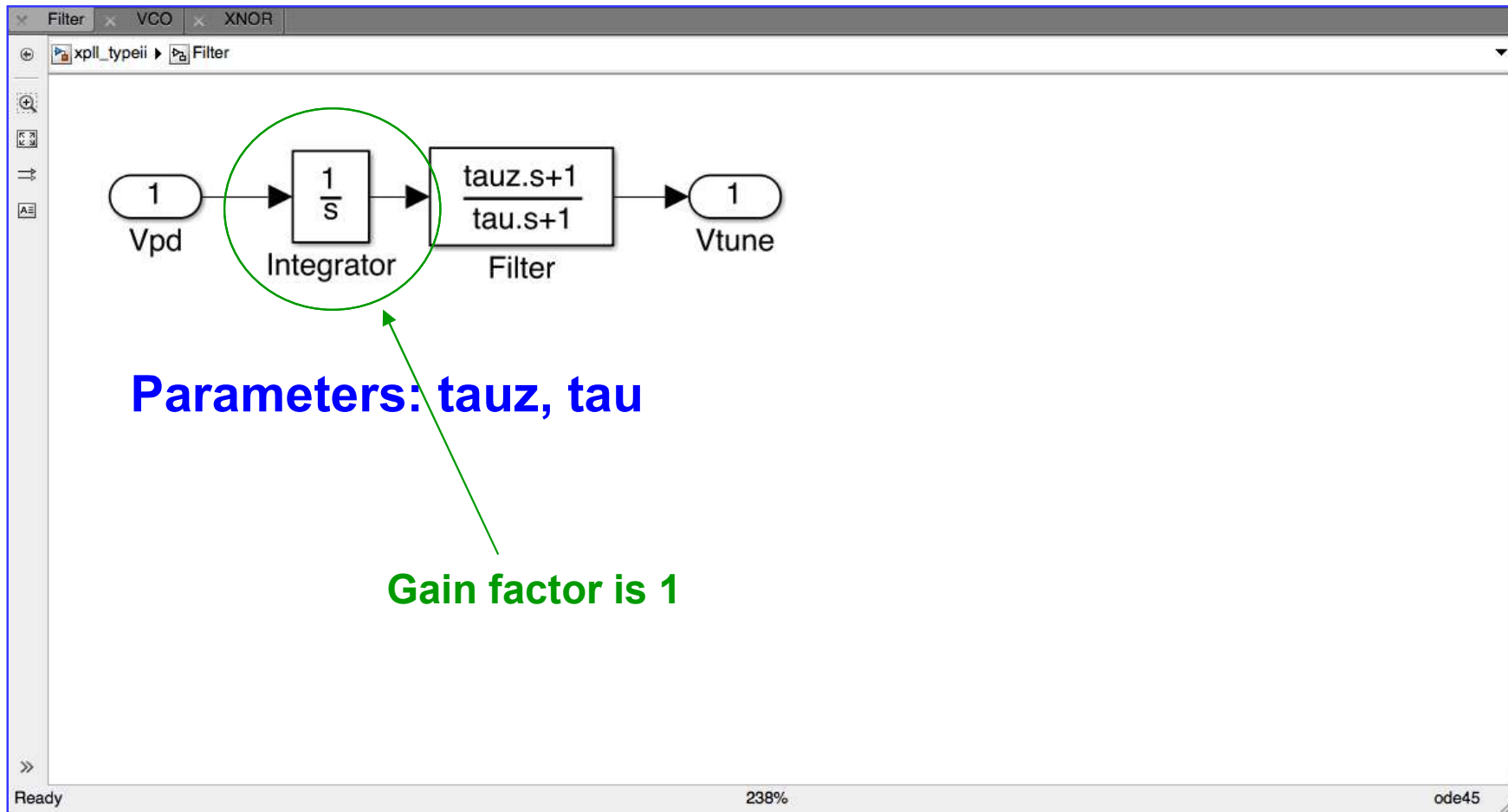

# VCO Block (Simulink)

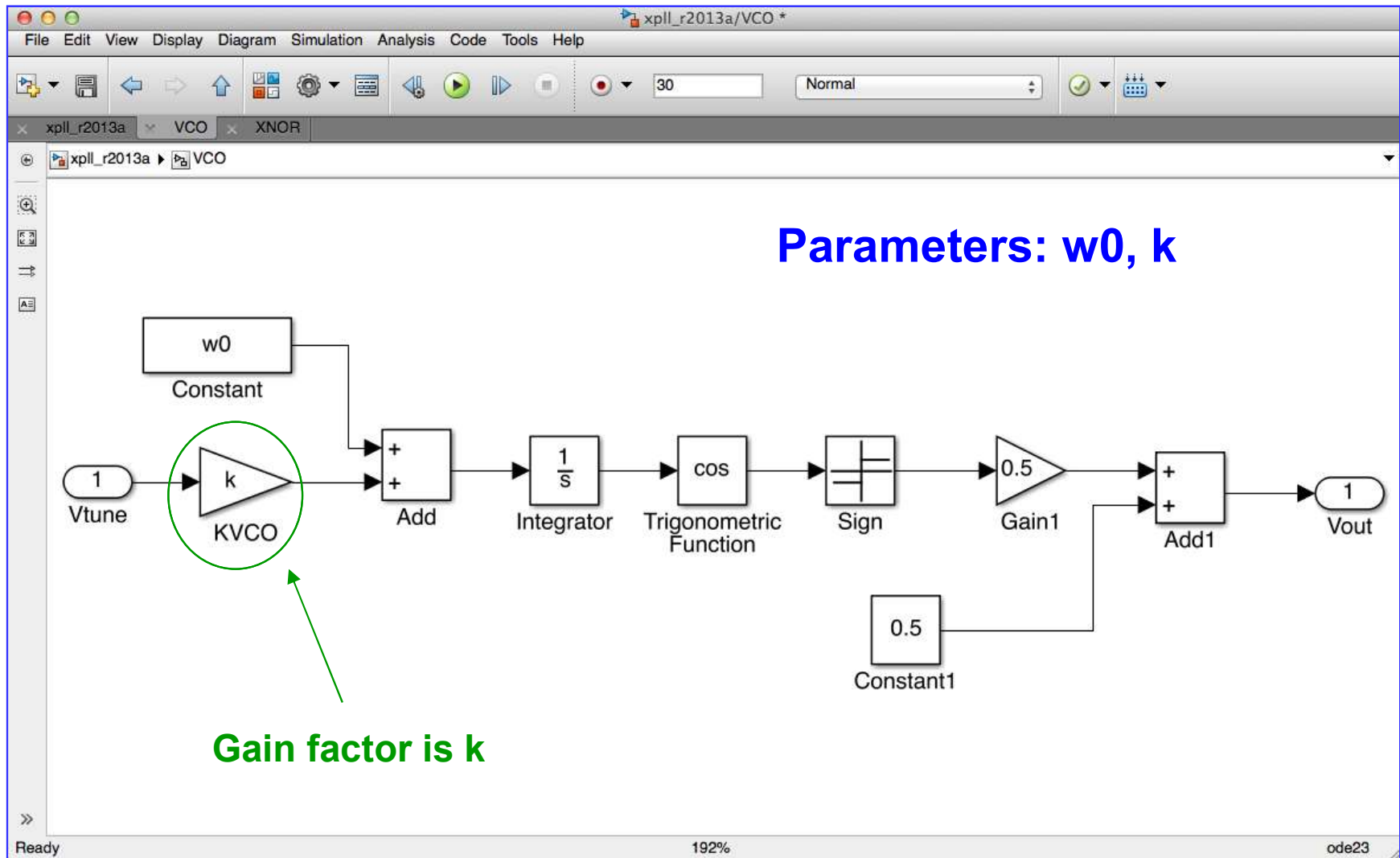


# Parameter Set


Parameter set:

$w_0 = 1e3$ ;  $dw = 0.1$ ;  $k = 1e-2$ ;


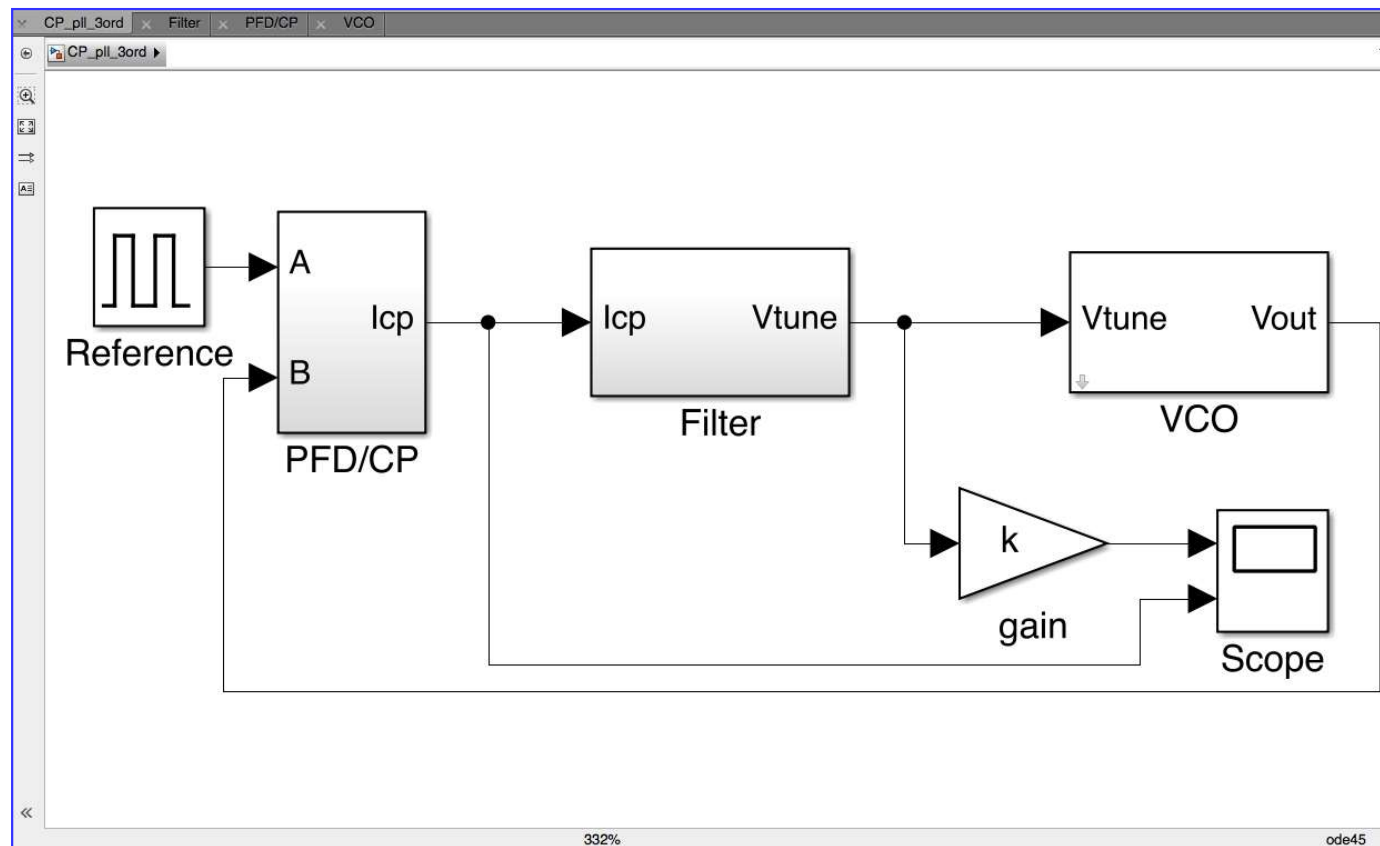
$\tau_{\text{auz}} = \sqrt{2/k}$ ;  $\tau = 1$ ;  $t_d = 1e-3$ ;  $\text{cpm} = 0.1$ ;



# Simulation of CP-PLL (Simulink)

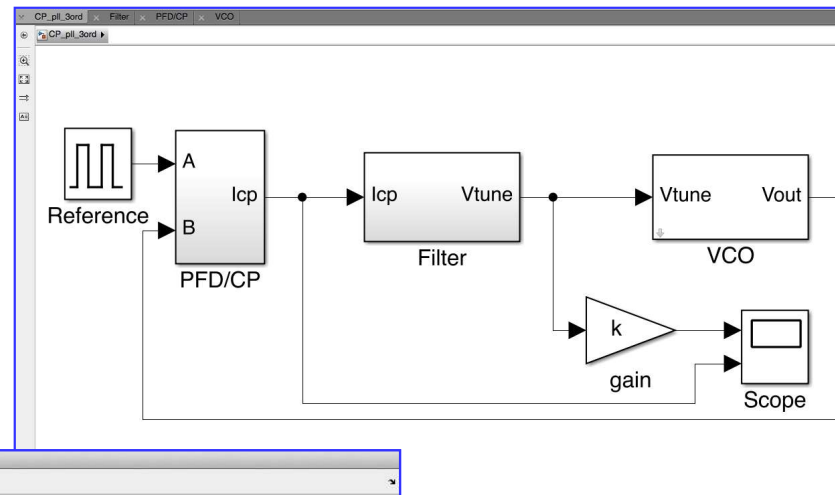

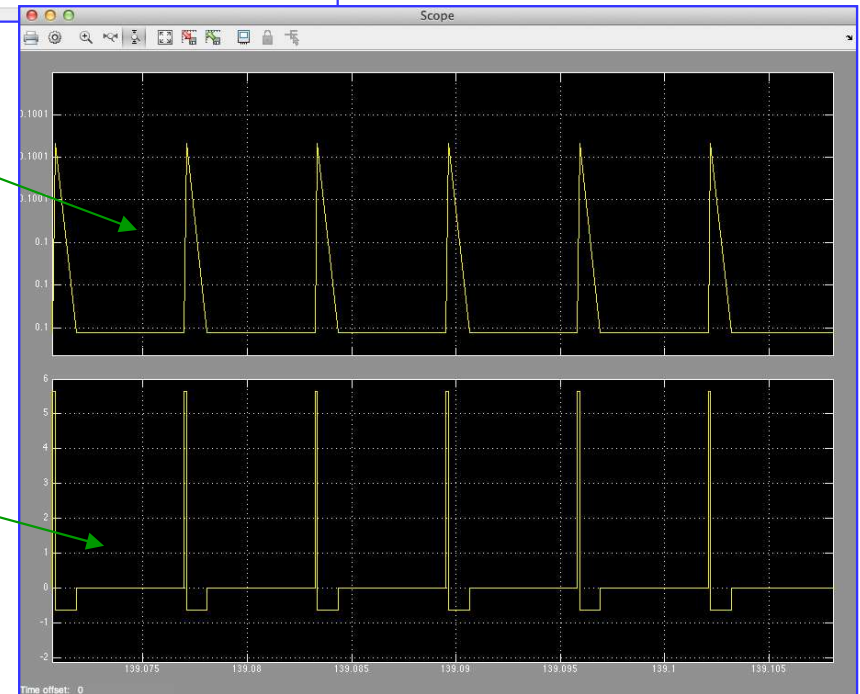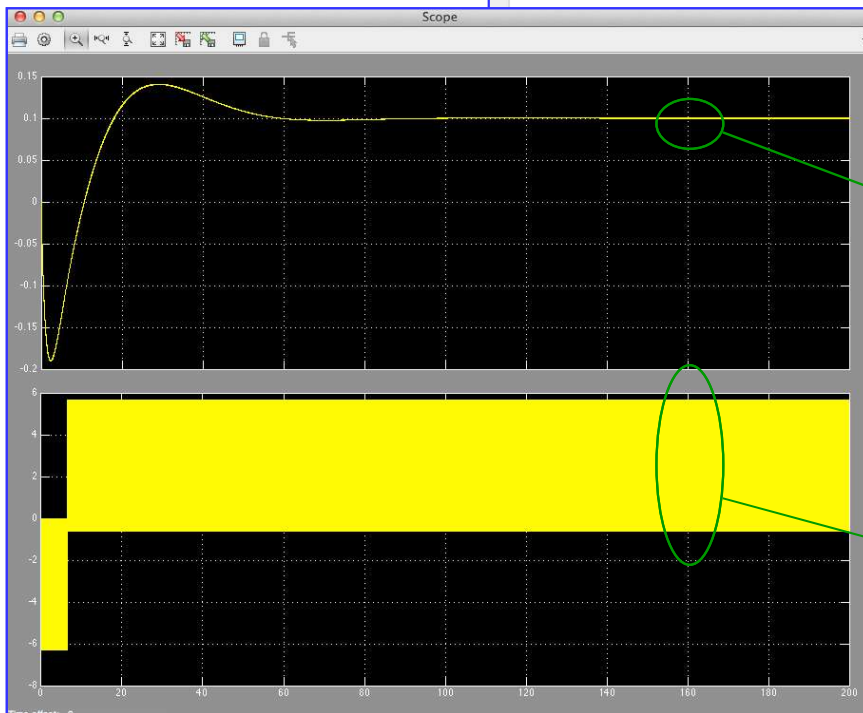$k = 1e-2$   
 $\tau_{\text{vco}} = 14.14$   
 $\tau = 1$



# Exercises

---

- Plot the **response of the output frequency to an input frequency step**, at different initial delays of the reference. Justify the result.
- Estimate the **ripple amplitude of the oscillator frequency** from **simulation** and justify quantitatively this result using **theory**.
- How does the ripple change applying a **mismatch of 20%** among the charge-pump branches?
- What if the reset delay in the PFD is **doubled**? Comment the result and draw the conclusion.