
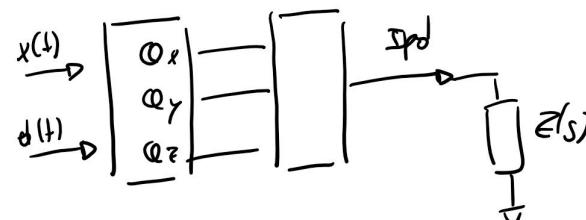
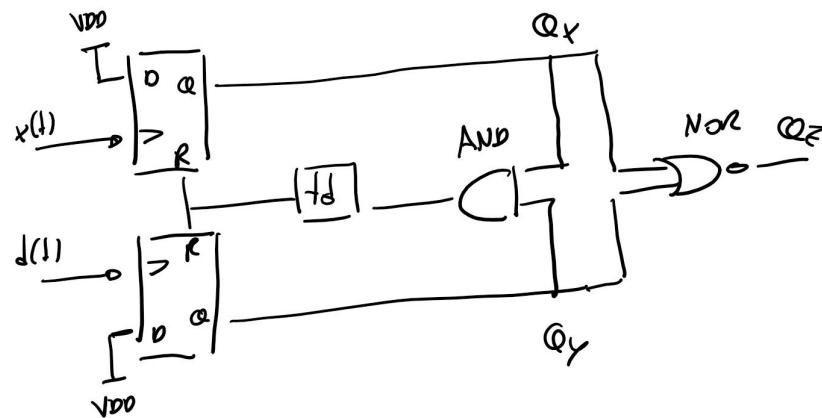


Ex 4.1

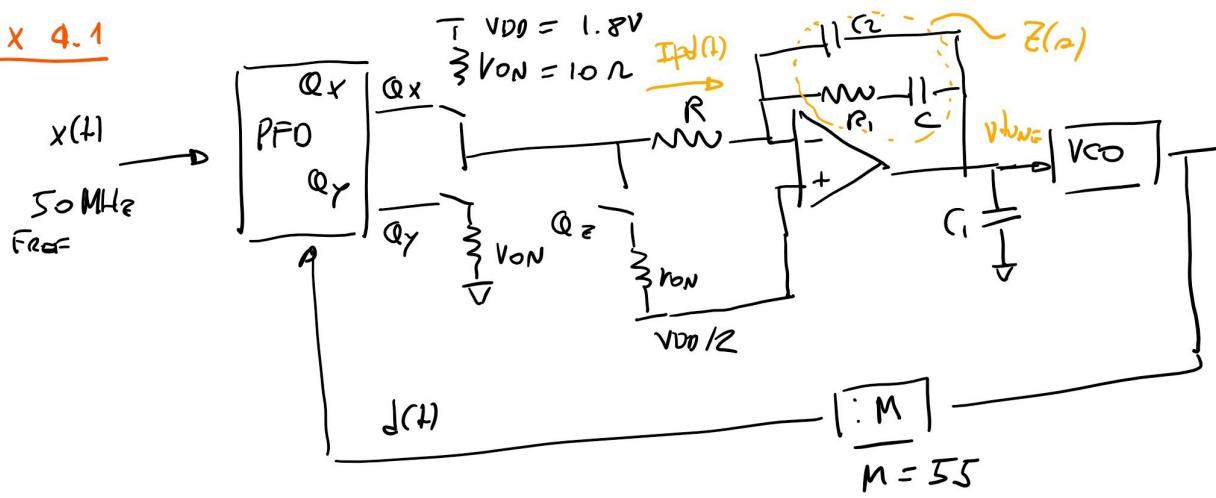


- POSSIBLE STATES OF Q_x, Q_y, Q_z


Q_x	Q_y	R	Q_z	$R = AND(Q_x, Q_y)$
0	0	0	1	$Q_z = NOR(Q_x, Q_y)$
0	1	0	0	
1	0	0	0	
1	1	1	0	

- ### RELATION BETWEEN $\theta_x, \theta_y, \theta_z$ AND θ_p
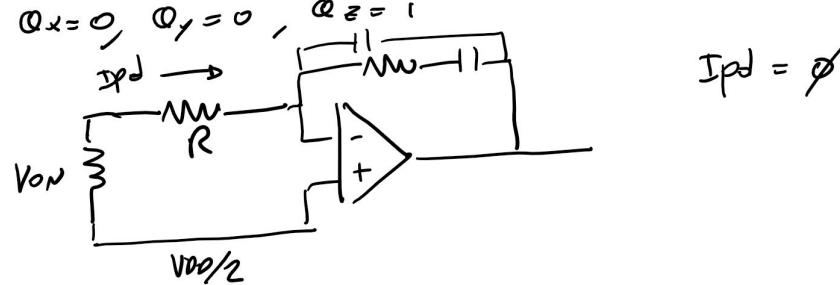
$$- \text{STATE } 1 \quad Q_x = 0, \quad Q_y = 0, \quad Q_z = 1$$




- STATE 2 $Q_x = 1, Q_y = 0, Q_z = 0$

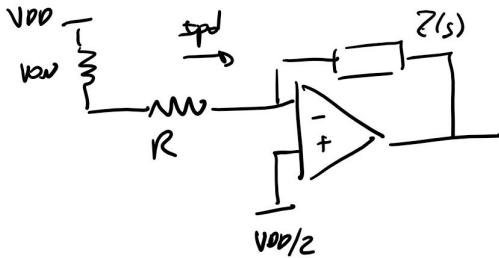

$$I_{pd} = \frac{(VDD - VDD/2)}{Von + R}$$


$$= I_{po}$$

- STATE 3 $Q_x = 0, Q_y = 1, Q_z = 0$

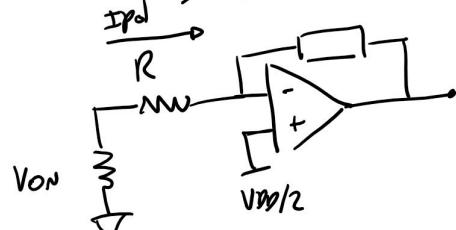

$$I_{pd} = \frac{(0 - VDD/2)}{Von + R} = -I_{po}$$

- STATE 4 $Q_x = 1, Q_y = 1, Q_z = 0$

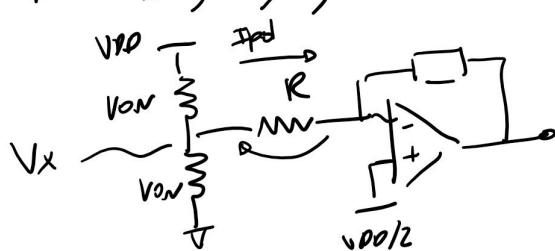



$$I_{pd} = \frac{(Vx - VDD/2)}{R}$$

$$Vx = \frac{(Von/R)}{(Von/R) + von} VDD + \frac{(Von/2) \frac{VDD}{2}}{Von/2 + R}$$



$$\sim \frac{Von}{Von + von} VDD \simeq \frac{VDD}{2}$$

$$I_{pd} \simeq 0$$

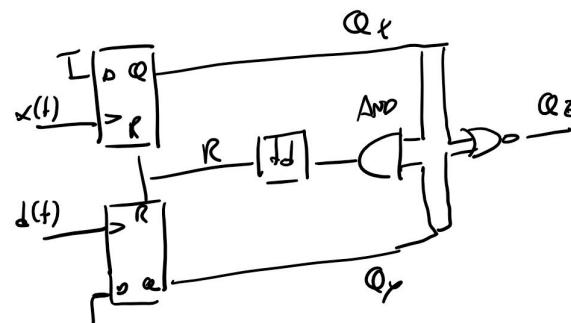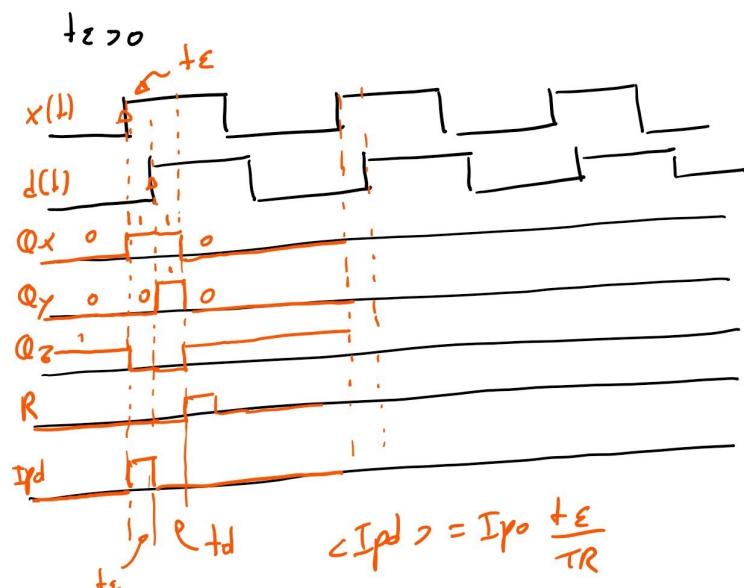
• DERIVE THE PHASE DETECTOR EQUIVALENT MODEL



Q_x	Q_y	Q_z	I_{pd}
0	0	1	0
1	0	0	I_{po}
0	1	0	$-I_{po}$
1	1	0	0

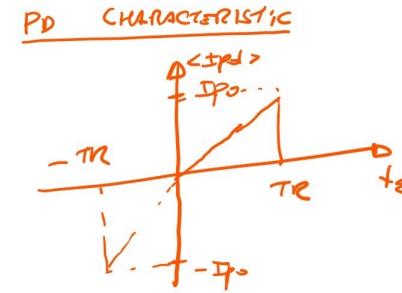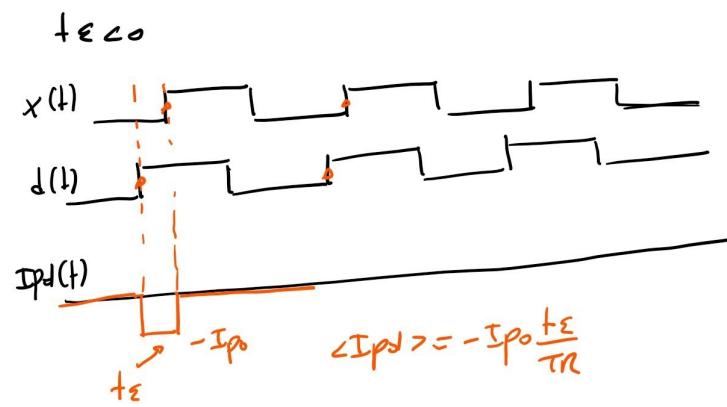

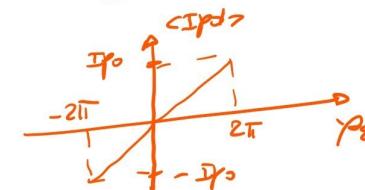
$$\gamma_\epsilon = \frac{2\pi}{Tr} + \epsilon$$




$$k_{pd} = \frac{\partial \langle Ipd \rangle}{\partial \psi_\epsilon} = \frac{Ipo}{2\pi}$$

• COMPLETE MODEL IN PHASE DOMAIN:

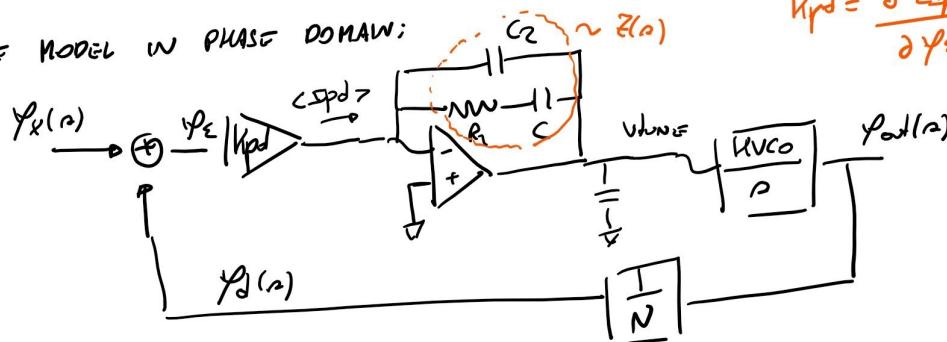

$$G_{loop}(\omega) = k_{pd} \tilde{z}(\omega) \frac{K_{VCO}}{\rho} \frac{1}{N} = k_{pd} \left[\left(R_1 + \frac{1}{\omega C} \right) // \frac{1}{\omega C_2} \right] \frac{K_{VCO}}{\omega} \frac{1}{N}$$
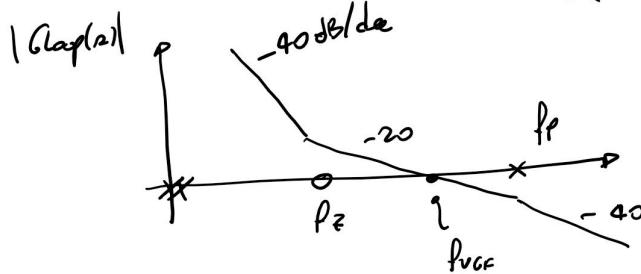
$$= k_{pd} \frac{(1 + \omega R_1)}{\omega(C + C_2) [1 + \omega(C//C_2)R_1]} \frac{K_{VCO}}{\omega} \frac{1}{N} = \frac{k}{\omega^2} \frac{(1 + \omega C_p)}{(1 + \omega C_p)}$$



$$\begin{cases} k = \frac{k_{pd} K_{VCO}}{(C + C_2) N} \\ \omega_p = L R_1 \\ C_p = R_1 (C // C_2) \end{cases}$$

a) Set R, C
closed loop poles @ 100 kHz
located @ 45° GAIN PLANE

$$1 + G_{loop}(\omega) = 0 \quad 1 + \frac{k(1 + \omega C_p)}{\omega^2(1 + \omega C_p)} = 0$$

since $f_p \gg f_{cutf}$ FOR STABILITY

$$(1 + \omega C_p) \left[1 + \frac{k(1 + \omega C_p)}{\omega^2(1 + \omega C_p)} \right] = 0 \Rightarrow (1 + \omega C_p)(\omega^2 + \omega k^2 C_p + k) = 0$$

↑
HF POLE NOT AFFECTED BY G_{loop}

$$\begin{cases} \omega^2 + n^2 \omega K + K = 0 \\ \omega^2 + \omega \frac{w_n}{Q} + w_n^2 = 0 \end{cases}$$

COMPARE WITH
CANONICAL FORM

$$w_n = 2\pi 100 \text{ kHz}$$


$$Q = \frac{\sqrt{2}}{2}$$

$$K = w_n^2$$

$$Z_2 = \frac{1}{w_n Q} = R_1 C \quad \leadsto$$

$$\begin{aligned} R_1 &= 100 \Omega \quad (\text{FROM DATA}) \\ C &= 22.51 \text{ nF} \end{aligned}$$
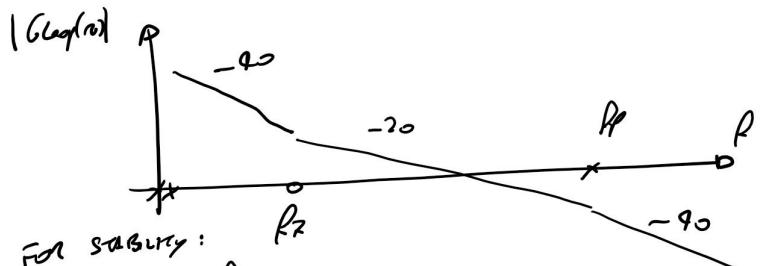
$$K = \frac{k_{pd} k_{vco}}{N(C + C_2)} = w_n^2$$



for stability: $P_F \gg P_Z$

$$\frac{1}{2\pi R_1(C//C_2)} \gg \frac{1}{2\pi R_1 C} \Rightarrow (C//C_2) \ll C$$

$$C_2 \ll C$$

$$K = \frac{k_{pd} k_{vco}}{N(C + C_2)} \approx \frac{k_{pd} k_{vco}}{NC} = w_n^2$$


$$k_{pd} = \frac{I_{po}}{2\pi} \quad \leadsto \quad I_{po} = 4.4 \text{ mA}$$

$$= \frac{(V_{DD}/2)}{R}$$


$$\leadsto [R = 199.5 \Omega]$$

b) $V_{ON} Q_x = 15 \Omega$ Set C_2 $f(\Delta f = 50 \text{ MHz}) = -80 \text{ dBc}$


- STATE 1 $Q_x=0, Q_y=0, Q_z=1$

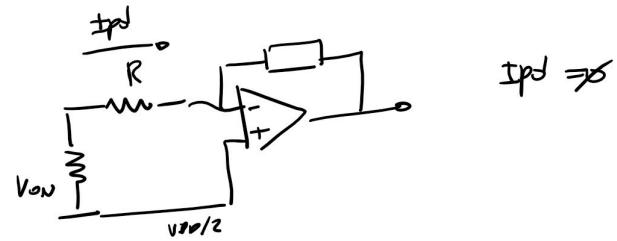


- STATE 2 $Q_x=1, Q_y=0, Q_z=0$

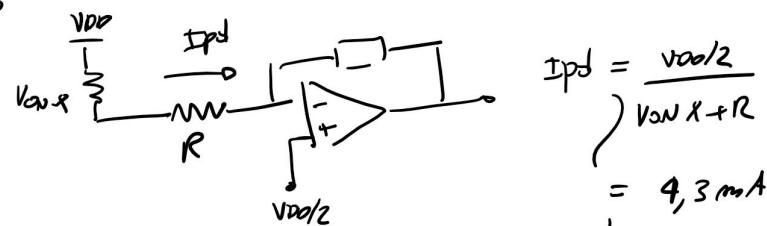

- STATE 3 $Q_x=0, Q_y=1, Q_z=0$

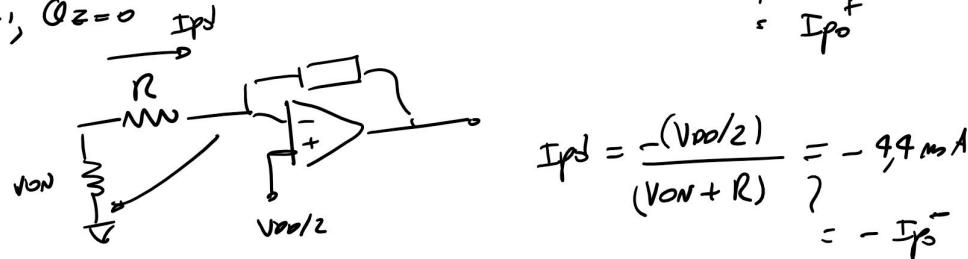


- STATE $Q_x=1, Q_y=1, Q_z=0$

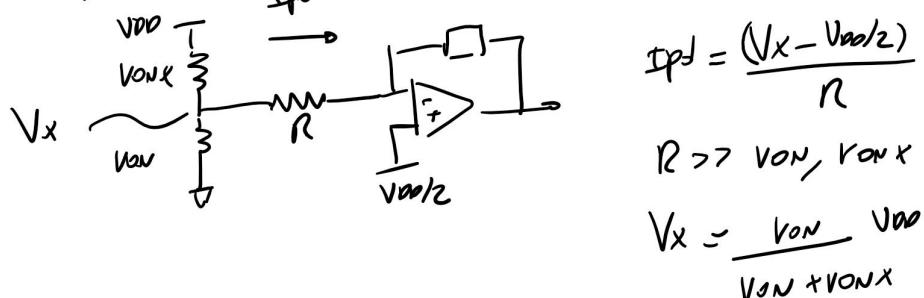

$$I_{pd} \approx -0,925 \text{ mA} = I_{os}$$


• ANALYZE STEADY STATE OPERATION OF PLL

• ideal steady state $t_c = 0$

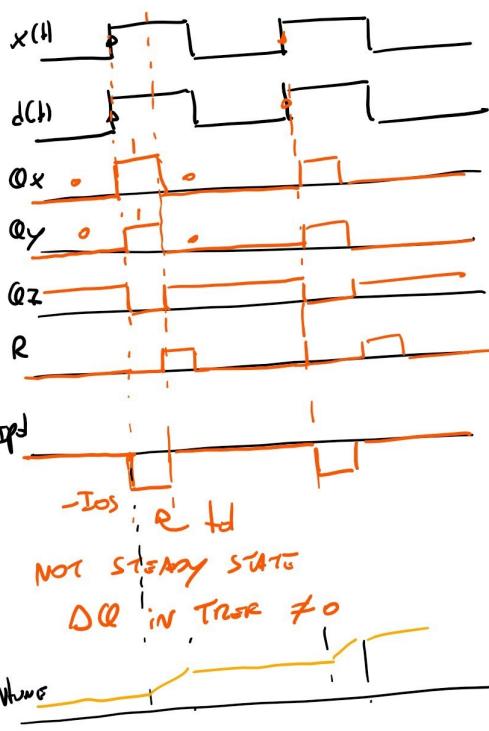

Q_x	Q_y	Q_z	I_{pd}
0	0	1	0
1	0	0	I_{pd}^+
0	1	0	$-I_{pd}^-$
1	1	0	$-I_{pd}$

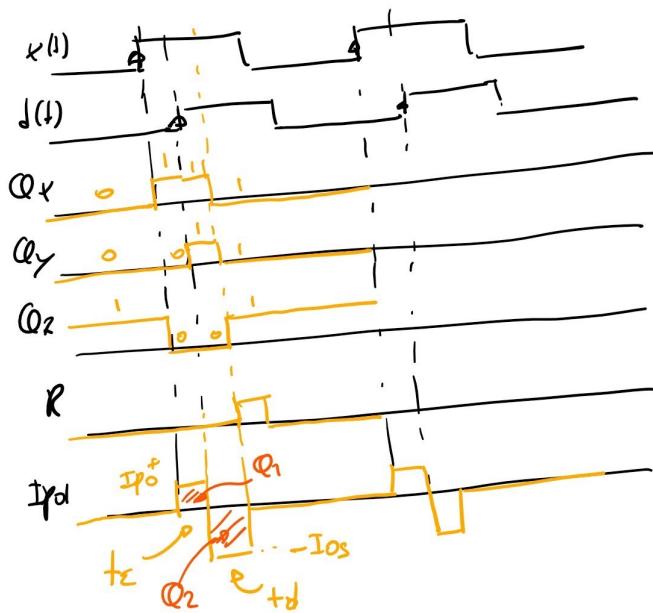REAL STEADY STATE
 $V_{mic} = \text{CONSTANT IN AVERAGE}$
 $t_c > 0$




• WE HAVE TO DERIVE $f/df = 50 \text{ MHz}$
AS FUNCTION OF THE 1ST HARMONIC OF $I_{pd}(t)$

@ STEADY STATE \rightarrow CHARGE BALANCE
 $|Q_2| = |Q_1|$

VOLUME CONSTANT IN AVERAGE

FOURIER SERIES OF PERIODIC FUNCTIONS

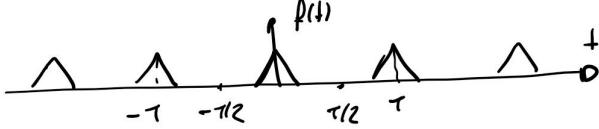


$$f(t) = f_0 + \sum_{n=1}^{+\infty} 2|y_n| \cos\left(\frac{2\pi n t}{T} + \delta y_n\right)$$

POLAR FORM

$$y_n = \frac{1}{T} \int_{-T/2}^{T/2} f(t) e^{-j\frac{2\pi n t}{T}} dt$$



RELATION BETWEEN y_n AND $F_T\{f_T(t)\}$

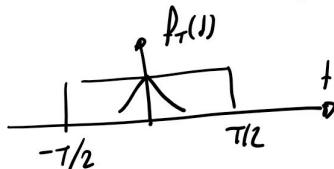


$$f_T(t) = f(t) \operatorname{rect}\left(\frac{t}{T}\right)$$

$$F_T\{f_T(t)\} = \int_{-\infty}^{+\infty} f_T(t) e^{-j2\pi f t} dt = \int_{-\infty}^{+\infty} f(t) \operatorname{rect}\left(\frac{t}{T}\right) e^{-j2\pi f t} dt = \int_{-T/2}^{T/2} f(t) e^{-j2\pi f t} dt$$

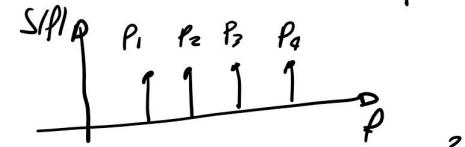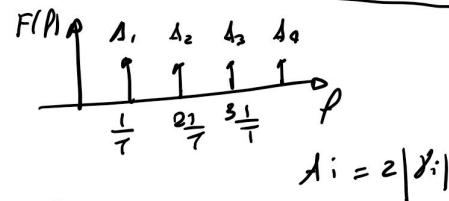
$$\boxed{y_n = \frac{1}{T} F_T\{f_T(t)\}_{f=\frac{n}{T}}}$$




$$P_i = \frac{1}{2} A_i^2 = \frac{1}{2} (2|y_i|)^2$$

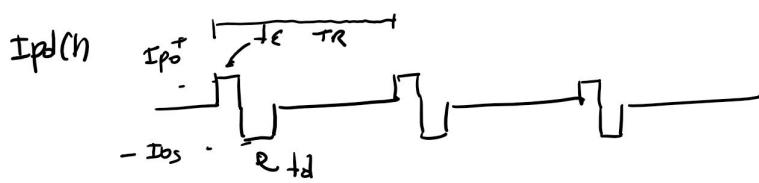

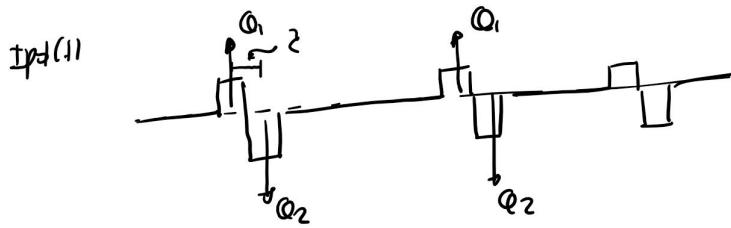Since $\frac{t\epsilon}{TR} \rightarrow 0$ and $\frac{t\delta}{TR} \rightarrow 0$



TRUNCATED VERSION OF I_{pd}

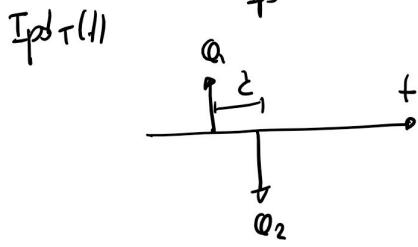

$$I_{pd\tau}(t) = |Q_1| \delta(t) - |Q_2| \delta(t-\tau) = Q [\delta(t) - \delta(t-\tau)]$$

$$|Q_1| = |Q_2|$$

WE WANT TO DERIVE THE FIRST HARMONIC

$$A_1 = 2 |\gamma_1| \quad P_1 = \frac{1}{2} A_1^2 = \frac{1}{2} (2 |\gamma_1|)^2$$

$$F_T \{ I_{pd\tau}(t) \} = Q [1 - e^{-j2\pi f \tau}]$$

since $\tau \rightarrow 0 \quad e^x \approx 1-x \text{ for } x \rightarrow 0$

$$\approx Q [1 - j2\pi f \tau]$$

$$A_1 = 2 |\gamma_1| = 2 \left| \frac{1}{T_R} F_T \{ I_{pd\tau}(t) \} \Big|_{f=\frac{n}{T_R}} \right| = 2 \left| \frac{1}{T_R} Q j2\pi \frac{n}{T_R} \tau \right|$$


$$\tau = \frac{t\epsilon}{2} + \frac{t\delta}{2}$$

$$Q = +\epsilon I_{p0+}$$

P_1 = power of 1st component of $I_{pd}(t)$

$$P_1 = \frac{1}{2} (2 |\gamma_1|)^2 = \frac{1}{2} \left(2 (F_{RCP})^2 \left(\frac{t\epsilon+t\delta}{2} \right) 2\pi (+\epsilon I_{p0+}) \right)^2$$

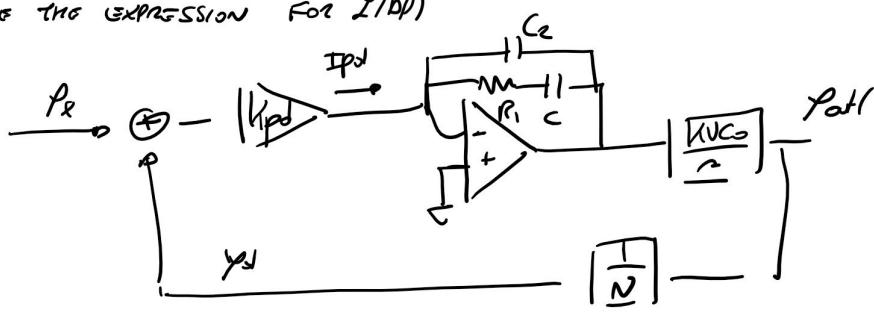• DERIVE THE EXPRESSION FOR $\frac{f}{df}$



$$\frac{f}{df} = \frac{1}{2} S_{df}(P)$$

$$\left. \begin{aligned} \frac{f}{df} &= \frac{1}{2} P_1 \left| \frac{(1 + \alpha R_1 C)}{\alpha(C + C_2)(1 + \alpha R_1(C/(C_2)))} \right|^2 \left| \frac{K_{VCO}}{\alpha} \right|^2 \left| \frac{1}{1 + G_{loop}(\alpha)} \right|^2 \\ &\quad \Delta f = 5\text{MHz} \end{aligned} \right\}$$


Graphs:

- Plot of P vs f : A curve starting at a peak frequency and decreasing towards zero.
- Plot of R_1 vs f : A curve starting at $\frac{1}{\alpha(C+C_2)}$ and decreasing towards $\frac{1}{\alpha C_2}$.
- Plot of S_{df} vs f : A curve starting at 5MHz and decreasing towards zero.

$$\begin{aligned} &= \frac{1}{2} P_1 \left| \frac{1}{\alpha C_2} \right| \left| \frac{K_{VCO}}{\alpha} \right|^2 \alpha = j 2\pi f_{REF} \\ &= \frac{1}{2} \left(2 f_{REF}^2 2\pi f_C I_{PD} C \right)^2 \left| \frac{K_{VCO}}{(2\pi f_{REF})^2 C_2} \right|^2 = -80 \text{dBc} = 10^{-8/10} \end{aligned}$$


$\Rightarrow \boxed{C_2 = 15 \text{ pF}}$
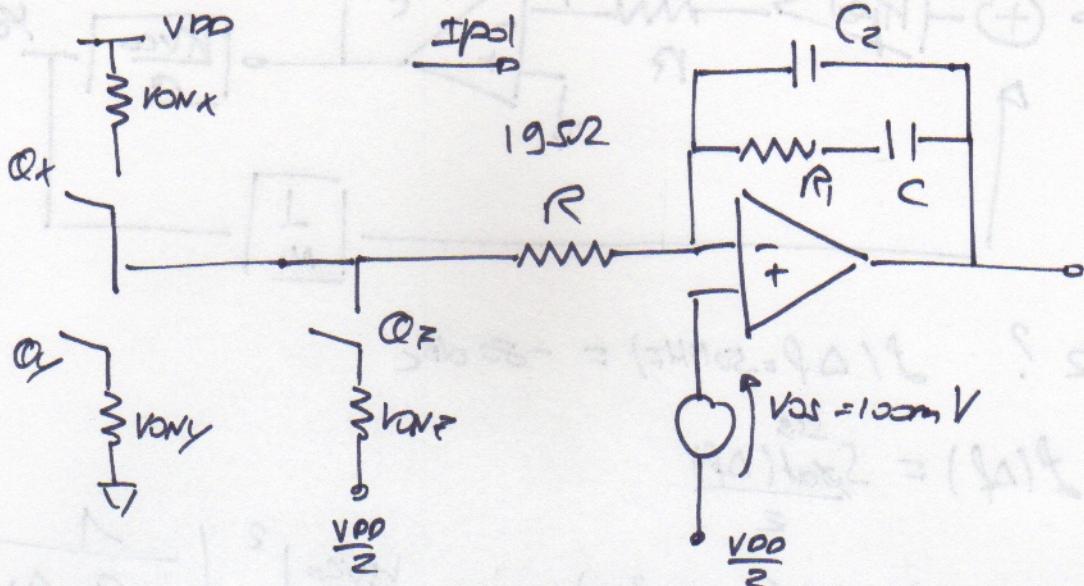
$$c) V_{ONX} = V_{ONY} = 10 \Omega, V_{OS \text{ opamp}} = 100 \text{ mV}$$




$$\bullet Q_x = 0, Q_y = 0, Q_z = 1$$
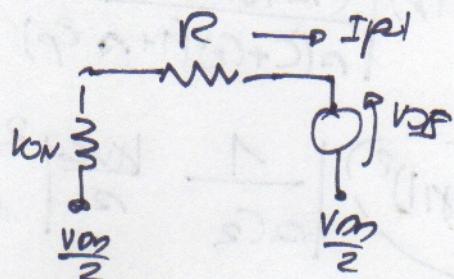
$$I_{PD1} = \frac{-V_{OS}}{(V_{ON} + R)} \approx -0.5 \text{ mA}$$




$$\bullet Q_x = 1, Q_y = 0, Q_z = 0$$

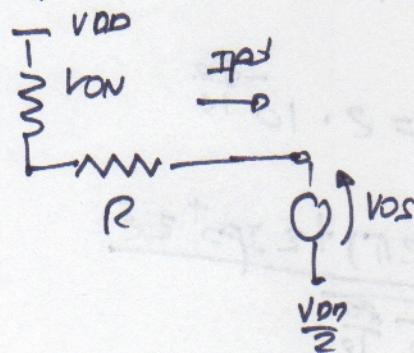


$$I_{PD1} = \frac{V_{DD} - [V_{OS} + \frac{V_{DD}}{2}]}{(V_{ON} + R)} \approx 3.92 \text{ mA} = I_P^+$$

$$\bullet Q_x = 0, Q_y = 1, Q_z = 0$$

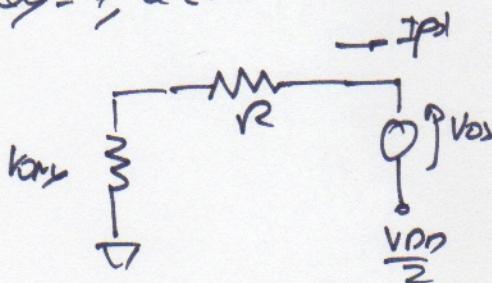


$$I_{PD1} = -\frac{(V_{DD} - V_{OS})}{(R + V_{ON})} \approx -4.9 \text{ mA}$$

$$\bullet Q_x = 1, Q_y = 1, Q_z = 0$$

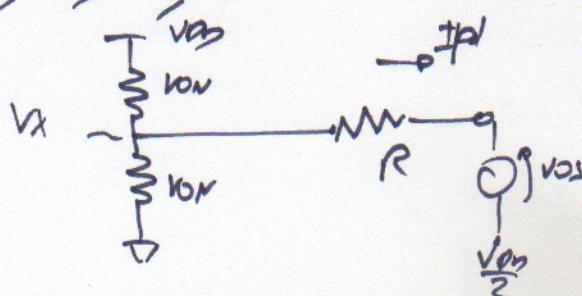


$$I_{PD1} = \frac{V_{DD} - [\frac{V_{OS}}{2} + V_{OS}]}{R} = -\frac{V_{OS}}{R} = -0.5 \text{ mA}$$

$\epsilon = 0$ (OPEN-LOOP)

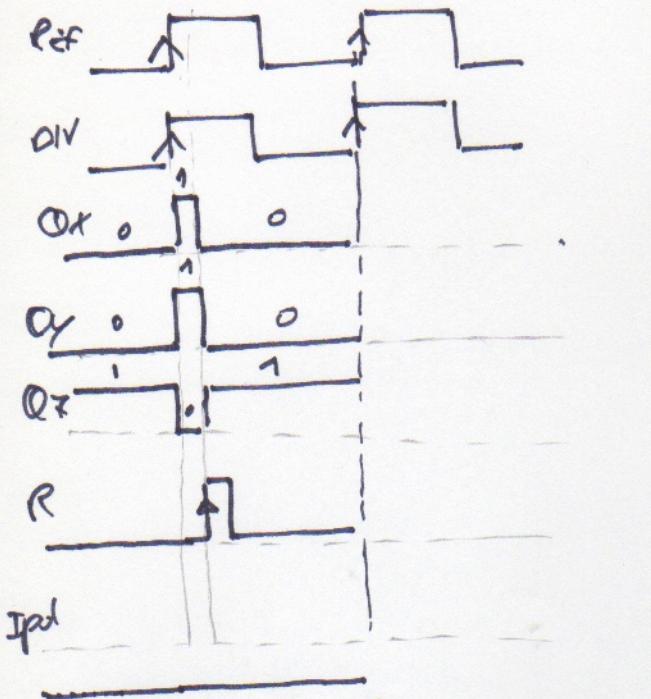

$$IL = -0.5 \text{ mA}$$

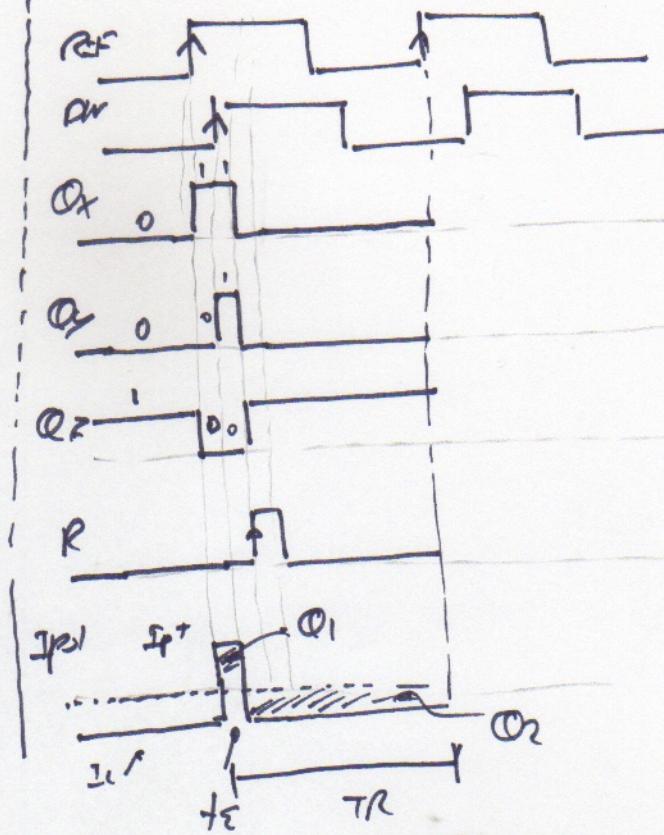$\epsilon > 0$ STEADY-STATE
CLOSED-LOOP. (5)



$$Ip^+ = 3.92 \text{ mA}$$

$$C_1 = C_2$$

$$Ip^+ + \epsilon = IL \cdot TR$$


$$\epsilon = \frac{IL \cdot TR}{Ip^+}$$

$$= 2.55 \text{ nsec.}$$

$$\rho / \Delta f = 50 \text{ MHz} = \frac{\rho_{out}^{SS13}}{2} (\rho = 50 \text{ MHz})$$

$$= \frac{1}{2} (2 |g_1|)^2 \left| \frac{1}{2\pi f_{REF} C_2} \right|^2 \left| \frac{KVC_0}{2\pi f_{REF} C_2} \right|^2 \cdot \frac{1}{2}$$

$Ipol(t)$

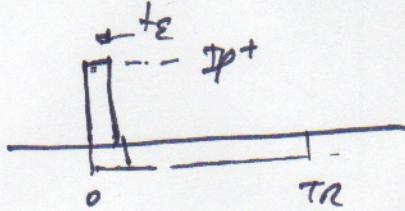


$$g_1 = Ip^+ \frac{\epsilon}{TR}$$

$$\rho / \Delta f = 50 \text{ MHz} = \frac{1}{2} (2 \cdot Ip^+ \cdot \epsilon \cdot f_{REF})^2 \frac{(KVC_0)^2}{(2\pi f_{REF})^2 C_2^2} \frac{1}{2} = -32,80 \text{ dBc}$$

T6

IMPEDANCE TRANSFORMATION:


• SERIES

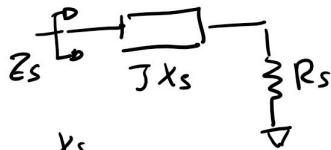

$$\Omega_s = \frac{X_s}{R_s}$$

SERIES TO
PARALLEL
TRANSFORMATION
@ ω_0

PARALLEL NETWORK

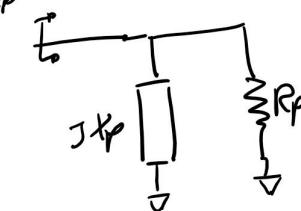

$$\Omega_p = \frac{R_p}{X_p}$$


 Ω_{ω_0}

$$Z_s(\omega_0) = Z_p(\omega_0)$$



$$\Omega_p(\omega_0) = \Omega_s(\omega_0) = \Omega_p(\omega_0) = \frac{X_s}{R_s} = \frac{R_p}{X_p}$$

$$R_p = R_s (1 + \Omega_p^2)$$

$$X_p = X_s \left(1 + \frac{1}{\Omega_p^2}\right)$$

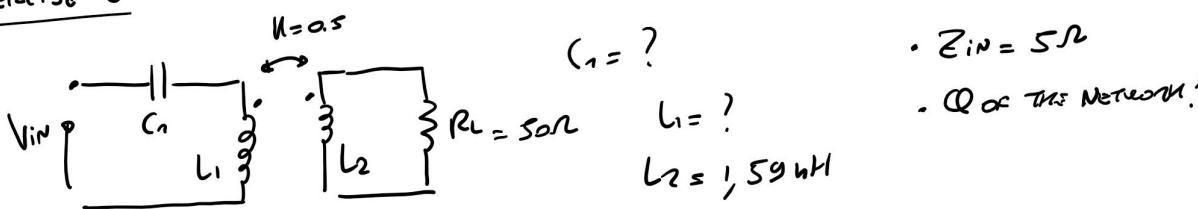EXERCISE 6

By model of the transformer:

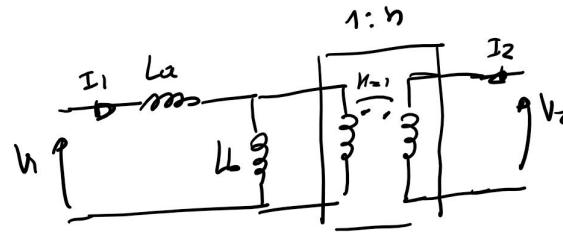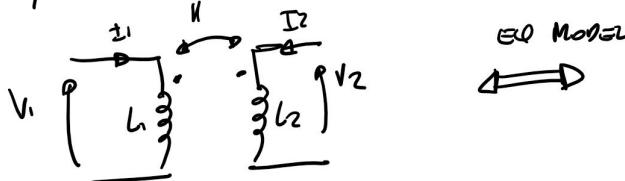

$$L_a = L_1 (1 - k^2)$$

$$L_b = L_1 k^2$$

$$L_1 = L_a + L_b$$

$$n = \frac{1}{k} \sqrt{\frac{L_2}{L_1}}$$



$$\begin{cases} V_1 = \alpha L_1 I_1 + \alpha M I_2 \\ V_2 = \alpha M I_1 + \alpha L_2 I_2 \end{cases}$$

$$M = K \sqrt{L_1 L_2}$$


$$M > 0$$

if both I_1 and I_2 ENTERS / LEAVES
the dot

• BACK TO EXERCISE

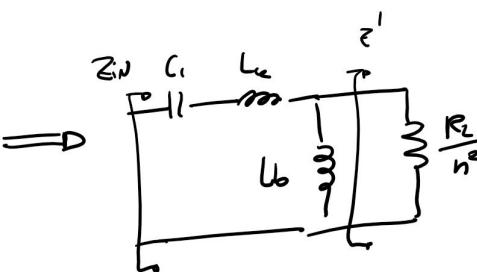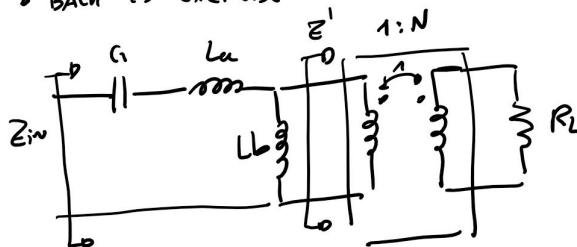


• PARALLEL TO SERIES TRANSFORMATION

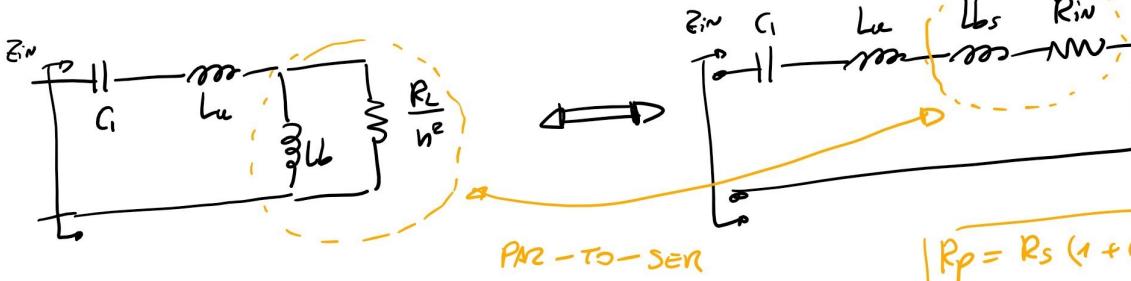

$$\left\{ \begin{array}{l} \frac{R_L}{w^2} = R_{in} (1 + Q_T^2) \\ w_0 L_b = w_0 L_{bs} \left(1 + \frac{1}{Q_T^2}\right) \\ Q_T = \frac{w_0 L_{bs}}{R_S} = \frac{R_L / w^2}{w_0 L_b} \end{array} \right.$$
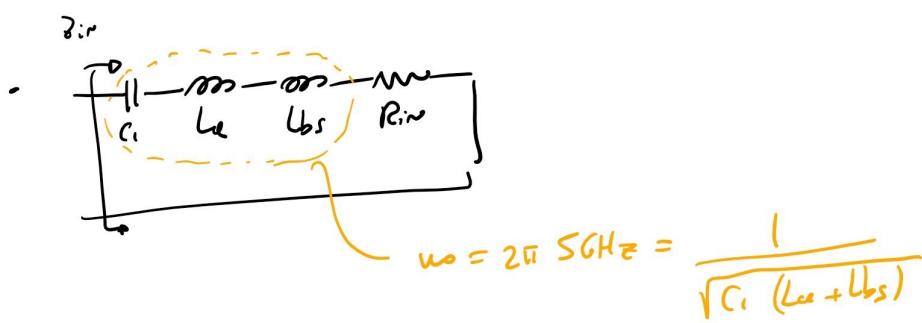
$$\boxed{\begin{aligned} R_p &= R_S (1 + Q_T^2) \\ X_p &= X_S \left(1 + \frac{1}{Q_T^2}\right) \\ Q_T &= \frac{X_S}{R_S} = \frac{R_p}{X_p} \end{aligned}}$$



$$R_{in} = 5 \Omega$$

$$\left. \begin{aligned} Q_T &= \frac{w_0 L_{bs}}{R_{in}} = \frac{(R_L / w^2)}{w_0 L_b} \\ &= \frac{R_L}{w_0 L_b K^2} = \frac{R_L \cancel{K^2 L_1}}{w_0 L_2} = 1 \\ &\text{at } 2\pi \text{ GHz} \end{aligned} \right. \quad \begin{aligned} w^2 &= \frac{1}{K^2} \frac{L_2}{L_1} \\ L_b &= L_1 K^2 \end{aligned}$$

$$L_{bs} = \frac{R_{in} Q_T}{w_0} = 159,15 \mu H$$

$$L_b = L_{bs} \left(1 + \frac{1}{Q_T^2}\right) = 318,3 \mu H$$

$$\boxed{L_1 = \frac{L_b}{K^2} = 1,273 \mu H}$$

$$L_c = L_1 - L_b = 957,75 \mu H$$


$$\boxed{C_1 = \frac{1}{w_0^2 (L_c + L_{bs})} = 909,61 \mu F}$$

$\left. \begin{aligned} \textcircled{1} \text{ of the network} &\quad \textcircled{2} \text{ at } w_0 \\ Z_{in} &= \frac{1}{R_{in} w_0 C_1} = 7 \\ &= \frac{w_0 (L_c + L_{bs})}{R_{in}} \end{aligned} \right.$

REMEMBER $Q_T \neq Q_{tot}$

• IMPEDANCE TRANSFORMATION

- SERIES

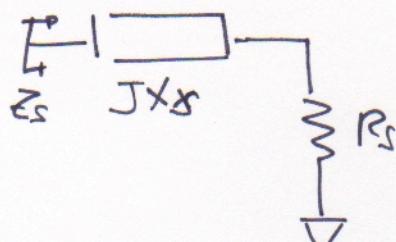


$$\Omega_s = \frac{X_s}{R_s}$$

$\xrightarrow{\text{SERIES TO PARALLEL TRANSFORMATION}}$

@ ω_0

PARALLEL

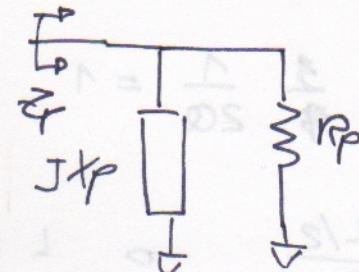

$$\Omega_p = \frac{R_p}{X_p}$$


$$Z_s(\omega_0) = Z_p(\omega_0)$$

$$\Omega @ \omega_0 = \Omega_s(\omega_0) = \Omega_p(\omega_0)$$

$$R_p = R_s (1 + \Omega^2)$$

$$X_p = X_s (1 + \frac{1}{\Omega^2})$$

EXERCISE 4.4

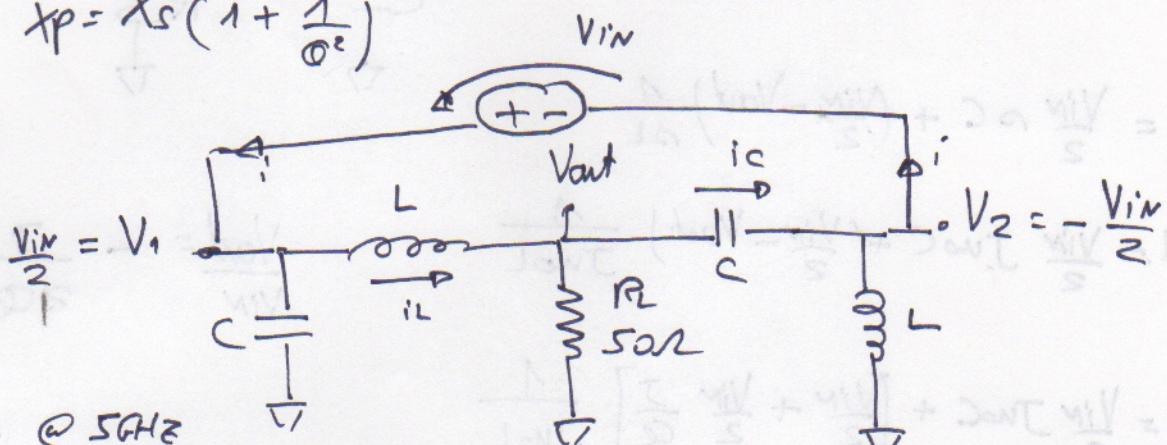

a) $L, C ?$

$$\left| \frac{V_{ant}}{V_1 - V_2} \right| = 1 @ 5\text{GHz}$$



$$\begin{cases} i = \frac{V_{in}}{2} \rho C + iL \\ i = iC - \left(-\frac{V_{in}}{2} \right) \frac{1}{\rho L} \\ V_{ant} = R_L(iL - iC) \end{cases}$$

$$\frac{V_{in}}{2} \rho C + iL = iC + \frac{V_{in}}{2} \frac{1}{\rho L}$$

$$(iL - iC) = \frac{V_{ant}}{R_L} = \frac{V_{in}}{2} \left[\frac{1}{\rho L} - \rho C \right]$$

$$\rho = J\omega_0$$
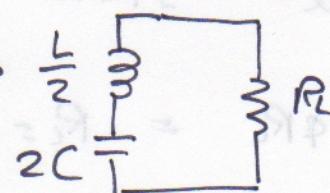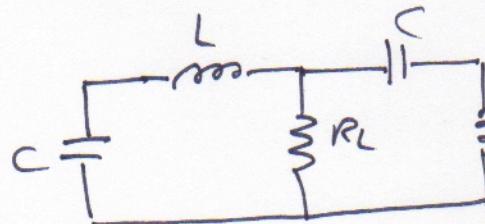
$$\frac{V_{ant}}{V_{in}} = \frac{R_L}{2} \left[\frac{1}{J\omega_0 L} - J\omega_0 C \right]$$



$$\Omega = \frac{\omega_0 L / 2}{R_L} = \frac{1}{\omega_0 2C R_L}$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{4} \left[\frac{2R_L}{J\omega L} - J\omega C R_L^2 \right] = \frac{1}{4} \left[\frac{1}{\omega Q} - \frac{J}{Q} \right] = \frac{1}{J^2 Q}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\frac{1}{2}}{\frac{1}{2Q}} = 1 \Rightarrow Q = \frac{1}{2}$$

$$Q = \frac{L/J}{R_L} \rightarrow L = 1,591 \text{ nH}$$

$$Q = \frac{1}{\omega C R_L} \rightarrow C = 636,62 \text{ pF}$$

b) DIFFERENTIAL IMPEDANCE:
@ 50Hz

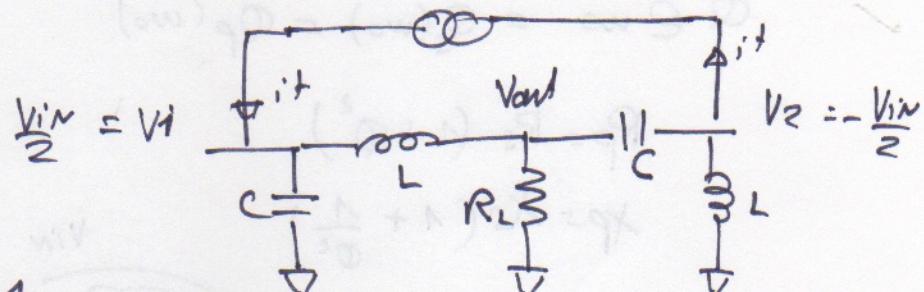

$$i_t = \frac{V_{in}}{2} \omega C + \left(\frac{V_{in}}{2} - V_{out} \right) \frac{1}{\omega L}$$

$$i_t = \frac{V_{in}}{2} J\omega C + \left(\frac{V_{in}}{2} - V_{out} \right) \frac{1}{J\omega L}$$

$$\frac{V_{out}}{V_{in}} = - \frac{J}{2Q}$$

$$i_t = \frac{V_{in}}{2} J\omega C + \left[\frac{V_{in}}{2} + \frac{V_{in}}{2} \frac{J}{Q} \right] \frac{1}{J\omega L}$$

$$= V_{in} \left[\frac{J\omega C}{2} + \frac{1}{2J\omega L} + \frac{1}{2Q\omega L} \right]$$


$$\frac{V_{in}}{i_t} = \frac{1}{\left[\frac{J\omega C}{2} + \frac{1}{2J\omega L} + \frac{1}{2Q\omega L} \right] \left(\frac{R_L}{2} \right) \frac{R_L}{R_L}}$$

$$= \frac{1}{\frac{J}{R_L Q} + \frac{1}{J R_L Q} + \frac{1}{Q^2 + R}} = \frac{1}{R_L Q} - \frac{J}{R_L Q^2} + \frac{1}{Q^2 + R}$$

$$\frac{V_{in}}{i_t} = Q^2 + R_L = R_L = 50 \Omega$$

$$\frac{R}{2} = \frac{1}{Q} = 0$$

EXERCISE 4.5

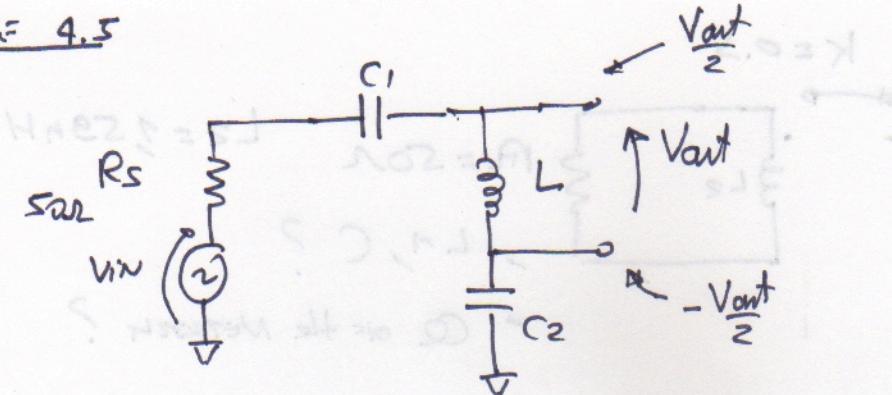

C₁, C₂, L


$$\frac{V_{out}}{V_{IN}} = 3 \text{ @ } 5 \text{ GHz}$$

- RESONANCE Freq of the network: $\omega_0 = \frac{1}{\sqrt{L(C_1/C_2)}}$

- $\frac{V_{out}}{\omega L} = -\frac{V_{out}}{2} \approx C_2 \quad \omega = j\omega \Rightarrow \frac{1}{j\omega L} = -\frac{j\omega}{2} C_2$

$$C = C_1 = C_2$$
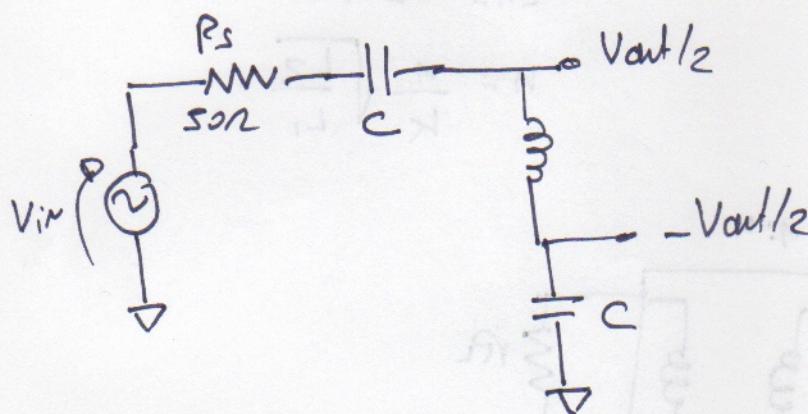
$$\omega_0 = \frac{1}{\sqrt{L \frac{C_2}{2}}}$$



$$\frac{[V_{IN} - \frac{V_{out}}{2}]}{R_S + \frac{1}{\omega C}} = -\frac{V_{out}}{2} \omega C$$

$$\frac{(V_{IN} - \frac{V_{out}}{2}) \omega C}{(1 + \omega C R_S)} = -\frac{V_{out}}{2} \omega C$$

$$V_{IN} - \frac{V_{out}}{2} = -\frac{V_{out}}{2} - \frac{V_{out}}{2} \omega C R_S$$

$$\left| \frac{V_{out}}{V_{IN}} \right| = \frac{2}{\omega_0 C R_S} = 3 \Rightarrow$$

$$C = \frac{2}{3} \frac{1}{\omega_0 R_S}$$

$$= 424,41 \text{ pF}$$

$$L = \frac{1}{\frac{C}{2} \omega_0^2} = 4,7754 \text{ H}$$