

RF Circuit Design


28




Static Phase Error

(residual error at steady state between ϕ_{out} and ϕ_{in})

ω_{ref}

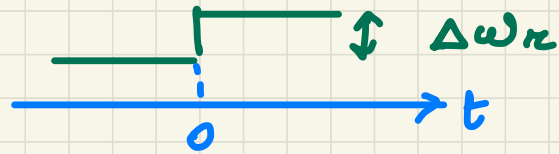


ω_{out}

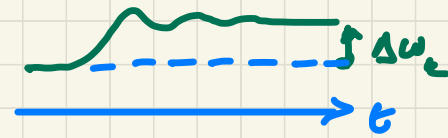

- What is the value of ϕ_E at steady state?




$$F(f=0) = 1$$

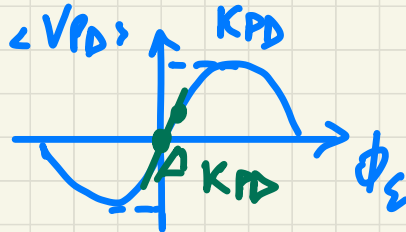


$$\begin{aligned} \phi_E &= \frac{\Delta\omega_{ref} / K_{VCO}}{K_{PD}} \\ &= \frac{\Delta\omega_{ref}}{K} \end{aligned}$$

- Why the static ϕ_E is not null, although $|LG| \rightarrow \infty$ at DC?
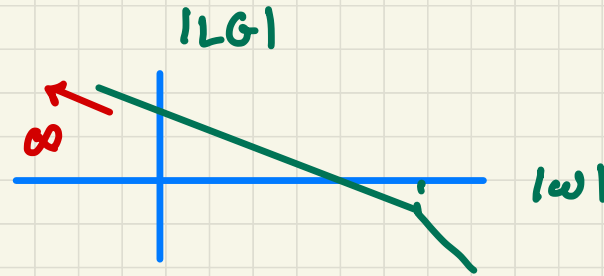
$$LG = \frac{1}{s} \cdot \frac{1}{1+s\tau}$$




voltage amplifier analogy

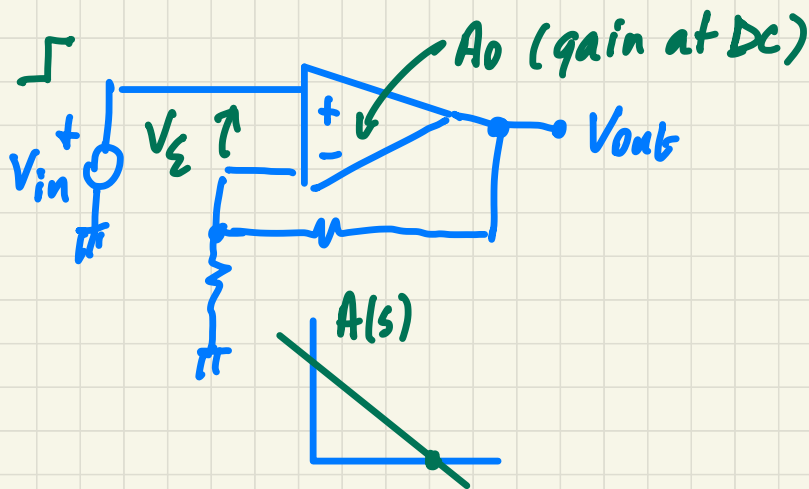

$$V_E = \frac{V_{out}}{A_0} \rightarrow 0$$

finite

∞

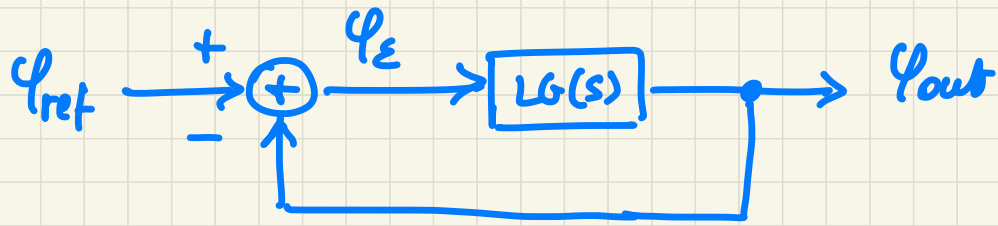

$$\underbrace{\lim_{t \rightarrow \infty} \varphi_E(t)}_{\text{Static phase error}} = \lim_{s \rightarrow 0} s \cdot \Phi_E(s)$$


$$\frac{\Phi_E(s)}{\Phi_{ref}(s)} = \frac{1}{1 + LG(s)} = 1 - T(s)$$

$$LG(s) = \frac{K}{s} \cdot \frac{1}{1+s\tau} \Rightarrow = \frac{s(1+s\tau)}{s(1+s\tau) + K}$$

- case of FREQUENCY step

$$\omega_{\text{ref}}(t) = \Delta\omega_r \cdot u(t)$$


ω_{ref}

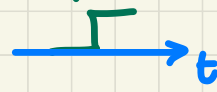

$$u(t) = \begin{cases} 1 & t > 0 \\ 0 & t < 0 \end{cases}$$

$$\Rightarrow \Omega_{\text{ref}}(s) = \frac{\Delta\omega_r}{s}$$
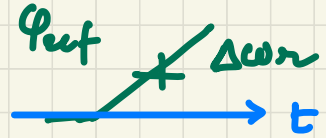
$$\Rightarrow \Phi_{\text{ref}}(s) = \frac{\Omega_{\text{ref}}(s)}{s} = \frac{\Delta\omega_r}{s^2}$$



$$\Phi_{\varepsilon}(s) = \frac{\Delta\omega_r}{s^2} \cdot \frac{s(1+s\tau)}{s(1+s\tau) + K}$$

$$\lim_{s \rightarrow 0} s \cdot \Phi_{\varepsilon}(s) = \lim_{s \rightarrow 0} \cancel{s} \cdot \frac{\Delta\omega_r}{\cancel{s^2}} \cdot \frac{\overset{0}{\cancel{s(1+s\tau)}}}{\underbrace{s(1+s\tau) + K}_{\rightarrow 0}} = \frac{\Delta\omega_r}{K}$$

$$\lim_{t \rightarrow \infty} \varphi_{\varepsilon}(t) = \frac{\Delta\omega_r}{K}$$

static phase error is not NULL

- case of phase step $\varphi_{ref} = \frac{\Delta\phi}{s}$


$$\lim_{t \rightarrow \infty} \varphi_E(t) = \lim_{s \rightarrow 0} s \Phi_E(s) = \lim_{s \rightarrow 0} \textcircled{s} \cdot \frac{\Delta\phi}{s} \cdot \frac{s(1+s\tau)}{s(1+s\tau)+K} = 0$$

static phase error is null


How can we build a PLL with zero static φ_E after an input frequency step?

?

FLL (freq. locked loop)

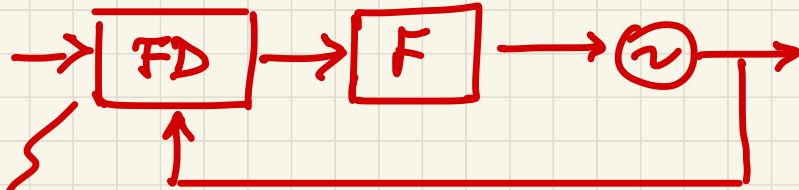

frequency detector

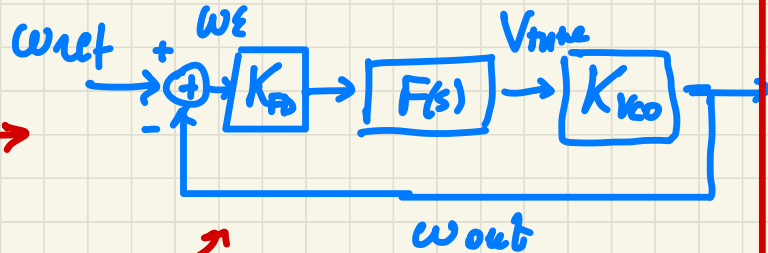

FLL model

no integrator!
→ no good

In general: LG has n integrators and ϕ_{ref} is of m -th order

$$\lim_{t \rightarrow \infty} \varphi_{\varepsilon}(t) = \lim_{s \rightarrow 0} \underbrace{\frac{\Delta}{s^m}}_{\phi_{ref}} \cdot \underbrace{\frac{s^n H(s)}{s^n H(s) + K}}_{\frac{1}{1+LG}} =$$

$$LG(s) = \frac{K}{s^n} \cdot \frac{1}{H(s)}$$

$$H(s) \neq 0 (s \rightarrow 0)$$


$$= \lim_{s \rightarrow 0} \frac{\Delta}{K} \cdot s^{n-m+1} = \begin{cases} \frac{\Delta}{K} & n=m-1 \\ 0 & \frac{n > m-1}{n \geq m} \end{cases}$$

static (phase) error is zero


IF the # of integrators in $LG(s)$ is at least equal to the order of the input perturbation

TYPE of a FEEDBACK SYSTEM is # of INTEGRATORS in LG

Phase Noise in PLLs

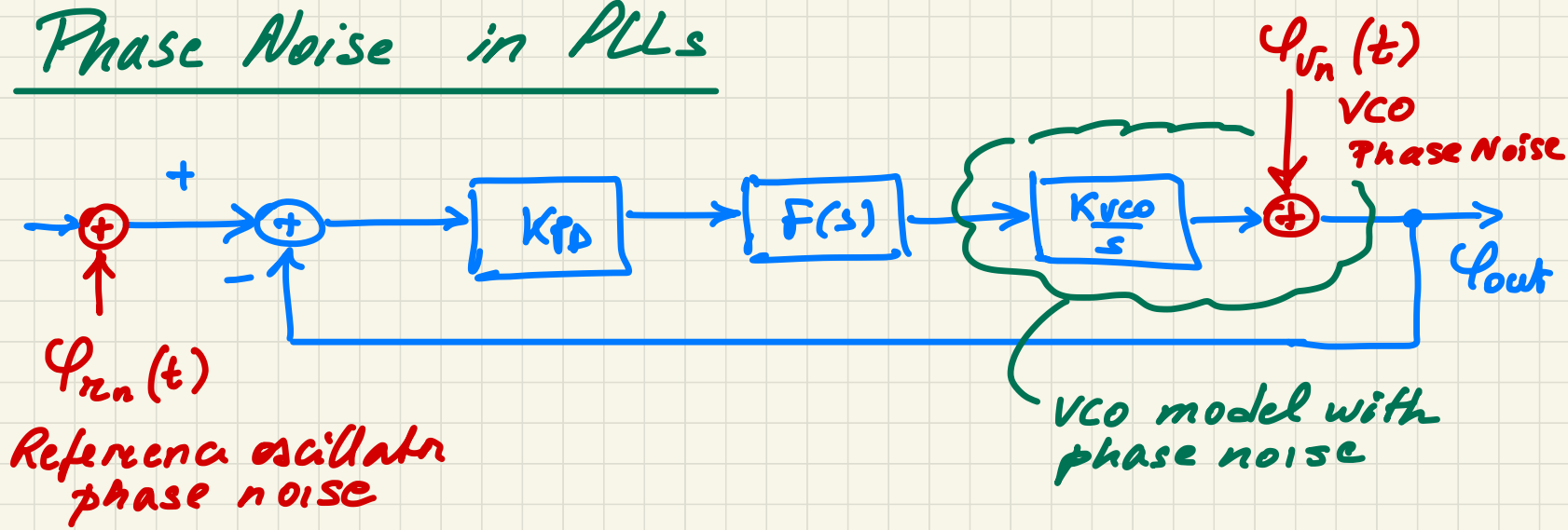


$$S_{\phi_{out}}(f) = S_{\phi_{rn}} \cdot \underbrace{|T(f)|^2}_{\text{low-pass}} + S_{\phi_{vn}} \cdot \underbrace{|1-T(f)|^2}_{\text{high pass}}$$

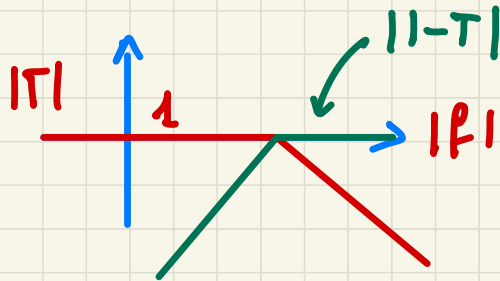

$$\phi_{rn} \rightarrow \phi_{out} : \frac{1}{1+LG} = 1-T(s)$$



Intuitive meaning: $S_{\phi_{out}}(f) = S_{\phi_{ref}} \cdot \underbrace{|T(f)|^2}_{\text{low-pass}} + S_{\phi_{vco}} \cdot \underbrace{|1-T(f)|^2}_{\text{high-pass}}$

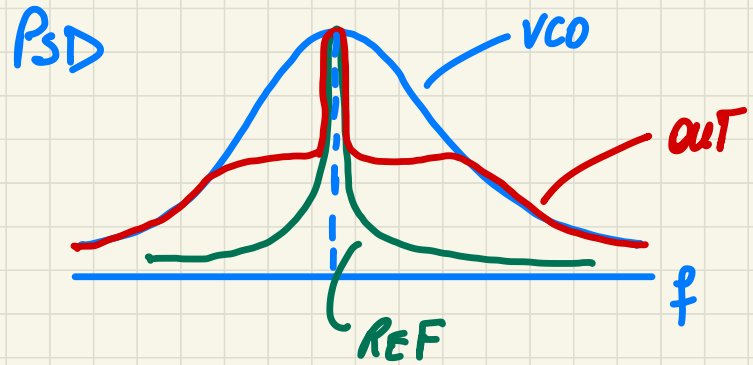- within PLL BW : the VCO follows the phase noise of the reference clock
- out-of-PLL-BW : the VCO follows its own phase noise



Capture Range
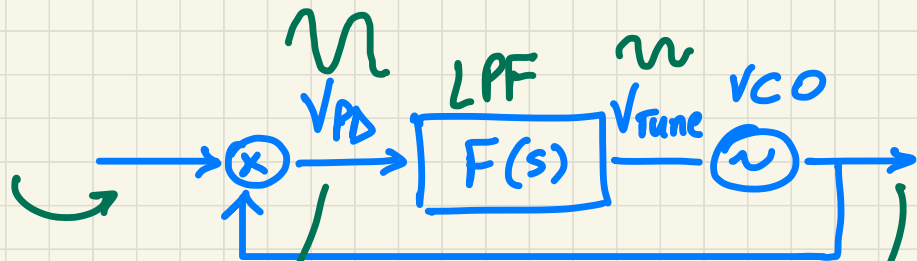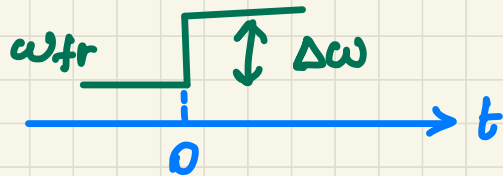
$$\cos \left(\underbrace{\omega_{fr} + \Delta\omega}_{\omega_{ref}} t \right)$$



$$\sin \left(\omega_{fr} t + \int_{-\infty}^t K_{VCO} V_{Tune}(t') dt' \right)$$

Let's neglect this term

$$V_{PD} \approx K_{PD} \cdot \sin [\Delta\omega t - o.t.]$$

$$V_{Tune} \approx K_{PD} \cdot |F(\Delta\omega)| \cdot \underbrace{\sin [\Delta\omega \cdot t + \phi F(\Delta\omega)]}_{1.1 \leq 1} \Rightarrow$$

$$|V_{\text{tune}}| \leq K_{PD} \cdot |F(\Delta\omega)|$$

\Downarrow

$$\left| \frac{\Delta\omega}{K_{VCO}} \right| \leq K_{PD} \cdot |F(\Delta\omega)|$$

\Downarrow

$$\Delta\omega_c = \underbrace{K_{VCO} \cdot K_{PD}}_K \cdot |F(\Delta\omega_c)|$$

CAPTURE or
HOLD RANGE

\rightarrow capture range in general \leq lock range