

# Questions for the Oral Examination

## *RF Circuit Design*

Salvatore Levantino  
Dipartimento di Elettronica e Informazione  
Politecnico di Milano

Year 2020/21

### **RF Front-end Architectures**

1. Effects of distortion.
2. Two-tone test and third-order intercept point (IIP3).
3. Theorem of maximum power transfer and its application to the impedance matching of amplifiers. Definition of power gains.
4. Matching networks: Resonant networks.
5. Matching networks: Transformers.
6. Noise figure of lossy circuits and cascaded systems.
7. *RF receivers*: Sensitivity and dynamic range.
8. *Heterodyne receivers*: Advantages. Image problem and filtering. Selectivity/Sensitivity trade-off. Block schematic from antenna to matched filter.
9. *Heterodyne receivers*: Problem of half-IF (IF/2).
10. Second-order nonlinearity. Intercept point IIP2 and link with 2nd-order harmonic distortion.
11. *Dual-IF receivers*: Architecture, advantages and drawbacks. Comparison with single-IF architecture.

12. *Zero-IF receivers*: Architecture, advantages and drawbacks. DC offsets and cancellation techniques.
13. *Zero-IF receivers*: Impact of I/Q mismatches on SNR. Impact of LO leakage.
14. *Image-reject receivers*: Shift-by-90 operation. Hartley architecture and effect of mismatches and Image-Rejection Ratio (IRR).
15. *Image-reject receivers*: Weaver architecture: advantages and drawbacks.
16. *Transmitters*: Effect of I/Q mismatches. Direct-conversion architecture.
17. *Transmitters*: Two-step transmitters. Single-Sideband (SSB) mixer.

## Frequency Synthesizers

18. AM and FM disturbances of a carrier. Relationship between phase spectrum and voltage spectrum of the carrier.
19. Effects of phase noise in RF receivers and transmitters: EVM degradation. Reciprocal mixing in presence of blockers.
20. Phase detectors based on multiplier. Derivation of the phase model of the PLL. Nonlinear differential equation.
21. *Second-order PLLs*: Analysis of stability and transfer functions. Static phase error after  $n$ -th order input signal, frequency response.
22. *Second-order PLLs*: Frequency tracking and lock acquisition.
23. *Charge-pump PLLs*: Phase-frequency detector, phase-domain model, stabilizing zero, analysis of loop dynamics.
24. Limits of validity of the continuous-time model of PLLs.
25. Sources of ripple in a PLL. Reference spur problem in an integer- $N$  loop. Methods to reduce the level of reference spur.
26. Design and simulation of a PLL.

## RF Circuits

27. *LNAs*: Scattering parameters, insertion loss, reverse isolation, stability, linearity. Methods to increase reverse isolation.
28. *LNAs*: MOS noise model. Common-gate and shunt-feedback LNA topology.
29. *LNAs*: Inductor-degenerated topology.
30. *LNAs*: Noise canceling technique and application to shunt-feedback topology.
31. *Oscillators*: Feedback model and Barkhausen criterion. Negative-resistance model. Amplitude stabilization methods. Oscillation startup and effective gain.
32. *Oscillators*: Frequency stabilization. Effect of loop delay in oscillators. Meaning of quality factor in oscillators.
33. *Oscillators*: Phase Noise calculation in LC oscillators.
34. *Oscillators*: Noise/Power Trade-off.
35. *Oscillators*: Circuit topologies of voltage-controlled oscillators (VCOs). Noise on tuning voltage: calculation of FM noise.
36. *Oscillators*: Single-transistor and differential LC oscillator topologies: analysis with feedback and negative-resistor model.
37. *Oscillators*: Design and simulation of an RF oscillators in CMOS.
38. *Mixers*: Return-to-zero passive mixers in CMOS, conversion gain, noise.
39. *Mixers*: Single-balanced and double-balanced topologies, port-to-port isolation.
40. *Mixers*: Active mixers in CMOS, conversion gain, noise, port-to-port isolation.