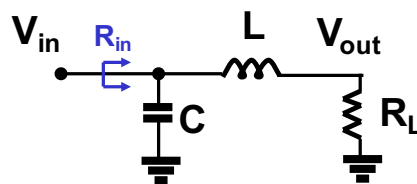


Tutorial T6


T6.1 Let us consider the L-match network in figure, where $R_L=50\Omega$.



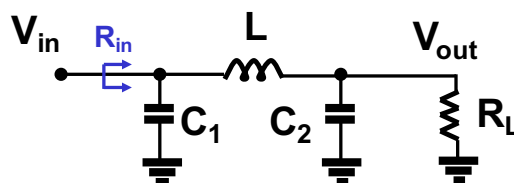- a) Size L and C in order to obtain $R_{in}=100\Omega$ at 5 GHz. What is the Q of the network?
- b) Driving the input port of the network with a current source, evaluate the complex transimpedance V_{out}/I_{in} at 5GHz.


[Solution: a. $C = 318\text{fF}$, $L = 1.59\text{nH}$; b. $V_{out}/I_{in} = 50\Omega - j50\Omega$]

T6.2 Let us consider the π -match network in figure, where $R_L=50\Omega$. Size L, C_1 and C_2 in order to obtain $R_{in}=100\Omega$ at 5GHz, and a quality factor of the resulting network equal to $Q=5$.




[Solution: a. $C_1 = 955\text{fF}$, $C_2 = 1.274\text{fF}$, $L = 1.59\text{nH}$]

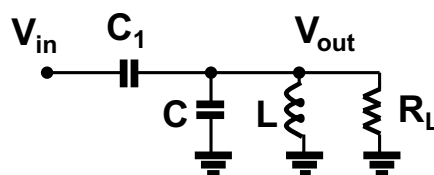T6.3 Let us consider the impedance transformation network in figure. Assuming $R_L=50\Omega$ and $C=2\text{pF}$, size L and C_1 to obtain an equivalent input impedance of 5Ω at 5GHz. What is the quality factor of the network?



[Solution: $L = 258\text{pH}$, $C_1 = 2.12\text{pH}$, $Q = 3$]

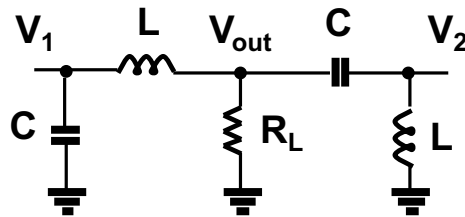
T6.4 We want to design a differential to single-ended signal converter. Let us consider the circuit in figure, where $R_L=50\Omega$.



- Find the values of L and C to have a gain $|V_{out}|/|V_1-V_2| = 1$ at 5GHz.
- Evaluate the differential impedance between V_1 and V_2 at 5GHz.


[Solution: a. $L=1.59\text{nH}$, $C=637\text{fF}$; b. $R_{diff}=50\Omega$]

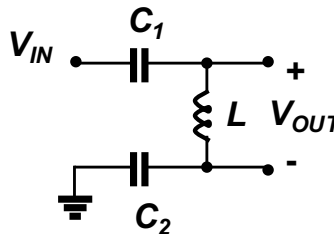T6.5 We want to design a single-ended-to-differential converter of a sinusoidal signal from V_{IN} to V_{OUT} , using the circuit in figure. Assuming a 50Ω source resistance for V_{IN} , set C_1 , C_2 , and L to achieve differential output and $V_{OUT}/V_{IN} = 3$ at 5GHz.



[Solution: $C_1 = C_2 = 424\text{fF}$, $L = 4.78\text{nH}$]

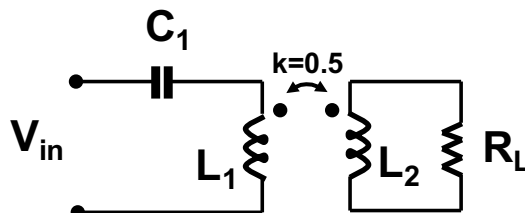T6.6 Let us consider the impedance-matching network in figure, based on a real transformer. Given a coupling factor $k=0.5$ between primary and secondary windings, $L_2 = 1.59\text{nH}$ and $R_L=50\Omega$, size L_1 and C_1 to obtain an equivalent input impedance of 5Ω at 5GHz. What is the Q of the resulting network?



[Solution: $L_1 = 1.237\text{nH}$, $C_1 = 909.5\text{fF}$, $Q=7$]