


RF Circuit Design**Prof. Salvatore Levantino**Available time: 90 minutes

Jun. 26, 2018

Final Test**Problem #1**

Assume the FETs' threshold voltage $V_t = 0.4\text{V}$, $\mu_n C_{ox}/2 = 0.2\text{mA/V}^2$, and $(W/L)_1 = 125$. Let $V_{dd} = 1.2\text{V}$, $I_1 = 1\text{mA}$, $R_S = 50\Omega$. Let $C_b = 1\text{pF}$, $R_b = 10\text{k}\Omega$ (Consider R_b only to determine the bias point and assume it to be very large otherwise). Let the bypass capacitances: $C_{b1} = C_{b2} = 100\text{pF}$. Assume the transformer to be real at DC and ideal at any other frequency.

- Derive the expressions of the **input impedance** at port "in" and the **voltage gain** (V_{out}/V_{in}) and set the **value of** $(W/L)_2$ to ensure input matching at 2.4GHz.
- Set the **values of** $(W/L)_3$ and R_F to have gain (V_{out}/V_{in}) equal to +20dB and to cancel the thermal noise of **M1** at "out".
- Recalculate the value of $(W/L)_3$ and R_F to have gain equal to +20dB and to cancel the thermal noise of **M2** at "out".

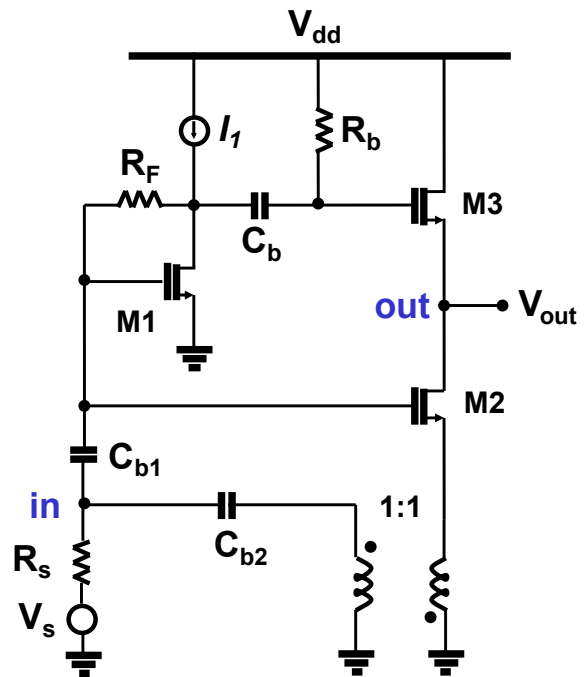
**Sol.:**

- a) $Z_{in} = 1/(g_{m1} + 2g_{m2})$, thus matching: $g_{m2} = 1/(4R_S)$. Gain is $V_{out}/V_{in} = 1 - g_{m1}R_F - 2g_{m2}/g_{m3}$;
 b) M1 noise gets cancelled if $v_{out} = v_1[1 - R_{eq}/(R_{eq} + R_F)g_{m2}/g_{m3}] = 0$, where $R_{eq} = 2R_S/3$; thus, $g_{m3} = 1/(2R_S + 3R_F)$. Under that condition, $V_{out}/V_{in} = -2R_F/R_S$, thus $R_F = 250\Omega$.

Problem #2

Consider the oscillator in figure and let $V_{dd} = 1\text{V}$, $R = 1\text{k}\Omega$, $L = 2\text{nH}$, $C = 2\text{pF}$, $I_0 = 1\text{mA}$. The r_o of M1 FETs is $1\text{k}\Omega$. Neglect the r_o of the tail FET.

- Calculate the g_m of the FETs **M1** for a gain margin of the oscillation startup equal to 2.
- Calculate the **differential oscillation amplitude** at *outp*, *outn* in **two cases**: (i) with $I_N(t) = 0$ and (ii) with $I_N(t) = 0.5\text{mA} \cdot \cos(2\omega_0 t)$, where ω_0 is the angular frequency of oscillation.

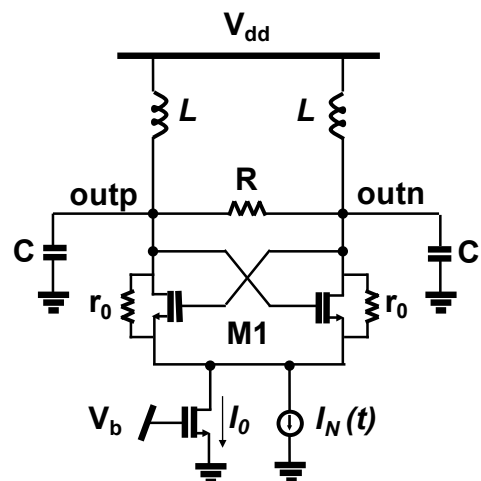**Sol.:**

- a) **Startup:** $2 \cdot (2/g_m) = (2r_o) \parallel R$, $g_m = 6\text{mS}$;
 b) (i) $A_0 = (2/\pi)I_0 \cdot (2r_o) \parallel R = 425\text{mV}$, (ii) $A_0 = [(2/\pi)I_0 + I_{Np}/\pi] \cdot (2r_o) \parallel R = 531\text{mV}$.