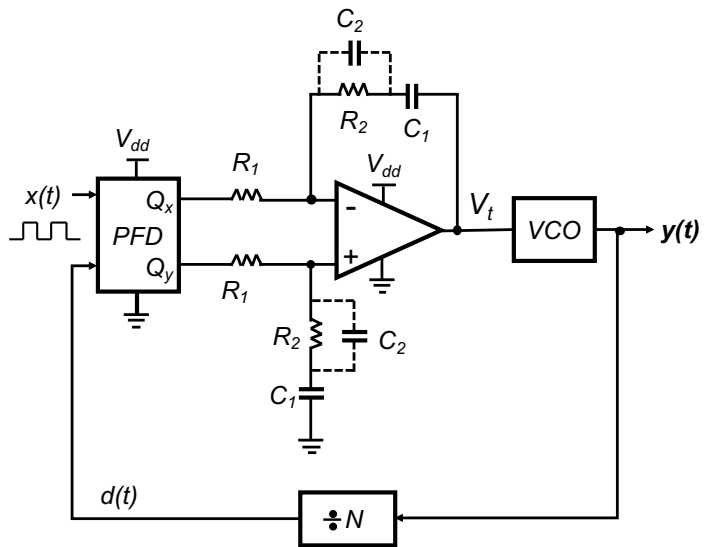


RF Circuit Design**Prof. Salvatore Levantino**Available time: 120 minutesApril 22nd, 2021**Mid-term Test****Problem #1**

Assume that $x(t)$ and $d(t)$ are square-wave signals between 0V and $V_{dd} = 2.5\text{V}$, with $x(t)$ being a 20MHz signal. The VCO has 5GHz free-running frequency and 500MHz linear tuning range from 0V to V_{dd} . Let $R_2 = 1\text{k}\Omega$, $N = 261$.


- Neglect the capacitors C_2 ($C_2=0$) and **calculate the values of R_1 and C_1** to have 50kHz loop bandwidth and maximally flat response from input to output.
- If the Op-Amp has input-referred voltage offset of 100mV, calculate **the value of the capacitor C_2** which is needed to keep the level of the reference spur at -50dBc.
- Assuming that the Op-Amp has an input-referred voltage noise of $20\text{nV}/\sqrt{\text{Hz}}$, calculate the **value of the output phase noise \mathcal{L}_y at 1kHz offset from the carrier**.



[Sol.: a) $C_1 = 4.5\text{nF}$, $R_1 = 4.3\text{k}\Omega$; b) $C_2 = 670\text{pF}$; c) $\mathcal{L}_y (1\text{kHz}) = -101\text{dBc/Hz}$]

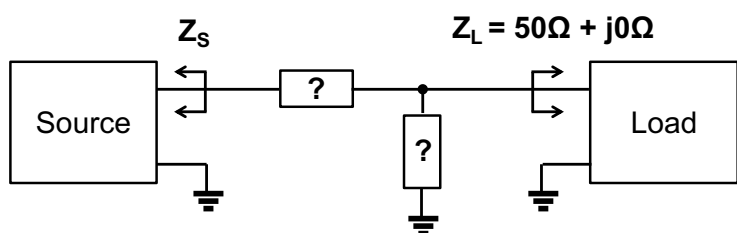Problem #2

The two unknown elements in the circuit are used to create conjugate matching from source to load at $f_0 = 2.5\text{GHz}$ frequency (for maximum power transfer) and lowpass transfer function.



- Find **the types and the values of the two unknown elements**, when $Z_s = 23\Omega + j0\Omega$.
- Find **the types and the values of the two unknown elements**, when $Z_s = 23\Omega + j11.5\Omega$.
- What is the **value of the voltage gain from input to output** at f_0 in the circuits found in b).

[Sol.:]

- $Z_{in} = 23\Omega$, Z_1 is an inductor $L = 1.58\text{nH}$, and Z_2 is a capacitor $C = 1.38\text{pF}$;
- $Z_{in} = 23\Omega - j11.5\Omega$, Z_1 is an inductor $L = 0.85\text{nH}$, and Z_2 is a capacitor $C = 1.38\text{pF}$;
- $\text{Re}\{Z_{in}\} = 28.7\Omega$, $|V_{out}/V_{in}| = \sqrt{(\text{Re}\{Z_L\}/\text{Re}\{Z_{in}\})} = 1.32$]