


**RF Circuit Design****Prof. Salvatore Levantino**Available time: 2 hours

23 Luglio 2014


**Problem #1**

Assume the FETs with  $V_t=0.4V$ , constant  $1/2\mu_nC_{ox}=0.2\text{mA/V}^2$  (for the nMOSFETs),  $1/2\mu_pC_{ox}=0.1\text{mA/V}^2$  (for the pMOSFETs).

- Neglecting the mutual inductance between the inductors, set **the value of the capacitance C and the inductance L** so that the zero-peak amplitude of the differential voltage ( $V_{outp}-V_{outn}$ ) be equal to 1V at 5GHz.
- Set the values of the voltage  $V_{dd}$  and the (W/L) of the pMOSFETs** to get a gain margin factor on the oscillation startup equal to 2 and to guarantee proper behavior of the transistors in DC biasing.
- Taking into account the **magnetic coupling** between the inductors L with coupling factor  $k=0.5$ , derive the **new values of  $V_{dd}$ , (W/L), L and C**, which fullfil the conditions in questions a) and b).

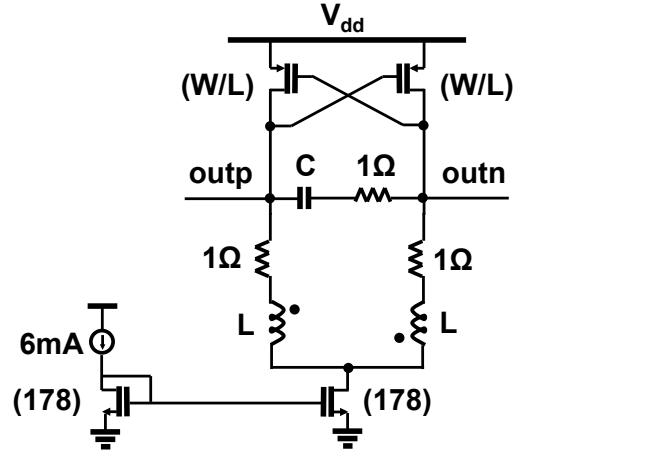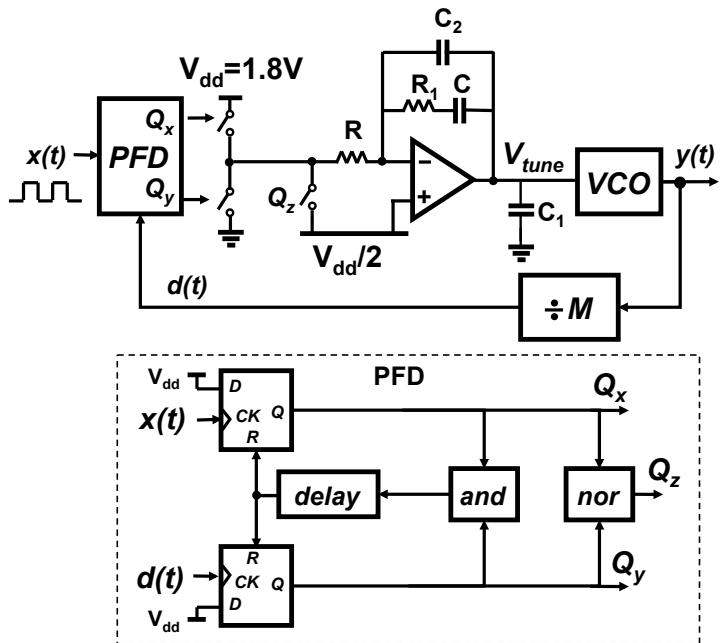**Problem #2**

The PLL in the figure embeds the PFD in the inset, where the block "delay" introduces a delay of 0.5ns. The switches have infinite resistance (when off) and  $10\Omega$  (when on). The reference clock  $x(t)$  has 50MHz frequency. The frequency-division factor is  $M=55$  and the VCO frequency varies in the range 1900-2100MHz, sweeping the  $V_{tune}$  from 0 to  $V_{dd}$ . Let the capacitors be  $C_1=100\text{pF}$  and the resistor  $R_1=100\Omega$ .




- Assuming an ideal opamp (with infinite gain and bandwidth), set **the value of R and C** to get two complex dominant (closed-loop) poles at 100kHz located at 45 degree on the Gauss plane.
- Assuming that the resistance of the switch driven by  $Q_X$  is  $15\Omega$  (when on), set the minimum **value of  $C_2$** , to get the level of the spur at 50 MHz in the spectrum of  $y(t)$  lower than -80dBc.
- Assuming all the switches with resistance  $10\Omega$  (when on), but an offset voltage of 100mV for the opamp, **can the loop lock?** If yes, what is the value of the **output frequency**, the **delay between  $x(t)$  and  $d(t)$  at steady state**, the **reference-spur level**?

Esercizio n. 1

Traccia di soluzione

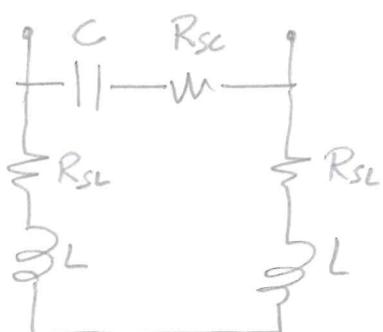a)  $V_{outp} - V_{outn} = A \cos \omega_0 t$

$$A = \frac{2}{\pi} I_{bias} R_{tank} ; \quad R_{tank} = \frac{\pi}{2} \frac{A}{I_{bias}} =$$



$$\text{ip. } Q^2 = \left( \frac{2\omega_0 L}{R_{sc} + 2R_{sl}} \right)^2 \gg 1$$

$$R_{tank} = \frac{(\omega_0 \cdot 2L)^2}{R_{sc} + 2R_{sl}} ; \quad 2\omega_0 L = \sqrt{R_{tank}(R_{sc} + 2R_{sl})}$$

$$L = \frac{1}{2\omega_0} \sqrt{R_{tank}(R_{sc} + 2R_{sl})} = \frac{1}{4\pi \cdot 5 \cdot 10^9} \sqrt{262 \cdot 3} = 0.45 \text{ nH}$$

$$C = \frac{1}{\omega_0^2 \cdot 2L} = 1.12 \text{ pF}$$

$Q = 9.62$  ip. verificata


b) Startup  $\frac{g_m R_{tank}}{2} = 2 ; \quad g_m = \frac{4}{R_{tank}}$

$$g_m = 2 \sqrt{K_p \frac{I_{bias}}{2}} \Rightarrow \left( \frac{w}{L} \right) = \left( \frac{g_m}{2} \right)^2 \frac{1}{K_p} \frac{2}{I_{bias}} =$$

$$= \frac{g_m^2}{4K_p} \frac{1}{I_{bias}} = \frac{1}{2} \frac{16}{(26.2)^2} \frac{1}{0.1 \cdot 10^{-3}} \frac{1}{6 \cdot 10^{-3}} = 194 \Rightarrow V_{ov} = 0.39 \text{ V}$$

$$V_{ovnmos} = \sqrt{\frac{I_{bias}}{K_n (\omega/L)_n}} = \sqrt{\frac{6 \cdot 10^{-3}}{0.2 \cdot 10^{-3} \cdot 178}} = 0.41 \text{ V}$$
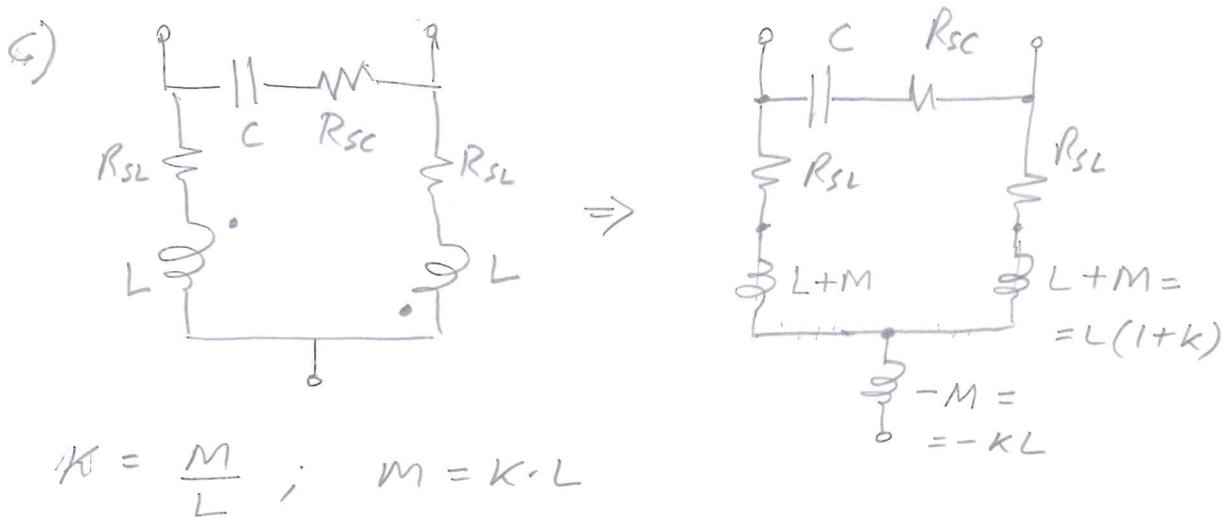
$$\frac{V_{dd} - V_{ovpmos} - V_T}{\text{DC voltage}} \geq V_{ovnmos} ; \quad V_{dd} \geq 1.2 \text{ V}$$



$$R_{\text{tank}} = \frac{[\omega_0 \cdot 2L(1+K)]^2}{R_{SC} + 2R_{SL}} ; \quad L = \frac{1}{2\omega_0(1+k)} \sqrt{R_{\text{tank}}(R_{SC} + 2R_{SL})} =$$

$$C = \frac{1}{\omega_0^2 2L(1+K)} = 1.12 \mu F$$

Esercizio n. 2

$$K_{CO} = 2\pi \cdot \frac{200 \cdot 10^6}{118} = 694 \frac{V}{rad}, \quad M = 55, \quad R_i = 100 \Omega$$

a)  $H_{\text{loop}} = \frac{V_{dd}/2}{2\pi} \cdot \frac{1}{R'} \cdot \frac{1}{s(C+C_2)} \cdot \frac{1+sR_1C}{1+sR_1 \frac{CC_2}{C+C_2}} \cdot \frac{K_{CO}}{sM} \approx$

$\cancel{\approx} \approx \frac{V_{dd}}{4\pi} \cdot \frac{1}{R'C} \cdot \frac{K_{CO}}{s^2 M} \cdot (1+sR_1C) \cdot \tau_2 \quad R' = R + r_{\text{eon}}$

$C_2 \ll C \quad K = \frac{K_{CO}}{s^2 M} \cdot (1+s\tau_2) = -1 ;$

$$s^2 + s\tau_2 \cdot K + K = 0$$

$$\Rightarrow \omega_n^2 = K \Rightarrow K = \omega_n^2 = (2\pi \cdot 10^5)^2$$


$$\Rightarrow 2\omega_n = K \cdot \tau_2 \Rightarrow \zeta = \frac{K \cdot \tau_2}{2\omega_n} = \frac{\omega_n^2 \cdot \tau_2}{2\omega_n}$$

$$\zeta = \frac{\sqrt{2}}{2} \Rightarrow \omega_n \cdot \tau_2 = \sqrt{2} ; \quad \tau_2 = \frac{\sqrt{2}}{\omega_n} = 2.25 \mu s$$

$$\Rightarrow C = 22.5 \text{ nF}$$

$$R' = 205 \Omega$$

$$R = RL_{\text{eon}} = 195 \Omega$$

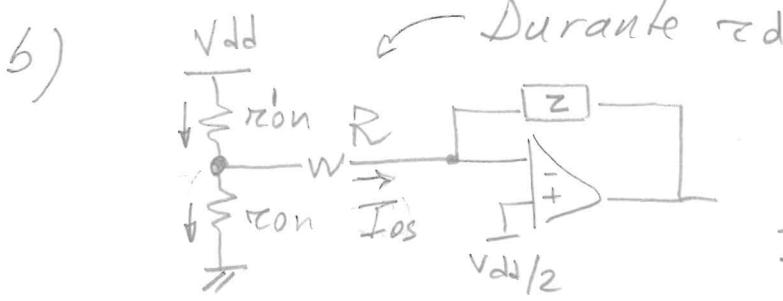


$$I_{os} \stackrel{(*)}{=} \frac{V_{dd}}{2} \cdot \frac{r_{on} - r'_{on}}{r_{on}r'_{on} + R(r_{on} + r'_{on})} = -11 \text{ mA}$$

$$I(t)$$

$$I_{os}$$

$$Q = I_{os} \cdot \tau_d$$

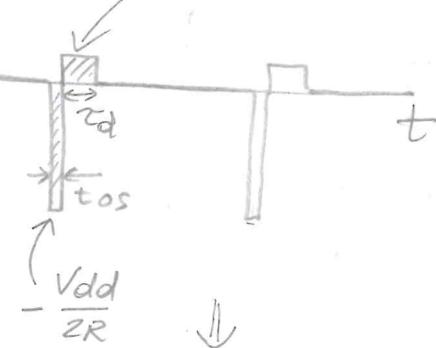

$$t_{os} = \frac{I_{os} \cdot \tau_d}{V_{dd}/2R} = \frac{0.105}{-0.92} = 0.11 \text{ ns}$$

$$I(t) = \frac{8Q}{T_{ref}} \cdot \omega_{ref} \cdot \frac{\tau_d + t_{os}}{2} \cos \omega_{ref} t + \dots$$


$$\mathcal{L} = \frac{S_4}{2} = \left( \frac{1}{2} \cdot \frac{K_{vco}}{\omega_{ref} Z_{II}} \cdot \frac{1}{C_{ref} C_2} \cdot \frac{Q}{T_{ref}} \cdot \omega_{ref} \cdot (\tau_d + t_{os}) \right)^2$$

$$\Rightarrow \frac{1}{4\pi} \cdot \frac{K_{vco}}{C_2} \cdot I_{os} \cdot \tau_d (\tau_d + t_{os}) = 10^{-4}$$


154

$$C_2 = \underline{189 \text{ pF}}$$

$$V_{dd}/2 + V_{os}$$

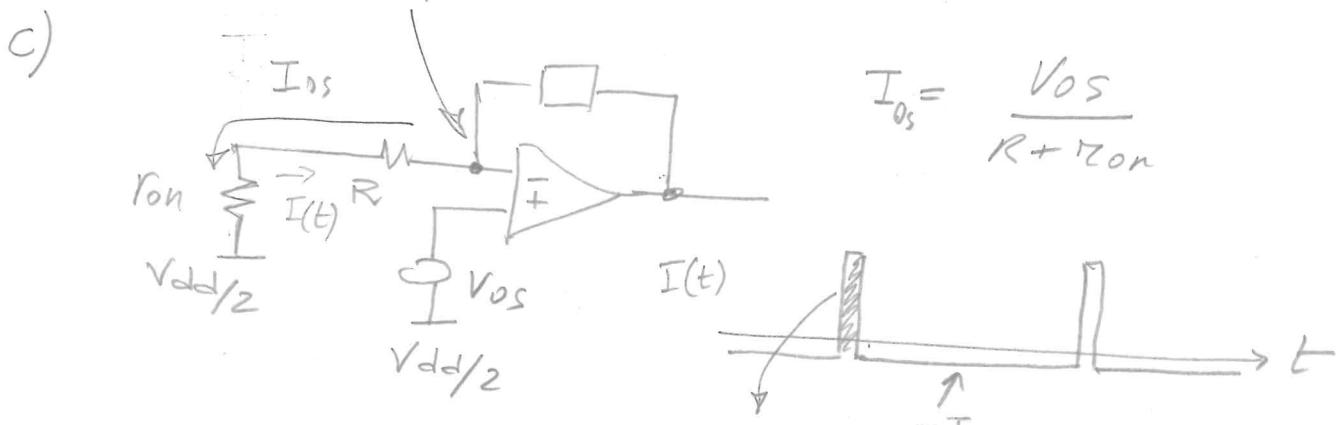

$$I_{os} = \frac{V_{os}}{R + r_{on}}$$

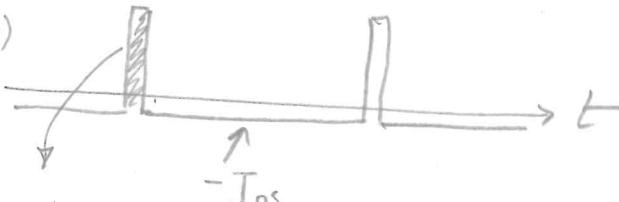


$$I(t) = \frac{2Q}{T_{ref}} \cos \omega_{ref} t = 2 \frac{V_{os}}{R + r_{on}} \cdot \frac{T_{ref}}{T_{ref}} \cos \omega_{ref} t$$

$$Q = I_{os} \cdot T_{ref} = \frac{V_{os}}{R + r_{on}} \cdot T_{ref}$$

$$\mathcal{L} = \left( \frac{1}{8} \frac{K_{vco}}{\omega_{ref}} \cdot \frac{1}{\omega_{ref} C_2} \cdot \frac{2 V_{os}}{R + r_{on}} \right)^2 = \underline{-32,8 \text{ dBc}}$$

(\*)

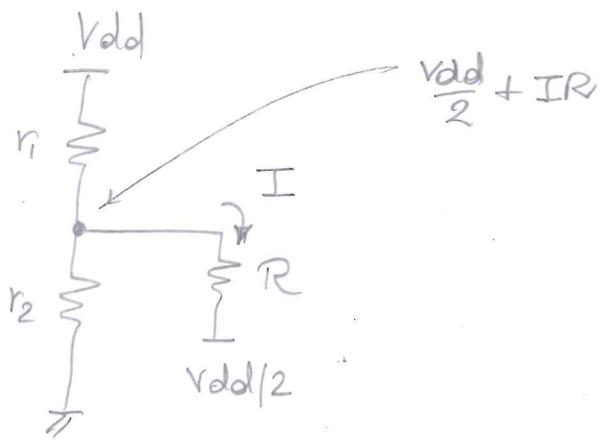

$$\frac{\frac{V_{dd}}{2} - IR}{r_1} = \frac{\frac{V_{dd}}{2} + IR}{r_2} + I$$

$$\frac{V_{dd}}{2} \left( \frac{1}{r_1} - \frac{1}{r_2} \right) = I \left( 1 + \frac{R}{r_2} + \frac{R}{r_1} \right)$$

$$I = \frac{V_{dd}}{2} \cdot \frac{\frac{r_2 - r_1}{r_1 r_2}}{1 + R \frac{r_1 + r_2}{r_1 r_2}} = \frac{V_{dd}}{2} \cdot \frac{r_2 - r_1}{r_1 r_2 + R(r_1 + r_2)}$$

**RF Circuit Design****Prof. Salvatore Levantino**


Available time: 2 hours

8 Luglio 2014

**Problem #1**

Assume  $R_b=750\Omega$ ,  $R=100k\Omega$ ,  $C_1=1nF$ ,  $C=1pF$ . The FETs have  $V_t=0.4V$ ,  $1/2\mu_nC_{ox}=0.2mA/V^2$  (for the nMOS),  $1/2\mu_pC_{ox}=0.1mA/V^2$  (for the pMOS),  $\gamma=2/3$  e  $\alpha=1$ . The (W/L) of the FETs are: (15/0.12) for M1, (6/0.12) for M3 and M5, and (18/0.12) for M4.

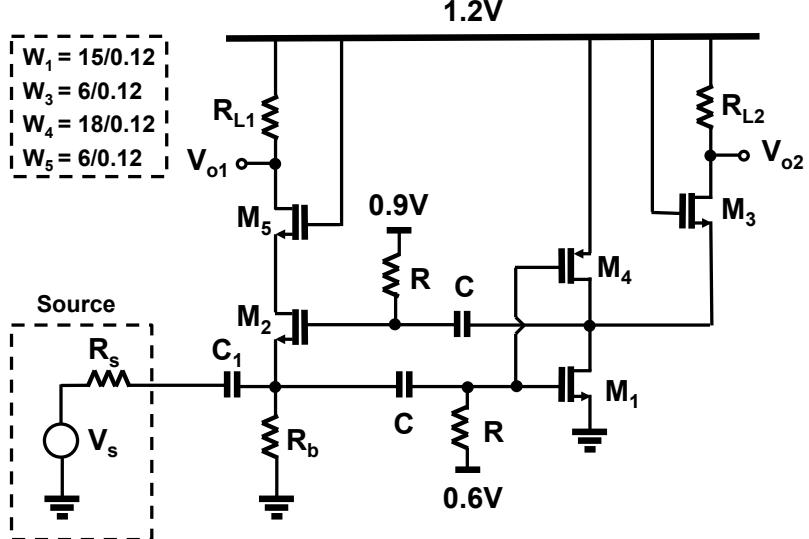- a) Set the value of (W/L) of M2 to get source matching ( $R_s=50\Omega$ ) at 1GHz, and derive the circuit DC biasing (Please




provide the values of DC currents/voltages at all branches/nodes, and verify the hypotheses).

- b) Set the values of the resistors  $R_{L1}$  and  $R_{L2}$  and verify the DC biasing of the circuit, so that:  
(i) the voltage gain  $(V_{o1}-V_{o2})/V_s$  is equal to 18dB at 1GHz and (ii) the thermal noise of M2 does not contribute to the amplifier noise figure at 1GHz.  
c) Calculate the noise figure at 1GHz, taking into account the noise of  $R_s$ ,  $R_b$ ,  $R_{L1}$ ,  $R_{L2}$ ,  $M5$ .

**Problem #2****Note: Take into account that  $C_1 \ll C$** 

The PLL in the figure embeds the PFD in the inset, where the block "delay" introduces a delay of 3ns. The current generators in the PLL are off when the switches in series are off. The reference clock  $x(t)$  has 50% duty cycle and 50MHz frequency. The frequency-division factor is  $M=55$ . The charge-pump currents:  $I_{p1}=I_{p2}=1.8mA$  and  $I_0=10\mu A$ . Let the capacitors be  $C=1\mu F$  and  $C_1=1nF$  and the resistor  $R=100\Omega$ .

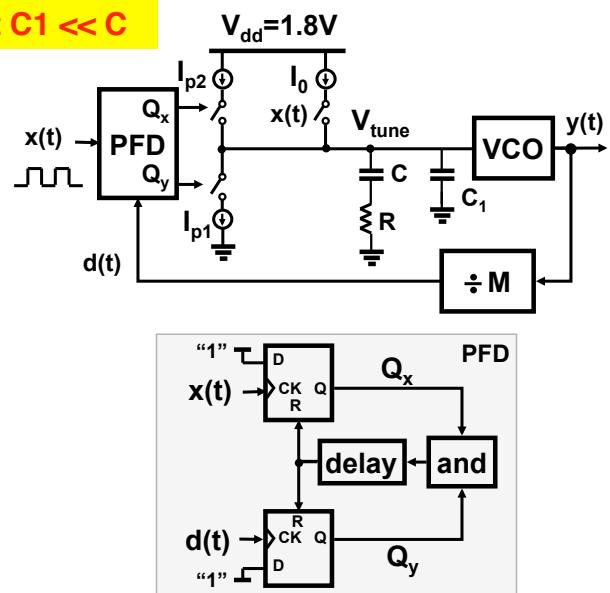- a) Set the value of the VCO gain  $K_{vco}$  to get the maximum loop phase-margin. What is the value of the phase margin (in degree) and the closed-loop bandwidth?
- b) Calculate the time delay between  $x(t)$  and  $d(t)$  at steady state, plot the total current injected into the loop filter versus time, and calculate the level of the spur in the spectrum of  $y(t)$ .
- c) Assuming  $x(t)$  to be affected by a white phase noise with SSCR = -155dBc/Hz and the free-running VCO to have 1/f<sup>2</sup> phase noise with SSCR = -135dBc/Hz at 10MHz offset from the carrier, evaluate the phase noise level of  $y(t)$  at 100Hz and at 10MHz offset from the carrier.



Esame del 8/7/14

Elettronica RF

Esercizio n. 1

Traccia di soluzione

a)

$$Z_{in} = R \parallel R_b \parallel \left( \frac{\frac{1}{g_{m2}}}{1 + \frac{g_{m1} + g_{m4}}{\frac{1}{g_{m3}} + \frac{1}{R}}} \right)$$

IP.  $m_1, m_4, m_3$  SAT.

$$I_{m4} = 0.6 \text{ mA}$$

$$I_{m3} = 0.4 \text{ mA}$$

$$g_{m4} = 6 \text{ mA/V}$$

$$g_{m3} = 4 \text{ mA/V}$$

$$I_{m1} = 1 \text{ mA}$$

$$V_{GDM1} = 0$$

$$g_{m1} = 10 \text{ mA/V}$$


$$V_{GDM4} = 0 \Rightarrow \begin{matrix} m_1, 4 \\ \text{sat.} \end{matrix}$$

$$Z_{in} \approx R_b \parallel \frac{\frac{1}{g_{m2}}}{1 + \frac{g_{m1} + g_{m4}}{g_{m3}}} = R_S = 50 \Omega$$

$$\Rightarrow g_{m2} = 3.7 \text{ mA/V}$$

$$\text{IP. } M_2 \text{ SAT. } V_{OVm2} = 0.209 \text{ V } I_{m2} = 0.39 \text{ mA}$$

$$(W/L)_{m2} = 5.3 / 0.12$$

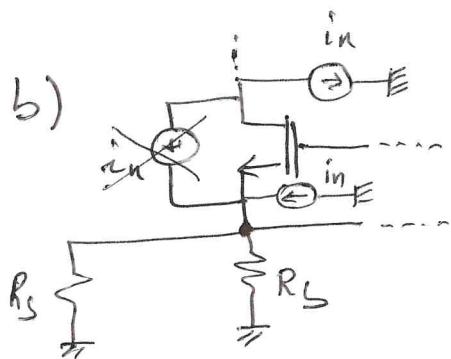

$$\frac{V_{O1} - V_{O2}}{i_{in}} = - \frac{R_{L1}}{2} \left( 1 + \frac{R_S}{R_L} \right) + \frac{R_S}{2} (g_{m1} + g_{m4}) i_{in} = 0$$

$$\Rightarrow R_{L1} \left( 1 + \frac{R_S}{R_L} \right) = R_S (g_{m1} + g_{m4}) R_{L2}$$

$$\text{Gain : } \frac{V_{O1} - V_{O2}}{V_{in}} = \frac{R_{L1}}{2R_S} \left( 1 - \frac{R_S}{R_L} \right) + \frac{(g_{m1} + g_{m4}) R_{L2}}{2} =$$

$$= \frac{R_{L1}}{R_S} \Rightarrow R_{L1} = 397 \Omega$$

$$R_{L2} = \frac{R_{L1}}{R_S} \frac{1 + \frac{R_S}{R_L}}{(g_{m1} + g_{m4})} = 1,33 \cdot R_{L1} = 529 \Omega$$

$$c) NF = 1 + \frac{R_S}{R_L} + \frac{R_{L1} + R_{L2}}{G^2 \cdot R_S} = 1,36 \rightarrow 1,34 \text{ dB}$$

$M_2, M_5$  non contribuiscono a  $NF$

## Esercizio n. 2


$$a) \omega_u = \frac{K_{VCO}}{M} \cdot \frac{I_P}{2\pi} \cdot R \Rightarrow K_{VCO} = \frac{M}{R} \frac{2\pi}{I_P} \frac{1}{R \sqrt{C_1}} = \\ \omega_u = \sqrt{\omega_z \cdot \omega_p} = \frac{1}{R \sqrt{C_1}} = 2\pi \cdot 96,6 \frac{\text{Mrad}}{\text{V} \cdot \text{s}}$$

$$\%_m = \text{atan} \left( \frac{\omega_u}{\omega_z} \right) - \text{atan} \left( \frac{\omega_u}{\omega_p} \right) = \omega_u = 2\pi \cdot 50,3 \frac{\text{Krad}}{\text{s}}$$


$$= \text{atan} \left( \frac{\omega_p}{\omega_z} \right) - \text{atan} \left( \sqrt{\frac{\omega_z}{\omega_p}} \right) =$$

$$= \frac{\pi}{2} - 2 \text{atan} \sqrt{\frac{\omega_z}{\omega_p}} \Rightarrow 86,4^\circ$$

b)

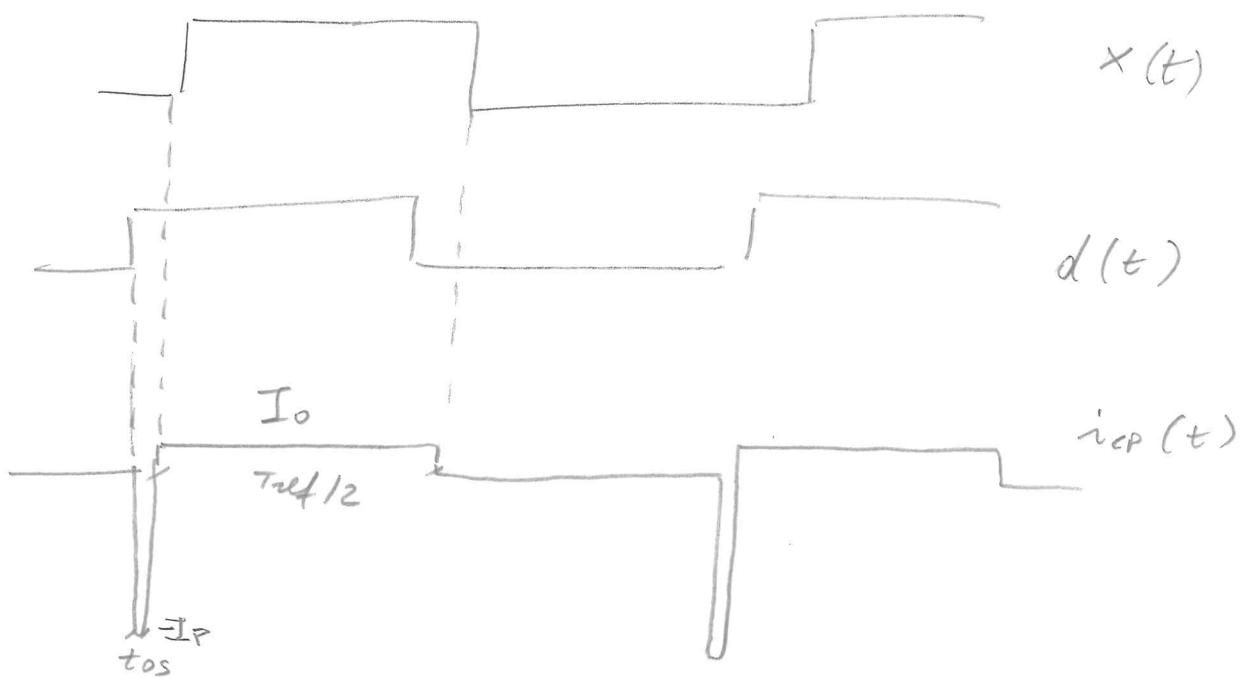

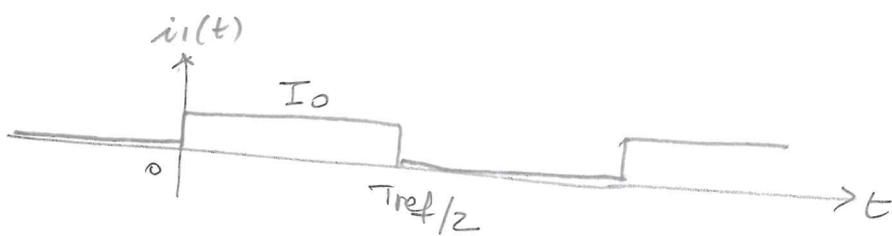
$$I_p t_{os} = I_o T_{ref}/2 \Rightarrow t_{os} = \frac{I_o}{I_p} \frac{T_{ref}}{2} = 55.5 \text{ ps}$$



$$i_{cp}(t) = i_1(t) + i_2(t)$$

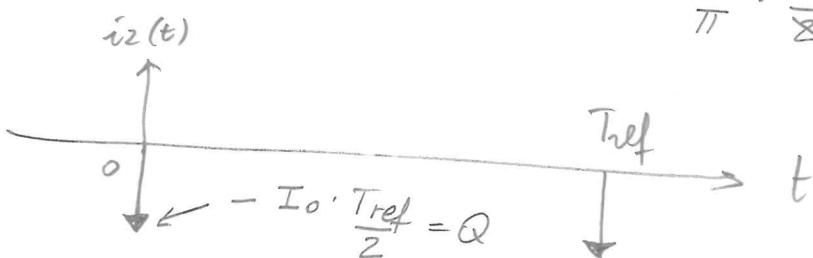→ First harmonic :  $\frac{2}{\pi} \cdot \frac{I_o}{8} \cdot \sin(\omega_{ref} \cdot t)$



→ First harmonic :  $\frac{2Q}{T_{ref}} \cdot \cos(\omega_{ref} t) = -8 \frac{I_o T_{ref}}{8 T_{ref}} \cos(\omega_{ref} t)$

⇒ First harmonic of  $i_{cp}(t)$  has amplitude :

$$\sqrt{\left(\frac{2}{\pi} I_o\right)^2 + I_o^2} = I_o \cdot \sqrt{\frac{4}{\pi^2} + 1}$$

$$\text{Ref. Spur} = \frac{S_Q}{2} = \frac{1}{2} \cdot \frac{1}{2} \cdot \left( \frac{K_{VCO}}{c_{ref}} \cdot I_o \sqrt{\frac{4}{\pi^2} + 1} \cdot \frac{1}{\omega_{ref} C_1} \right)^2 \rightarrow -89 \text{ dBc}$$

$$c) S_{\phi_y} = S_{\phi_x} \cdot M^2 \cdot \left| \frac{G_{loop}}{1+G_{loop}} \right|^2 + S_{\phi_{vco}} \cdot \left| \frac{1}{1+G_{loop}} \right|^2$$

$$G_{loop} = \frac{K}{S^2} \cdot \frac{1+S\tau_z}{1+S\tau_p}$$

At 100 Hz

$$\begin{aligned} & \cdot \begin{cases} S\tau_z \ll 1 \\ S\tau_p \ll 1 \end{cases} : G_{loop}(s) \approx \frac{K}{S^2} \Rightarrow \end{aligned}$$

$$\Rightarrow \frac{G_{loop}}{1+G_{loop}} = \frac{K}{K+S^2} \approx 1$$

$$\boxed{\frac{1}{1+G_{loop}} \ll 1}$$

$$\frac{1}{1+G_{loop}} = \frac{S^2}{K+S^2} \approx 0$$

At 10 MHz

$$\cdot \begin{cases} S\tau_z \gg 1 \\ S\tau_p \gg 1 \end{cases}$$

$$G_{loop} \approx \frac{K}{S^2} \cdot \frac{\tau_z}{\tau_p} = \frac{K}{S^2} \cdot \frac{\omega_p}{\omega_z}$$

$$\frac{K\omega_p}{\omega_z} = (2\pi \cdot 320 \frac{\text{Krad}}{\text{s}})^i$$

$$\Rightarrow \frac{G_{loop}}{1+G_{loop}} = \frac{K \cdot \omega_p / \omega_z}{K \omega_p / \omega_z + S^2} \approx 0$$

$$\boxed{\frac{1}{1+G_{loop}} \gg 1}$$

$$\frac{1}{1+G_{loop}} = \frac{S^2}{K \omega_p / \omega_z + S^2} \approx 1$$

$$\begin{aligned} SSCR_y(100\text{Hz}) &= SSCR_x + 20 \log M = \\ &= -155 + 34,8 = -120,2 \text{ dBc/Hz} \end{aligned}$$

$$SSCR_x(10\text{MHz}) = SSCR_{vco}(10\text{MHz}) = -135 \text{ dBc/Hz}$$


**RF Circuit Design****Prof. Salvatore Levantino**Maximum available time: 2 hours

July 24, 2013

**Problem #1**


Let the source impedance be  $R_1=50\Omega$  and the capacitor  $C_1$  equal to  $1nF$ . Let the MOSFET device have threshold voltage  $V_T=0.5V$ , coefficient  $(1/2)\mu C_{ox}=200\mu A/V^2$  and noise parameter  $(\gamma/\alpha)=2/3$ . Let the inductor  $L$  be equal to  $1nH$ , the resistors  $R_2=2k\Omega$  ed  $R_3=8k\Omega$ .

- After having derived the **bias point** (the voltages at all nodes, the currents at all branches and the working condition of the FET), compute the values of  $\mathbf{R}_4$ ,  $\mathbf{C}_2$  and aspect ratio (**W/L**) of the FET that guarantee (i) input matching, (ii) maximum gain at 3.3GHz and (iii) noise figure equal to 2.7dB, assuming  $C_3=30pF$  and accounting for the thermal noise of ALL the resistors in the circuit and of the FET channel.
- Let modify the circuit in figure, tying the terminal of  $C_2$  to the GATE of the FET (instead of tying it at ground). On the modified circuit, keeping the same values of the other devices, update the values of  $\mathbf{C}_2$ ,  $\mathbf{C}_3$  and (**W/L**) of the FET, so to achieve input matching at 3.3GHz, but noise figure equal to 1.2dB.
- What is the value of the **transducer power gain in decibels**?

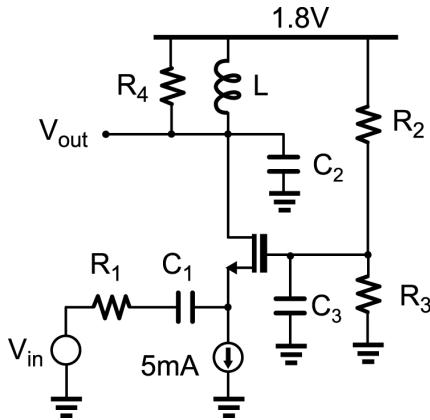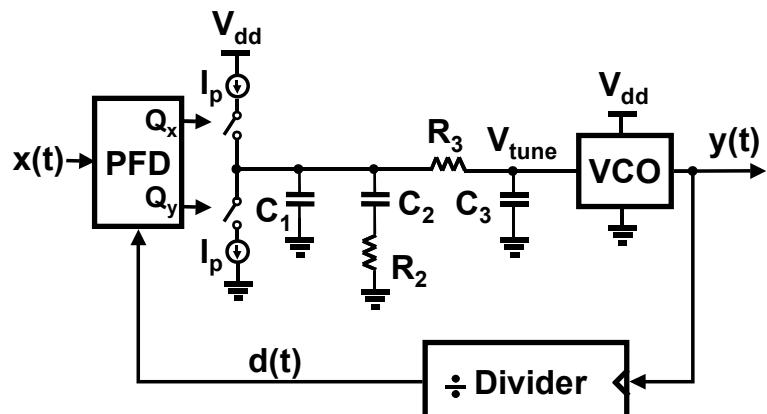**Problem #2**

Let  $V_{dd} = 3.3V$ ,  $x(t)$  a periodic signal whose frequency is 1MHz and the divider modulus equal to 1350. Let us assume a linear tuning characteristic of the VCO between 1200 and 1500MHz, when  $V_{tune}$  is varied from 0 to  $V_{dd}$ . Let  $R_2=1k\Omega$  and  $C_2=50nF$ .

- Neglecting  $R_3$  and  $C_3$  (i.e.  $R_3=0$  and  $C_3=0$ ), compute the values of the current  $I_p$  and the capacitor  $C_1$  so to have (i) phase margin equal to 60 degrees and (ii) bandwidth (approximated as the unity-gain frequency of the loop gain) equal to 10kHz.
- Assuming  $R_3=1k\Omega$  and  $C_3=350pF$  and under proper approximations (to be verified), update the values of **phase margin and unit-gain frequency**, after the insertion of  $R_3$  and  $C_3$ ?
- Accounting for  $R_3$ ,  $C_3$  and for a constant leakage current, which is drained by the charge pump, equal to 10nA, compute the **level of the spurious tone** in the spectrum of  $y(t)$ .



# Written Test of RF Circuit Design Solutions

Prof. Salvatore Levantino  
Politecnico di Milano

May 21<sup>st</sup>, 2014

## Problem #1

a)

Input matching requires

$$\frac{1}{g_m} = R_1 = 50 \Omega \quad (1)$$

Thus, the aspect ratio  $W/L$  has to be 100 and the bias point of the FET is given by  $V_D = 1.80V$ ,  $V_G = 1.44V$ ,  $V_S = 0.44V$ .

Gain is maximum when the capacitor  $C_2$  resonates with the inductor  $L$ . So, we impose

$$C_2 = \frac{1}{w_0^2 L} = 2.33 \text{ pF}. \quad (2)$$

After some computations, we get the following expression of the noise figure

$$NF = 1 + \frac{\gamma}{\alpha} + \frac{4R_1}{R_4} + \frac{R_{23}}{R_1} \cdot \frac{1}{1 + \omega^2 R_{23}^2 C_3^2} \quad (3)$$

where  $R_{23} = R_2 || R_3 = 1.6 \text{ k}\Omega$ .

Finally, imposing  $NF = 10^{-0.27} = 1.86$ , we obtain

$$\frac{4R_1}{R_4} \approx 0.2 \quad (4)$$

So,  $R_4 = 1 \text{ k}\Omega$ .

b)

Let us assume that the equivalent resistance  $R_{23}$  in parallel to  $C_3$  gives negligible variation of the parallel resistance of the  $LC$  resonator. In other words, let assume

that (I)  $Q_3 = \omega R_{23} C_3 \gg 1$ . This means that  $R_{23}$  can be equivalently placed in parallel to  $R_4$  after multiplication by  $1/n^2$ , where

$$n = \frac{C_2}{C_2 + C_3} \quad (5)$$

Thus, the equivalent resistance in parallel to the load resonator is  $R_L = R_4 \parallel \frac{R_{23}}{n^2}$ . After some computations, we get the following expression of the noise figure

$$NF = 1 + \frac{\frac{\gamma}{\alpha}}{g_m R_1} + \frac{R_1}{R_L} \left( 1 + \frac{1}{g_m R_1} \right)^2 \quad (6)$$

Imposing  $NF = 10^{-0.12} = 1.32$ , (6) gives an equation in the unknowns  $g_m$  and  $n$ . To simplify the solution of (6), we make the assumption (II)  $R_L \approx R_4$ . Thus, being  $R_4 = 1 \text{ k}\Omega$  and  $R_1 = 50 \text{ k}\Omega$ , the last term in (6) can be neglected. Doing so, we get

$$g_m R_1 \approx 2.1 \quad (7)$$

$$\frac{1}{g_m} = 24 \Omega \quad (8)$$

Thus, the aspect ratio  $W/L$  has to be increased to 434 and the bias point of the FET is slightly modified to  $V_D = 1.80\text{V}$ ,  $V_G = 1.44\text{V}$ ,  $V_S = 0.7\text{V}$ .

In the modified circuit, input matching requires

$$\frac{1}{g_m} + n \cdot R_4 = R_1 = 50 \Omega \quad (9)$$

It follows that  $n$ , given in (5), has to be approximately equal to  $1/38$ .

Gain is maximum when the capacitor  $C_{23} = n \cdot C_3$  resonates with the inductor  $L$ . So, we impose

$$C_3 = \frac{1}{nw_0^2 L} \approx 89.6 \text{ pF} \quad (10)$$

and

$$C_2 = \frac{C_{23}}{1 - n} \approx 2.39 \text{ pF.} \quad (11)$$

Finally, we verify our initial hypotheses. (I)  $Q_3 = \omega R_{23} C_3 = 2970$ , which is much greater than one, and (II)  $R_{23}/n^2 \approx 2.37 M\Omega$ , which is much greater than  $R_L$ .

**c)**

The transducer power gain is defined as the ratio between the output power and the available input power. It is given by

$$G = 10 \log_{10} \left( \frac{\frac{V_{out}^2}{2R_L}}{\frac{V_{in}^2}{8R_1}} \right) \quad (12)$$

Substituting the expression of the voltage gain

$$\frac{V_{out}}{V_{in}} = \frac{R_L}{2R_1} \quad (13)$$

we obtain

$$G = 10 \log_{10} \left( \frac{R_L}{R_1} \right) = 13 \text{ dB.} \quad (14)$$

## Problem #2

**a)**

From the VCO tuning characteristic, we get

$$K_{vco} = 2\pi \cdot \frac{f_H - f_L}{V_{dd}} = 2\pi \frac{1500 - 1200}{3.3} \text{ Mrad/(Vs)} = 570.9 \text{ Mrad/(Vs).} \quad (15)$$

The loop gain of the PLL can be written as

$$H(s) = \frac{I_p}{2\pi} \frac{K_{vco}}{sN} Z(s) = \frac{I_p}{2\pi} \frac{K_{vco}}{sN} \frac{1}{s(C_1 + C_2)} \cdot \frac{1 + s/\omega_z}{1 + s/\omega_p} \quad (16)$$

where

$$\omega_z = \frac{1}{R_2 C_2} \quad (17)$$

$$\omega_p = \frac{1}{R_2 C_{12}} \quad (18)$$

being

$$C_{12} = \frac{C_1 C_2}{C_1 + C_2}. \quad (19)$$

The stability constraint imposes that the loop gain crosses the 0-dB axis with  $-20$  dB/decade slope. Under this condition, the *crossover frequency* is given by

$$\omega_u = \frac{K_{vco} I_p R_2}{2\pi N} \cdot \frac{C_2}{C_1 + C_2} \quad (20)$$

If we assume that  $C_1 \ll C_2$  and we impose  $\omega_u = 2\pi \cdot 10$  krad/s (being  $R_2 = 1\text{ k}\Omega$  and  $N = 1350$ ), it follows that  $I_p = 0.932$  mA.

The *phase margin* is given by

$$\phi_m \approx \arctan\left(\frac{\omega_u}{\omega_z}\right) - \arctan\left(\frac{\omega_u}{\omega_p}\right) \quad (21)$$

Substituting the value of  $\omega_z$

$$\omega_z = \frac{1}{R_2 C_2} = 2\pi \cdot 3.2 \text{ krad/s} \quad (22)$$

and imposing  $\phi_m = 60$  degrees, we get

$$\omega_p \approx 4.51 \cdot \omega_u = 2\pi \cdot 45.1 \text{ krad/s} \quad (23)$$

Thus,

$$C_{12} \approx 3.53 \text{ nF} \quad (24)$$

and

$$C_1 = \frac{C_2 C_{12}}{C_2 - C_{12}} = 3.80 \text{ nF} \quad (25)$$

We can iterate this computation by substituting the value of  $C_1$  into (20). Doing so, we obtain a new, more accurate value of  $I_p$ , that is 1.002 mA.

## b)

Taking into account  $R_3$  and  $C_3$ , another pole is added into the loop gain

$$H_1(s) = \frac{1}{2\pi} \frac{K_{vco}}{sN} \frac{I_p}{s(C_1 + C_2)} \cdot \frac{1 + s/\omega_z}{(1 + s/\omega_p)(1 + sR_3C_3) + \frac{C_3}{C_1 + C_2} \cdot (1 + s/\omega_z)} \quad (26)$$

The last equation shows that, as long as

$$C_3 \ll C_1 + C_2 \quad (27)$$

and

$$C_3 \ll C_1 + \frac{R_3}{R_2} \cdot \left(1 + \frac{C_1}{C_2}\right) \cdot C_3, \quad (28)$$

the two poles does not interact and the new pole is placed at  $1/(R_3C_3)$  and the loop gain is approximately given by

$$H_1(s) \approx \frac{1}{2\pi} \frac{K_{vco}}{sN} \frac{I_p}{s(C_1 + C_2)} \cdot \frac{1 + s/\omega_z}{(1 + s/\omega_p)(1 + sR_3C_3)} \quad (29)$$

Being  $C_3 \ll C_1$ , both (27) and (28) hold true. Thus, looking at (29), we can conclude that the *crossover frequency* is unchanged, whereas the *phase margin* is reduced by

$$\Delta = \arctan(\omega_u R_3 C_3) \approx 1.3 \text{ degrees} \quad (30)$$

**c)**

The constant leakage current causes a ripple on  $V_{tune}(t)$  at the reference frequency. At this frequency the filter trans-impedance can be approximated as:

$$Z_m(s) \approx \frac{1}{s(C_1 + C_3)} \cdot \frac{1}{1 + sR_3 \frac{C_1 C_3}{C_1 + C_3}} \quad (31)$$

The spur level can be calculated from the following expression


$$\text{SFDR} \approx 10 \log \left[ \frac{K_{vco}^2 I_1^2}{4\omega_{ref}^6 C_1^2 R_3^2 C_3^2} \right] \quad (32)$$

where  $I_1$  is the first harmonic of the steady-state current drained from the filter. Being  $I_1 = 2 \cdot Q_{leakage}/T_{ref} = 20 \text{ nA}$ , SFDR is about -95.2 dBc.

# ESERCIZIO 4 (LNA)

FATTO IL 26/5/2014

## (a) Polarizzazione

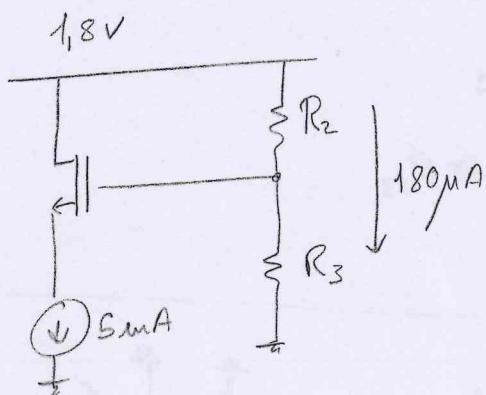

$$V_G = 1.8V \cdot \frac{R_3}{R_3 + R_2} = 1.44V$$

$$g_{mI} = \frac{1}{S_{mI}} = \frac{2 I_D}{V_{GS} - V_T}$$

input  
matching

$$\Rightarrow V_{GS} - V_T = 0.5V \Rightarrow V_S = 0.44V$$

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \Rightarrow \frac{W}{L} = \frac{S_m}{200 \mu} \cdot \frac{1}{(0.5)^2} = 100 = \frac{W}{L}$$

$$\omega_0^2 = \frac{1}{L C_2} \rightarrow C_2 = \frac{1}{\omega_0^2 L} = 2.33 \text{ pF}$$


quadagno  
massime

## Noise Figure


Hp:  $C_1$  corto circuitato @ 3.36 Hz

$$\Rightarrow Z_{c1} = \left( R_1 + \frac{1}{g_{mI}} \right) C_1 = 100 \text{ mS} \Rightarrow \text{passa alto con job a}$$


$1.6 \text{ Hz} \ll 3.36 \text{ Hz}$

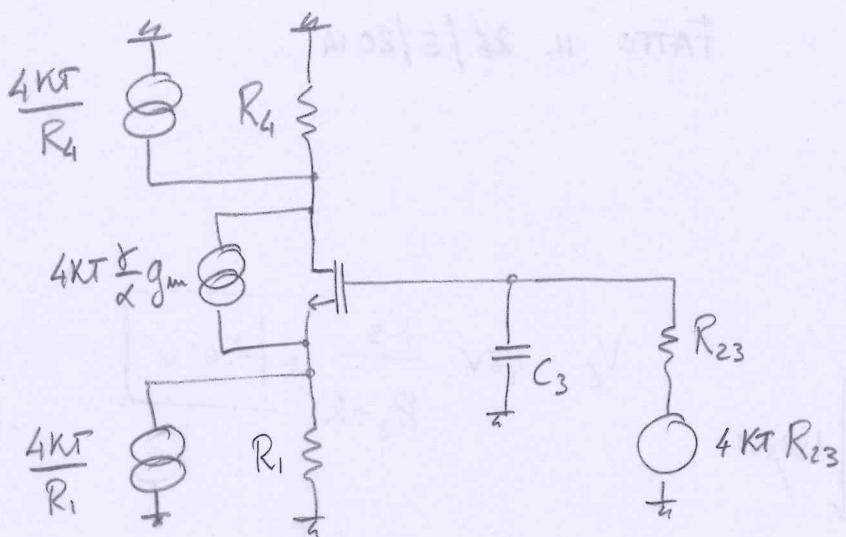

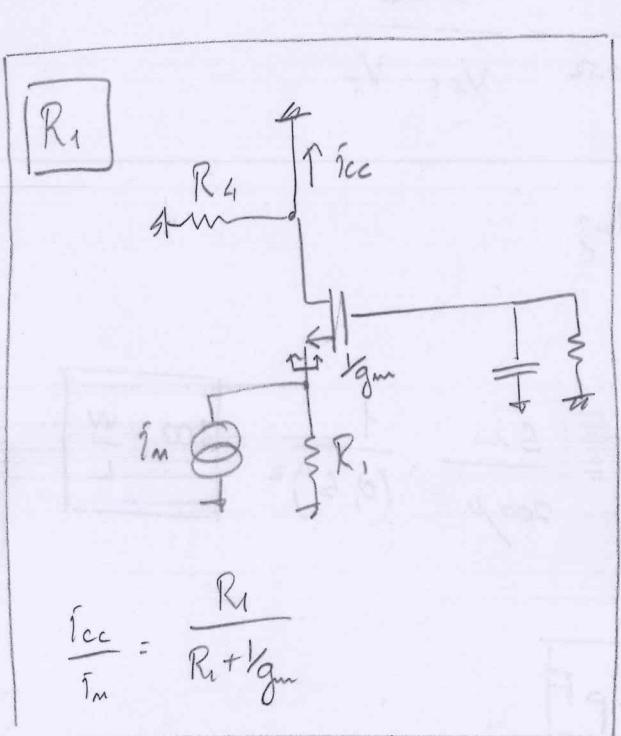
$$R_{23} \triangleq R_2 \parallel R_3 = 1,6 \text{ k}\Omega$$



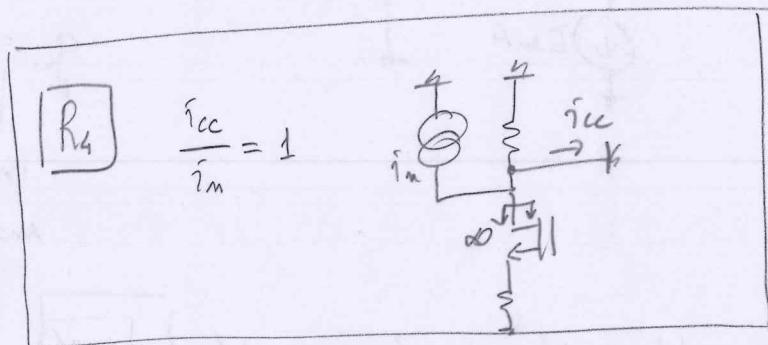
$$\frac{i_{cc}}{i_m} = \frac{R_1}{R_1 + \frac{1}{g_{gm}}}$$



$$\frac{i_{cc}}{i_m} = 1$$

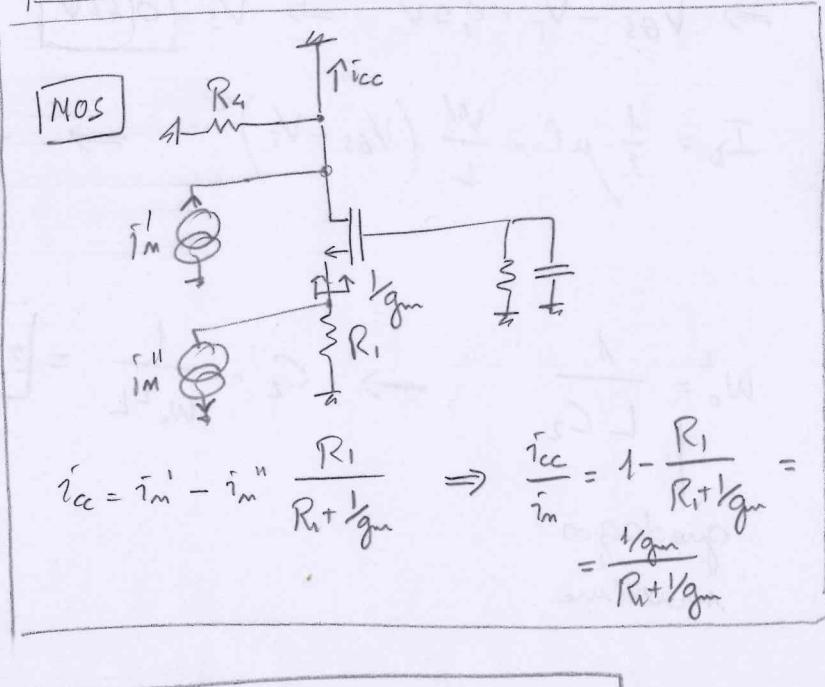
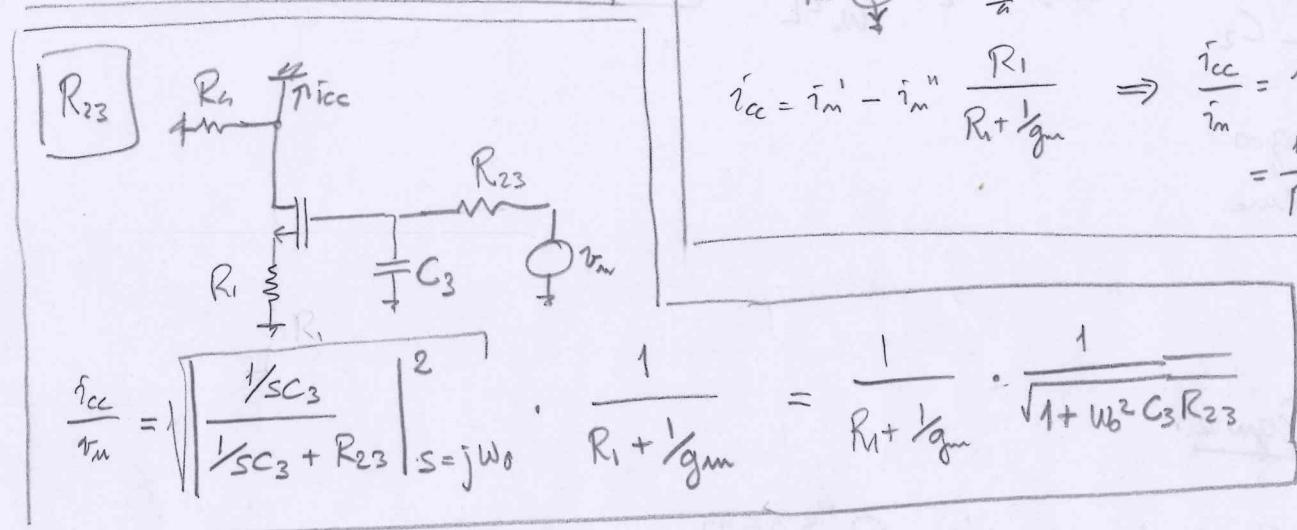
$$i_{cc} = i_m' - i_m \cdot \frac{R_1}{R_1 + \frac{1}{g_{gm}}} \Rightarrow \frac{i_{cc}}{i_m} = 1 - \frac{R_1}{R_1 + \frac{1}{g_{gm}}} = \frac{\frac{1}{g_{gm}}}{R_1 + \frac{1}{g_{gm}}}$$



$$\frac{i_{cc}}{i_m} = \sqrt{\left| \frac{\frac{1}{j\omega C_3}}{\frac{1}{j\omega C_3} + R_{23}} \right|^2} \cdot \frac{1}{R_1 + \frac{1}{g_{gm}}} = \frac{1}{R_1 + \frac{1}{g_{gm}}} \cdot \frac{1}{\sqrt{1 + (\omega C_3 R_{23})^2}}$$


$$NF = 1 + \frac{\frac{4KT}{R_4}}{\frac{4KT}{R_1} \cdot \left( \frac{R_1}{R_1 + \frac{1}{g_{gm}}} \right)^2} + \frac{4KT \frac{1}{\alpha} g_{gm} \left( \frac{1}{\frac{1}{g_{gm}} + R_1} \right)^2}{\frac{4KT}{R_1} \cdot \left( \frac{R_1}{R_1 + \frac{1}{g_{gm}}} \right)^2} + \frac{4KT R_{23} \left( \frac{1}{R_1 + \frac{1}{g_{gm}}} \right)^2 \cdot \frac{1}{1 + (\omega C_3 R_{23})^2}}{\frac{4KT}{R_1} \cdot \left( \frac{R_1}{R_1 + \frac{1}{g_{gm}}} \right)^2}$$

$$NF = 1 + \frac{R_1}{R_4} \cdot \frac{(R_1 + \frac{1}{g_{mu}})^2}{R_1} + \frac{\gamma}{\alpha} \cdot g_{mu} \cdot \frac{1}{g_{mu}^2} \cdot \frac{R_1}{R_1} + \frac{R_{23}}{R_1} \cdot R_1 \cdot \frac{1}{1 + w_0^2 C_3 R_{23}}$$


$$\text{Per } R_1 = \frac{1}{g_{mu}} \quad NF = 1 + \frac{4R_1}{R_4} + \frac{\gamma}{\alpha} + \frac{R_{23}}{R_1} \cdot \frac{1}{1 + w_0^2 C_3 R_{23}} = 10^{-\frac{2,7}{10}} = 1,86$$

$$\Rightarrow \frac{4R_1}{R_4} \approx 0,19 \Rightarrow \boxed{R_4 = 1K\Omega}$$

(b)


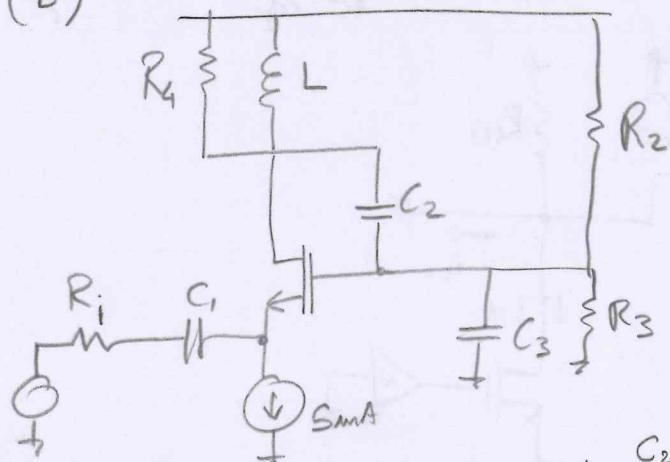

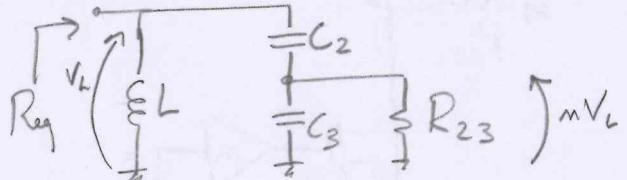
$$\text{Hyp. } R_{23} \gg \frac{1}{w_0 C_3}$$



$$\frac{V_L^2}{R_{\text{eq}}} = \frac{(mV_L)^2}{R_{23}} \Rightarrow R_{\text{eq}} = \frac{R_{23}}{m^2}$$

@ 3,3 GHz

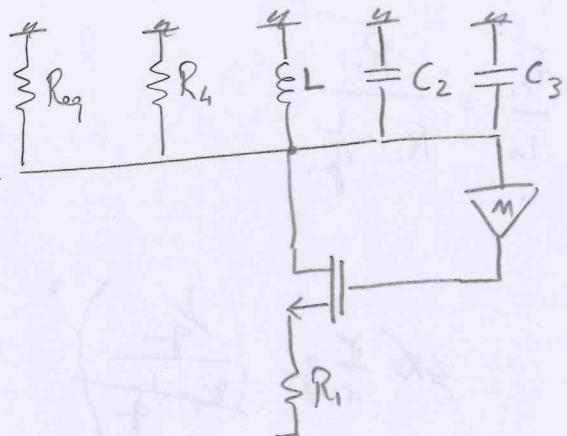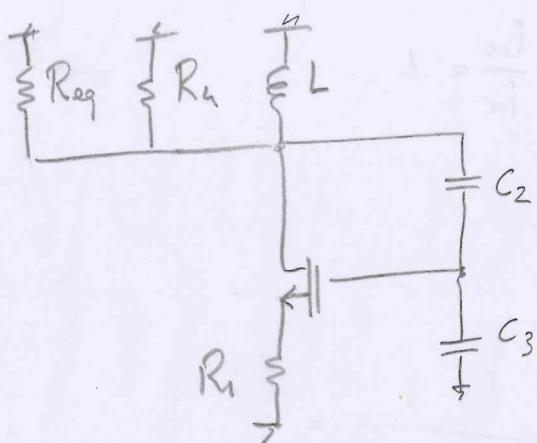


$$R_{423} \triangleq R_{\text{eq}} // R_4$$


Guadagno massimo

$$w_0^2 = \frac{1}{L \frac{C_2 C_3}{C_2 + C_3}}$$


## Noise figure

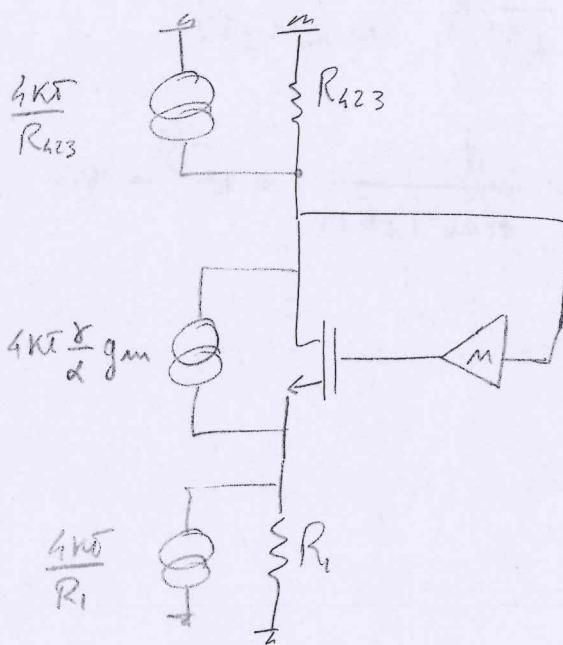


HOS

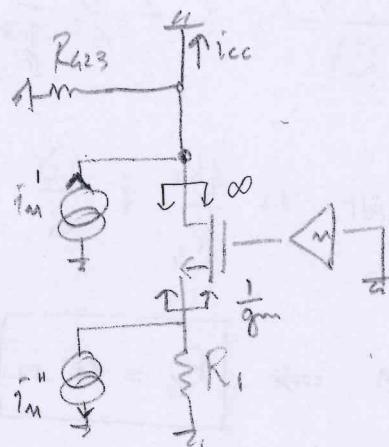

$R_h$

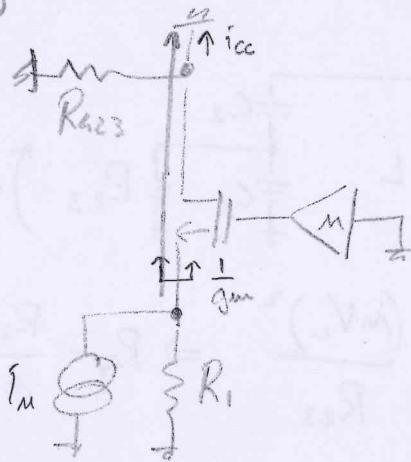

$R_{423}$

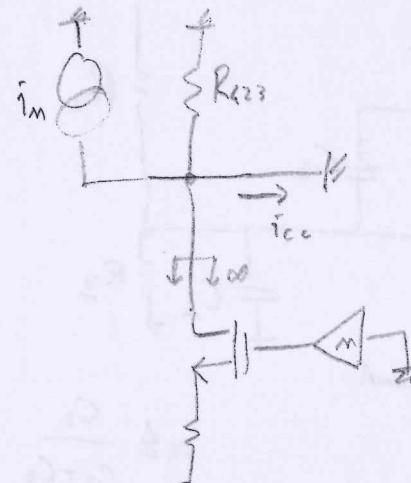


$$\frac{i_{cc}}{i_m} = \frac{R_1}{R_1 + \frac{1}{g_m}}$$

$$\frac{i_{cc}}{i_m} = 1$$

$$\frac{4KT}{\alpha g_m} \left( \frac{\frac{1}{g_m}}{R_1 + \frac{1}{g_m}} \right)^2$$

$$NF = 1 + \frac{\frac{4KT}{R_{423}} \cdot \left( \frac{R_1}{R_1 + \frac{1}{g_m}} \right)^2}{\frac{4KT}{R_1} \cdot \left( \frac{R_1}{R_1 + \frac{1}{g_m}} \right)^2} + \frac{\frac{4KT}{R_{423}}}{\frac{4KT}{R_1} \left( \frac{R_1}{R_1 + \frac{1}{g_m}} \right)^2} = 1 + \frac{\frac{1}{\alpha} \cdot \frac{1}{g_m R_1}}{\frac{4KT}{R_1}} + \frac{R_1}{R_{423}} \cdot \left( 1 + \frac{1}{g_m R_1} \right)^2$$

## input matching

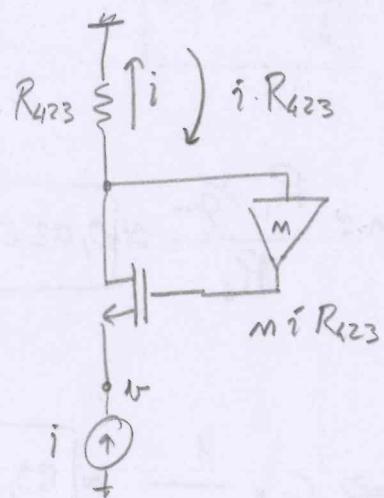

$$i = -g_m (m R_{423} i - v)$$

$$i (1 + g_m m R_{423}) = g_m v$$

$$\frac{v}{i} = \boxed{\frac{1}{g_m} + m R_{423} = R_1}$$

$$\Rightarrow NF = 1 + \frac{\delta/\alpha}{g_m R_1} + \frac{R_1}{R_{423}} \left(1 + \frac{1}{g_m R_1}\right)^2 = 10^{-12\%} = 1,32$$

$$R_{423} \triangleq R_4 \parallel \frac{R_{23}}{m^2}$$

Hp2  $R_4 \ll \frac{R_{23}}{m^2} \Rightarrow R_{423} \approx R_4$

$$\Rightarrow NF \approx 1 + \frac{\delta/\alpha}{g_m R_1} + \frac{R_1}{R_4} \left(1 + \frac{1}{g_m R_1}\right)^2 = 1,32$$

Hp3:  $\frac{R_1}{R_4} \left(1 + \frac{1}{g_m R_1}\right)^2 \ll 1$

$$\Rightarrow NF \approx 1 + \frac{\delta/\alpha}{g_m R_1} = 1,32 \Rightarrow \frac{1}{g_m} = 24 \Omega \quad (g_m R_1 = 2,1)$$

$$g_m = \frac{2 I_D}{V_{GS} - V_T} \Rightarrow \frac{1}{24} = \frac{2 \cdot 5 \mu}{V_{GS} - V_T} \Rightarrow V_{GS} - V_T = 0,24 V$$

$$\text{Can } V_G = 1,64 \text{ V} \Rightarrow V_S = 0,7 \text{ V}$$

$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{DS} - V_T)^2 = 5 \text{ mA} \Rightarrow \boxed{\frac{W}{L} = 634}$$

input matching:  $\frac{1}{g_m} + m R_{423} = R_i \Rightarrow m \approx \frac{R_i - \frac{1}{g_m}}{R_4} \approx 0,026$

Graechgros max:  $\omega_0^2 = \frac{1}{L \left( \frac{C_2 |C_3|}{C_2 + C_3} \right)} = \frac{1}{L m C_3} \Rightarrow C_3 = \frac{1}{\omega_0^2 m L} = 89,6 \text{ pF}$

$$\frac{C_2}{C_2 + C_3} = m \Rightarrow \frac{1}{1 + \frac{C_3}{C_2}} = m \Rightarrow \frac{C_3}{C_2} = \frac{1-m}{m} \Rightarrow C_2 = \frac{m C_3}{1-m} = 2,4 \text{ pF}$$

Verifica delle ipotesi

H<sub>1</sub>  $R_{23} \gg \frac{1}{\omega_0 C_3}$   $1600 \gg 0,54$  OK!

H<sub>2</sub>  $R_4 \ll \frac{R_{23}}{m^2}$   $1000 \ll 2,37 \cdot 10^6$  OK!

H<sub>3</sub>  $\frac{R_1}{R_4} \left( 1 + \frac{1}{g_m R_1} \right)^2 \ll 1$   $0,1 \ll 1$  OK!

(c) Guadagno di potenza di trasmissione

$$G \triangleq 10 \log_{10} \left( \frac{V_{\text{out}}^2 / 2R_4}{V_{\text{in}}^2 / 8R_1} \right) = 10 \log_{10} \left( \left( \frac{V_{\text{out}}}{V_{\text{in}}} \right)^2 \cdot 4 \frac{R_1}{R_4} \right)$$

guadagno di tensione  $\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R_4}{2R_1}$

$$\Rightarrow G \triangleq 10 \log_{10} \left( \frac{R_4^2}{4R_1^2} \cdot 4 \frac{R_1}{R_4} \right) = 10 \log_{10} \left( \frac{R_4}{R_1} \right) \approx \boxed{13 \text{ dB}}$$

## **Elettronica a Radiofrequenza**

**Prof. Salvatore Levantino**


Tempo massimo a disposizione: 3 ore

26/09/2011

## Problema 1

Siano  $L = 8\text{nH}$ ,  $R = 8\Omega$ ,  $V_t = 0.5\text{V}$ ,  $K_n = 4\text{mA/V}^2$ .

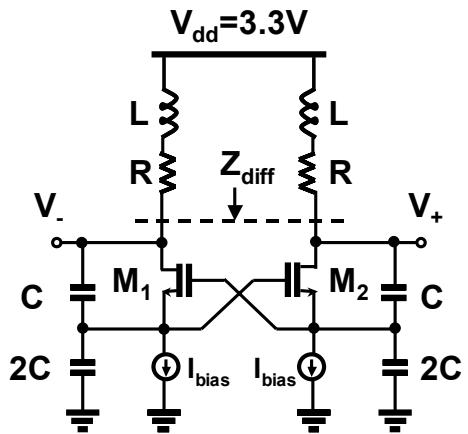- a) Ricavare l'espressione dell'impedenza differenziale  $Z_{\text{diff}}(\omega)$ .
  - b) Dimensionare  $I_{\text{bias}}$  e  $C$  per garantire un margine di un fattore 2 sull'innesto dell'oscillazione e frequenza di oscillazione di 3GHz.
  - c) Ricavato il guadagno d'anello del circuito, calcolare l'ampiezza d'oscillazione di  $V_+$  e  $V_-$ , approssimando la corrente in M1/M2 con un treno di impulsi.




## Problema 2

- a) Nel sistema in figura, il VCO ha frequenza di free-running di 3GHz e sensitività di 300MHz/V,  $M=100$ ,  $I_p=0.1\text{mA}$ . Dopo aver ricavato il modello equivalente lineare, dimensionare  $R$  e  $C$ , per garantire poli ad anello chiuso a frequenza di 10kHz e a  $45^\circ$  sul piano di Gauss.

b) Quanto vale il contributo del rumore termico della resistenza  $R$  sullo spettro di  $y(t)$  a 1MHz dalla portante?

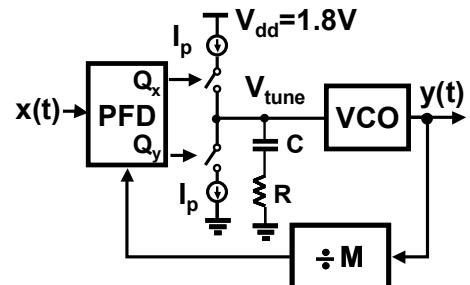c) Tenuto conto che il segnale periodico  $x(t)$  ha spettro di fase bianco pari a  $-140\text{dBc/Hz}$  e considerato il rumore termico di  $R$ , disegnare su grafico quotato lo spettro di fase totale di  $y(t)$ .




## Problema 3

Assumere FET con (W/L) in figura, soglia  $V_t=0.5V$ , costante  $1/2\mu C_{ox}=0.1mA/V^2$  e rumore termico con  $\alpha=1$  e  $\gamma=2/3$  (tralasciare gate-induced noise).

- a) Dopo aver polarizzato il circuito, ricavare alla frequenza di risonanza il guadagno di potenza disponibile a  $50\Omega$ .


b) Ricavare la figura di rumore del circuito.

c) Assumendo di connettere due filtri passabanda, rispettivamente all'ingresso e all'uscita del circuito, e che tali filtri abbiano perdita di potenza di 3dB (in banda passante) e avendo un segnale all'ingresso della catena di potenza disponibile -100dBm, quanto vale in uscita il rapporto segnale/rumore nella banda di 1MHz.

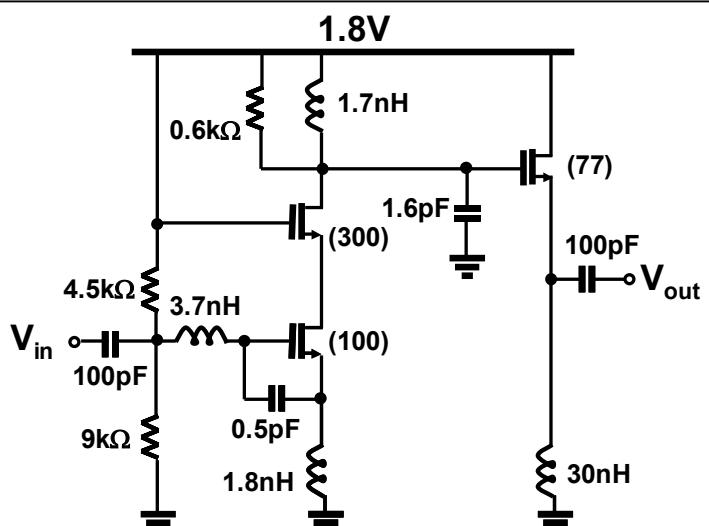

Problema 1

a)

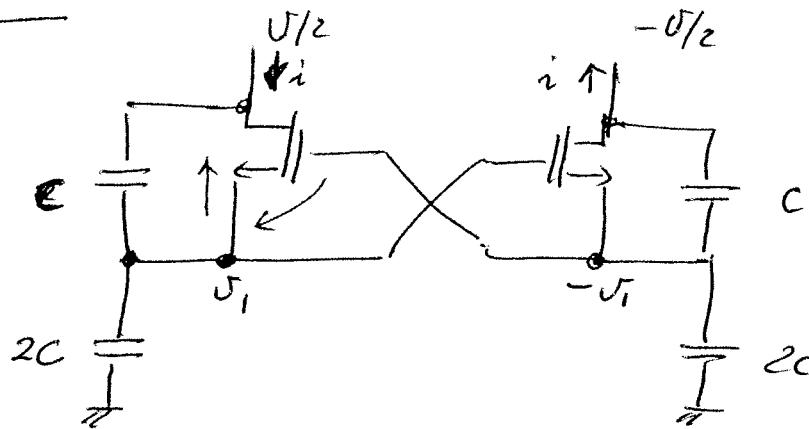

$$\begin{cases} i = (\frac{V_1}{2} - V_1) \cdot sC - g_m \cdot 2V_1 \\ (\frac{V_1}{2} - V_1) \cdot sC - g_m \cdot 2V_1 = s2C \cdot V_1 \\ sC \frac{V_1}{2} = (s2C + sC + 2g_m) \cdot V_1 \end{cases}$$


$$V_1 = \frac{sC/2}{s3C + 2g_m} \cdot V_E$$

$$i = \frac{V_E}{2} \cdot sC - (2g_m + sC) \cdot \frac{sC/2}{s3C + 2g_m} \cdot V$$

$$\begin{aligned} i_V &= \frac{sC}{2} \cdot \frac{\cancel{s3C+2g_m} - \cancel{2g_m} - sC}{\cancel{s3C+2g_m}} = \frac{sC}{2} \cdot \frac{-sC}{\cancel{s3C+2g_m}} = \\ &= \frac{-s^2 C^2}{s3C + 2g_m} \end{aligned}$$

$$Z_{\text{diff}} = \frac{V}{i} = \frac{2g_m}{s^2 C^2} + \frac{s3C}{s^2 C^2} \Big|_{s=j\omega} = -\frac{2g_m}{\omega^2 C^2} + \frac{3}{j\omega C}$$


b)

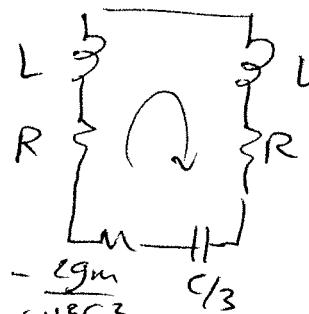

Condizioni di oscillazione  $Z_{\text{tot}} = 0$ :

$$1) \operatorname{Re}(Z_{\text{tot}}) = 0 : \cancel{2R} - \frac{2g_m}{\omega^2 C^2} = 0$$
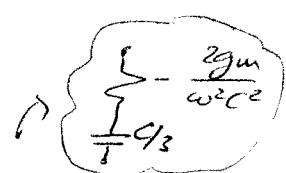
$$2) \operatorname{Im}(Z_{\text{tot}}) = 0 : \omega = \frac{1}{\sqrt{2L \cdot C/3}}$$




$$g_{m\min} = \omega_0^2 C^2 R = 0.79 \text{ mA/V}$$

$$2) \quad \omega = \frac{1}{\sqrt{2L \cdot \frac{1}{C}}} = \omega_0 \rightarrow C = \frac{1}{\omega_0^2} \cdot \frac{1}{L} \cdot \frac{3}{2} = 528 \text{ fF}$$

Per avere margine di fattore 2 su startup:

$$g_m = 2g_{m\min} = 1.58 \text{ mA/V}$$

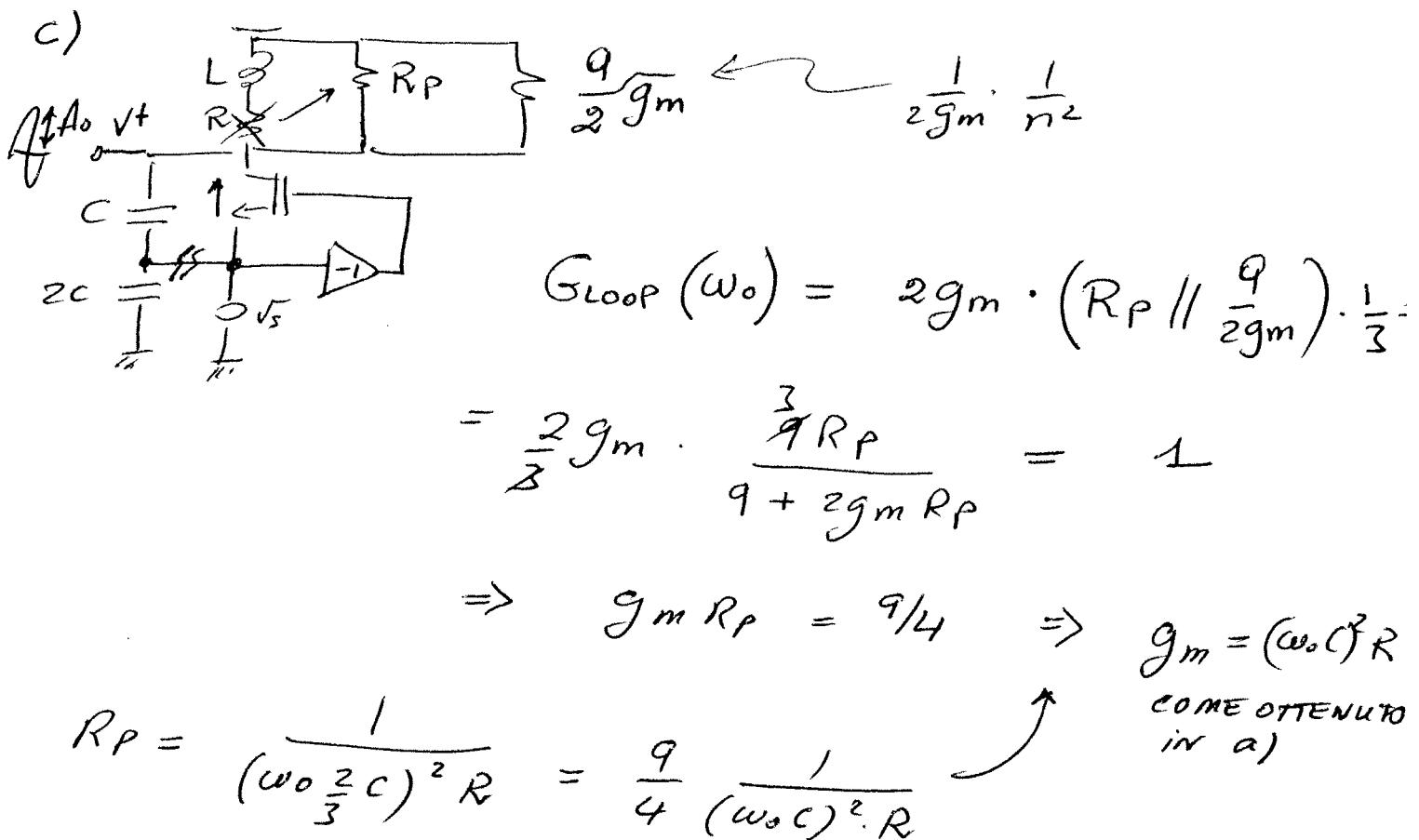
$$g_m = 2\sqrt{k \cdot I_{bias}} \Rightarrow I_{bias} = \frac{g_m^2}{4} \cdot \frac{1}{k} = 157 \mu\text{A}$$



Per grande segnale :  $G_{\text{eff}} = (\omega_0 C)^2 R$



d'altra parte  $G_{\text{eff}} \approx \frac{2 \cdot I_{bias}}{A_0/3} \Rightarrow$
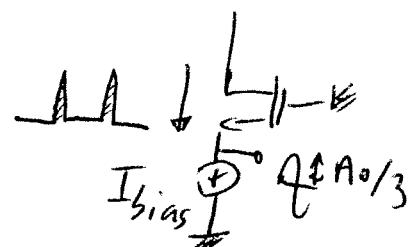
$$\Rightarrow A_0 = \frac{6 I_{bias}}{(\omega_0 C)^2 \cdot R} \approx 1.2 \text{ V}$$


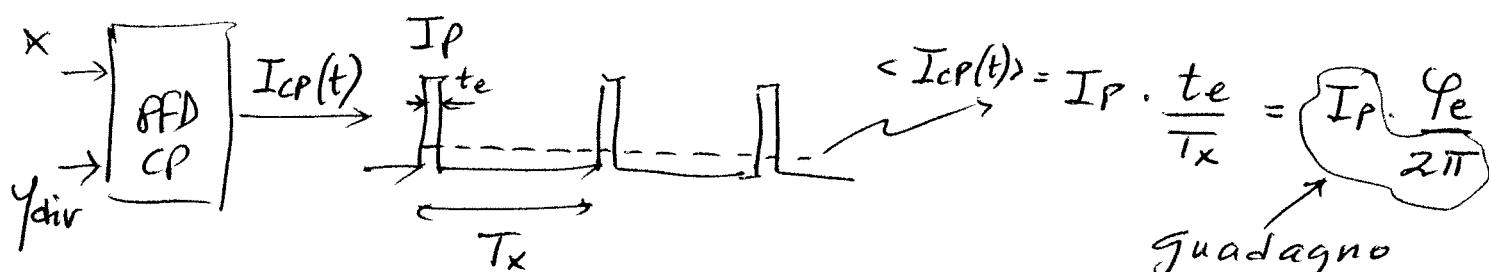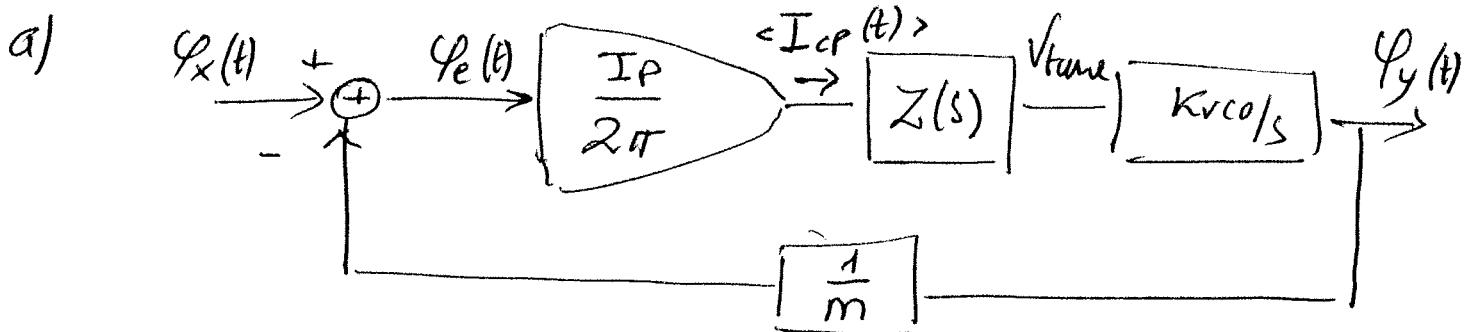
## Problema 2

$$\begin{cases} M = 100 \\ K_{rco} = 2\pi \cdot 300 \text{ Nrad/sV} \\ I_P = 0.1 \text{ mA} \end{cases}$$



Hipotizzando che  $Z(s)$  sia filtro a banda più stretta di  $\frac{1}{T_x}$

Possiamo considerare la sola componente DC di  $I_{cp}$

$$G_{loop}(s) = \frac{I_P}{2\pi} \left( R + \frac{1}{sC} \right) - \frac{K_{rco}}{sM}$$

$$1 - G_{loop}(s) = 0 : s^2 + \underbrace{\frac{I_P R K_{rco}}{2\pi M}}_{2\zeta\omega_n} s + \underbrace{\frac{I_P K_{rco}}{2\pi M C}}_{\omega_n^2} = 0$$



$$\Rightarrow \omega_n = \sqrt{\frac{I_P K_{rco}}{2\pi M C}}$$

$$\zeta = \frac{R}{2} \sqrt{\frac{I_P K_{rco} C}{2\pi M}} \Rightarrow C = \left( \frac{I_P \cdot K_{rco}}{2\pi \cdot M} \right)^* \frac{1}{\omega_n^2} = 76 \text{ nF}$$


$$\omega_n = 2\pi \cdot 10 \text{ k}$$

$$\zeta = \sqrt{2}/2$$
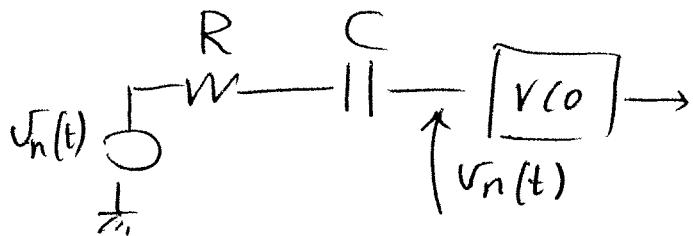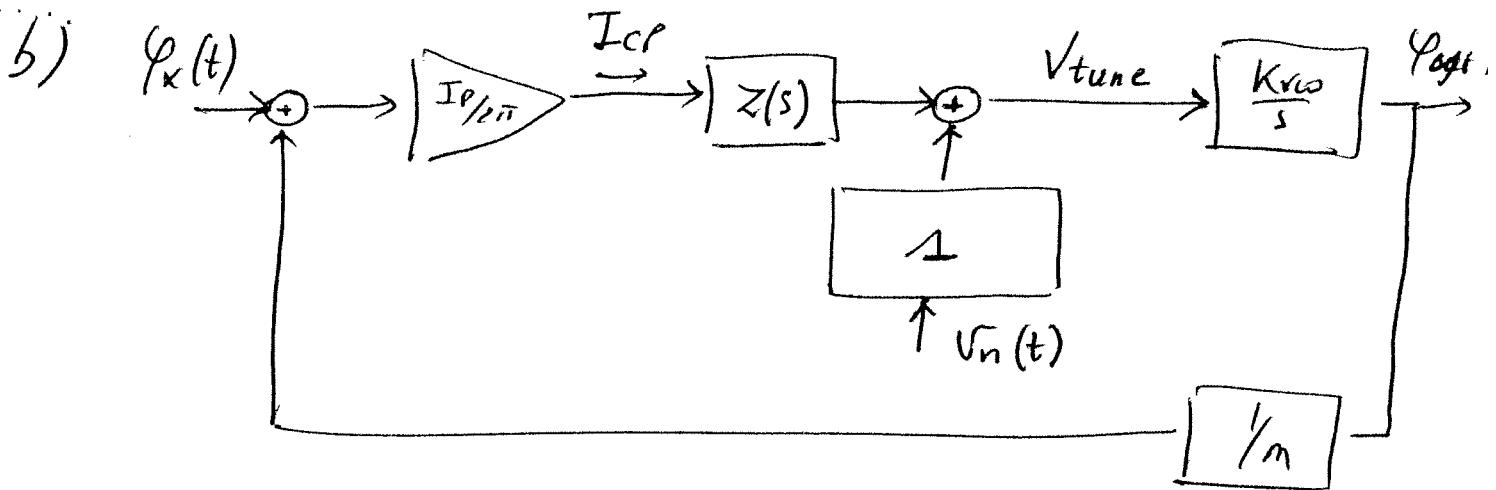
$$R_v = \frac{2\zeta}{\sqrt{\frac{I_P K_{rco} C}{2\pi M}}} = 296 \Omega$$




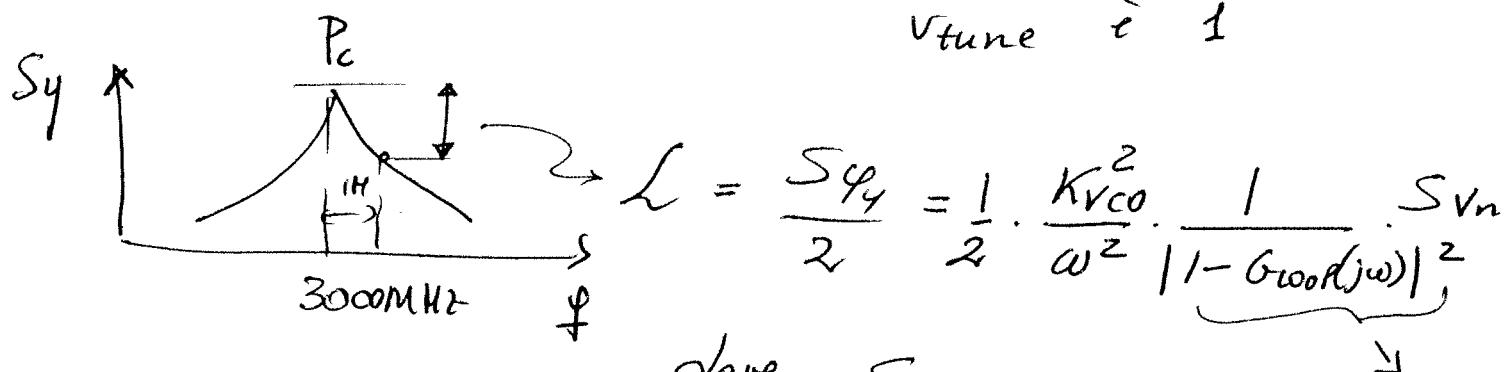guadagno ad anello  
aperto da  $v_n(t)$  a  
 $v_{tune}$  è 1



$$\begin{aligned} L(\omega = 2\pi \cdot 1M) &\approx \frac{1}{2} \cdot \frac{K_{VCO}^2}{\omega^2} \cdot 4KTR = \\ &= \frac{1}{2} \cdot (300)^2 \cdot 16 \cdot 10^{-21} \cdot 256 \rightarrow -126.7 \frac{dBc}{Hz} \end{aligned}$$

a 1MHz  
(essendo  
banda  
a 10kHz)

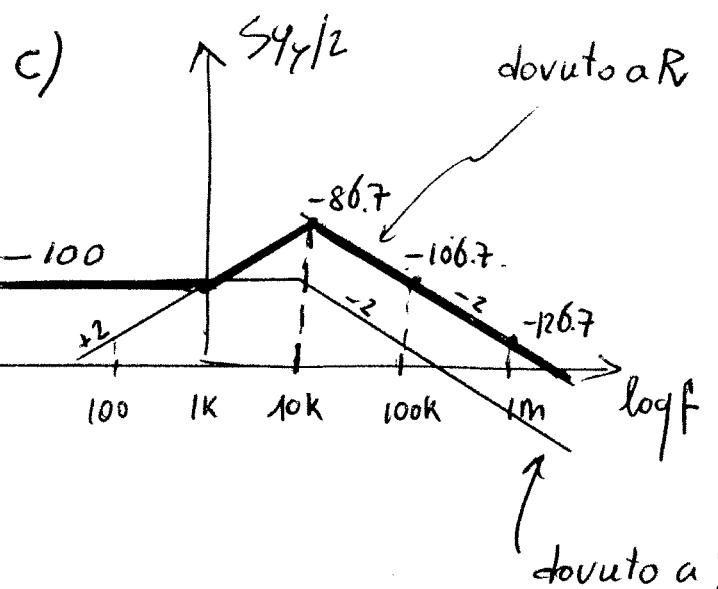

$$\frac{\varphi_y}{\varphi_x} = \frac{M(1 + SR_C)}{1 + \frac{2S_2}{\omega_m} + \frac{S_2^2}{\omega_m^2}}$$

zero  
a 7kHz  
2 poli C.C.  
a 10kHz

$$M = 100 \rightarrow 40 dB$$


$$S_y/2 = -140 dBc/Hz$$

$$\text{In banda } \frac{S_y}{2} = -100 dBc/Hz$$

### Problema 3

a) Polarizzazione

Transistori  
in  $\geq$ . di sat.

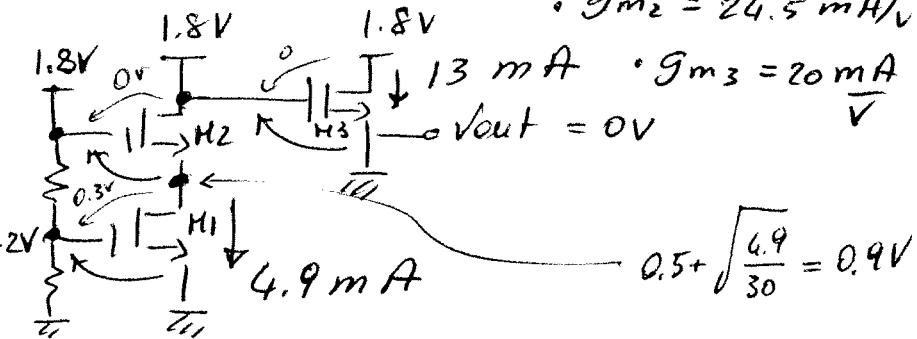

$$1) \bullet f = f_{RES} =$$

$$= \frac{1}{2\pi} \frac{1}{\sqrt{(L_g + L_s) \frac{C_{in}(g_s)}{C_{int}(g_s)}}}$$

$$\approx \frac{1}{2\pi} \frac{1}{\sqrt{5.5n \cdot 0.5p}} =$$

$$= 3.04 \text{ GHz}$$

$$\bullet Z_{in} = \omega_T L_s =$$



$$= \frac{g_{m1}}{C_{gs}} \cdot L_s = 50 \Omega$$


$$\bullet \frac{V_{out}}{V_s} = g_{m1} \cdot Q \cdot R_o \cdot \left( \frac{R_L}{R_L + \cancel{\frac{1}{g_{m2}}}} \right) = 50 \Omega = 11.15 \quad \downarrow$$

$$Q = \frac{1}{\omega_{RE} C_{gs} \cdot 2R_s} = \frac{1}{2\pi \cdot 3G \cdot 0.5p \cdot 100} = 1.06$$

ossia  $R_s + Z_{in}$
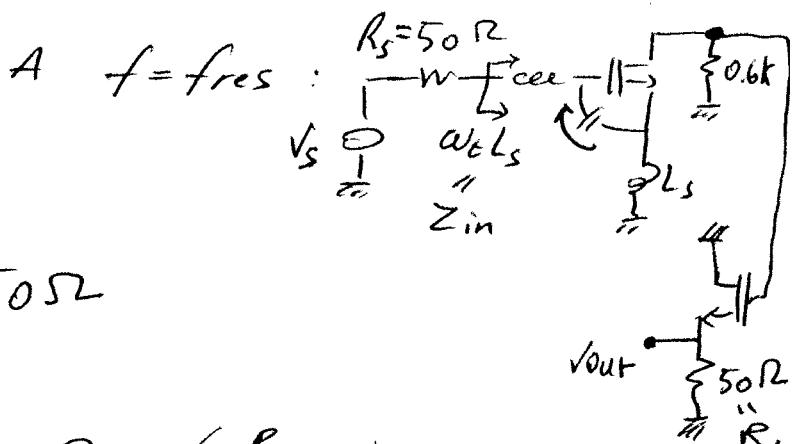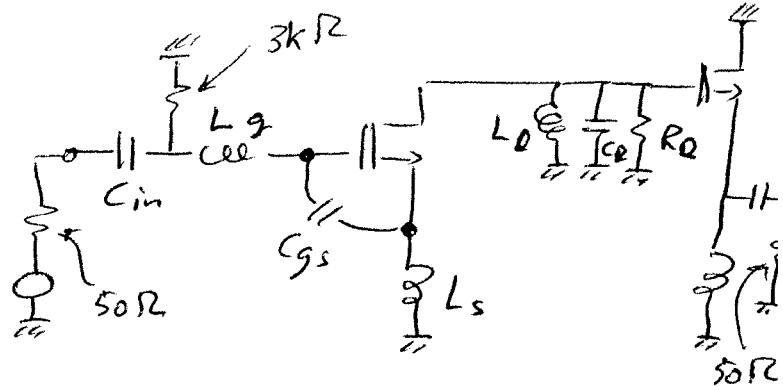
$$\Rightarrow GP = \frac{P_{out,av}}{P_{in,av}} = \frac{V_{out}^2 / 8R_L}{V_s^2 / 8R_s} = \left( \frac{V_{out}}{V_s} \right)^2 \Rightarrow 13 \text{ dB}$$




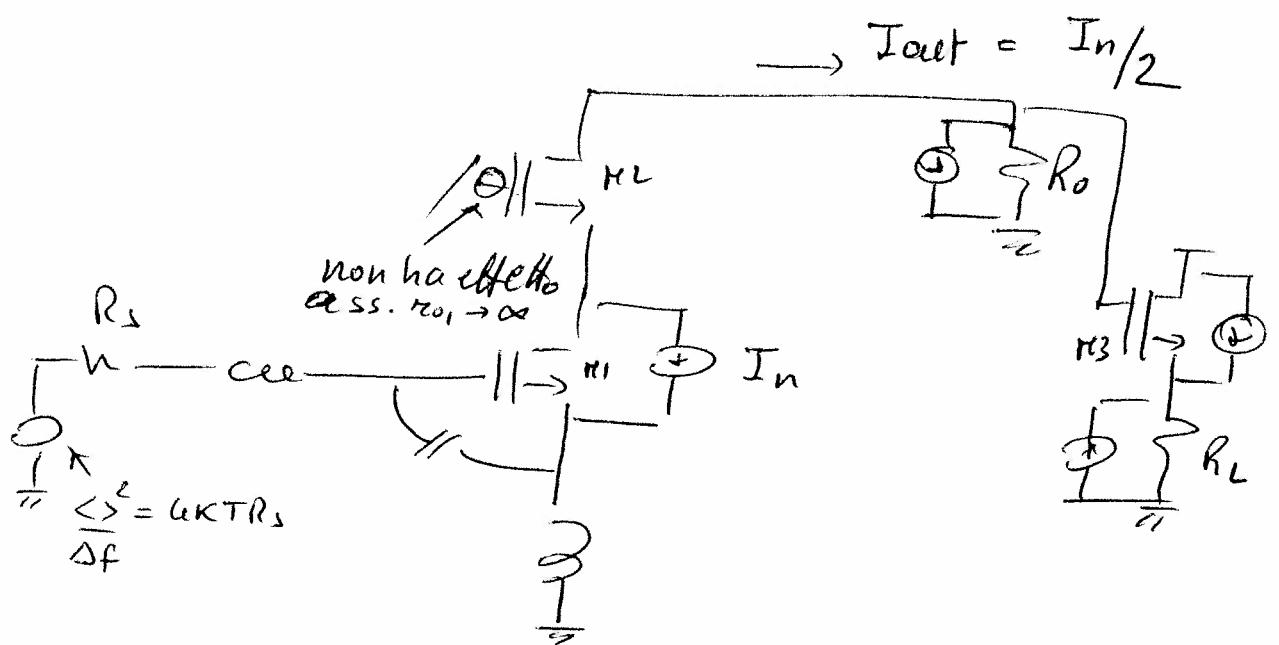

Si può illustrare che  $I_{out} = I_n/2$  (...)

$$\begin{aligned}
 \Rightarrow NF &= 1 + \frac{\frac{KXT}{3}g_m \cdot \frac{1}{Q^2}}{KXT R_s \cdot (g_m Q)^2} + \\
 &+ \frac{KXT R_o}{KXT R_s (g_m Q)^2} + \frac{(KXT \frac{2}{3} g_m + KXT / R_L) R_L^2}{KXT R_s \cdot G_p} = \\
 &= 1 + \frac{1}{6} \frac{1}{g_m R_s} \frac{1}{Q^2} + \frac{1}{R_o R_s g_m^2 Q^2} + \frac{KXT R_L (\frac{2}{3} + 1)}{KXT R_s \cdot G_p} = \\
 &= 1 + \frac{1}{6} \frac{1}{g_m R_s} \frac{1}{Q^2} + \frac{1}{R_o R_s g_m^2 Q^2} + \frac{5}{3} \frac{1}{G_p} = \\
 &= 1 + 0.21 + 0.15 + 0.08 = 1.44 \\
 &\quad \downarrow \\
 &\quad 1.59 \text{ dB}
 \end{aligned}$$

c)

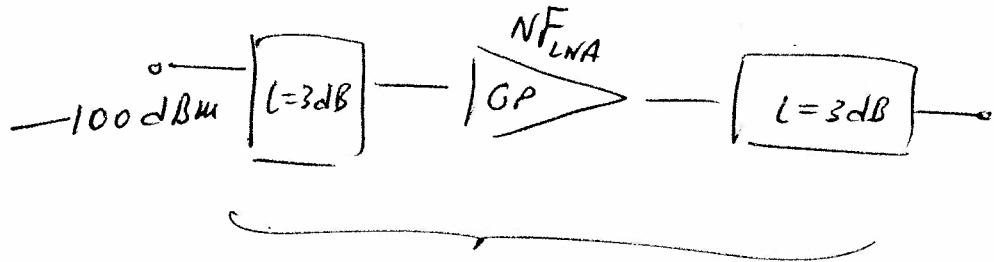

$$NF = L + \frac{NF_{LNA} - 1}{1/L} + \frac{L-1}{GP} =$$

$$L = 3 \text{ dB}$$

↓

$$= L \cdot NF_{LNA} + \frac{L(L-1)}{GP} =$$

$$= 2.75 \cdot 1.44 + \frac{2.75 \cdot 1}{20} =$$

$$= 2.88 + 0.1 = 2.98$$

↓  
4.6 dB

$$SNR = \frac{P_S}{P_N} = \frac{P_S}{\frac{4KT B_S \cdot NF \cdot BW}{HBS}} = \frac{P_S}{K T \cdot NF \cdot BW} \underset{1 \text{ MHz}}{\cancel{}} =$$

$$\Rightarrow \frac{P_S}{P_N} = -100 \text{ dBm} + 174 \frac{\text{dBm}}{\text{Hz}} - 4.6 \text{ dB} - 60 =$$

$$= 9.4 \text{ dB}$$


**Elettronica a Radiofrequenza****Prof. Salvatore Levantino**

Tempo massimo a disposizione: 3 ore


30/06/2011

**Problema 1**Si trascuri la capacità  $C_\mu$  del BJT e si consideri  $\beta \gg 1$ .

- Ricavare l'espressione dell'impedenza  $Z_1(\omega)$ , trascurando la corrente di base del BJT.
- Dimensionare L, C e la R limite per garantire 1) innesco dell'oscillazione a 2GHz ( $f_0$ ) e 2) fattore Q della rete RLC (isolata) pari a 5 ( Imporre le condizioni di oscillazione e approssimare per  $f_0 \ll f_T$ , con  $f_T$  frequenza di taglio del BJT).
- Con i valori ottenuti, ma con corrente ridotta a  $50\mu\text{A}$ , ricalcolare frequenza di oscillazione e condizione d'innesto (approssimando per  $f_0 \gg f_T$ ).

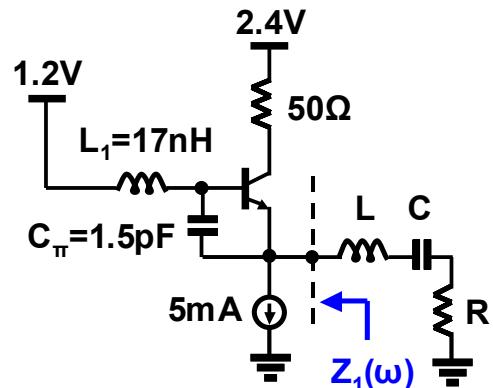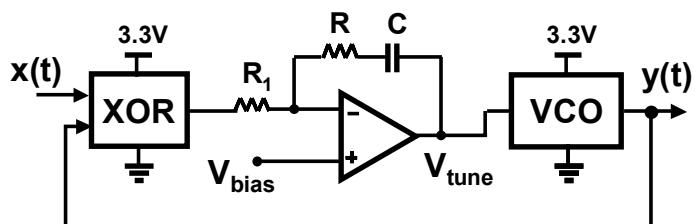**Problema 2**Sia la frequenza di  $x(t)$  pari a 200 kHz.


Assumere nulla l'impedenza d'uscita della porta XOR, amplificatore operazione ideale e VCO con caratteristica di tuning lineare sull'intervallo 0-3.3V.



- Ipotizzando  $V_{bias}$  pari a 1.65V, ricavare e disegnare il modello equivalente di fase, e dimensionare i parametri  $R_1$ ,  $R$ ,  $C$ ,  $K_{VCO}$  per avere 1) massima corrente in uscita alla XOR pari a 1mA, 2) tuning range pari a 50kHz, 3) margine di fase  $60^\circ$ , 4) frequenza di crossover del guadagno d'anello pari a 1kHz.
- Ricavare lo sfasamento in gradi tra  $x(t)$  e  $y(t)$  in funzione della tensione  $V_{bias}$  tra 0 e 3.3V.
- Fissando  $V_{bias}$  a 1.65V, valutare l'effetto sul funzionamento del sistema di un offset di tensione di 10mV e di una corrente di bias di  $10\mu\text{A}$  dell'amplificatore operazionale: l'anello rimane agganciato e perché? Se sì, con che relazione di fase tra  $x(t)$  e  $y(t)$ ?

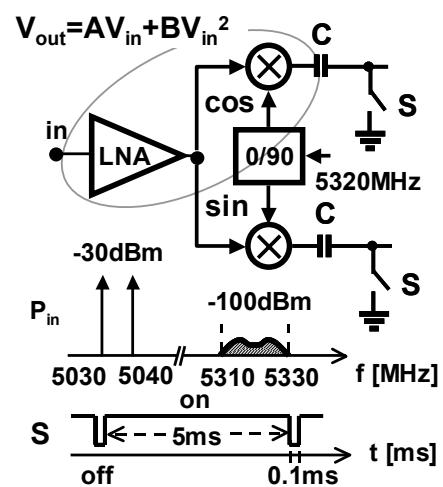
**Problema 3**Assumere che il segnale d'ingresso durante un "burst" abbia spettro di potenza (riferito a  $50\Omega$ ) riportato in figura, che il guadagno di LNA/mixer sia 20dB e che gli interruttori S siano chiusi/aperti quando il ricevitore è inattivo/attivo.

- Considerando i due blocker all'ingresso di -30dBm ciascuno, discutere l'impatto della nonlinearietà del secondo ordine e ricavare la massima IIP2 tollerabile del ricevitore per avere un rapporto segnale/interferenti di almeno 20dB.
- Dopo aver discusso la funzione degli switch S, ricavare il valore di C che garantisca un SNR di almeno 20dB, tenuto conto del rumore termico degli interruttori S con  $r_{on}=1\text{k}\Omega$ .
- Spiegare perché il ricevitore in figura utilizza due mixer e non solamente uno.



### ES. 1

a)

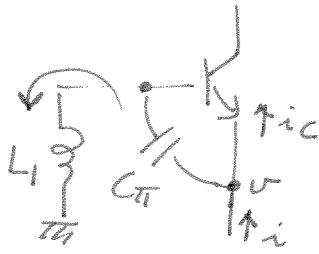

$$\left\{ \begin{array}{l} i = i_c + \frac{V - i_c/g_m}{sL_1} \\ \frac{V - i_c/g_m}{sL_1} \cdot \frac{1}{sC_\pi} = \frac{i_c}{g_m} \end{array} \right.$$

$$\begin{aligned} L_1 &= 17 \text{nH} \\ C_\pi &= 1.5 \text{pF} \\ f_0 &= 2.6 \text{MHz} \\ f_T &= \frac{10^{12}}{2\pi \cdot 5 \cdot 1.5} = 21.26 \text{MHz} \end{aligned}$$

$$\Rightarrow Z(j) = \frac{V}{i} = \frac{1 + s^2 L_1 C_\pi}{g_m + s C_\pi}$$

$$\frac{1}{g_m} = \frac{25 \mu}{5 \mu} = 5 \Omega$$

$$Z(\omega) = \frac{1 - \omega^2 L_1 C_\pi}{g_m (1 + j\omega/\omega_T)} = \frac{1}{g_m} \frac{(1 - \omega^2 L_1 C_\pi)}{1 + (\omega/\omega_T)^2} (1 - j\omega/\omega_T)$$

b)  $\omega_0 \ll \omega_T : Z(\omega_0) \approx \frac{1}{g_m} (1 - \omega_0^2 L_1 C_\pi) (1 - j\omega_0/\omega_T)$

II)  $-\operatorname{Re}(Z(\omega_0)) = R ; R_{\max} = \frac{1}{g_m} (\omega_0^2 L_1 C_\pi - 1) \approx 15.1 \Omega$

III)  $-\operatorname{Im}(Z(\omega_0)) = j(\omega_0 L_1 - \frac{1}{\omega_0 C}) ; \frac{1}{g_m} (\omega_0^2 L_1 C_\pi - 1) \frac{\omega_0}{\omega_T} = \frac{1}{\omega_0 C} - \omega_0 L_1$

$$R \cdot \frac{\omega_0}{\omega_T} = \frac{1}{\omega_0 C} - \omega_0 L_1 ; \omega_0 = \frac{1}{\sqrt{C(L + R/\omega_T)}} \Rightarrow C = \frac{1}{\omega_0^2 (L + R/\omega_T)} =$$

$$Q = \frac{\omega_0 L_1}{R} = 5 \Rightarrow L = \frac{Q \cdot R}{\omega_0} = \frac{5 \cdot 15.1}{2\pi \cdot 21.26} = 6 \text{nH} \quad \approx 1.037 \text{pF}$$

c)  $\omega_0 \gg \omega_T : Z(\omega_0) \approx \frac{1}{g_m} \cdot \frac{1 - \omega_0^2 L_1 C_\pi}{\omega_0^2 / \omega_T^2} \cdot (1 - j\omega_0/\omega_T) =$

$$f_T = \frac{10^{12}}{2\pi \cdot 500 \cdot 1.5} = 212 \text{MHz}$$



$$= \frac{1}{g_m} \left( \frac{\omega_T}{\omega_0} \right)^2 - \omega_T L_1 + j\omega_0 L_1 + \frac{1}{j\omega_0 C_\pi}$$

I)  $\omega_T L_1 - \frac{1}{g_m} \left( \frac{\omega_T}{\omega_0} \right)^2 \geq R ; 22.6 - 12.2 \Omega = 10.4 \Omega \leq 15.1 \Omega \Rightarrow \text{no startup}$

II)  $\omega_0 = \frac{1}{\sqrt{(L + L_1) \cdot \frac{C C_\pi}{C + C_\pi}}} = \sqrt{\frac{1}{23 \cdot 10^{-9} \cdot 0.6 \cdot 10^{-12}}} = 8.5 \text{Grad}$

$$\Rightarrow f_0 = 1.355 \text{ GHz}$$

## ES. 2

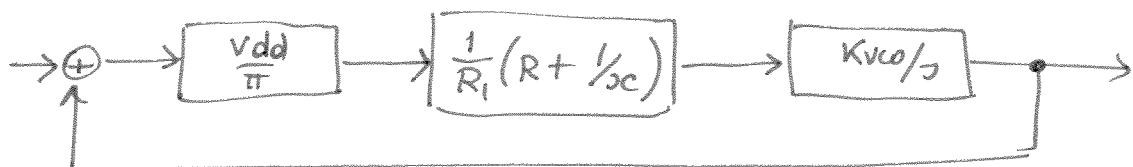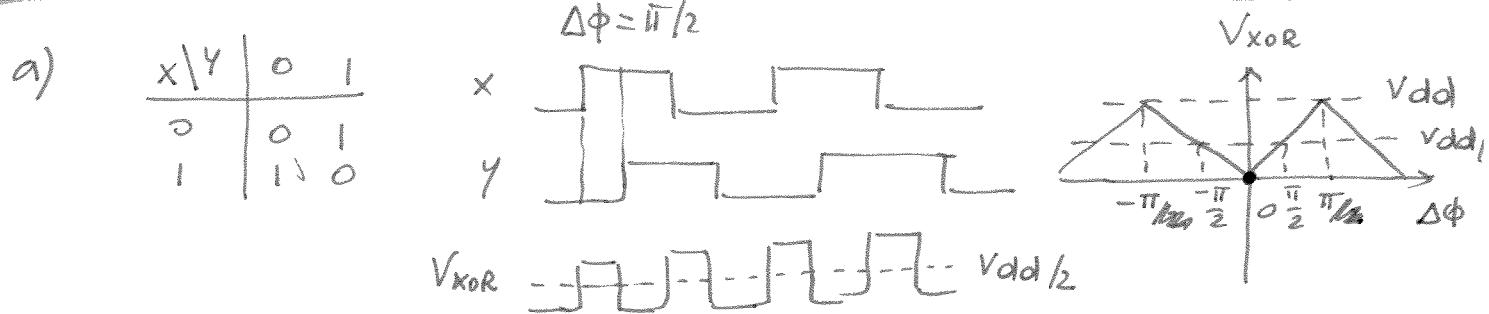

$$1) R_1 = \frac{V_{dd}/2}{I_{max}} = \frac{1.65V}{1mA} = 1.65k\Omega$$

$$2) K_{vco} = 2\pi \cdot \frac{50k}{3.3} = 95.2 \text{ krad/Vs}$$

$$3) G_{loop}(\gamma) = \left( \frac{V_{dd}}{\pi} \cdot \frac{K_{vco}}{\gamma} \frac{R}{R_1} \right) \left( 1 + \frac{1}{\gamma RC} \right)$$

\*\*  $|G_{loop}(\omega_u)| = \frac{K}{\omega_u} \sqrt{1 + \frac{\omega_z^2}{\omega_u^2}}$

ess.  $\omega_u/\omega_z = \sqrt{3}$  :

$$\omega_u = K \cdot \sqrt{1 + 1/3} = 1.15 \cdot K$$


$$|G_{loop}(\omega_u)| \approx \frac{V_{dd}}{\pi} \frac{K_{vco}}{\omega_u} \frac{R}{R_1} = 1 \Rightarrow \omega_u = \frac{V_{dd} \cdot K_{vco} \cdot R}{\pi \cdot R_1} =$$

$$\Rightarrow \frac{R}{R_1} = \frac{2\pi \cdot 1k \cdot \pi}{V_{dd} \cdot K_{vco}} = \frac{2\pi \cdot 1k \cdot \pi}{2\pi \cdot 50k} = 0.0628 \Rightarrow R = 103.62 \Omega \quad (90\Omega)$$

$$\nexists G_{loop}(\omega_u) = \arctan\left(\frac{\omega_u}{\omega_z}\right) = \frac{\pi}{3} \Rightarrow \frac{\omega_u}{\omega_z} = \sqrt{3} \Rightarrow$$

$$\omega_z = \frac{\omega_u}{\sqrt{3}} \Rightarrow RC = \frac{\sqrt{3}}{\omega_u} = 246 \mu s \Rightarrow C = 2.66 \mu F \quad (3.06 \mu F)^{**}$$

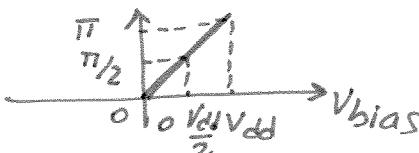b)  $\Delta\gamma = 90^\circ$  per  $V_{bias} = 1.65V$   $\rightarrow$





Assumendo che vco abbia guadagno negativo (ovia frequenza aumentata al diminuire della tensione di controllo)

c)  $V_{bias} = 1.65V$

$$V_{bias} + V_{os} + I_B R_1$$

$$\Delta\gamma = 90^\circ + \frac{V_{os} \cdot 180^\circ}{V_{dd}} + I_B R_1 \cdot \frac{180^\circ}{V_{dd}} =$$
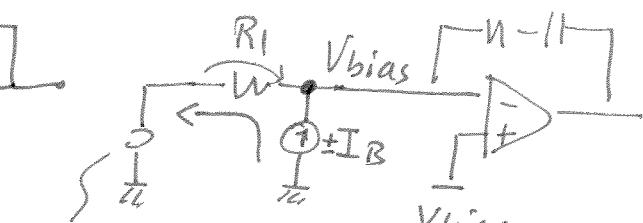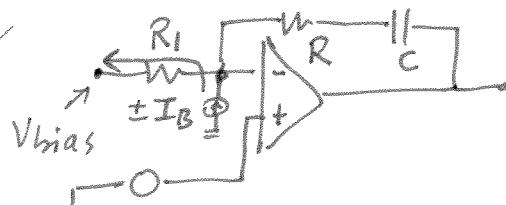
$$= 90^\circ + \frac{0.01}{3.3} \cdot 180^\circ + \frac{0.0165}{3.3} \cdot 180^\circ = 90^\circ + 0.54^\circ + 0.95^\circ = 91.49^\circ$$



### E.S. 3

a)  $11P_2 = \Delta P + P_{in} = 90 - 30 = 60 \text{ dBm}$   
 $\uparrow$   
 $-30 - (-120) = +90$

b)  $P_n = -100 \text{ dBm} \Rightarrow C = \frac{KT}{P_n} = \frac{4 \cdot 10^{-21} V^2}{50 \Omega} =$   
 $= 800 \mu F$